

---

# Lecture12: Impedance


Sung-Min Hong ([smhong@gist.ac.kr](mailto:smhong@gist.ac.kr))

Semiconductor Device Simulation Lab.  
School of Electrical Engineering and Computer Science  
Gwangju Institute of Science and Technology
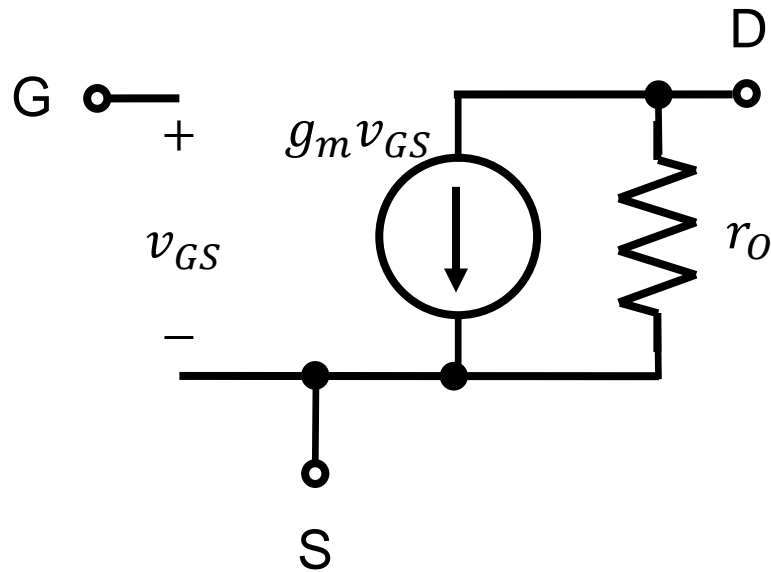
# Summary

---

- Small-signal MOSFET model
  - Two branches are related with two partial derivatives.



# Simple math

---

- Following relations are useful.
  - Sine and cosine functions can be expanded with  $e^{+j\omega t}$  and  $e^{-j\omega t}$ .

$$\sin \omega t = -\frac{j}{2} e^{+j\omega t} + \frac{j}{2} e^{-j\omega t}$$

$$\cos \omega t = \frac{1}{2} e^{+j\omega t} + \frac{1}{2} e^{-j\omega t}$$

- Therefore, for a function of  $f(t) = f_s \sin \omega t + f_c \cos \omega t$ , the expansion is

$$f(t) = \left( -j \frac{f_s}{2} + \frac{f_c}{2} \right) e^{+j\omega t} + \left( +j \frac{f_s}{2} + \frac{f_c}{2} \right) e^{-j\omega t}$$

- A single complex number,  $-j \frac{f_s}{2} + \frac{f_c}{2}$ , is enough to represent  $f(t)$ .

# Impedances

---

- Resistance,  $V(t) = R I(t)$ 
  - It is assumed that  $V(t)$  and  $I(t)$  are in the same phase.
  - Consider  $V(t) = V_0 \sin \omega t$  and  $I(t) = I_0 \cos \omega t$ . Then, what is the resistance?
  - In this case, we can introduce a phasor voltage,  $V(\omega)$ , and a phasor current,  $I(\omega)$ .
  - The relation between  $V(t)$  and  $V(\omega)$  is
$$V(t) = \text{Re}[V(\omega)e^{j\omega t}]$$
  - When  $V(t) = V_0 \sin \omega t$ , the phasor voltage is  $V(\omega) = -jV_0$ .
  - When  $I(t) = I_0 \cos \omega t$ , the phasor voltage is  $I(\omega) = I_0$ .
- Impedance,  $V(\omega) = Z(\omega)I(\omega)$ 
  - In the above example,  $Z(\omega) = -j \frac{V_0}{I_0}$ . A purely imaginary number.

# Multi-terminal devices


---

- When the number of terminals is 3,
  - We can defined 9 ( = 3 X 3 ) different impedances.
- Termination condition is important.
  - Depending on the termination condition, the impedance can be heavily changed.
  - In many cases, it is obvious from the problem.
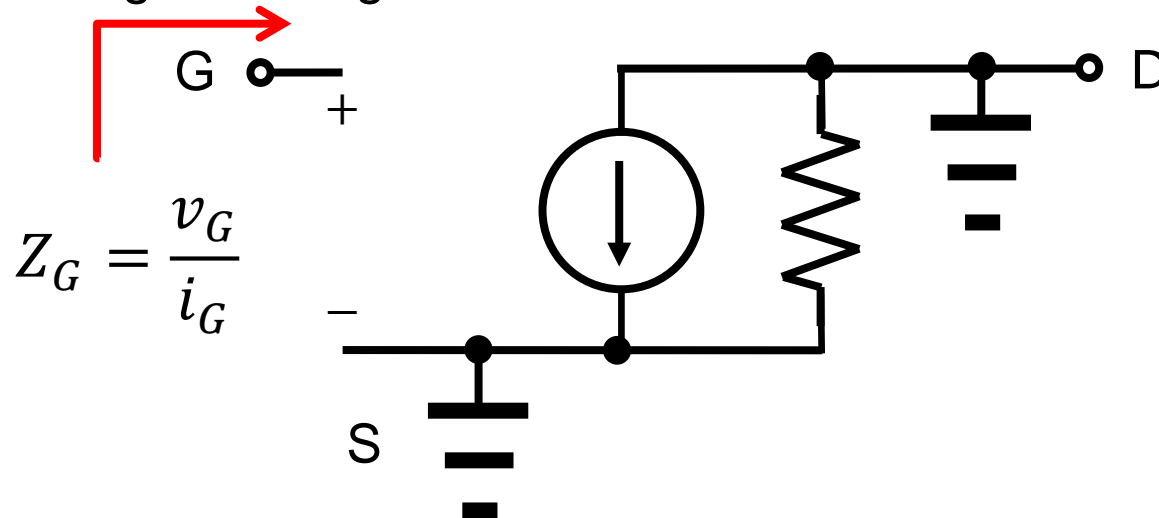
# Impedances of MOSFET

---

- “Looking into the TERMINAL,” we see the impedance of the TERMINAL.
  - Consider the following cases:
  - 1) Looking into the gate. The source and drain are ac-grounded.



- 2) Looking into the drain. The source and gate are ac-grounded.
- 3) Looking into the source. The gate and drain are ac-grounded.