
Lecture19:

Common-gate amplifier

Sung-Min Hong (smhong@gist.ac.kr)

Semiconductor Device Simulation Lab.
School of Electrical Engineering and Computer Science
Gwangju Institute of Science and Technology


Configurations

- Three terminals of the MOSFET
 - The common terminal, the input terminal, and the output terminal

Source	Gate	Drain	Remark
Common	Input	Output	Common-source amp.
Common	Output	Input	X
Input	Common	Output	It will be covered.
Output	Common	Input	X
Input	Output	Common	X
Output	Input	Common	It will be covered.


Common-gate amplifier

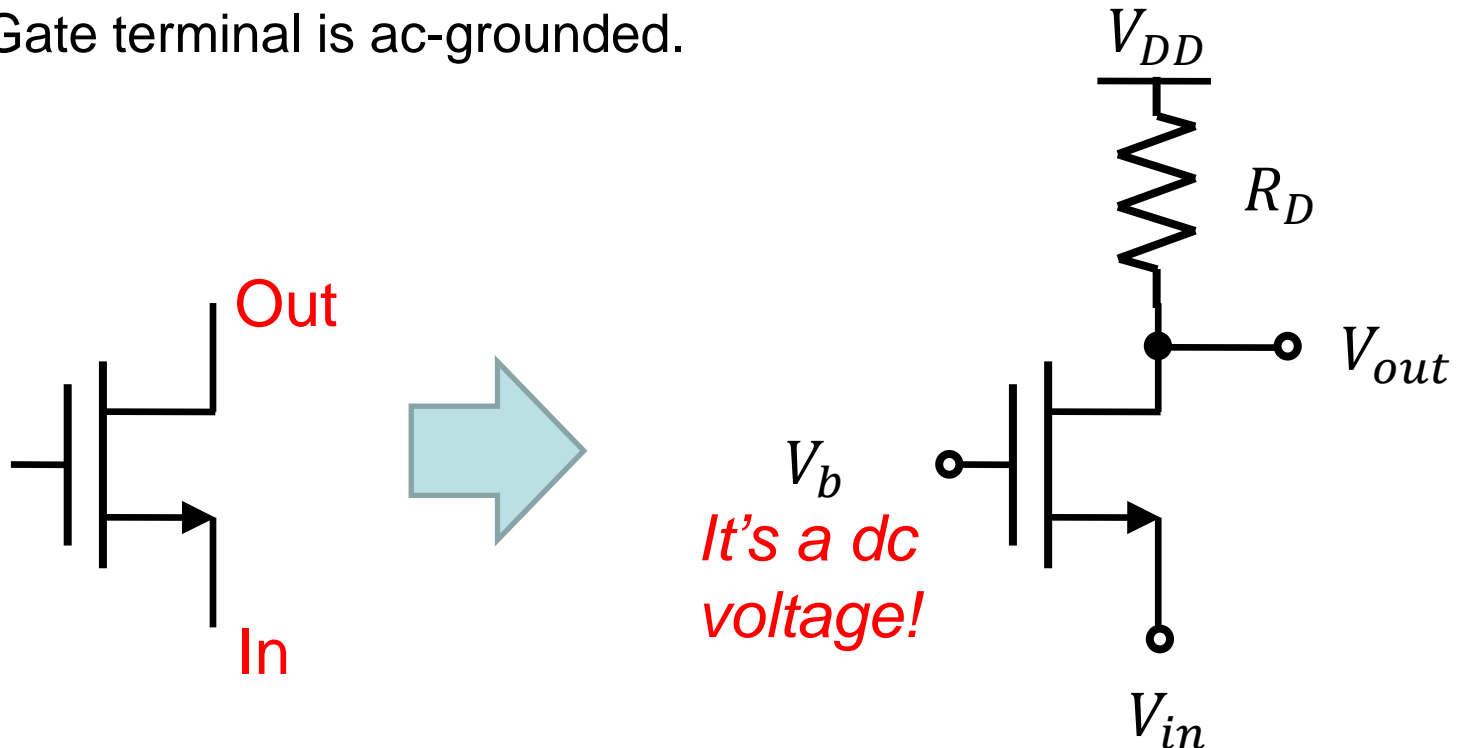- Why do we study other amplification topologies?
 - Different circuit properties
- Common-gate amplifier
 - Gate terminal is ac-grounded.



Small-signal model

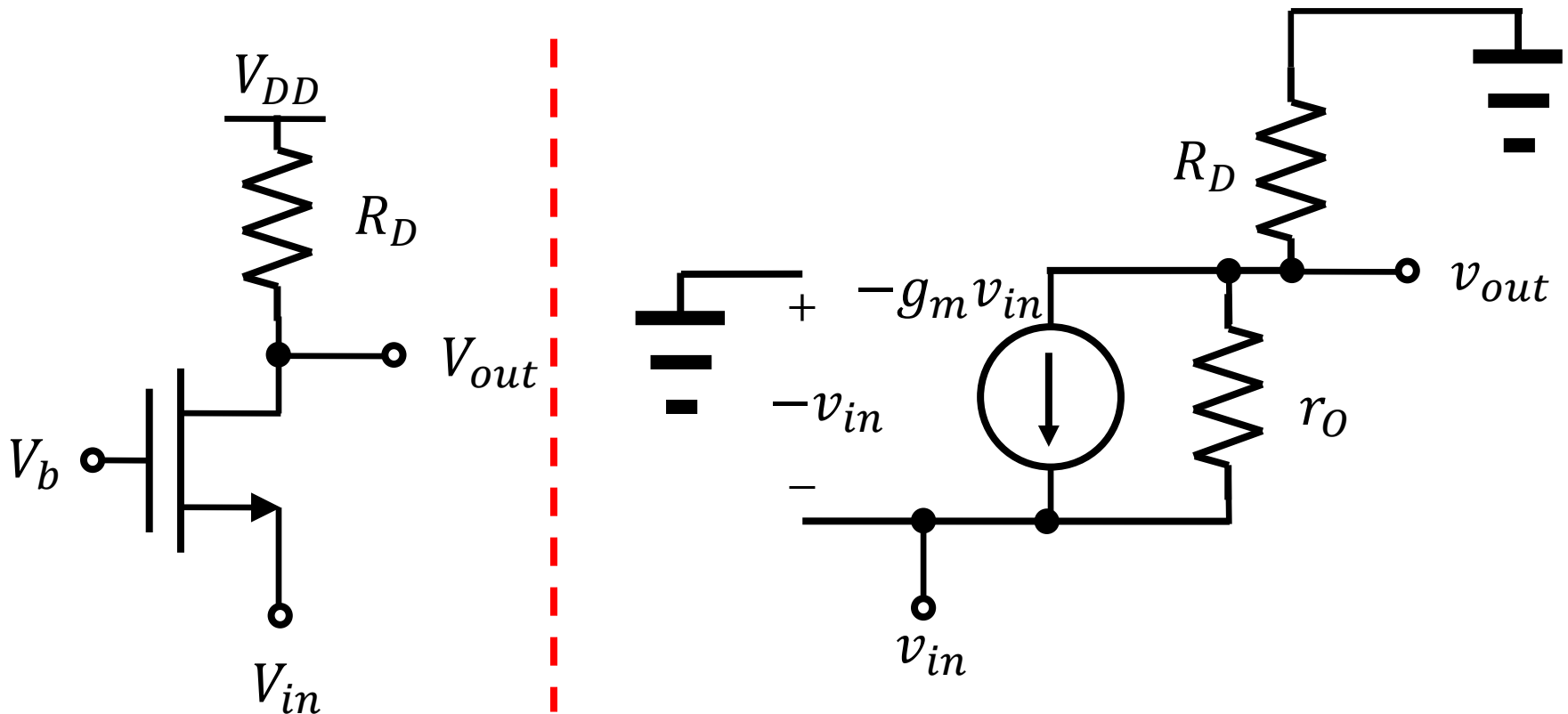- Let's draw the small-signal model together!



Gain & input impedance (1/2)

- Neglect the output resistance, r_o .


- Voltage gain

$$A_v = +g_m R_D$$

- Input impedance

$$R_{in} = \frac{1}{g_m}$$

It's small!

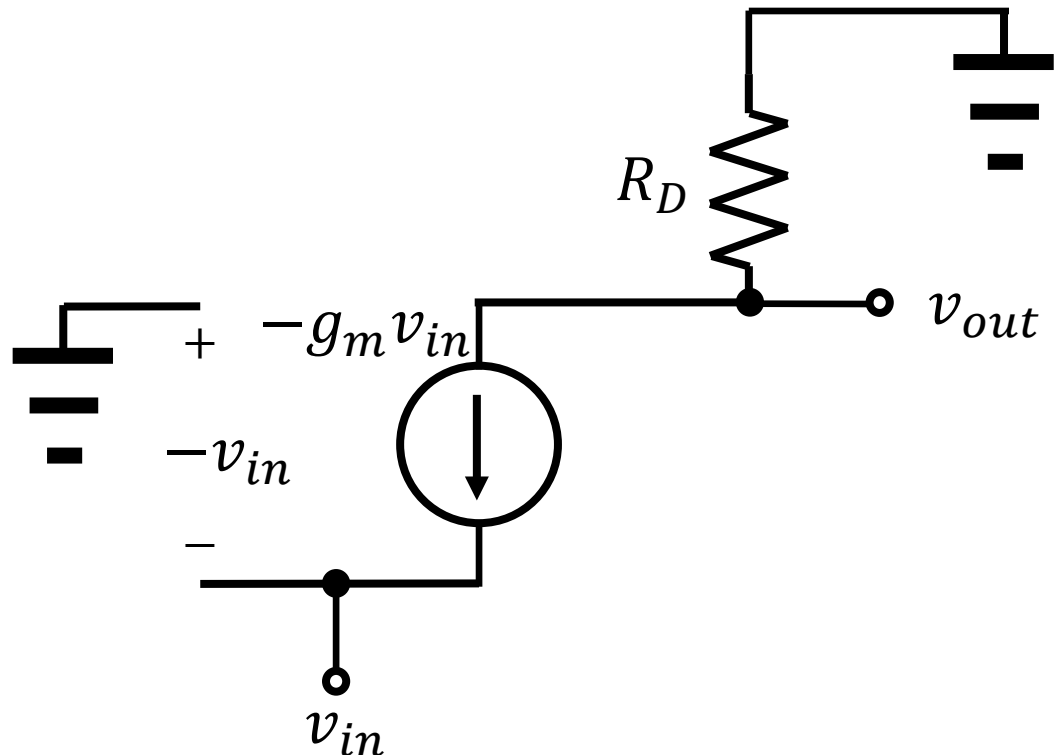

Gain & input impedance (2/2)

- Consider the output resistance, r_o .


- Voltage gain

$$A_v = + \left(g_m + \frac{1}{r_o} \right) (R_D || r_o)$$

- Input impedance


$$R_{in} = \frac{r_o + R_D}{g_m r_o + 1}$$

It's small!

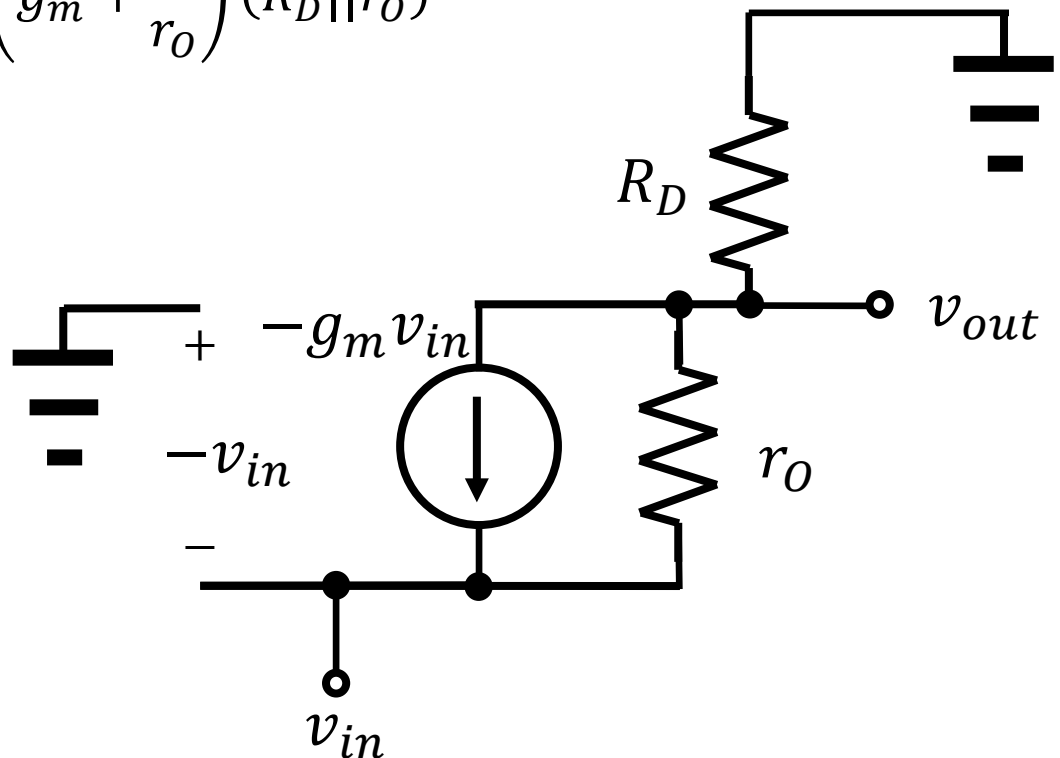


Output impedance

- Without a finite source resistance, $R_{out} = r_o || R_D$

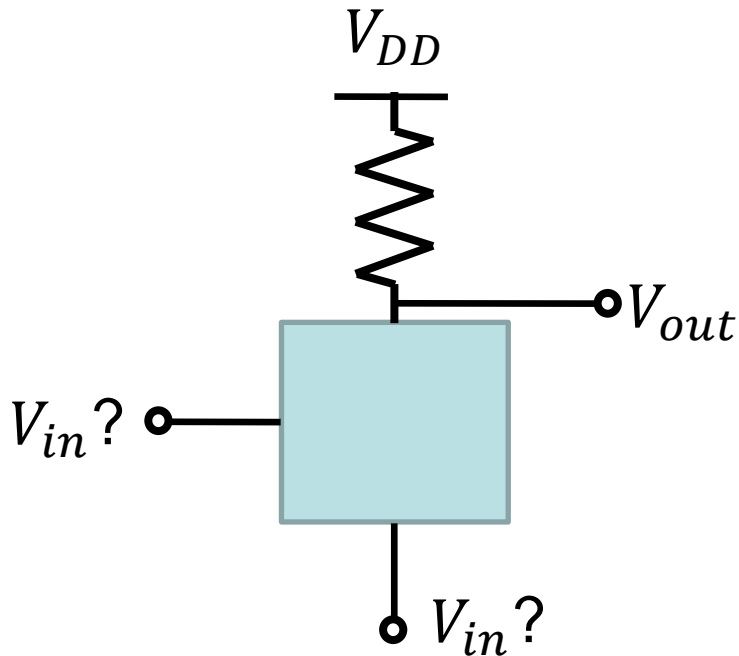

Generic form of CS and CG stages

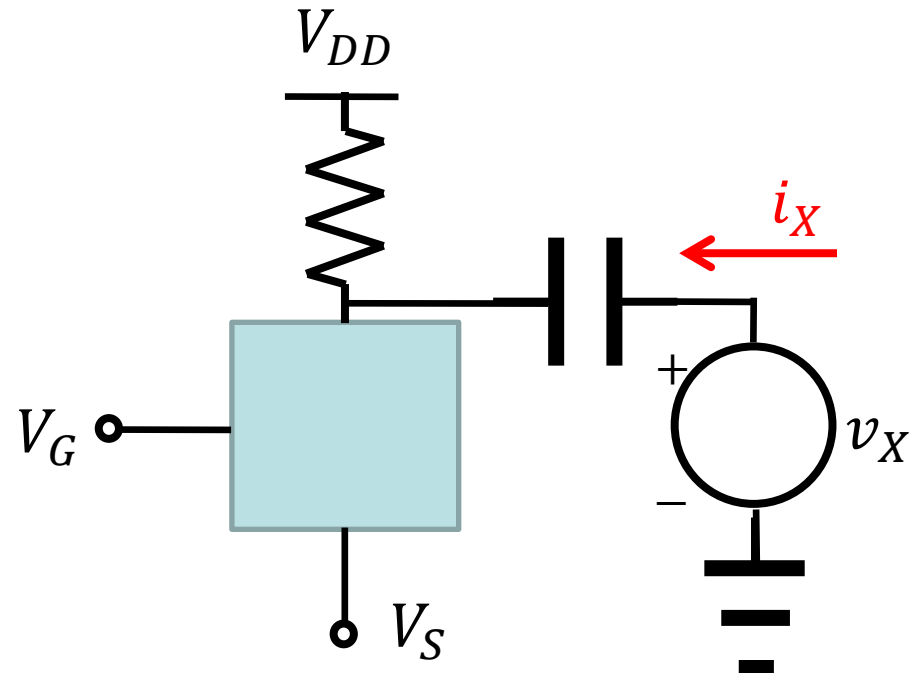

Setting for calculating R_{out}

Homework#8 (Again)

- Due: 09:00, **May 20 (Mon)**
- Solve the following problems of the final exam in 2017.
 - P33
 - P34
 - P38
 - P39
 - P40
 - P41