
Lecture20:

Digital CMOS circuits (3)

Sung-Min Hong (smhong@gist.ac.kr)

Semiconductor Device Simulation Lab.
School of Electrical Engineering and Computer Science
Gwangju Institute of Science and Technology

RC circuit


- Consider a serial RC circuit.

- The KCL states

$$\frac{V_{out} - V_{in}}{R} + C \frac{dV_{out}}{dt} = 0$$


- Assume a step-wise change of V_{in} at $t = 0$. It becomes V_{DD} .
- Initial output voltage is V_0 .
- Its solution is given by
 
$$V_{out}(t) = V_{DD} + (V_0 - V_{DD}) \exp\left(-\frac{t}{RC}\right)$$




Speed of inverter (1/4)

 - VTC merely describes the dc behavior.
 - Input voltages with different frequencies (1 kHz, 1 MHz, 1 GHz, 1 THz, ...)
- Time-dependent behavior
 - Can a resistor introduce time-lagging effect? No.



Speed of inverter (2/4)

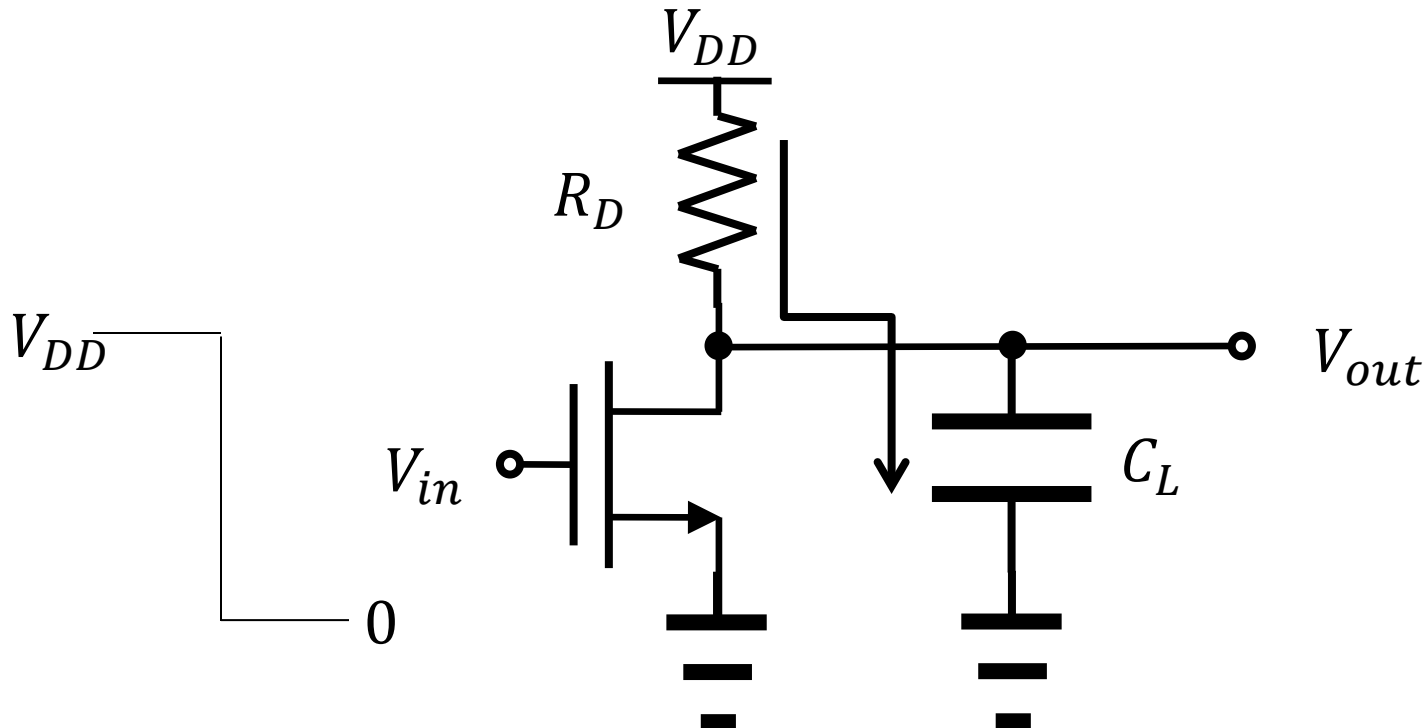- A rapid transition of V_{in} from V_{DD} to 0
 - Then, the capacitor should be charged.
 - What is the electrical route to charge the capacitor?



Speed of inverter (3/4)

- Simply, it is a RC circuit.

- Then, the solution is simply


$$V_{out}(t) = V_{out}(0^-) + [V_{DD} - V_{out}(0^-)] \left(1 - \exp \frac{-t}{R_D C_L} \right)$$

- Since $\exp(-3) \approx 0.05$, after $3R_D C_L$, V_{out} reaches $0.95 V_{DD}$.
 - Yes, it takes time to get the stable output voltage...
 - The delay restricts the maximum signal frequency.

Speed of inverter (4/4)


- A rapid transition of V_{in} from 0 to V_{DD} to 0
 - At the initial phase, the resistor does not conduct.
 - Also the MOSFET is operated in its saturation mode.
 - Then,
 
$$I_{D,sat} + C_L \frac{dV_{out}}{dt} = 0$$



Origin of C_L ?

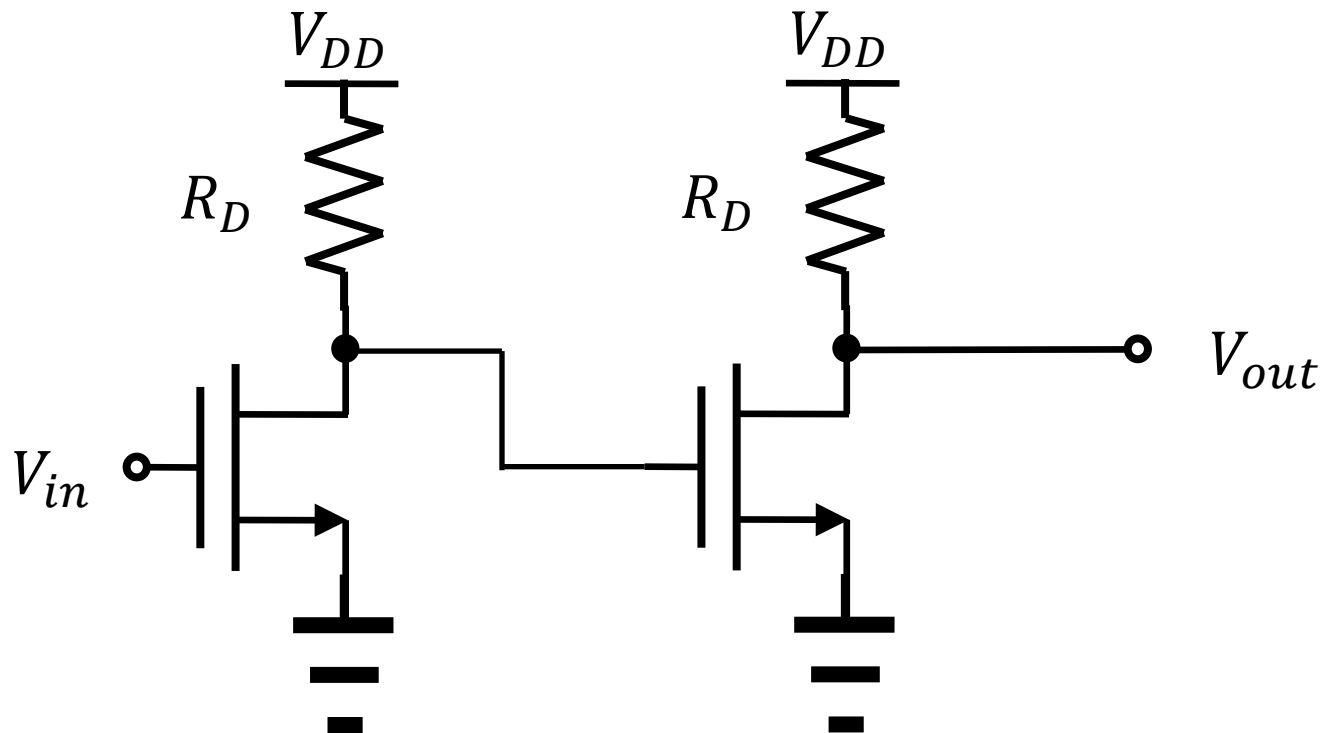- Consider an inverter chain.
 - Then, what is the load capacitance for the first stage?



- Another origin → Interconnect

Fan-out

- (It is not “Pan out” written in the lecture. Sorry!)
- The fan-out of a logic gate output is the number of gate inputs it can drive.
 - In order to minimize the delay, a large fan-out should be avoided.

Homework#9

- Due: 09:00, May 28
- Solve the following problems of the final exam in 2017.
 - P35
 - P36
 - P37
 - P38
 - P39
 - P41
 - P42
 - P43