
Lecture18: CMOS amplifiers (2)

Sung-Min Hong (smhong@gist.ac.kr)

Semiconductor Device Simulation Lab.
School of Electrical Engineering and Computer Science
Gwangju Institute of Science and Technology

Summary

- MOS structure
 - Two different mechanisms to provide negative charges
 - Threshold voltage
 - Once the MOS is inverted, it is a capacitor.
- MOS IV
 - Current as a product of density and velocity
 - Triode region and saturation region
 - Concept of transconductance
 - Channel length modulation
 - Body effect
 - Velocity saturation
 - Subthreshold swing

Introduction to G-SPICE

- What is the SPICE?
 - Simulation Program with Intergrated Circuit Emphasis
- G-SPICE is a “SPICE-like” program.
 - It will be serviced through the EDISON website.
 - Today, (unfortunately) the off-line demonstration is made.

A resistor

- Biasing a resistor
 - Input file

```
tstep = 1e-9 ;  
tnum = 1000 ;  
vsweep = 1 ;  
vsweep_value = 1.0 ;  
vsweep_num = 100 ;  
vsweep_node1 = 0 ;  
vsweep_node2 = 1 ;  
r[0] = 1 ;  
r_value[0] = 1e3 ;  
r_node1[0] = 0 ;  
r_node2[0] = 1 ;
```

Two resistors

- Biasing two resistors
 - Input file

```
tstep = 1e-9 ;
tnum = 1000 ;
vsweep = 1 ;
vsweep_value = 1.0 ;
vsweep_num = 100 ;
vsweep_node1 = 0 ;
vsweep_node2 = 2 ;
r[0] = 1 ;
r_value[0] = 1e3 ;
r_node1[0] = 0 ;
r_node2[0] = 1 ;
r[1] = 1 ;
r_value[1] = 1e3 ;
r_node1[1] = 1 ;
r_node2[1] = 2 ;
```

MOSFET

- MOSFET Id-Vds
 - Input file
 - Change the gate voltage
 - Channel length modulation?

```
tstep = 1e-9 ;
tnum = 1000 ;
vdc = 1 ;
vdc_value = 1.8 ;
vdc_node1 = 0 ;
vdc_node2 = 1 ;
vsweep = 1 ;
vsweep_value = 1.8 ;
vsweep_num = 100 ;
vsweep_node1 = 0 ;
vsweep_node2 = 2 ;
mos[0] = 1 ;
mos_type[0] = 0 ;
mos_vt0[0] = 0.4 ;
mos_kp[0] = 200e-6 ;
mos_w[0] = 2.0 ;
mos_l[0] = 0.18 ;
mos_lambda[0] = 0.1 ;
mos_node1[0] = 0 ;
mos_node2[0] = 1 ;
mos_node3[0] = 2 ;
```

Amplifier

- Guess its schematic
 - Its input-output characteristic?

```
tstep = 1e-3 ;
tnum = 1000 ;
vdc = 1 ;
vdc_value = 1.8 ;
vdc_node1 = 0 ;
vdc_node2 = 3 ;
vsweep = 1 ;
vsweep_value = 1.8 ;
vsweep_num = 100 ;
vsweep_node1 = 0 ;
vsweep_node2 = 1 ;
mos[0] = 1 ;
mos_type[0] = 0 ;
mos_vt0[0] = 0.4 ;
mos_kp[0] = 100e-6 ;
mos_w[0] = 2.0 ;
mos_l[0] = 0.18 ;
mos_lambda[0] = 0.0 ;
mos_node1[0] = 0 ;
mos_node2[0] = 1 ;
mos_node3[0] = 2 ;
r[0] = 1 ;
r_value[0] = 5e3 ;
r_node1[0] = 2 ;
r_node2[0] = 3 ;
```

One more...

- Imposing a sinusoidal signal
 - How about the output voltage?


```
tstep = 1e-3 ;
tnum = 1000 ;
vdc = 1 ;
vdc_value = 1.8 ;
vdc_node1 = 0 ;
vdc_node2 = 4 ;
vsweep = 1 ;
vsweep_value = 1.0 ;
vsweep_num = 100 ;
vsweep_node1 = 0 ;
vsweep_node2 = 1 ;
vsin = 1 ;
vsin_amp = 0.01 ;
vsin_freq = 10 ;
vsin_node1 = 1 ;
vsin_node2 = 2 ;
mos[0] = 1 ;
mos_type[0] = 0 ;
mos_vt0[0] = 0.4 ;
mos_kp[0] = 100e-6 ;
mos_w[0] = 2.0 ;
mos_l[0] = 0.18 ;
mos_lambda[0] = 0.0 ;
mos_node1[0] = 0 ;
mos_node2[0] = 2 ;
mos_node3[0] = 3 ;
r[0] = 1 ;
r_value[0] = 5e3 ;
r_node1[0] = 3 ;
r_node2[0] = 4 ;
```


Large-signal model (1/2)

- Saturation region

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$$

 - Drain current is determined by gate voltage. (*voltage-controlled current source*)
- Channel-length modulation?




Large-signal model (2/2)

- Triode region


$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} [2(V_{GS} - V_{TH})V_{DS} - V_{DS}^2]$$

- Still, it can be described by a *voltage-controlled current source*.

 

 Example 6.13


- Always in the saturation region!
 - Any necessary condition?




Gate and drain are tied.
They are connected to V_{DD} .

Small-signal model

 - The large-signal model is complete (within its accuracy limitation).
 - But, for small-signal analysis, it is convenient to have the small-signal model.



 
$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$$



What is g_m and r_o ?

Time-dependent one?


 
- Everything was in the dc steady-state...
 - How about the frequency-dependent case?
 - Capacitive components can be seen.
 - Their physical origin?



High-frequency, equivalent-circuit model for the case in which the source is connected to the substrate

CMOS

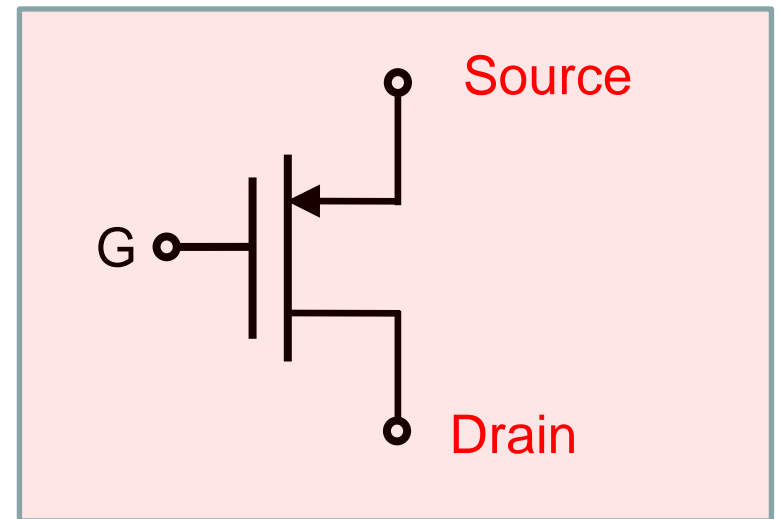 
- 9's complementary of 123?
 - 876
- Complementary MOS
 - Here we have an NMOSFET.
 - A device where the transport is dominated by holes



- Why is it important?

Why amplifiers?

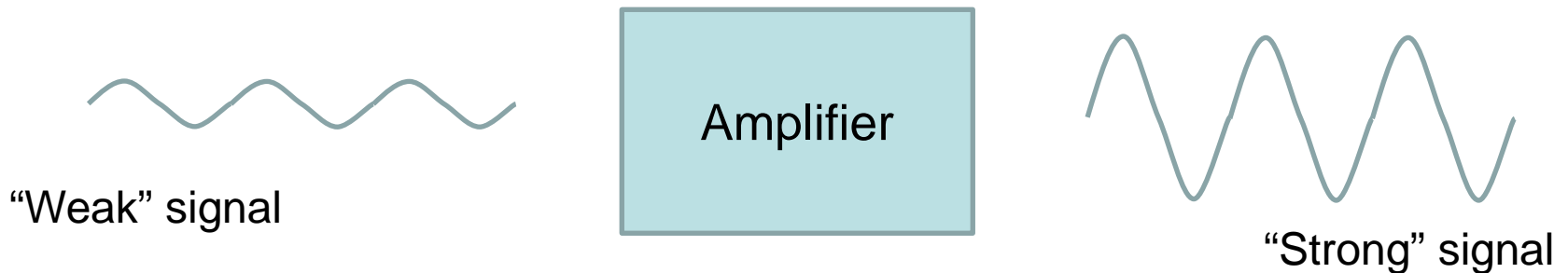
- Signal amplification
 - Usually, signals are “weak.” (in the μV or mV range)
 - It is too small for reliable processing.
 - If the signal magnitude is made larger, processing is much easier.



- Desirable properties
 - Low power consumption
 - High speed operation
 - Low noise


Impedances (1/3)

 - A MOSFET with three terminals
 - Looking into the gate, we see the infinite impedance.
 - (Strictly valid at the low-frequency range)




Impedances (2/3)

 - A MOSFET with three terminals
 - Looking into the drain, we see r_o if the source is ac grounded.




Impedances (3/3)

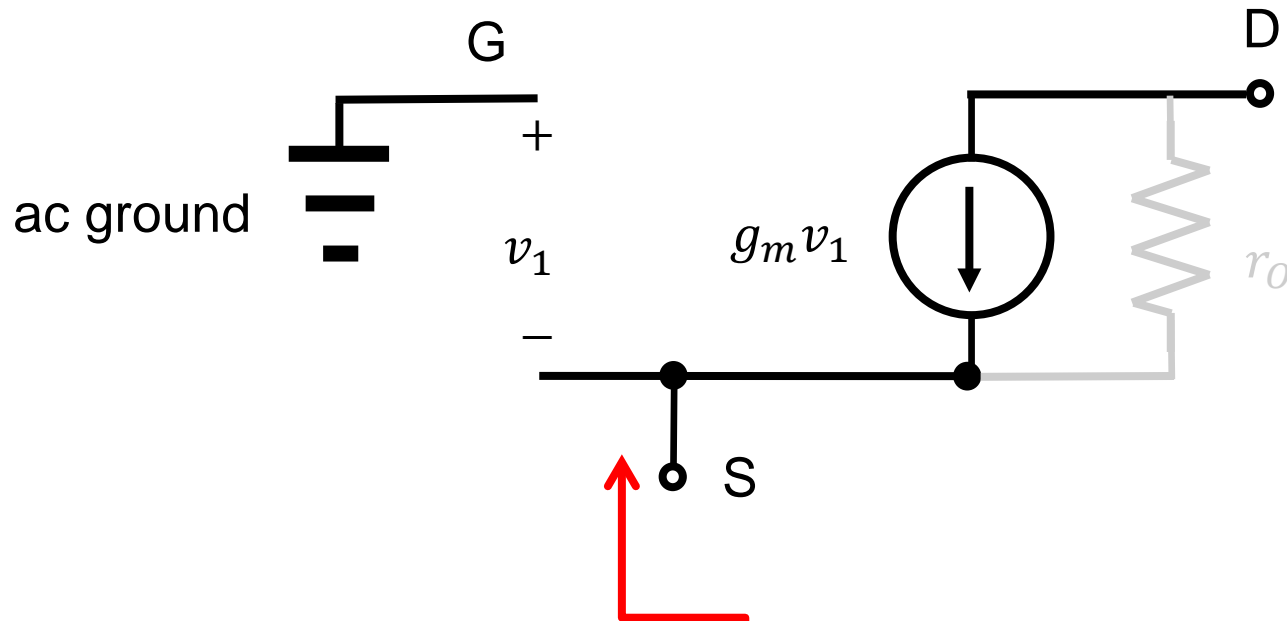- A MOSFET with three terminals
 - Looking into the source, we see $1/g_m$ if the gate is ac grounded and channel-length modulation is neglected.




Transistor turned off

 - The example 17.5 shows an amplifier circuit.
 - But, the transistor is not turned on.
 - The circuit generates no output signal.



This is a solution.

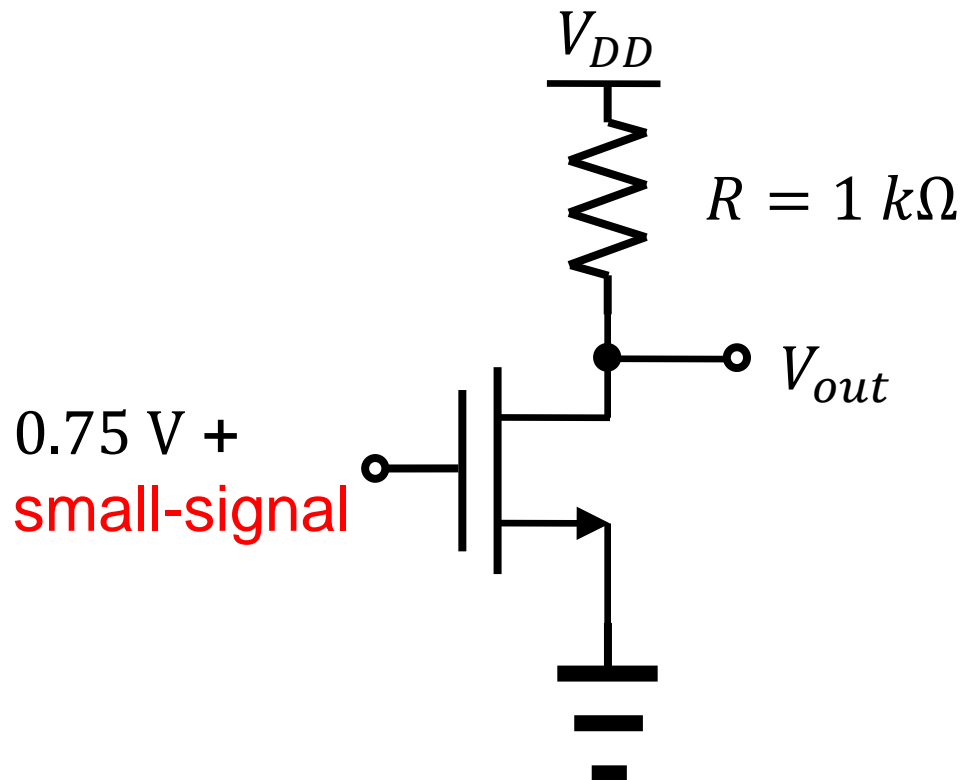- The example 16.7 shows a revised circuit.
 - Then, how can we generate 0.75 V, for example?
 - Use of a separate battery can be a way.



Simple biasing (1/2)


- A better way

- The gate bias voltage is

$$V_{GS} = \frac{R_2}{R_1 + R_2} V_{DD} \quad (17.10)$$


- The drain current is
 
$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \left(\frac{R_2}{R_1 + R_2} V_{DD} - V_{TH} \right)^2 \quad (17.12)$$




Simple biasing (2/2)

 - How to apply the small-signal input
 - Use a capacitor!



Source degeneration (1/2)

 - A resistor placed in series with the source terminal



Source degeneration (2/2)

- Now we have to find the source voltage.
 - (Saturation current of the MOSFET) = (Current flowing through R_S)
 - After a simple manipulation, we can find


$$V_S = V_G + V_1 - V_{TH} - \sqrt{V_1^2 + 2(V_G - V_{TH})V_1}$$

- Here,

$$V_1 = \frac{1}{\mu_n C_{ox} \frac{W}{L} R_S}$$

Self-biasing

 
- Already covered in Example 6.13.
 - Always in the saturation region.



Gate and drain are tied.







Biasing of PMOS devices

 - Different polarity
 - The amount of “gate overdrive” is 1.2 V.
 - It is not 0.6 V.









CMOS amplifiers (1/2)

      - Select one input. Then, select one output.
 - What are possible topologies?




CMOS amplifiers (2/2)

      - Only three are possible.
 - Each of them has own name.




Common-source

- Source terminal is grounded.

 

Small-signal model

 - Let's draw the small-signal model together!



Gain


- Now, calculate the v_{out} .

- KCL for the v_{out} node gives

$$v_{out} = -g_m(R_D || r_o)v_{in}$$

- Therefore, the voltage gain, A_v , is

$$A_v = -g_m(R_D || r_o)$$

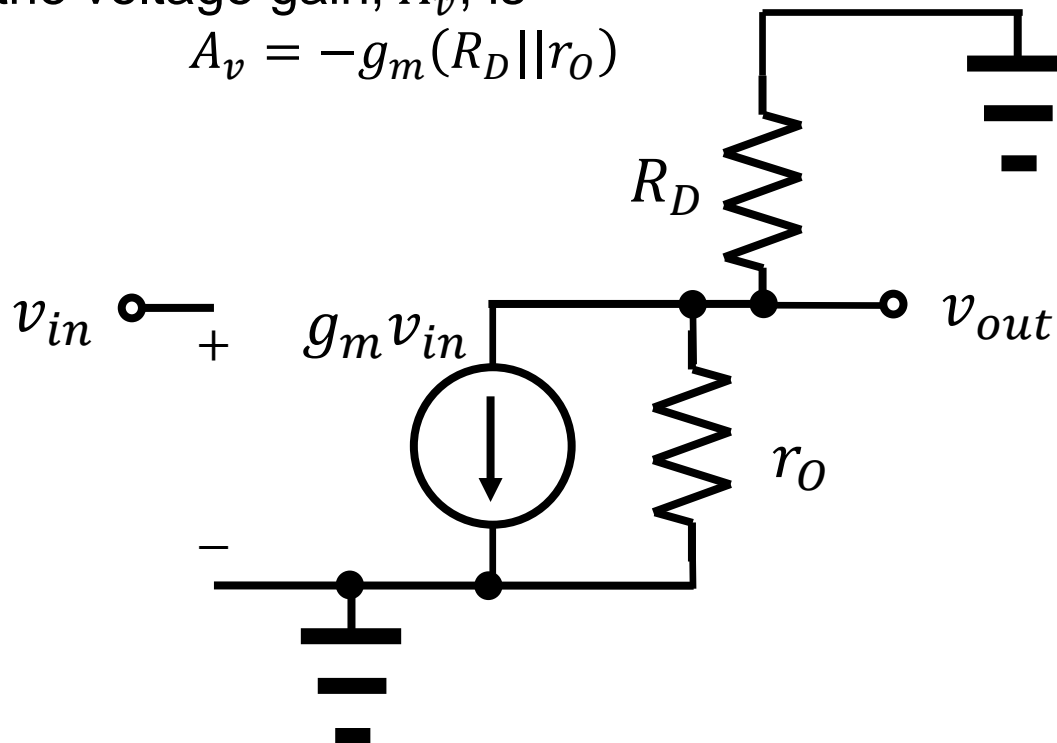


Input/output impedances

- Input impedance

$$R_{in} = \infty$$

- Output impedance

$$R_{out} = R_D || r_o$$

 

Current-source load

- When $R_D \rightarrow \infty$,
 - The gain can be maximized.

