
Lecture23: CMOS inverter

Sung-Min Hong (smhong@gist.ac.kr)

Semiconductor Device Simulation Lab.
School of Electrical Engineering and Computer Science
Gwangju Institute of Science and Technology

RC circuit


- Consider a serial RC circuit.

- The KCL states

$$\frac{V_{out} - V_{in}}{R} + C \frac{dV_{out}}{dt} = 0$$


- Assume a step-wise change of V_{in} at $t = 0$. It becomes V_{DD} .
 - Initial output voltage is V_0 .
 - Its solution is given by
 
$$V_{out}(t) = V_{DD} + (V_0 - V_{DD}) \exp\left(-\frac{t}{RC}\right)$$




Speed of inverter (1/4)

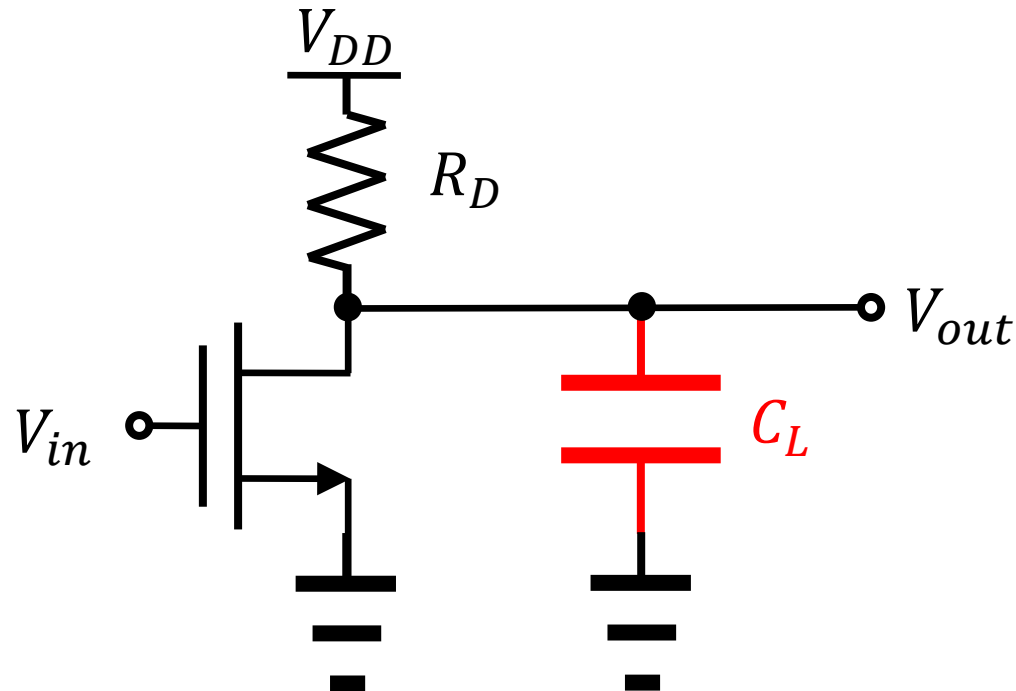- VTC merely describes the DC behavior.
 - Input voltages with different frequencies (1 kHz, 1 MHz, 1 GHz, ...)
 - Time-dependent behavior



Speed of inverter (2/4)

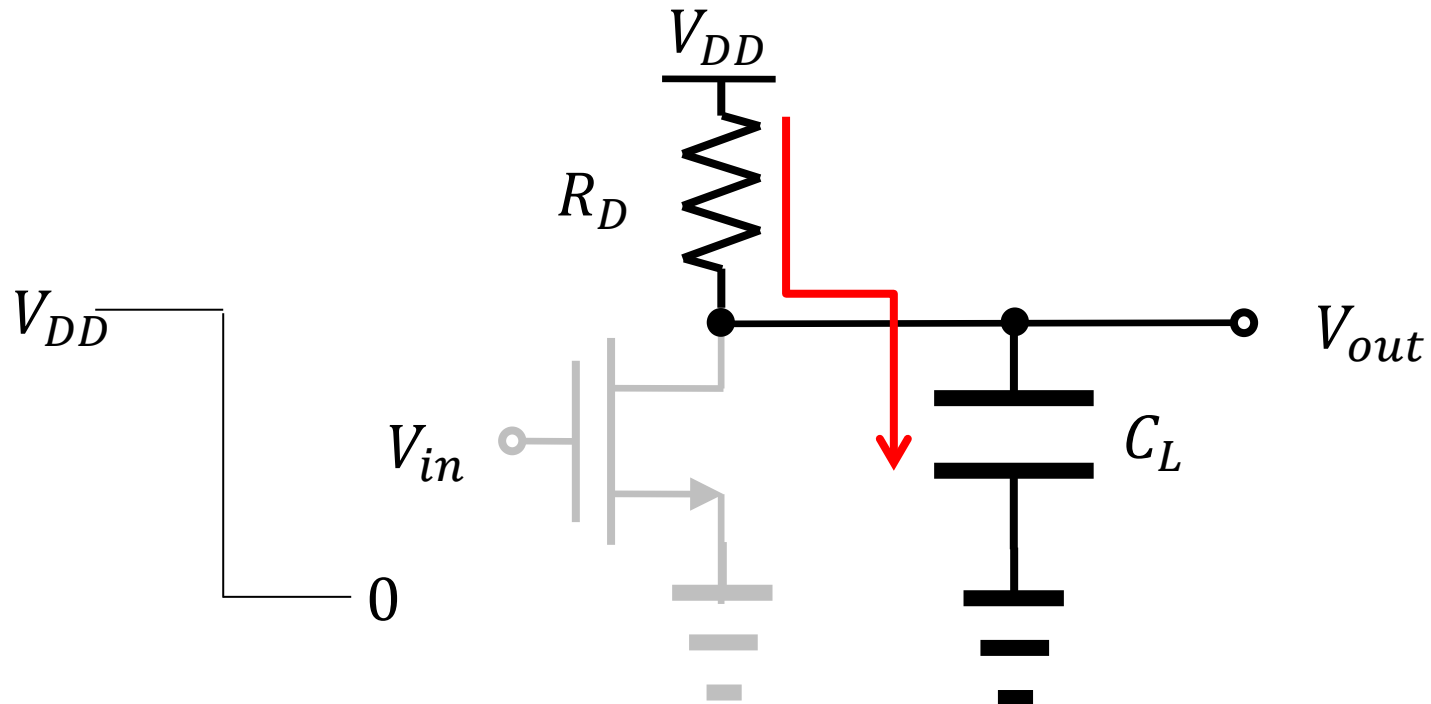- A rapid transition of V_{in} from V_{DD} to 0
 - The capacitor should be charged.



Speed of inverter (3/4)

- Simply, it is a RC circuit.

- Then, the solution is simply


$$V_{out}(t) = V_{out}(0^-) + [V_{DD} - V_{out}(0^-)] \left(1 - \exp \frac{-t}{R_D C_L} \right)$$

- Since $\exp(-3) \approx 0.05$, after $3R_D C_L$, V_{out} reaches $0.95 V_{DD}$.
 - Yes, it takes time to get the stable output voltage...
 - The delay restricts the maximum signal frequency.

Speed of inverter (4/4)


- A rapid transition of V_{in} from 0 to V_{DD} to 0
 - At the initial phase, the resistor does not conduct.
 - Also the MOSFET is operated in its saturation mode. Then,
 
$$I_{D,sat} + C_L \frac{dV_{out}}{dt} = 0$$



Origin of C_L ?

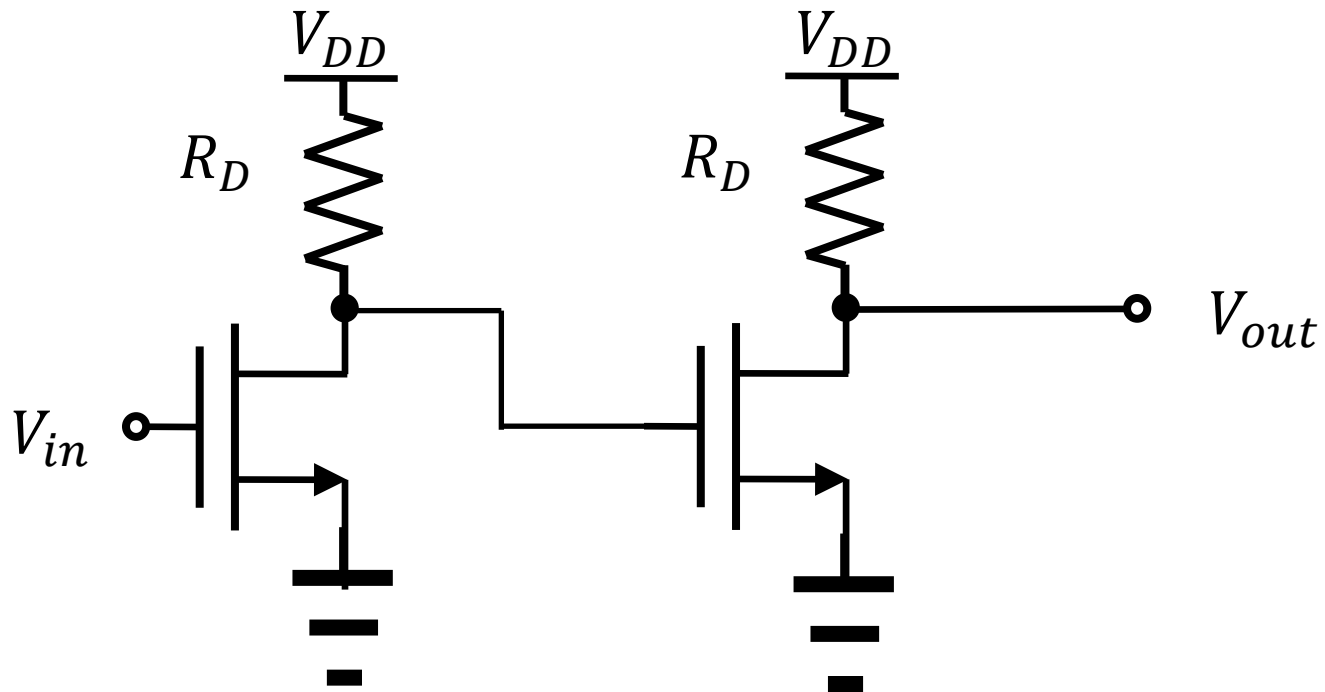- Consider an inverter chain.
 - Then, what is the load capacitance for the first stage?




- Interconnect

Standby(!) power

- The biggest problem in the NMOS inverter
 - When $V_{in} = 0$, no standby power
 - When $V_{in} = V_{DD}$?
 - The power consumption is (approximately) $\frac{V_{DD}^2}{R_D}$.
 - If $V_{DD} = 1.8 \text{ V}$ and $R_D = 10 \text{ k}\Omega$,
324 μW !
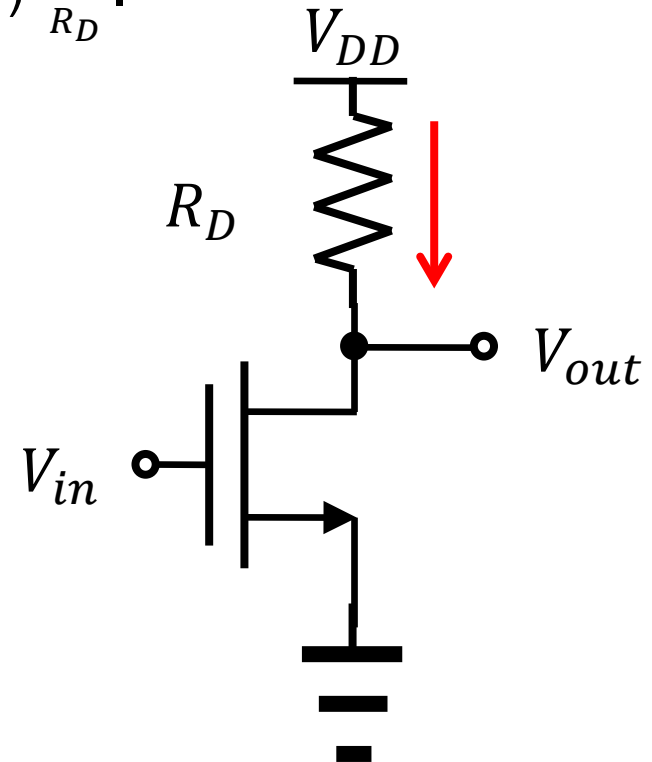
$$I_D = \frac{V_{DD} - V_{out}}{R_D} \approx \frac{V_{DD}}{R_D}$$



NMOS inverter

- Passive “pull-up” device

- (a) Degradation of output level

Too small R_D , when $V_{in} = V_{DD}$.

In this case, large R_D is desirable.

- (b) Risetime limitation

Too small current for 1 \rightarrow 0 transition. ($V_{in} = 0$)


In this case, a better capability to charge the C_L is desirable.

- (c) Static power consumption

No ability to block the current, when $V_{in} = V_{DD}$.


In this case, no current conduction is desirable.

- (a) & (c) \leftrightarrow (b)

 


CMOS inverter

 - Ideal “pull-up” should have the following properties.
 - When $V_{in} = V_{DD}$, no current conduction.
 - When $V_{in} = 0$, improved current conduction.
- PMOS can do those jobs!





CMOS inverter

 - Voltage transfer curve of a CMOS inverter




Noise margin?

  - Greatly improved!
 - Steeper transition




Speed of CMOS inverter (1/4)

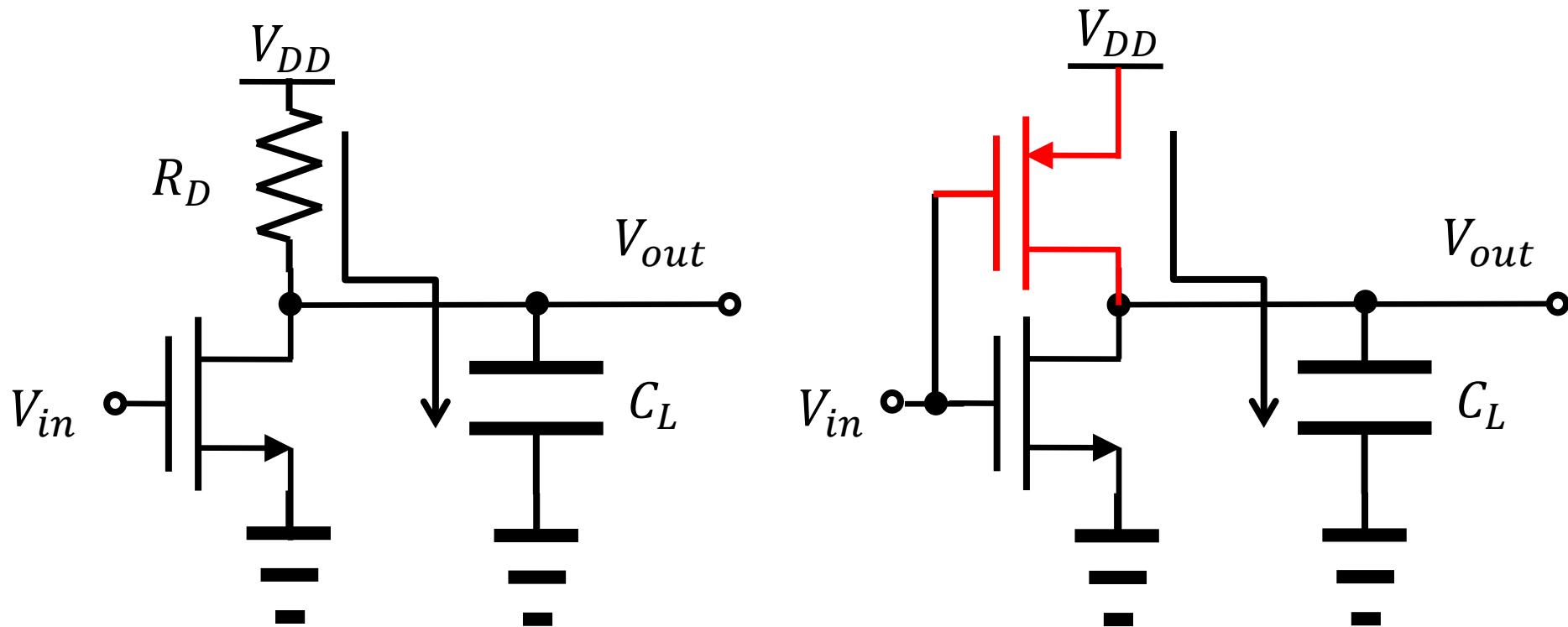- Consider the input transition from HIGH to LOW.
 - Instead of the resistor (R_D), now the PMOS pulls up the V_{out} .



Speed of CMOS inverter (2/4)

 - Guess the charging speed.
 - The PMOS current matters. ($I_{PMOS} = C_L \frac{dV_{out}}{dt}$)
 - Initially, the PMOS is in the saturation.
 - Later, the PMOS is in the triode.
 - When does the transition happen?
- $V_{in} - V_{DD} - V_{TH2} = V_{out} - V_{DD}$
- Therefore, when $V_{out} = -V_{TH2}$




Speed of CMOS inverter (3/4)

- The first case (charge up to $-V_{TH2}$)
 - PMOS saturation current (constant)
 - Time to reach $|V_{TH2}|$

$$T_{PLH1} = \frac{C_L |V_{TH2}|}{\frac{1}{2} \mu_p C_{ox} \frac{W}{L} (V_{DD} - |V_{TH2}|)^2}$$

$$T_{PLH1} = R_{on2} C_L \frac{2|V_{TH2}|}{V_{DD} - |V_{TH2}|}$$

 

Speed of CMOS inverter (4/4)

- The second case (charge up to $\frac{V_{DD}}{2}$)
 - PMOS triode current
$$\frac{1}{2} \mu_p C_{ox} \frac{W}{L} [2(V_{DD} - |V_{TH2}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2] = C_L \frac{dV_{out}}{dt}$$
 - Time to reach $\frac{V_{DD}}{2}$
$$T_{PLH2} = R_{on2} C_L \ln \left(3 - 4 \frac{|V_{TH2}|}{V_{DD}} \right)$$
- The overall propagation delay is
 - $T_{PLH} = R_{on2} C_L \left[\frac{2|V_{TH2}|}{V_{DD} - |V_{TH2}|} + \ln \left(3 - 4 \frac{|V_{TH2}|}{V_{DD}} \right) \right]$

Power consumption

- No static power dissipated!
 - Only the “dynamic” power dissipation is determined.
 - High → Low → High → ...
 - It involves charging and discharging the load capacitance.
 - The energy stored in the load capacitance

$$\frac{1}{2} C_L V_{DD}^2$$

- The energy dissipated by the PMOS is also $\frac{1}{2} C_L V_{DD}^2$.
- Therefore, $C_L V_{DD}^2$ is dissipated during T_{in} .

$$P_{av} = f_{in} C_L V_{DD}^2$$

Homework#10, the final

- Due: 09:00, **June 3 (Mon)**
- Solve the following problems of the final exam in 2018.
 - P26
 - P27
 - P28
 - P29
 - P30