

---

# Lecture22:

## Operational amplifier (1)


Sung-Min Hong ([smhong@gist.ac.kr](mailto:smhong@gist.ac.kr))

Semiconductor Device Simulation Lab.  
School of Electrical Engineering and Computer Science  
Gwangju Institute of Science and Technology
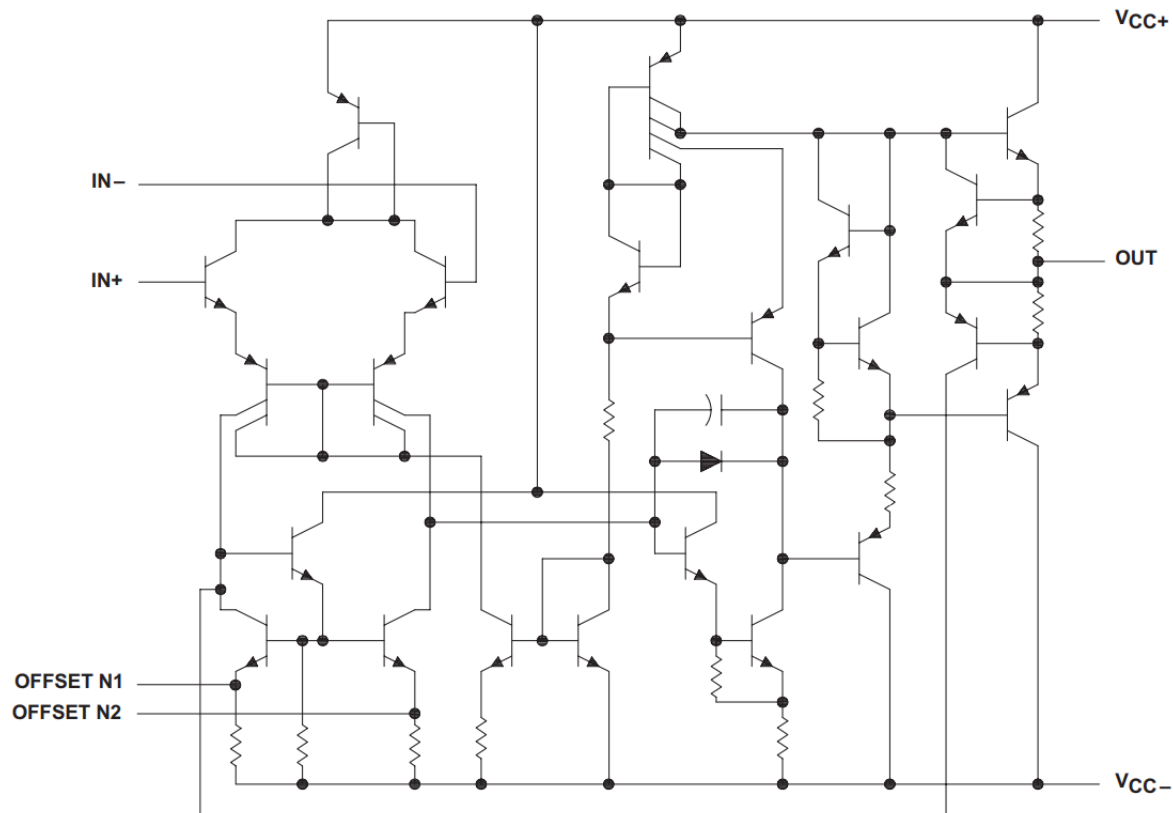
# Operational amplifier

---



- As a black box
  - We will follow Razavi's book.
- Its inside



Circuit schematic of a 741 op amp (Texas Instruments)

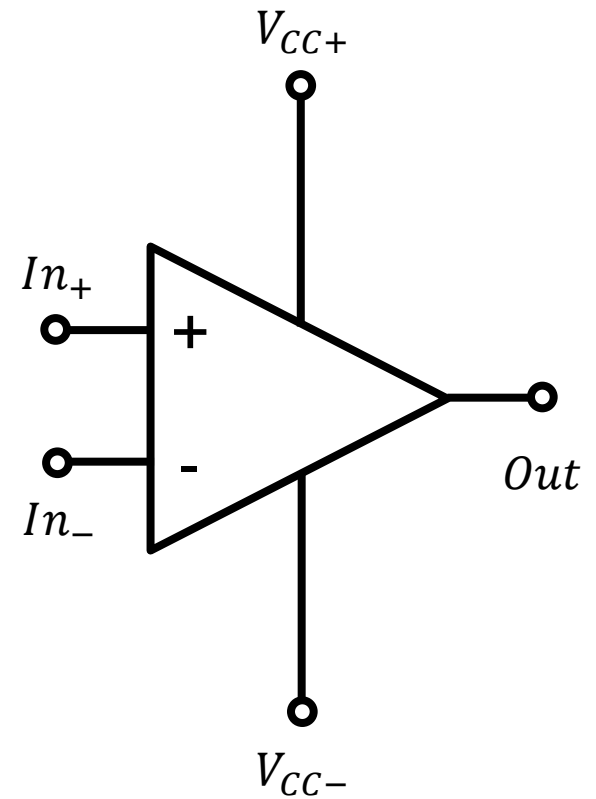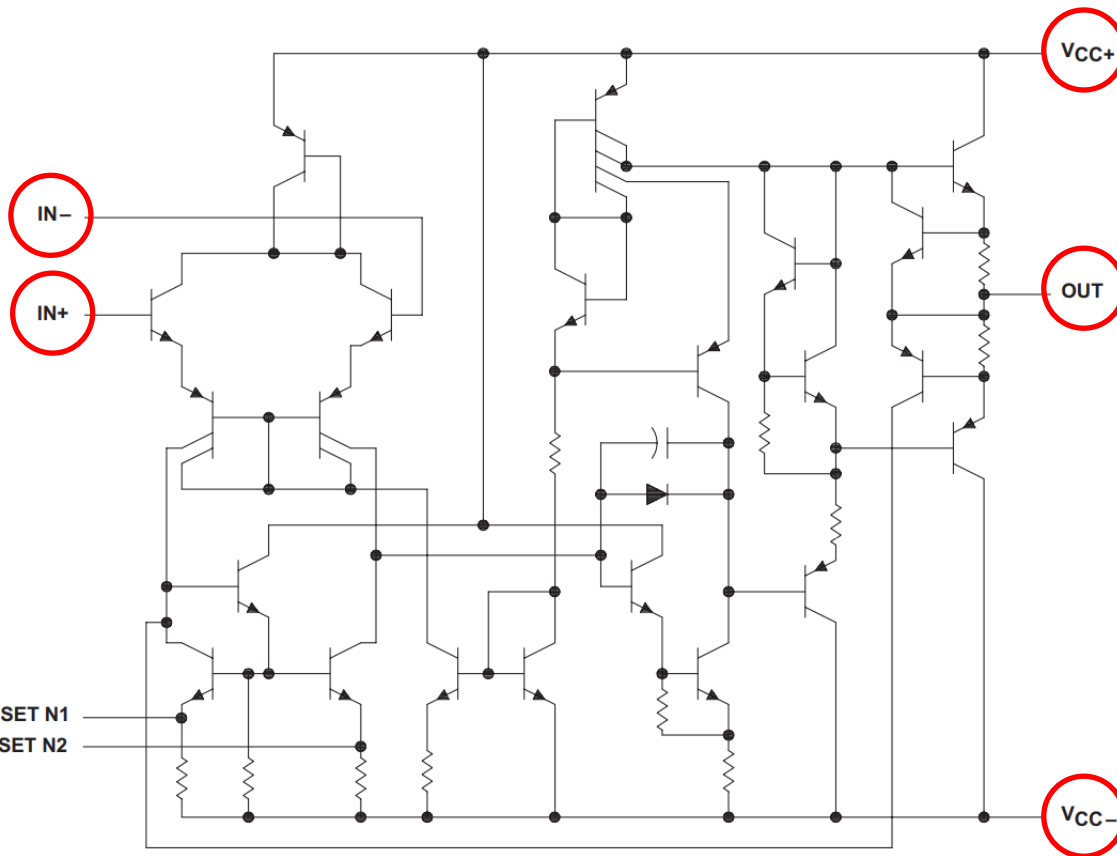
# Symbol

- It is a differential amplifier with a single output.


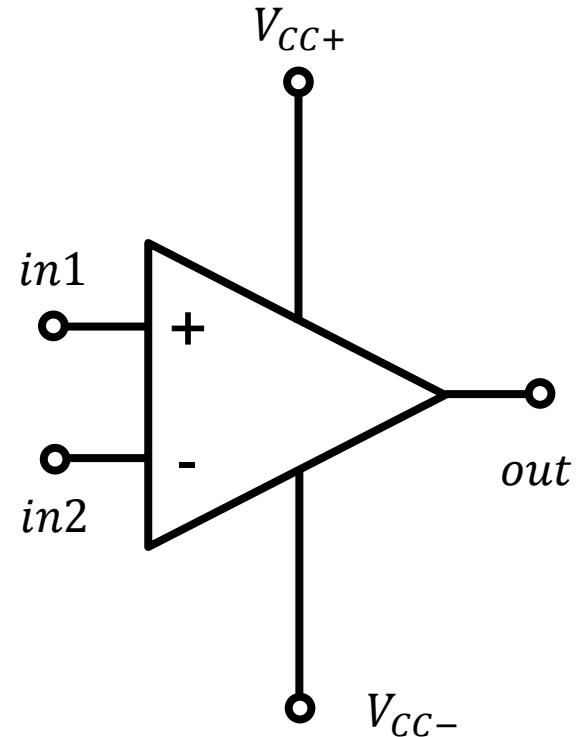
# Operating condition

- In order to operate it,
  - The supply voltage is required.




			MIN	MAX	UNIT
$V_{CC+}$ Supply voltage			5	15	V
			-5	-15	
$T_A$ Operating free-air temperature	$\mu A741C$		0	70	$^{\circ}C$

Recommended operating conditions (Texas Instruments)
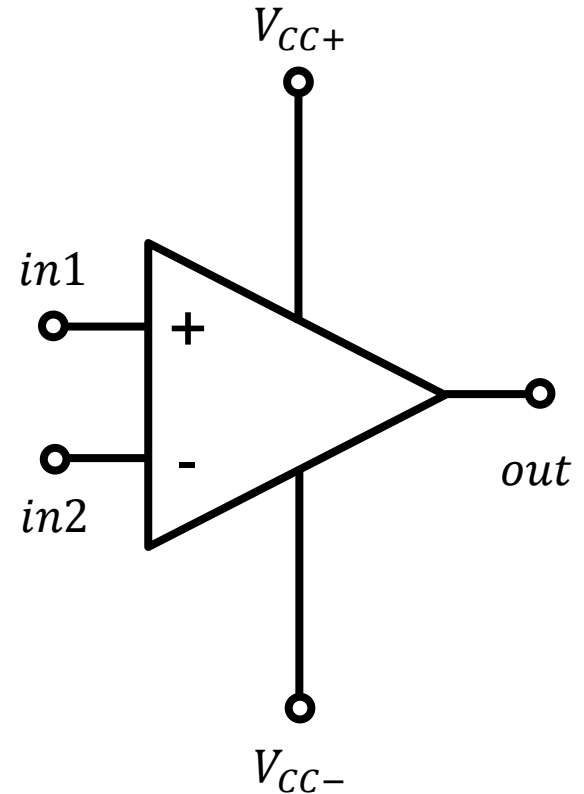
# Open-loop gain

- The open-loop gain,  $A_0$ 
  - The output voltage is given by
$$V_{out} = A_0(V_{in1} - V_{in2})$$
  - Noninverting input:  $V_{in1}$
  - Inverting input:  $V_{in2}$



PARAMETER		TEST CONDITIONS <sup>(1)</sup>		MIN	TYP	MAX	UNIT
$A_{VD}$	Large-signal differential voltage amplification	$R_L \geq 2 \text{ k}\Omega$	25°C	20	200		V/mV
		$V_O = \pm 10 \text{ V}$	Full range	15			

Open-loop gain of a 741 op amp (Texas Instruments)

# Very large open-loop gain


---

- If the output voltage is bounded,
  - The difference between two inputs is also bounded.

$$V_{out} = A_0(V_{in1} - V_{in2})$$

- Since the open-loop gain is very large,
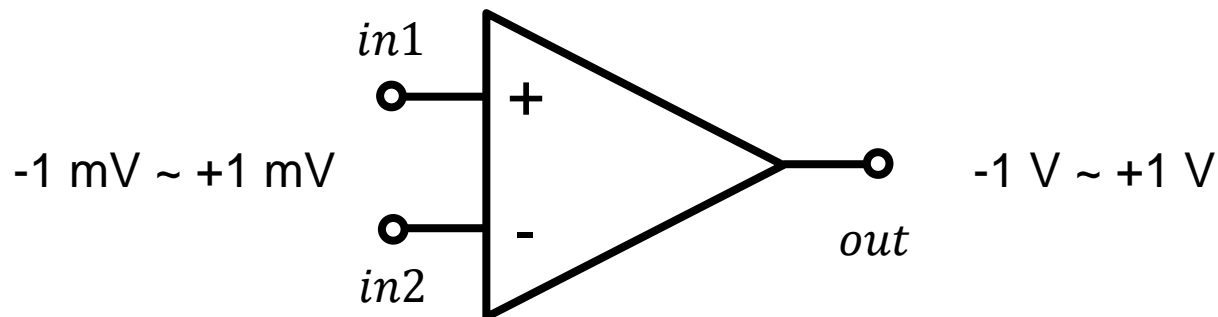
$$V_{in1} - V_{in2} = \frac{V_{out}}{A_0} \approx 0$$



An example) Open-loop gain of 1000

# Input/output resistances

---

- Input resistance
  - It is very large.
- Output resistance
  - It is very small.



PARAMETER		TEST CONDITIONS <sup>(1)</sup>		MIN	TYP	MAX	UNIT
$r_i$	Input resistance	25°C		0.3	2		MΩ
$r_o$	Output resistance	$V_O = 0$ ; see <sup>(2)</sup>	25°C		75		Ω

Input/output resistances of a 741 op amp (Texas Instruments)

- “Ideal” op amp
  - Infinite voltage gain
  - Infinite input impedance
  - Zero output impedance
  - Infinite speed
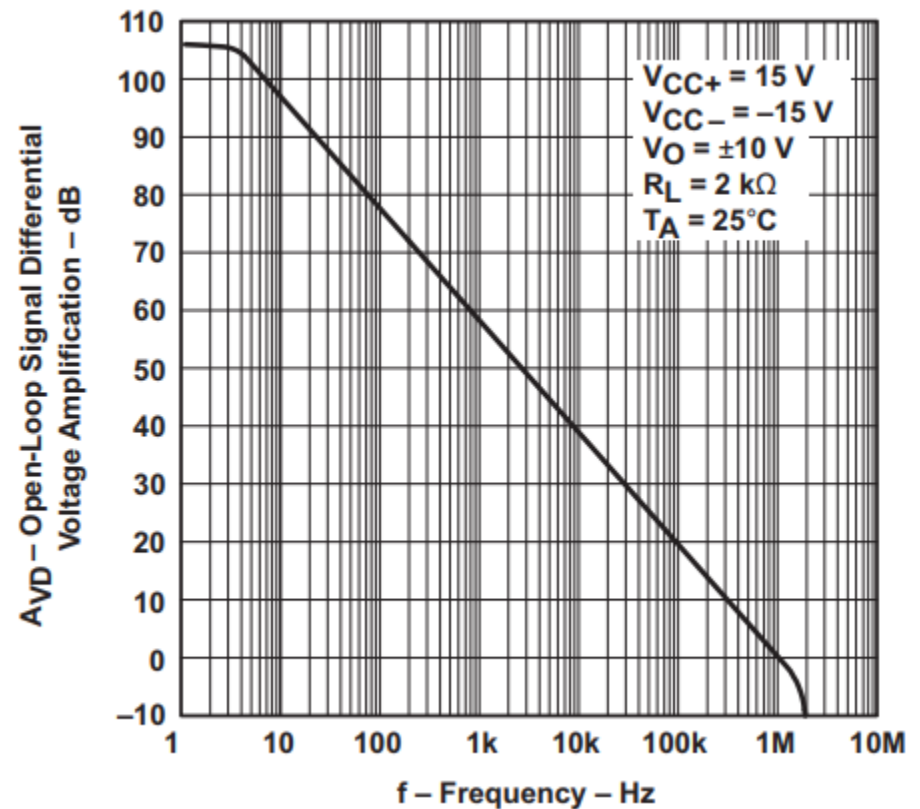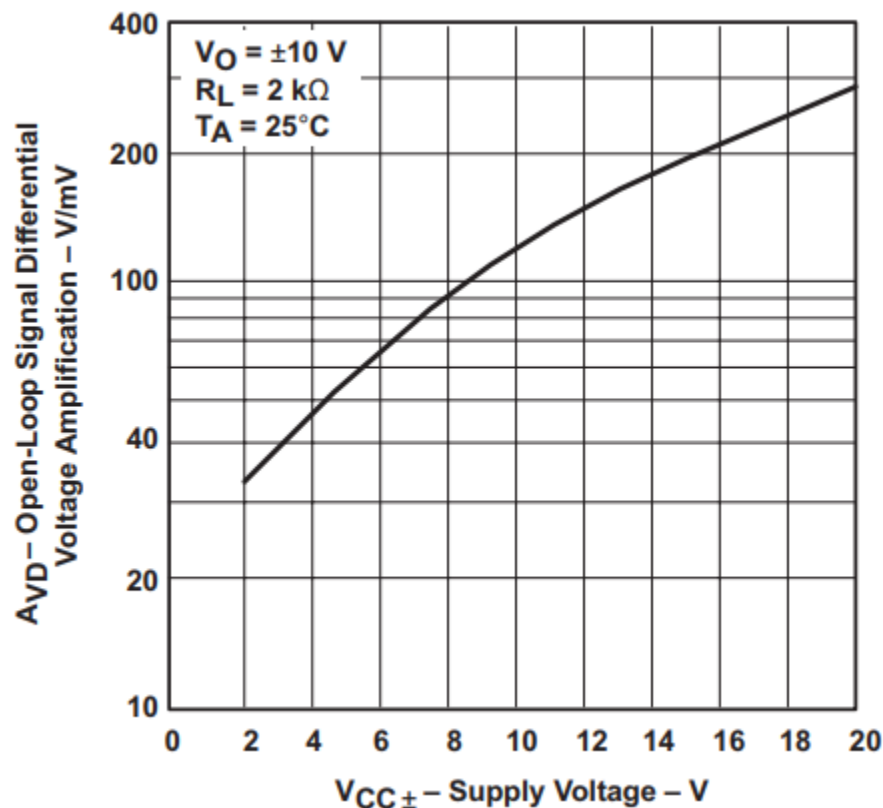
# Typical characteristics

- Graphs taken from the Texas Instruments' datasheet.






# Example 8.1

---

- “Unit-gain” buffer
  - What is  $V_{out}$ ?

$$V_{out} = A_0(1 - V_{out})$$

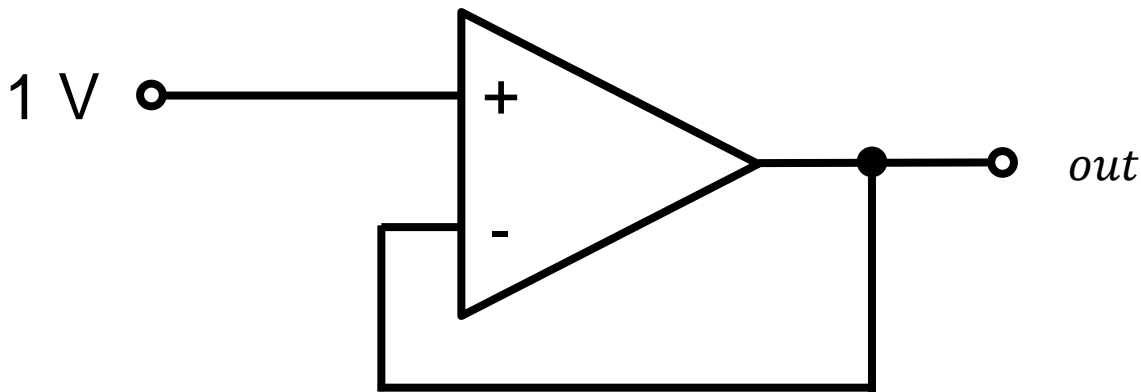

# Homework#10 (Last one)

---

- Due: 09:00, June 4
- Solve the following problems of the final exam in 2017.
  - P44
  - P45
  - P46
  - P47
  - P48
  - P49
  - P50