

---

# Lecture22:

## Bipolar amplifiers (1)

Sung-Min Hong ([smhong@gist.ac.kr](mailto:smhong@gist.ac.kr))

Semiconductor Device Simulation Lab.  
School of Information and Communications  
Gwangju Institute of Science and Technology

# Final exam

---


- June 10 (Wed)
  - PM 01:00 ~ 02:14 (Class time)
- Lecture schedule
  - L22 (Today): BJT amplifiers
  - For remaining 4 lectures, op amp and digital circuits will be covered.

# Small-signal model

---

- Useful expressions

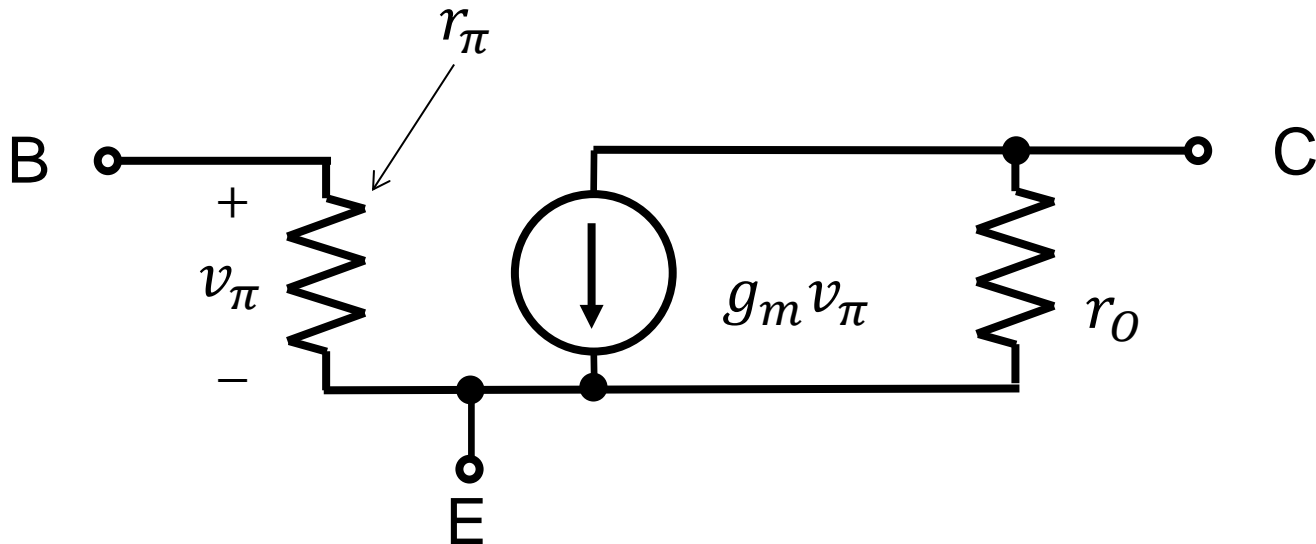
$$g_m = \frac{I_C}{V_T}$$
$$r_\pi = \frac{\beta}{g_m}$$
$$r_o \approx \frac{V_A}{I_C}$$



# Biasing

---

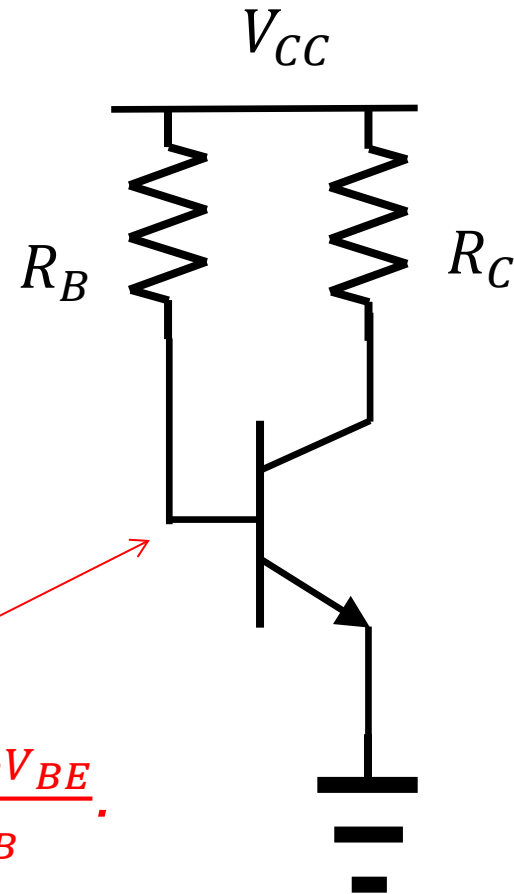- Example 5.7
  - DC analysis?
  - (Recall its MOS counterpart.)
  - Specific values
    - $V_{CC} = 2.5 \text{ V}$
    - $R_B = 100 \text{ k}\Omega$
    - $R_C = 1 \text{ k}\Omega$



*Voltage?*

*It would be  $\frac{V_{CC} - V_{BE}}{R_B}$ .*

# Self-biased stage


---

- Which one is higher?
  - Collector voltage or base voltage?
  - In the forward active region!

$$I_C = \frac{V_{CC} - V_{BE}}{R_C + \frac{R_B}{\beta}} \quad \leftarrow \text{Why?}$$

- Uncertain  $V_{BE}$  and  $\beta$
- What can we do?

$$R_C \gg \frac{R_B}{\beta}$$

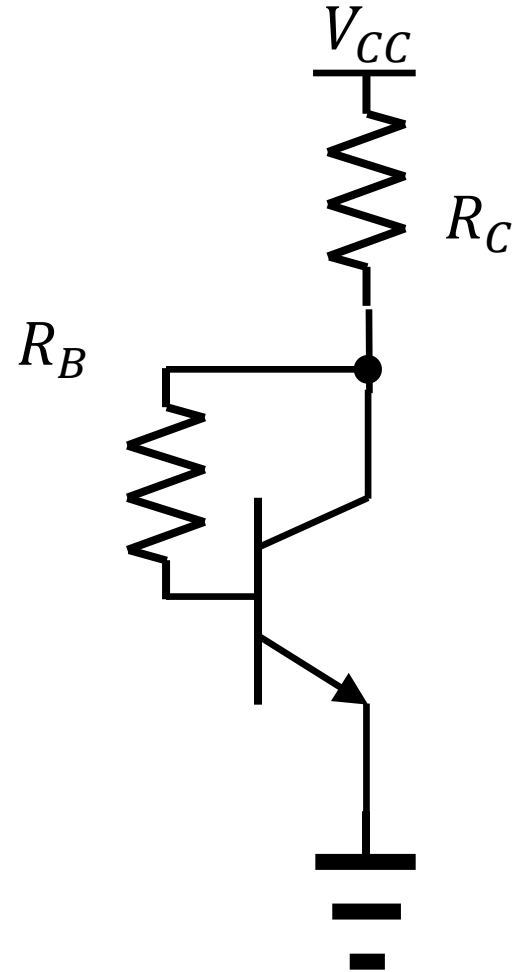

# Example 5.14


- Design the self-biased stage.

- In this example, we assume

$$R_C \approx 10 \frac{R_B}{\beta}$$



- It means  $I_C = \frac{V_{CC} - V_{BE}}{1.1 R_C}$ .
  - We want to have  $g_m$  of  $\frac{1}{13 \Omega}$  in this example.
  - For BJTs,  $g_m = \frac{I_C}{V_T}$ . Therefore,  $I_C = 2 \text{ mA}$ .
  - Then,
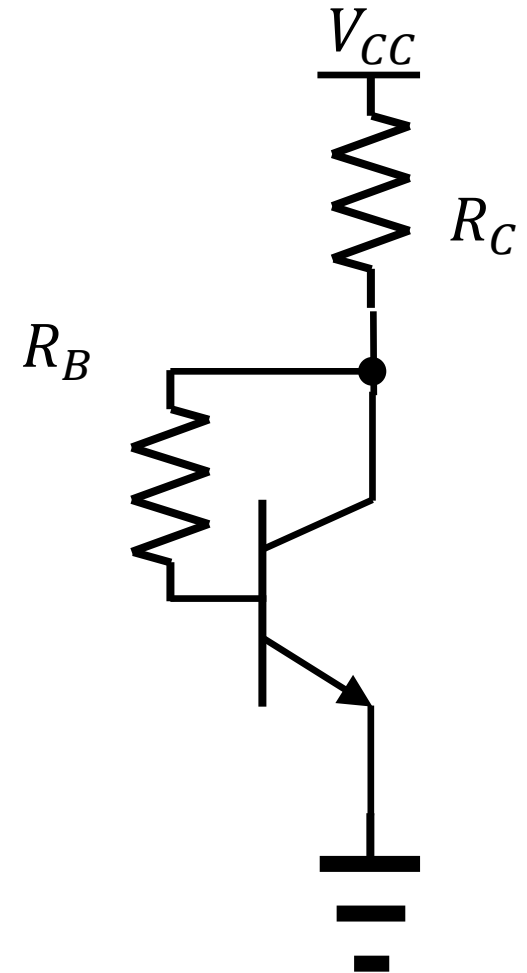
$$R_C \approx \frac{V_{CC} - V_{BE}}{1.1 I_C} = 475 \Omega$$


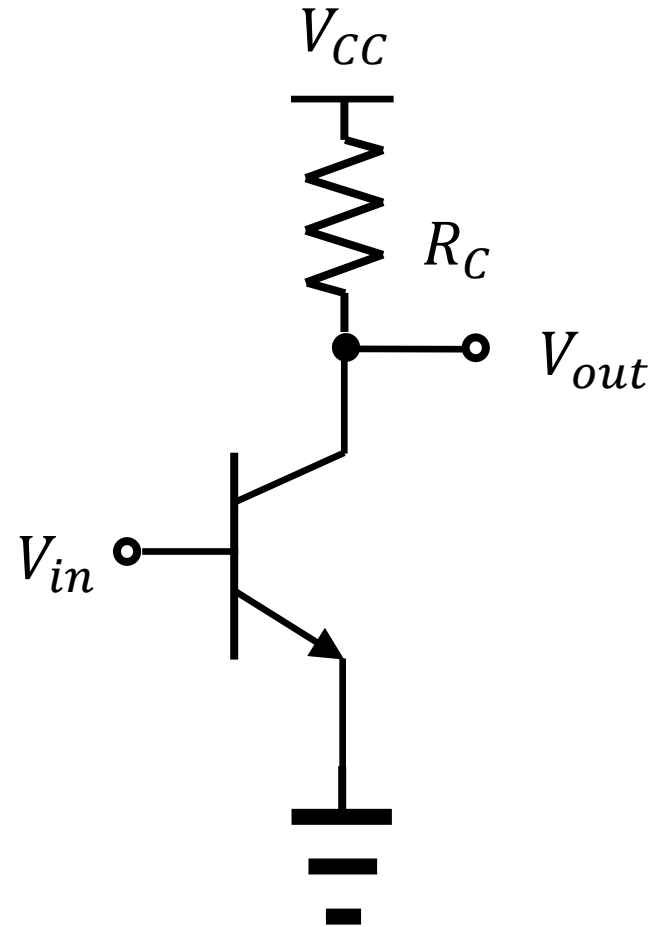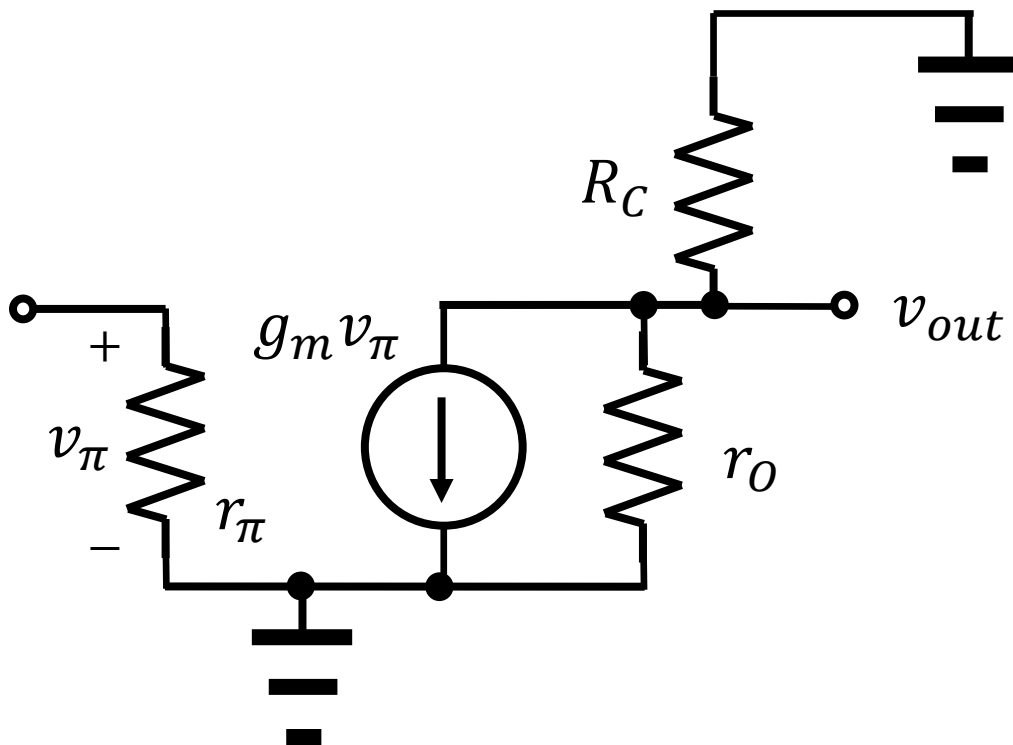
# Common-emitter (1/2)

- You can easily imagine that
  - There is a common-emitter configuration.



# Common-emitter (2/2)

---

- Voltage gain?

- Same with the CS stage:

$$A_v = -g_m(R_C || r_o)$$

- Impedances?

- Input impedance

$$R_{in} = r_{\pi} = \frac{\beta}{g_m}$$

- Output impedance

$$R_{out} = R_C || r_o$$



# Common-emitter (2/2)

---

- Voltage gain?

- Same with the CS stage:

$$A_v = -g_m(R_C || r_O)$$

- When we have a very large  $R_C$ ,  $A_v \rightarrow -g_m r_O$ .

- For BJTs,  $g_m = \frac{I_C}{V_T}$  and  $r_O = \frac{V_A}{I_C}$ .

- Impedances?

- Input impedance

$$R_{in} = r_\pi = \frac{\beta}{g_m}$$

- Output impedance

$$R_{out} = R_C || r_O$$

# Example 5.21

---

- Collector current of 1 mA and  $R_C = 1\text{ k}\Omega$ .

- Then,  $g_m$  is readily available.

$$g_m = \frac{1}{26\ \Omega}$$

- When, the Early voltage is 10 V,  $r_o = \frac{10\text{ V}}{1\text{ mA}} = 10\text{ k}\Omega$ .

- Overall,  $R_C || r_o = \frac{1}{1.1}\text{ k}\Omega \approx 0.91\text{ k}\Omega$ .