

---

# Lecture19:

# Common-gate amplifier

Sung-Min Hong ([smhong@gist.ac.kr](mailto:smhong@gist.ac.kr))

Semiconductor Device Simulation Lab.  
School of Electrical Engineering and Computer Science  
Gwangju Institute of Science and Technology

# Configurations

---


- Three terminals of the MOSFET
  - The common terminal, the input terminal, and the output terminal

Source	Gate	Drain	Remark
Common	Input	Output	Common-source amp.
Common	Output	Input	X
Input	Common	Output	It will be covered.
Output	Common	Input	X
Input	Output	Common	X
Output	Input	Common	It will be covered.
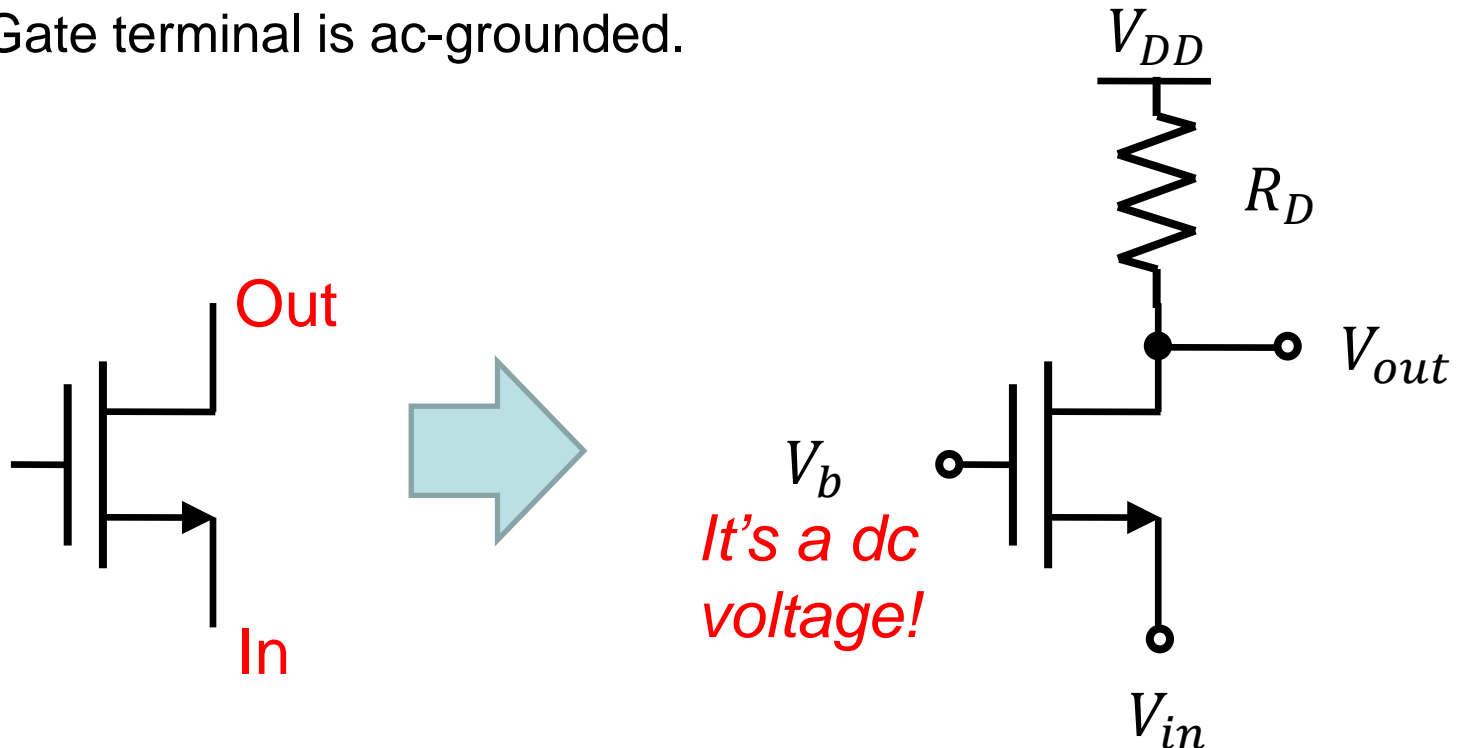
# Common-gate amplifier

---


- Why do we study other amplification topologies?
  - Different circuit properties
- Common-gate amplifier
  - Gate terminal is ac-grounded.


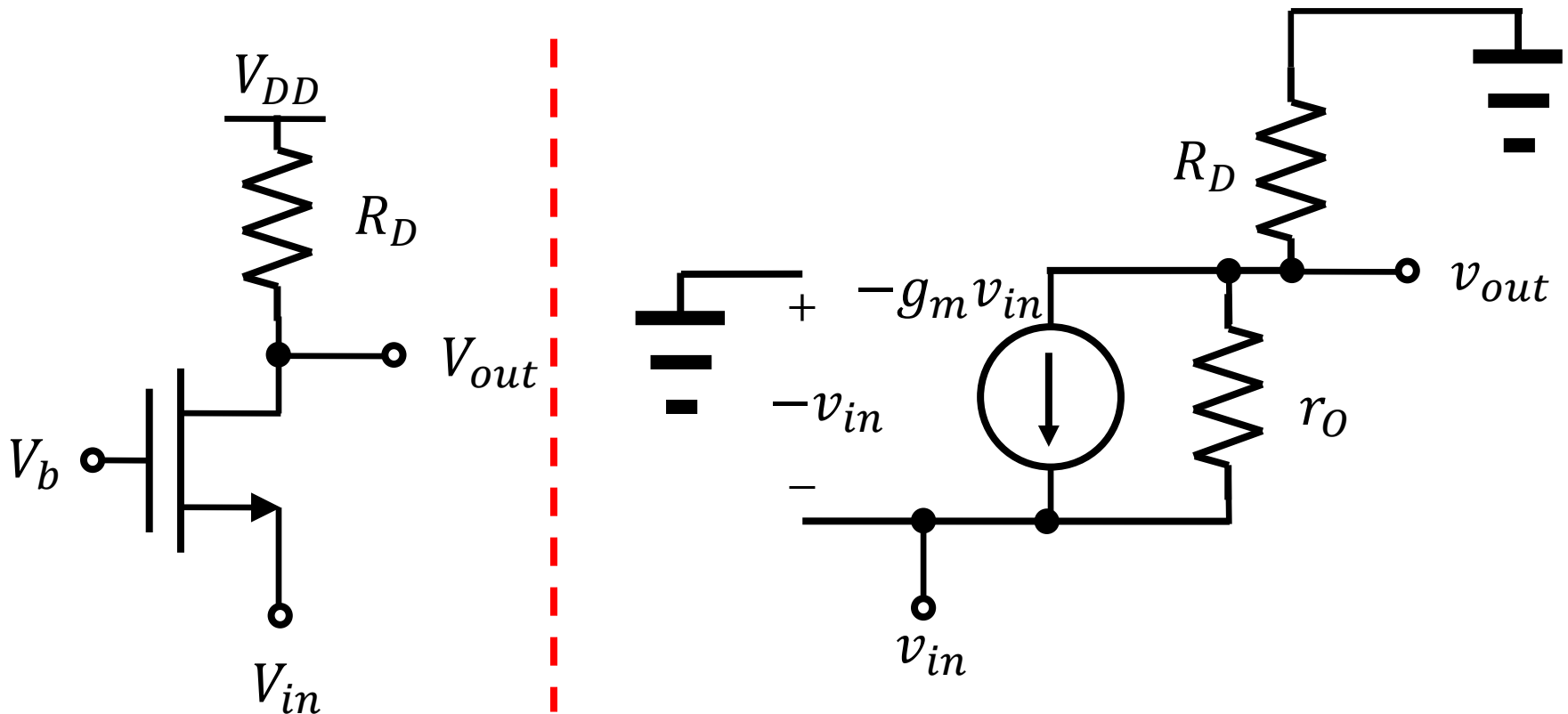
# Small-signal model

---

- Let's draw the small-signal model together!



# Gain & input impedance (1/2)

- Neglect the output resistance,  $r_o$ .


- Voltage gain

$$A_v = +g_m R_D$$

- Input impedance

$$R_{in} = \frac{1}{g_m}$$

*It's small!*

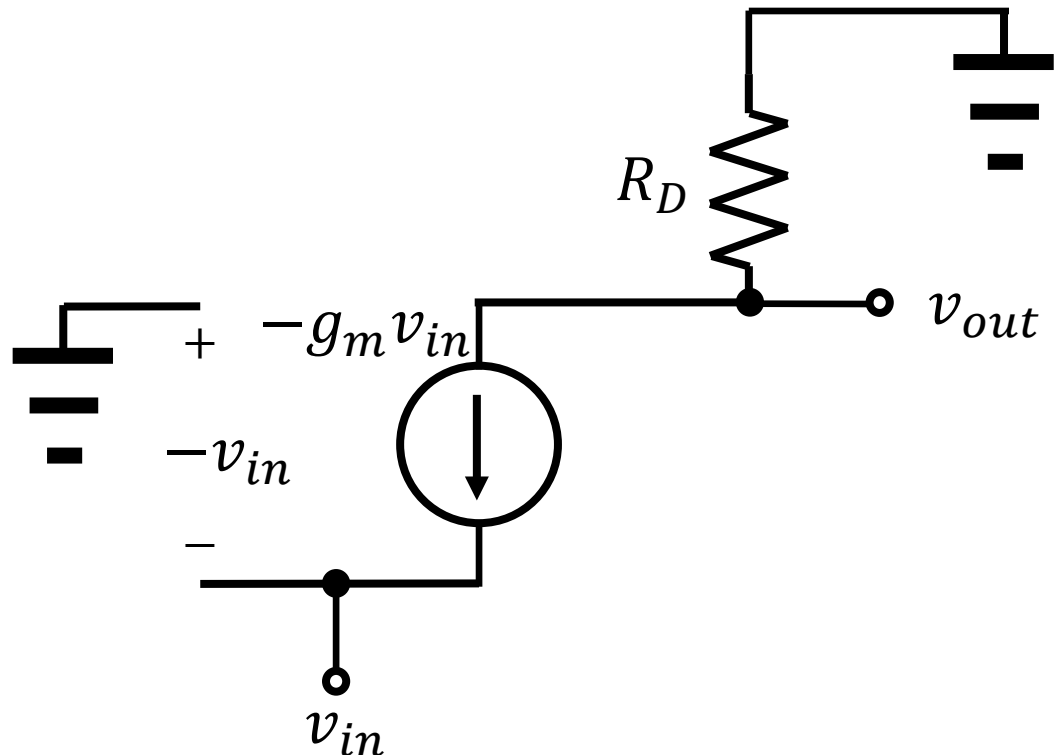

# Gain & input impedance (2/2)

- Consider the output resistance,  $r_o$ .


- Voltage gain

$$A_v = + \left( g_m + \frac{1}{r_o} \right) (R_D || r_o)$$

- Input impedance


$$R_{in} = \frac{r_o + R_D}{g_m r_o + 1}$$

*It's small!*

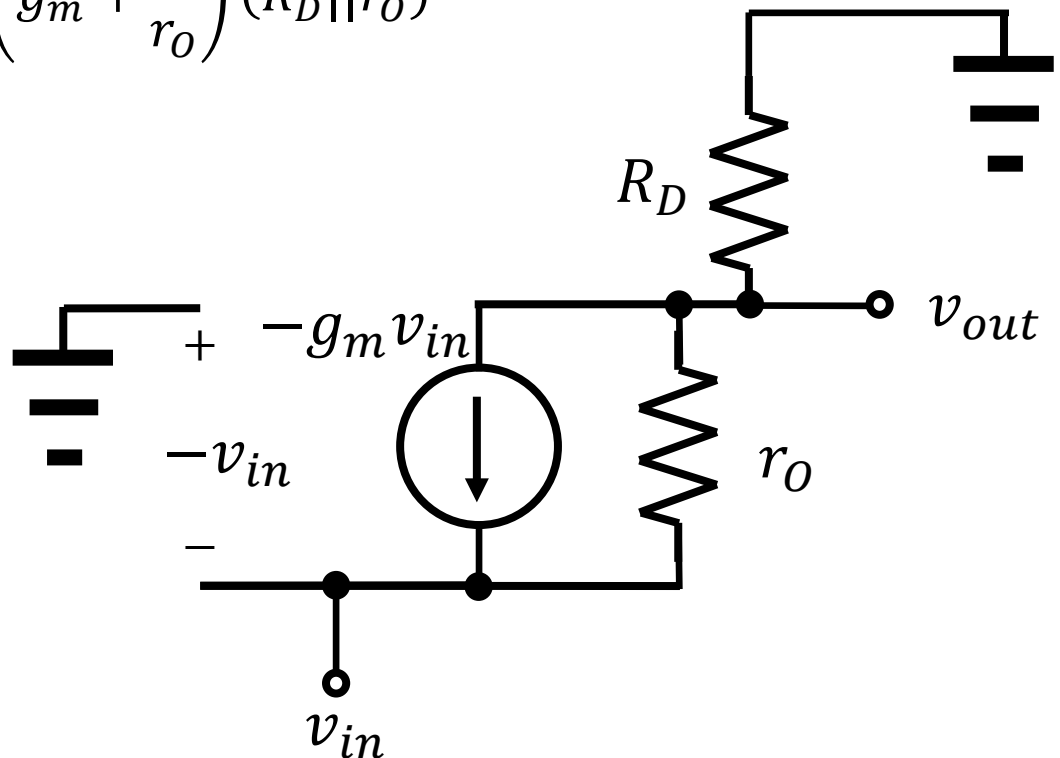


# Output impedance

- Without a finite source resistance,  $R_{out} = r_o || R_D$

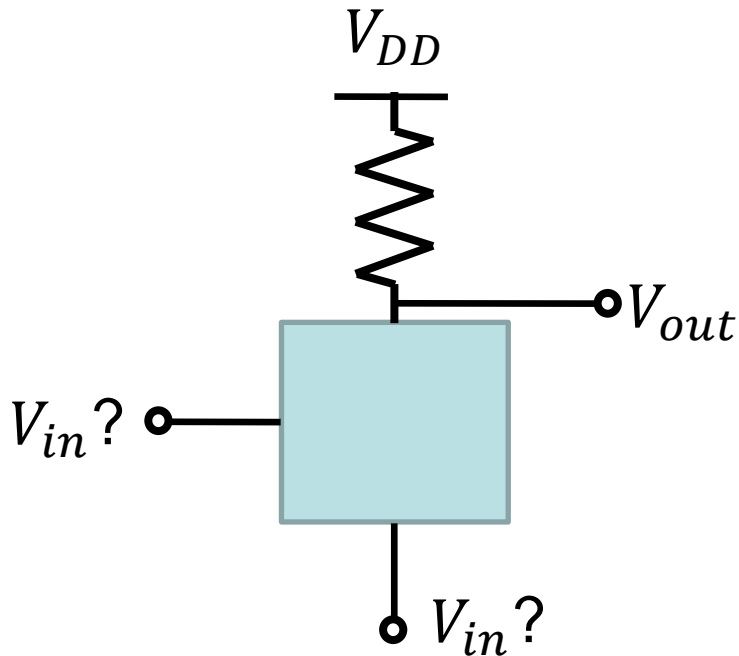

Generic form of CS and CG stages



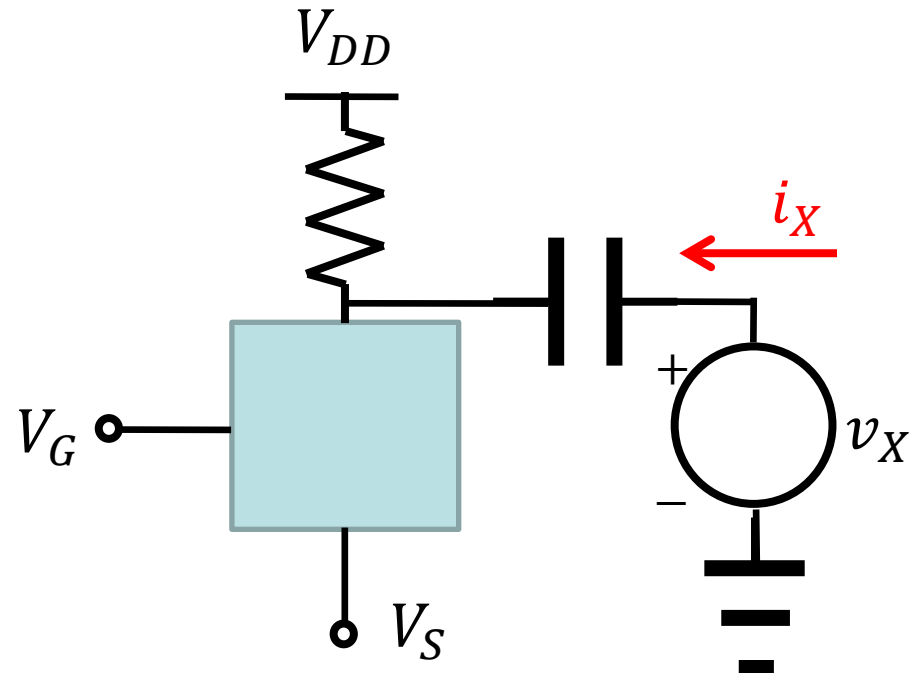


Setting for calculating  $R_{out}$
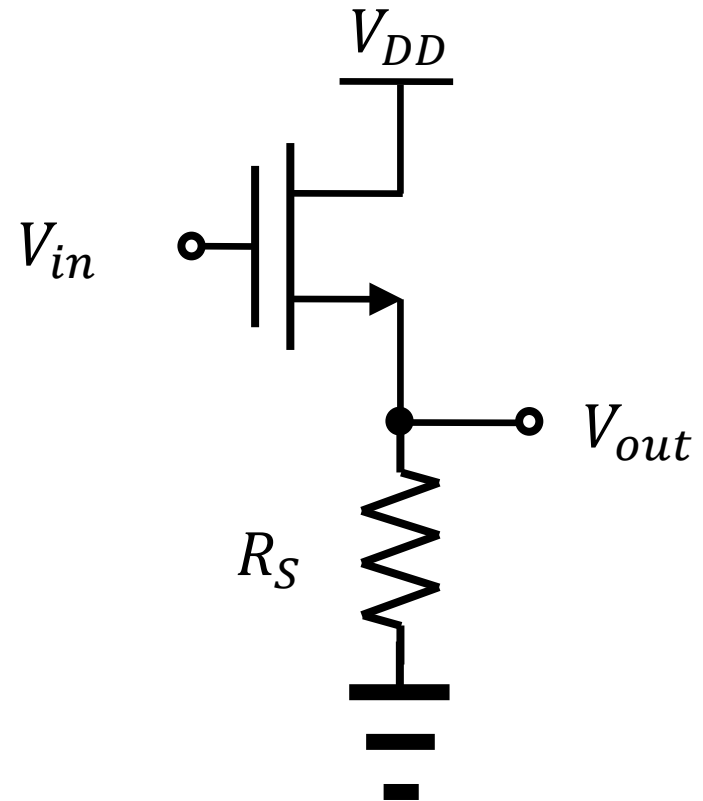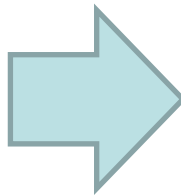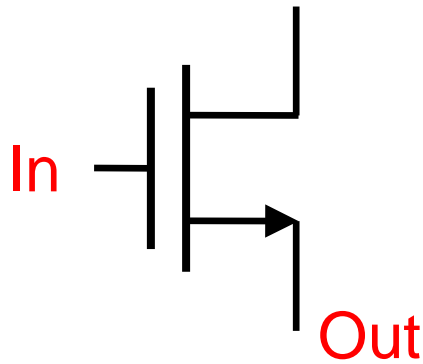
# Source follower

---

- Also called the “common-drain” stage
  - The drain is ac grounded.
- Wait a minute!
  - Is it a real amplifier?






# Its core

---

- Gain is less than 1?? (Neglecting  $r_o$ )

$$A_v = + \frac{g_m R_S}{1 + g_m R_S}$$

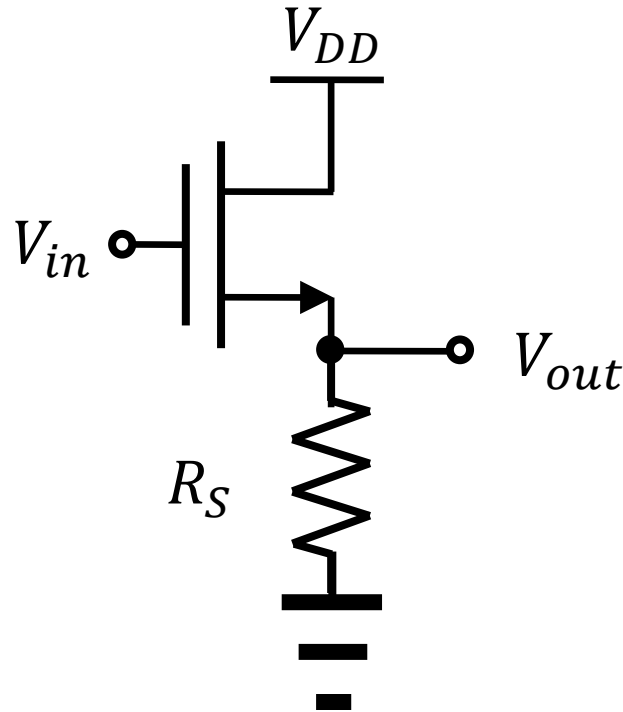

*You should be able to draw the small-signal model.*


# Useless?

---

- Calculate the input and output impedances.
  - Since the gate is the input terminal, the input impedance is very high at low frequencies.
  - How about the output impedance?

$$R_{out} = \frac{1}{g_m} || r_o || R_S$$

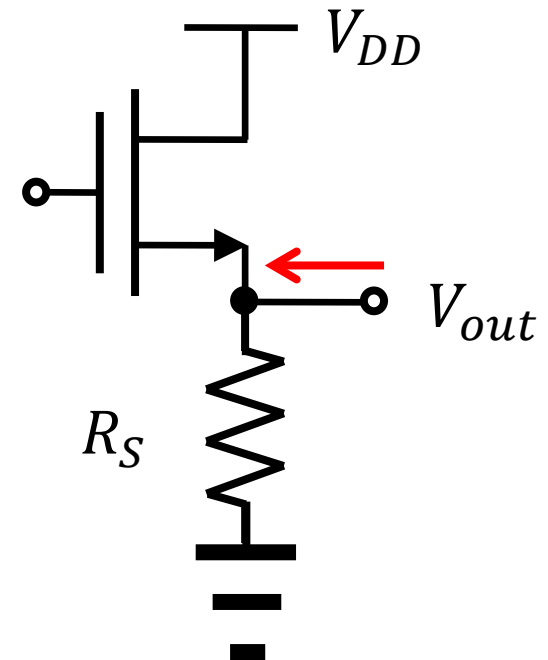
- It is relatively low.
- High input imp., low output imp.
  - They can serve as good “buffers.”


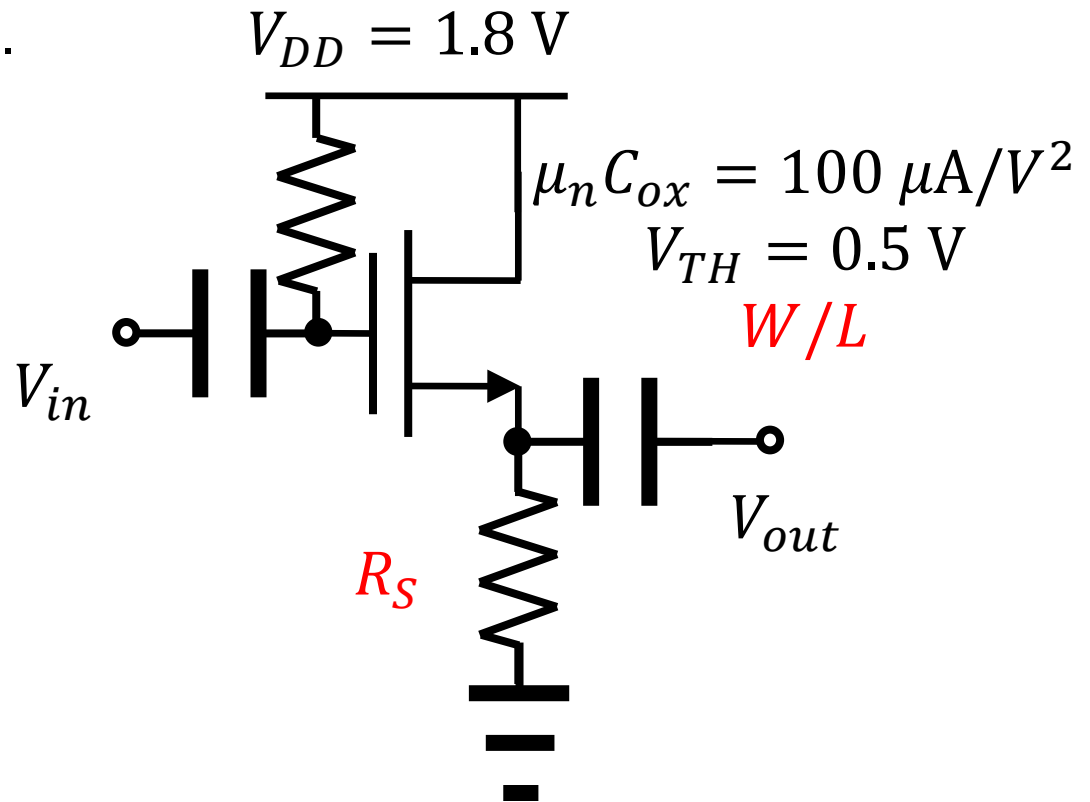
# Razavi, example 17.39

---

- Design the source follower.
  - Determine  $W/L$  and  $R_S$ .
  - The DC drain current is 1 mA.
  - The voltage gain is 0.8.



# Homework#8 (Again)

---

- Due: 09:00, **May 20 (Mon)**
- Solve the following problems of the final exam in 2017.
  - P33
  - P34
  - P38
  - P39
  - P40
  - P41