

---

# Lecture1: Circuit theory


Sung-Min Hong ([smhong@gist.ac.kr](mailto:smhong@gist.ac.kr))

Semiconductor Device Simulation Lab.  
School of Electrical Engineering and Computer Science  
Gwangju Institute of Science and Technology
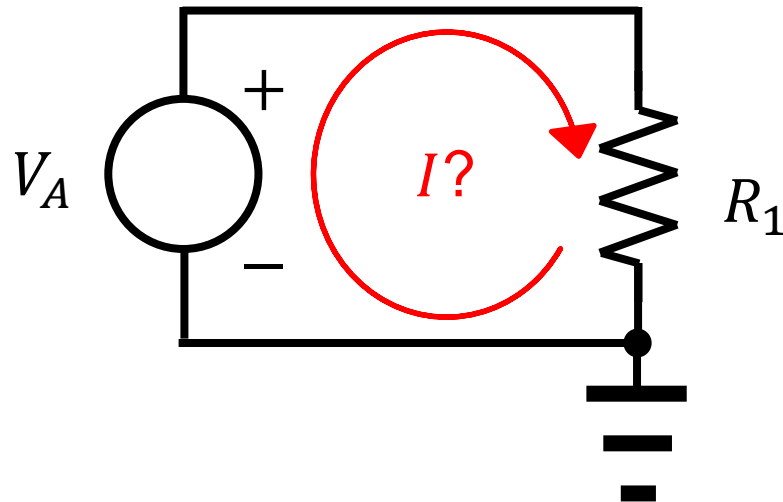
# A simple problem

---

- Solve the problem.
  - What is the current?




- It is an easy problem.
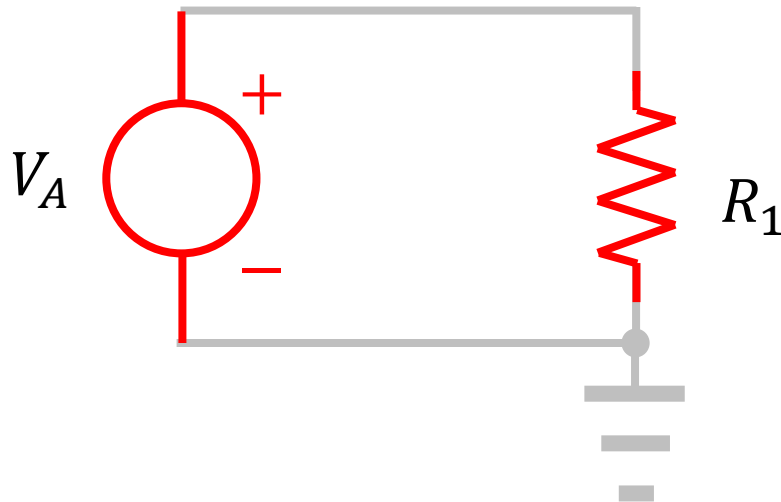
# Elements

---


- Resistors, capacitors, etc
  - They can have multiple terminals.
  - A resistor has two terminals.
  - A diode has two terminals.
  - A MOSFET has three (or four) terminals.


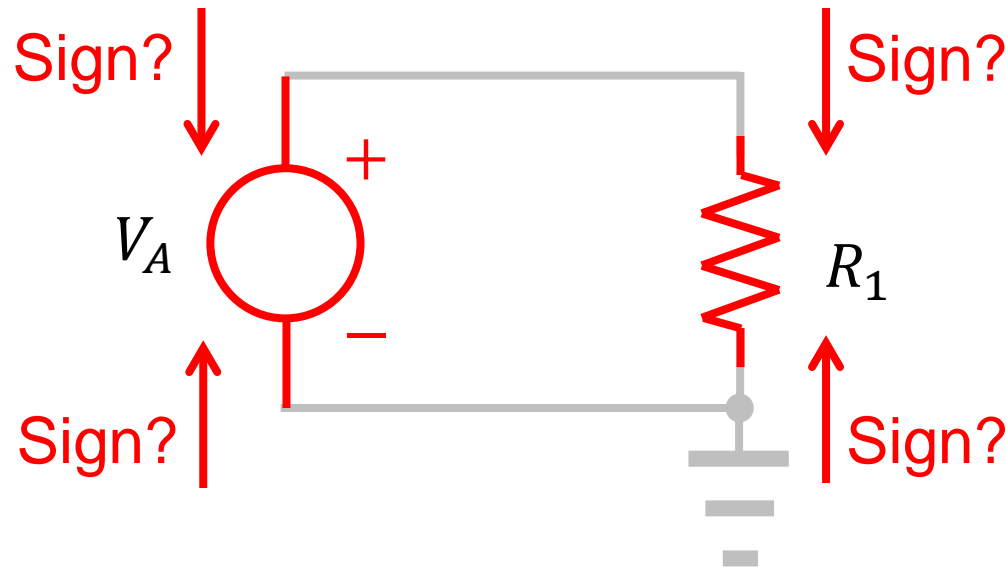
# Convention for current

---


- Terminal current
  - Conventionally, an in-coming current is regarded as positive.


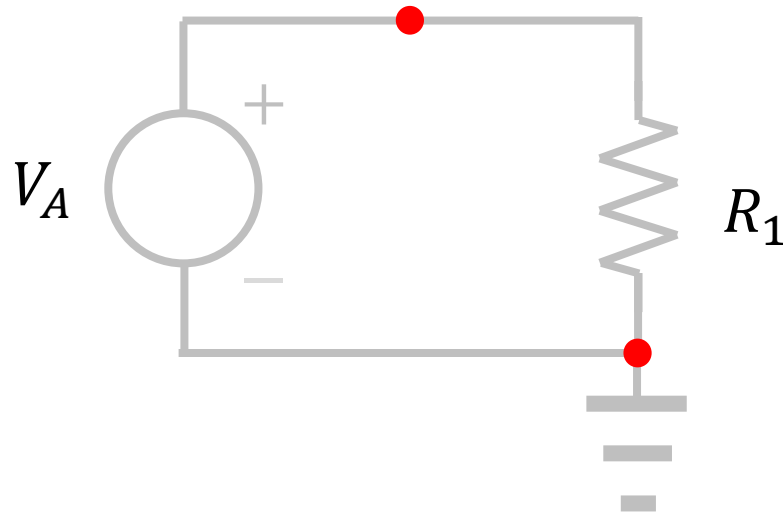
# Nodes

---

- A point to which multiple terminals are tied.
  - (Usually, a dot is used to represent a node.)
  - There is a special node, GND.




# How to describe a circuit

---

- Of course, we can draw a circuit schematic. What else?
- A netlist for this circuit looks like:

```
va out 0 1.0  
r1 out 0 1000
```

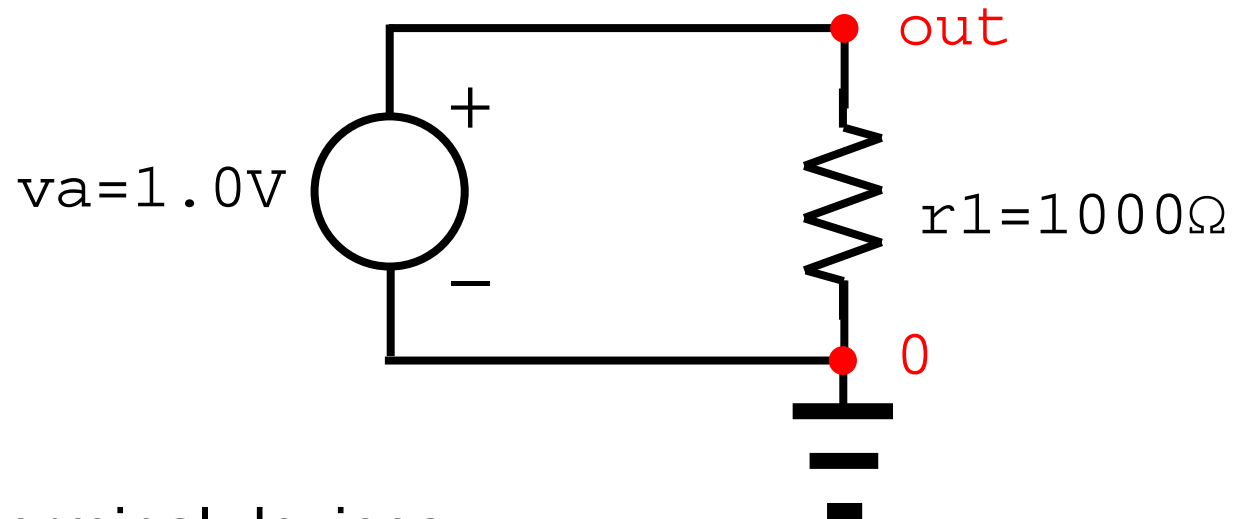

- Format for two-terminal devices  
elementlabel node1 node2 value

# RC filter


---

- A netlist for this circuit looks like:

```
c1 in out 5e-12
```

```
r1 out 0 2e6
```


```
vin in 0 1.5
```

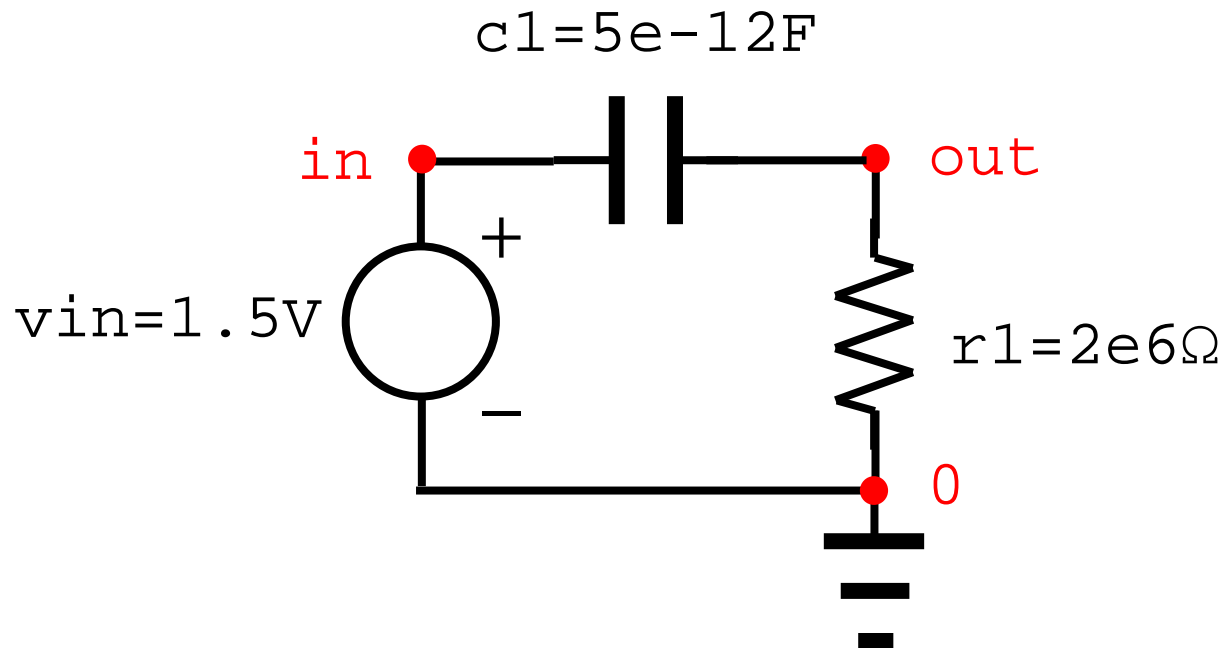
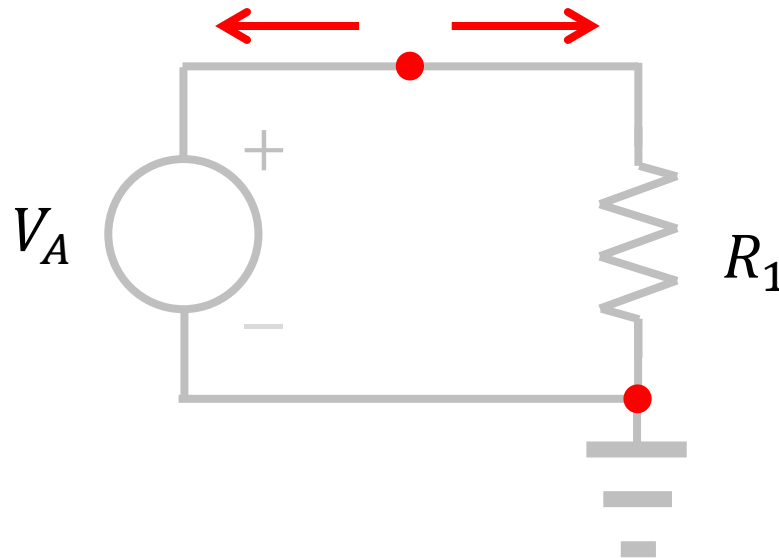
# Circuit analysis (1)

---

- The basis principle of circuit analysis is...
  - Kirchhoff's current law (KCL)!
  - At any node in an electrical circuit, the sum of currents flowing into that node is equal to the sum of currents flowing out of that node.





# Circuit analysis (2)


---

- Our simple problem
  - Following equations are identified.

$$I_{va} + I_{r1} = 0 \quad \text{KCL}$$

$$V(out) - 0.0 = 1.0 \quad \text{Voltage source}$$
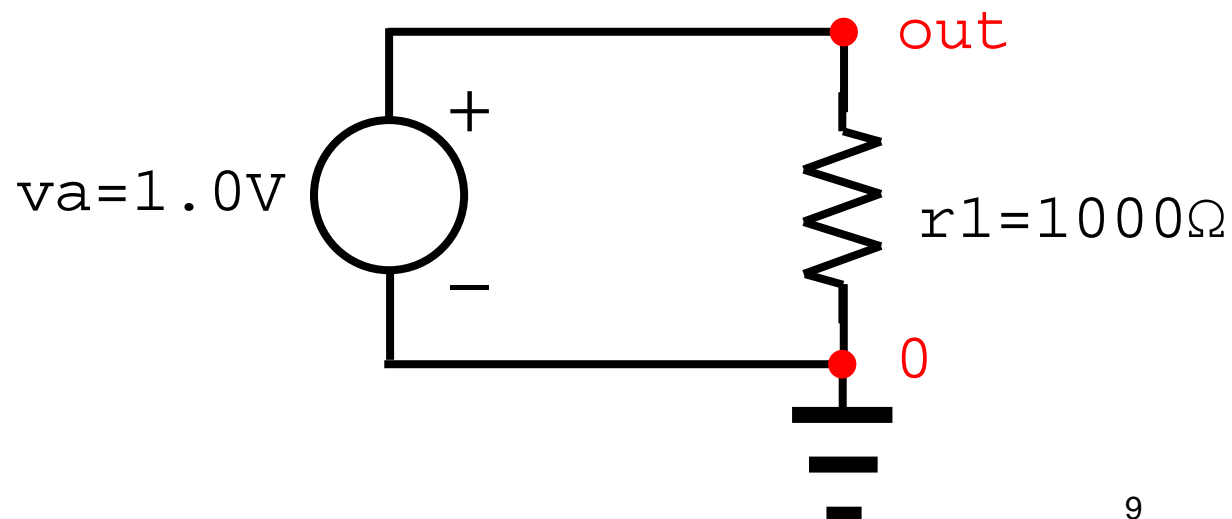
$$I_{r1} = \frac{V(out)}{1000} \quad \text{Resistor}$$



# Circuit analysis (2)


---

- Our simple problem
  - Following equations are identified.

$$I_{va} + I_{r1} = 0 \quad \text{KCL}$$

$$V(out) - 0.0 = 1.0 \quad \text{Voltage source}$$

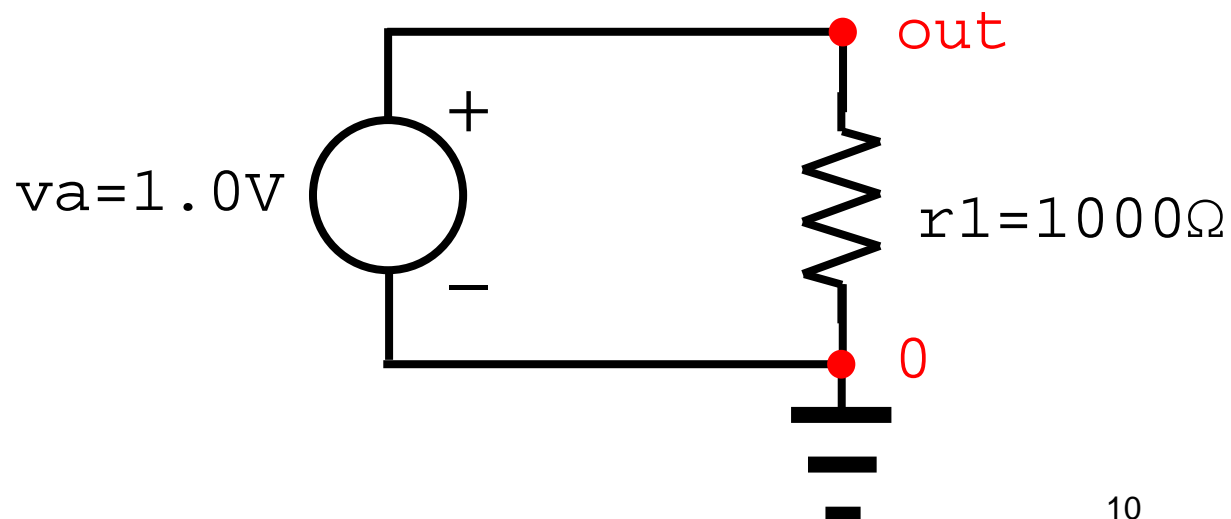
$$I_{r1} = \frac{V(out)}{1000} \quad \text{Resistor}$$


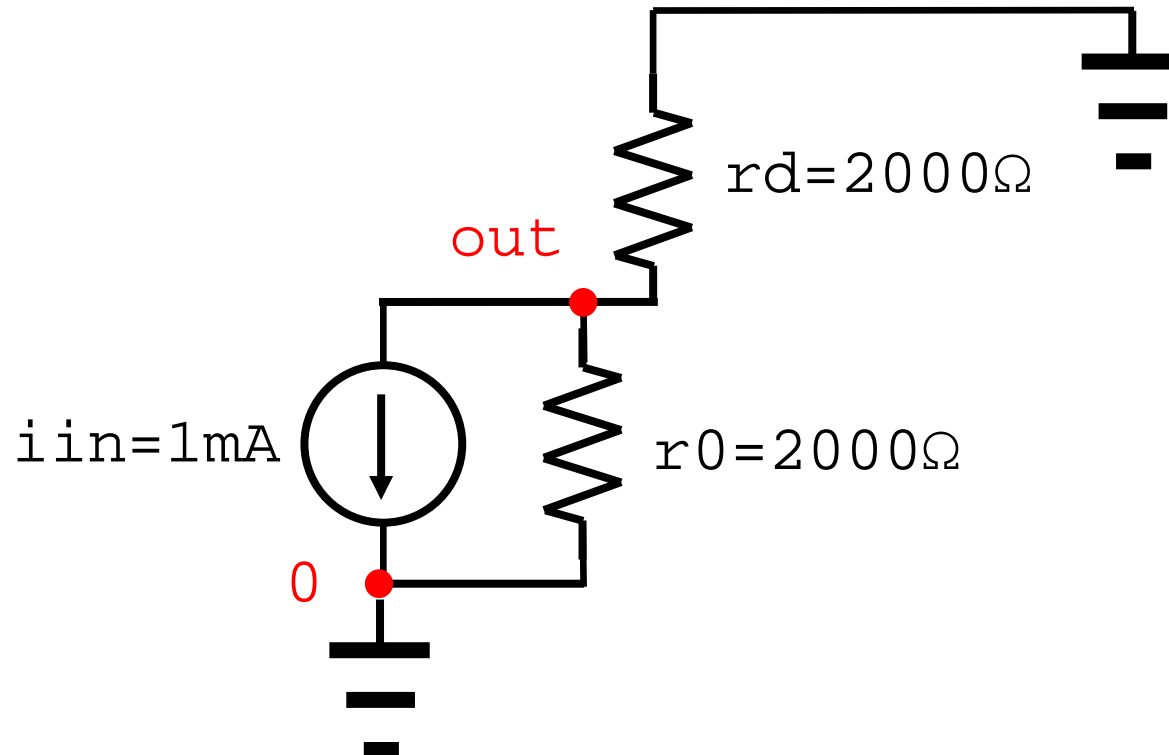
# Circuit analysis (3)

---

- Our real-world example
  - Write a netlist.
  - Calculate the node voltage of `out`.



# Homework#1 (1)

---

- Due: 09:00, March 12
  - Submit your Homework answer sheet (hardcopy) to Mr. Geon-Tae Jang, our TA.
  - His office: EECS building C-411
- Write a simple program.
  - It accepts an input file name.
  - It prints “Hello, world!”
  - It prints the contents for the input file.
  - It prints “Bye!”
  - (Attach the source code and the screen shot.)

# Homework#1 (2)

---

- Draw a circuit schematic of the following netlist.

```
v1 batt 0 1.5
```

```
r1 batt xx 1000
```

```
r2 xx yy 2000
```

```
r3 yy 0 2000
```

```
r4 yy 0 3000
```