

---

# Lecture14: CMOS amplifier, common-source (1)

Sung-Min Hong ([smhong@gist.ac.kr](mailto:smhong@gist.ac.kr))

Semiconductor Device Simulation Lab.  
School of Electrical Engineering and Computer Science  
Gwangju Institute of Science and Technology

# Simple biasing (1/3)


- A better way to provide the gate voltage

- The gate bias voltage is

$$V_{GS} = \frac{R_2}{R_1 + R_2} V_{DD} \quad (17.10)$$

- The drain current is

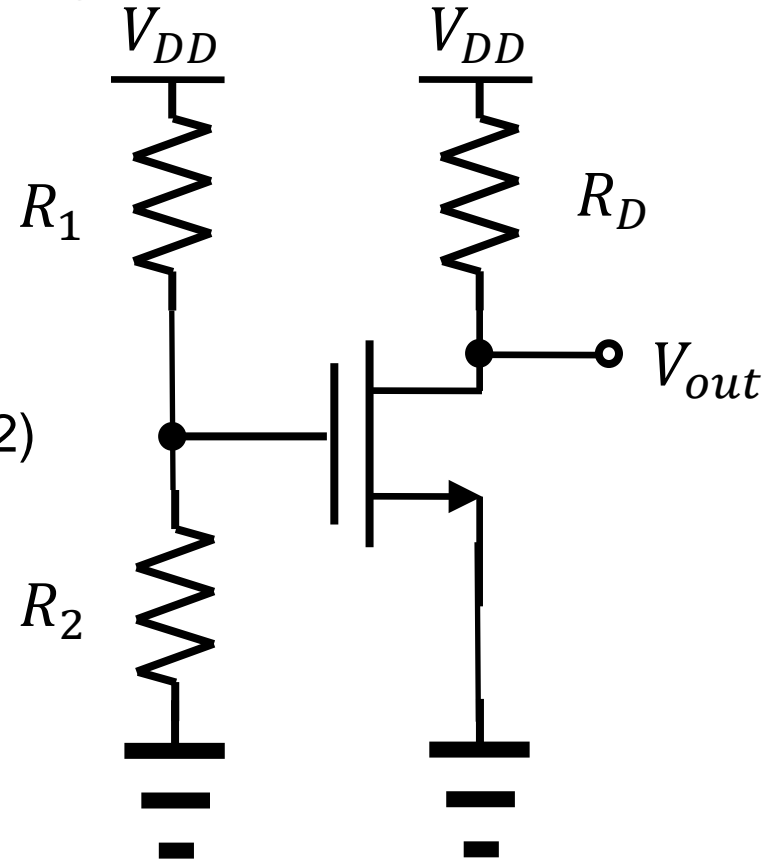
$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \left( \frac{R_2}{R_1 + R_2} V_{DD} - V_{TH} \right)^2 \quad (17.12)$$


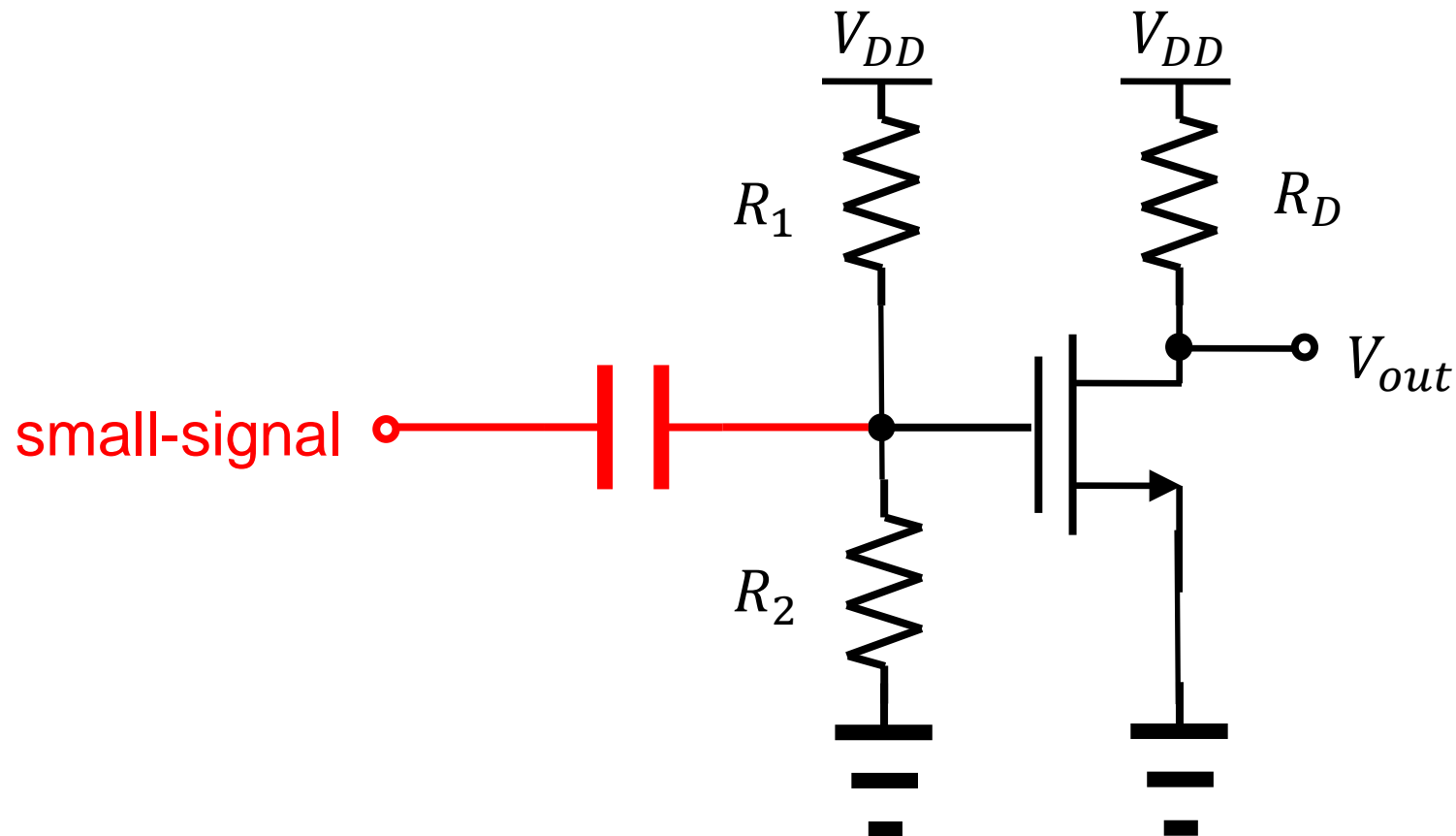
# Simple biasing (2/3)

---


- How to apply the small-signal input
  - Use a capacitor!


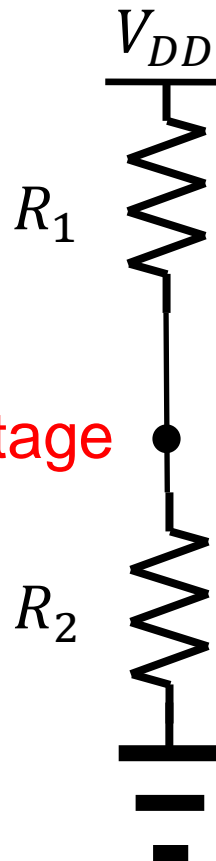
# Simple biasing (3/3)


- DC and AC
  - When  $\omega C \gg 1$ , the small-signal voltage occurs at the gate.

The capacitor  
& small-signal voltage  
do not contribute.



small-signal  
voltage


$$Z(\omega) = \frac{1}{j\omega C}$$

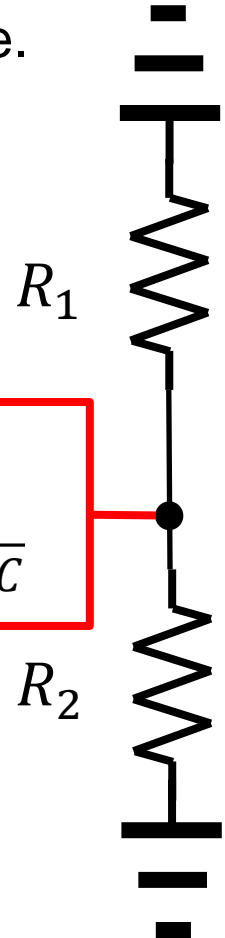
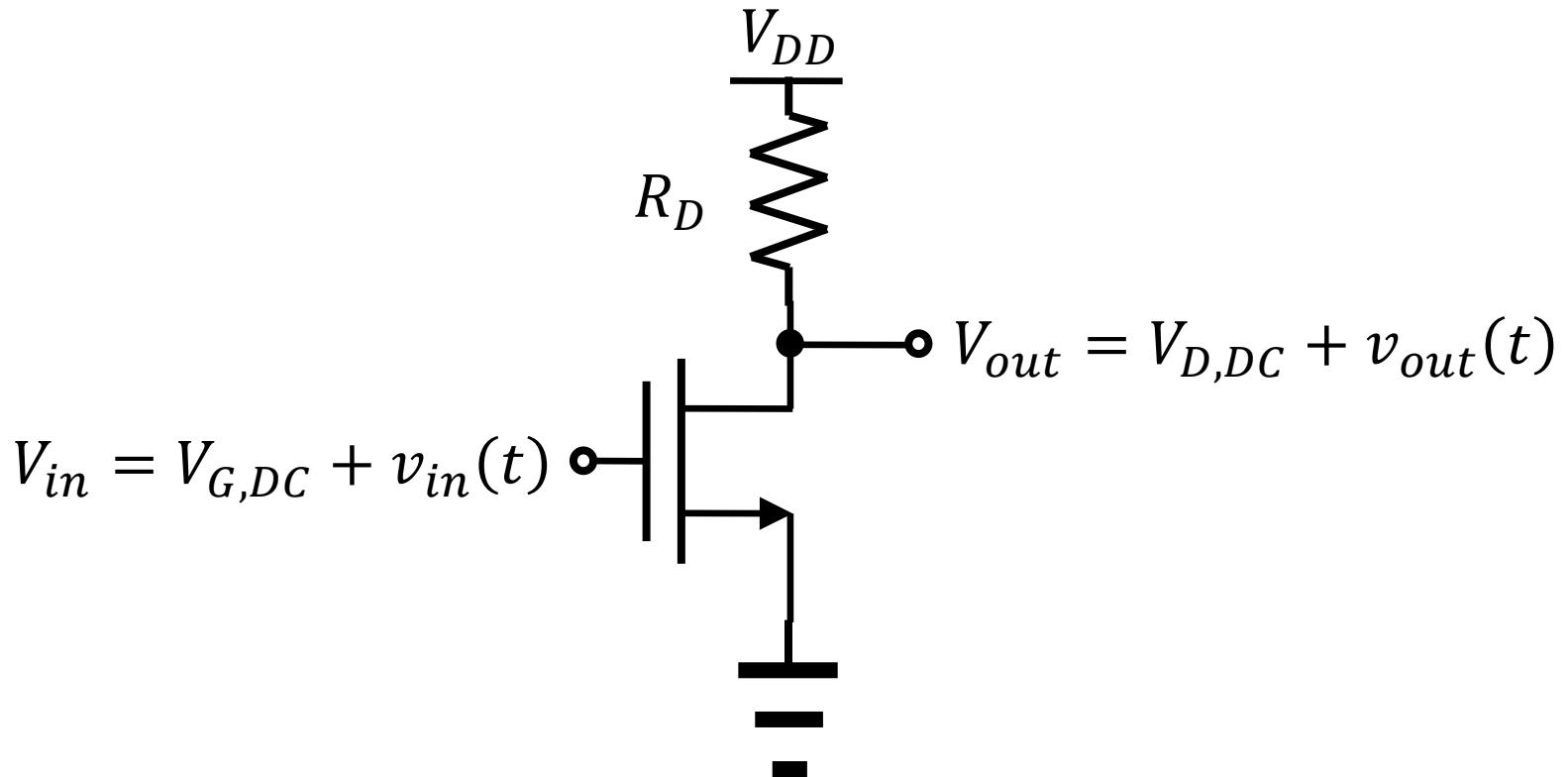
# Common-source amplifier

---


- The source terminal is the reference.
  - The small-signal gate voltage changes the drain current.
  - The output voltage,  $V_{out} = V_{DD} - I_D R_D$ , is affected.


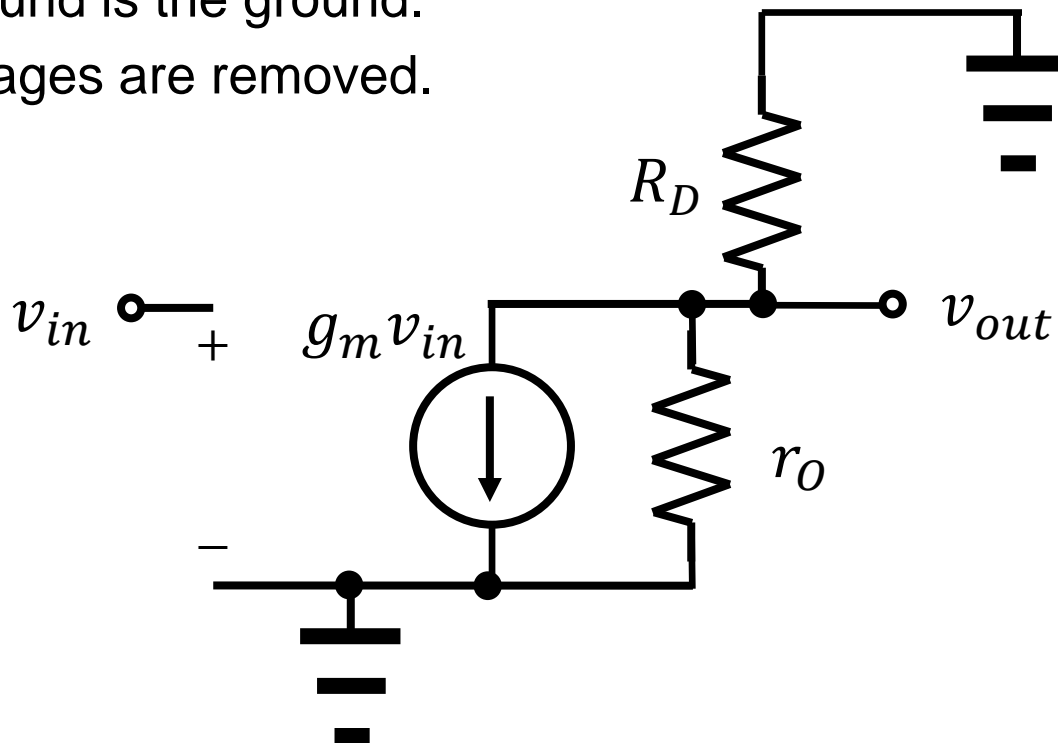
# Small-signal model

---

- Let's draw its small-signal model together!
  - A transistor small-signal model is introduced.
  - Resistors are resistors.
  - The ground is the ground.
  - DC voltages are removed.



# Gain

---

- Now, calculate the  $v_{out}$ .
  - KCL for the  $v_{out}$  node gives
$$v_{out} = -g_m(R_D || r_o)v_{in}$$
  - Therefore, the voltage gain,  $A_v$ , is
$$A_v = -g_m(R_D || r_o)$$

