
Lecture24:



Digital CMOS circuits (2)

Sung-Min Hong (smhong@gist.ac.kr)

Semiconductor Device Simulation Lab.
School of Information and Communications
Gwangju Institute of Science and Technology


Review of last lecture

  - Numeric calculation can be done with a binary system.
- Inverters and NAND gates are important.
- And, the NMOS inverter was introduced.



Noise margin

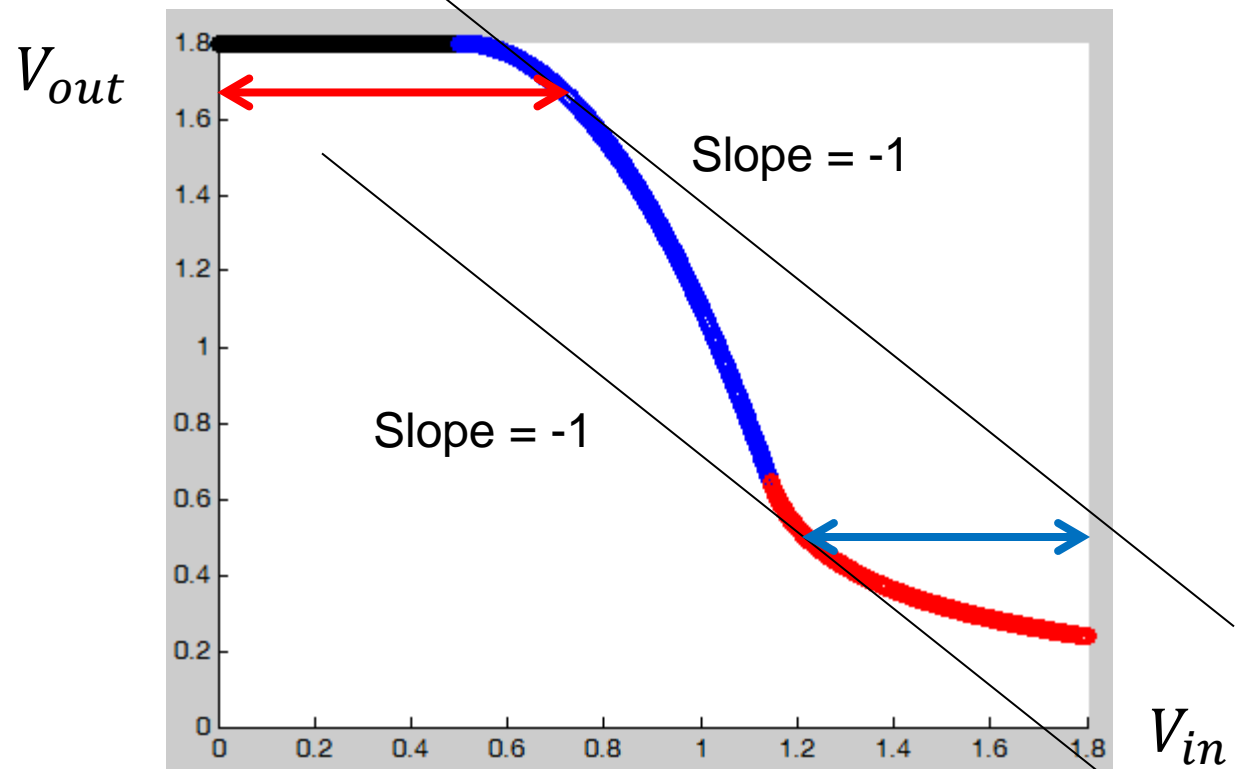- Verbatim
 - “Noise margin is the maximum amount of degradation (noise) at the input that can be tolerated before the output is affected significantly.”



Noise margin of CS stage

- Let's calculate NM_L .

- In this case,

$$V_{out} = V_{DD} - \frac{1}{2} \mu_n C_{ox} \frac{W}{L} R_D (V_{in} - V_{TH})^2$$

- Taking the differentiation w. r. t. V_{in} ,

$$\frac{\partial V_{out}}{\partial V_{in}} = -\mu_n C_{ox} \frac{W}{L} R_D (V_{in} - V_{TH})$$


- At $V_{in} = NM_L$, the slope becomes -1,

$$NM_L = \frac{1}{\mu_n C_{ox} \frac{W}{L} R_D} + V_{TH}$$

- (Stronger NMOS yields a reduces NM_L .)


Speed of inverter (1/3)

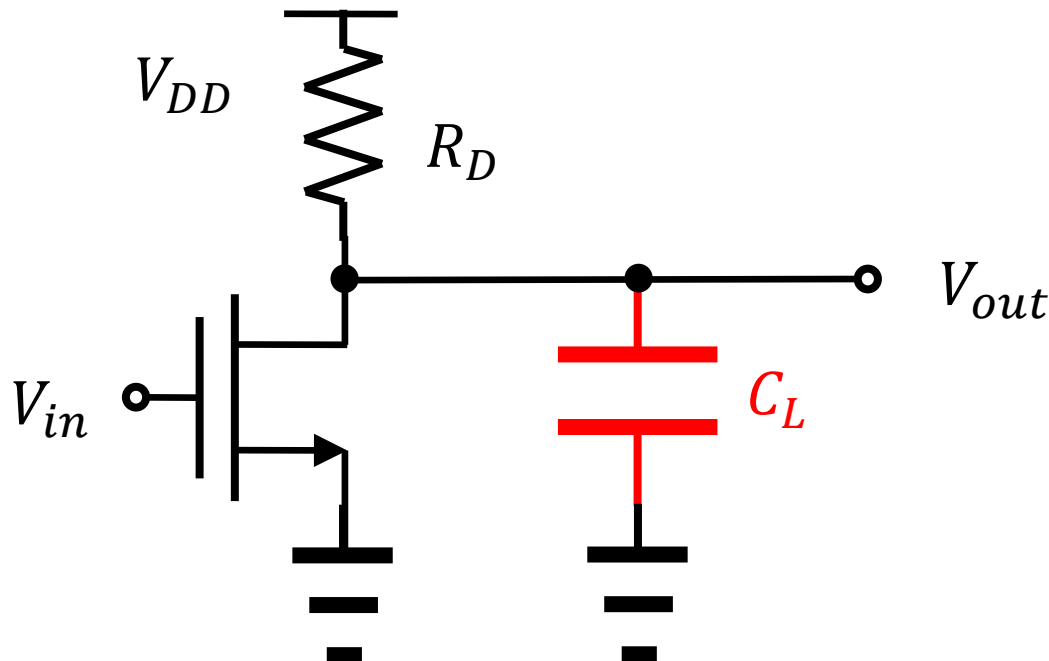- VTC merely describes the dc behavior.
 - Input voltages with different frequencies (1 kHz, 1 MHz, 1 GHz, 1 THz, ...)
- Time-dependent behavior
 - Can a resistor introduce time-lagging effect?



Speed of inverter (2/3)

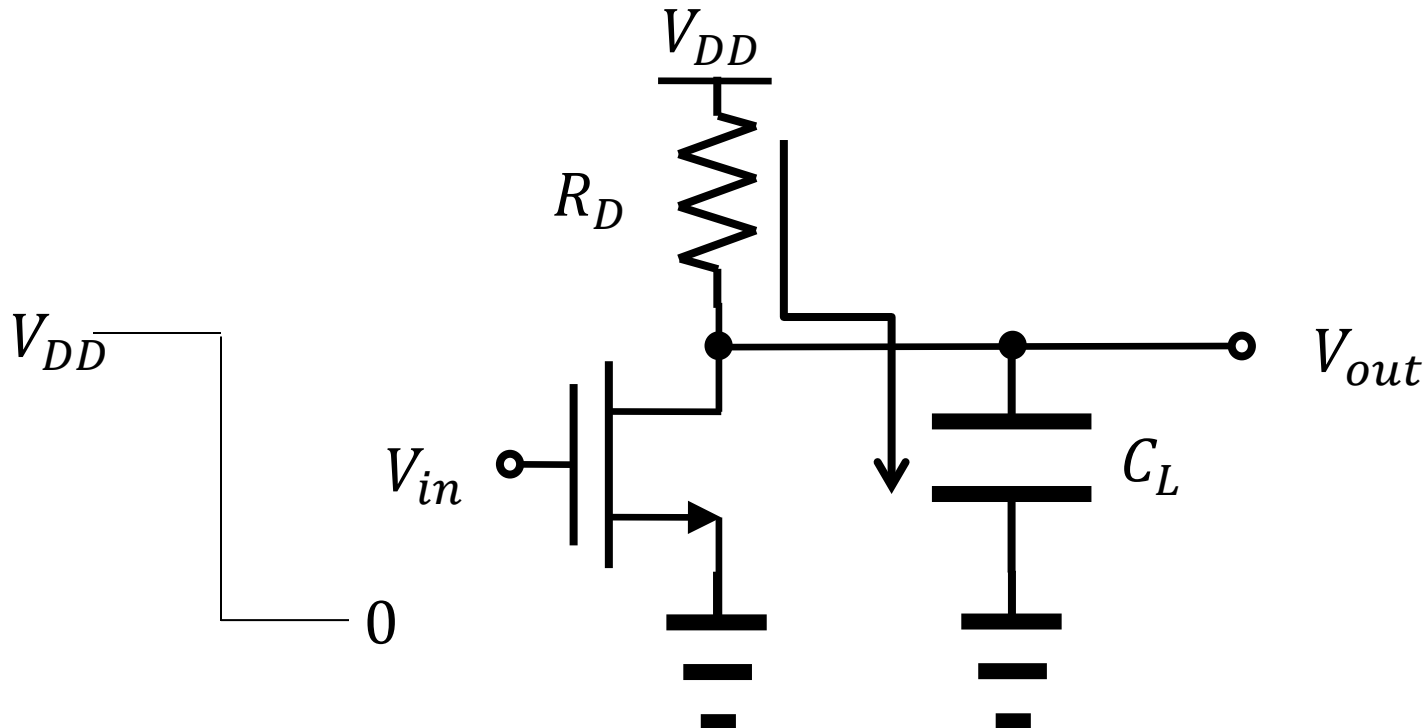- A rapid transition of V_{in} from V_{DD} to 0
 - Then, the capacitor should be charged.
 - What is the electrical route to charge the capacitor?



Speed of inverter (3/3)

- Simply, it is a RC circuit.


- Then, the solution is simply

$$V_{out}(t) = V_{out}(0^-) + [V_{DD} - V_{out}(0^-)] \left(1 - \exp \frac{-t}{R_D C_L} \right)$$

- Since $\exp(-3) \approx 0.05$, after $3R_D C_L$, V_{out} reaches $0.95 V_{DD}$.
 - Yes, it takes time to get the stable output voltage...

Origin of C_L ?

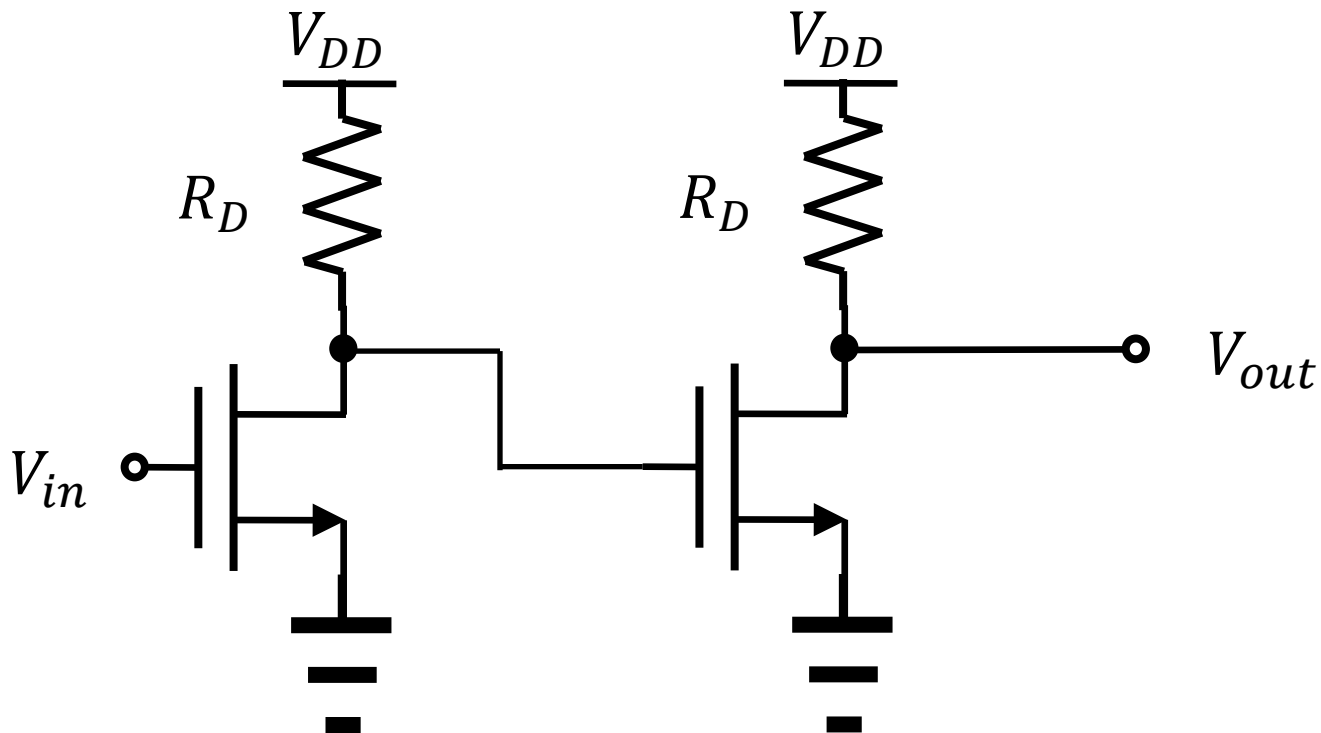- Consider an inverter chain.
 - Then, what is the load capacitance for the first stage?



- Another origin → Interconnect

Standby(!) power

- The biggest problem in the NMOS inverter
 - When $V_{in} = 0$, no standby power
 - When $V_{in} = V_{DD}$, the power consumption is (approximately) $\frac{V_{DD}^2}{R_D}$.
 - If $V_{DD} = 1.8 \text{ V}$ and $R_D = 10 \text{ k}\Omega$,
324 μW !

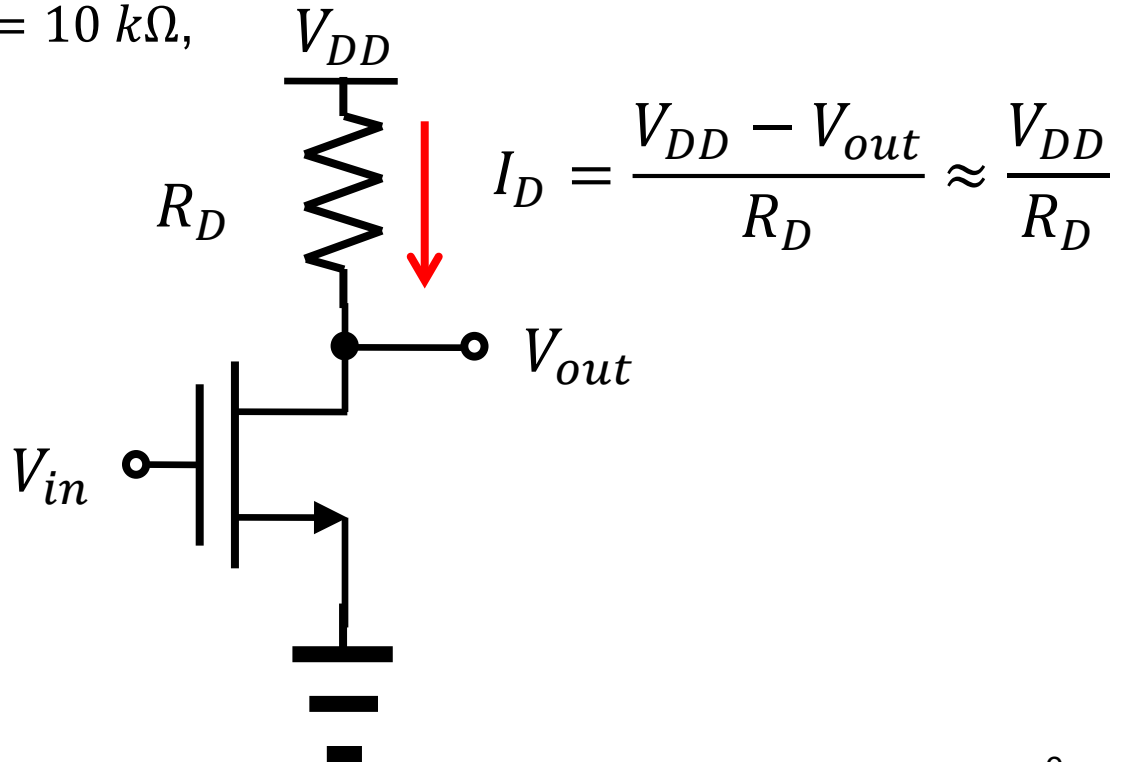


Figure 16.14

- Passive “pull-up” device

- (a) Degradation of output level

Too small R_D , when $V_{in} = V_{DD}$.

In this case, large R_D is desirable.

- (b) Risetime limitation

Too small current for 1 \rightarrow 0 transition. ($V_{in} = 0$)

In this case, a better capability to charge the C_L is desirable.

- (c) Static power consumption


No ability to block the current, when $V_{in} = V_{DD}$.

In this case, no current conduction is desirable.

 - (a) & (c) \leftrightarrow (b)

CMOS inverter

- Ideal “pull-up” should have the following properties.
 - When $V_{in} = V_{DD}$, no current conduction.
 - When $V_{in} = 0$, improved current conduction.
- PMOS can do those jobs!



Draw it! (Homework#3)

- Only 1 problem
- Same parameters as before
 - $\mu_n C_{ox} = 100 \mu\text{A}/\text{V}^2$, $\mu_p C_{ox} = 75 \mu\text{A}/\text{V}^2$, $V_{TH,n} = 0.5 \text{ V}$, $V_{TH,p} = -0.5 \text{ V}$, $\frac{W}{L} = \frac{10}{0.18}$, and $V_{DD} = 1.8 \text{ V}$
 - Using the computer, draw the voltage transfer curve.
- Due: June 3rd (This Wednesday!)