
Lecture4: Diode circuits

Sung-Min Hong (smhong@gist.ac.kr)


Semiconductor Device Simulation Lab.
School of Electrical Engineering and Computer Science
Gwangju Institute of Science and Technology

PN junction as a diode

- Exponential model


$$I_D = I_s \left(\exp \frac{V_D}{V_T} - 1 \right)$$

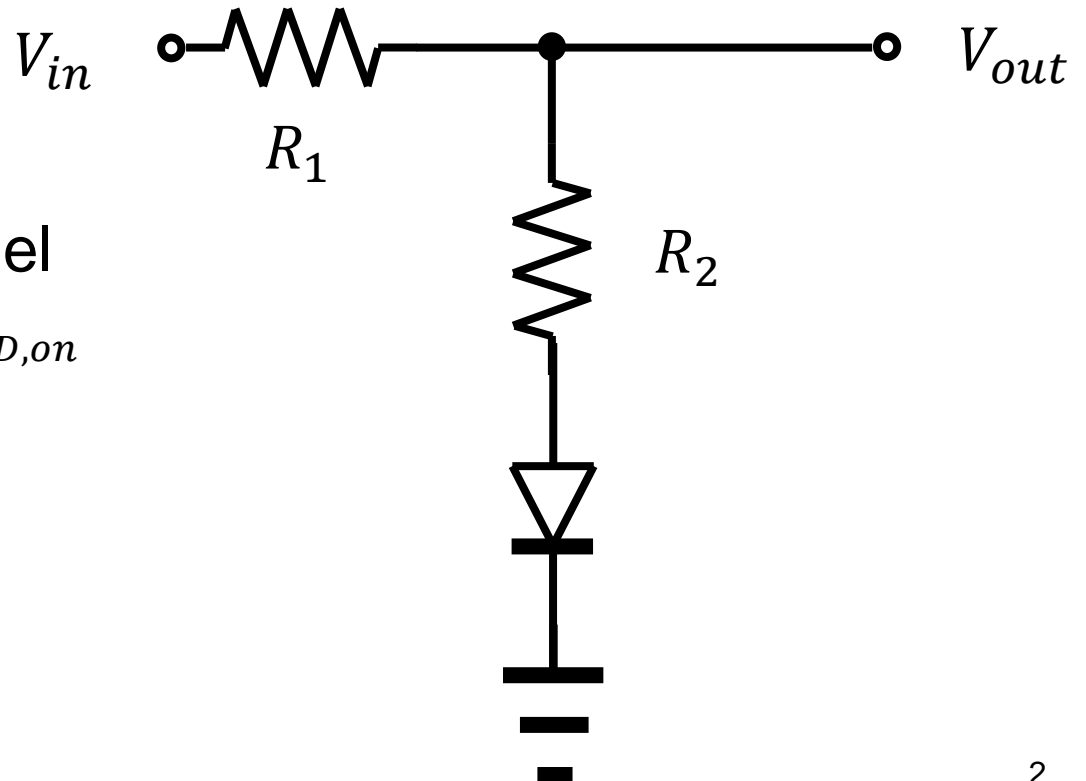- Constant-voltage model
 - An “offset” voltage of $V_{D,on}$





Rectifier

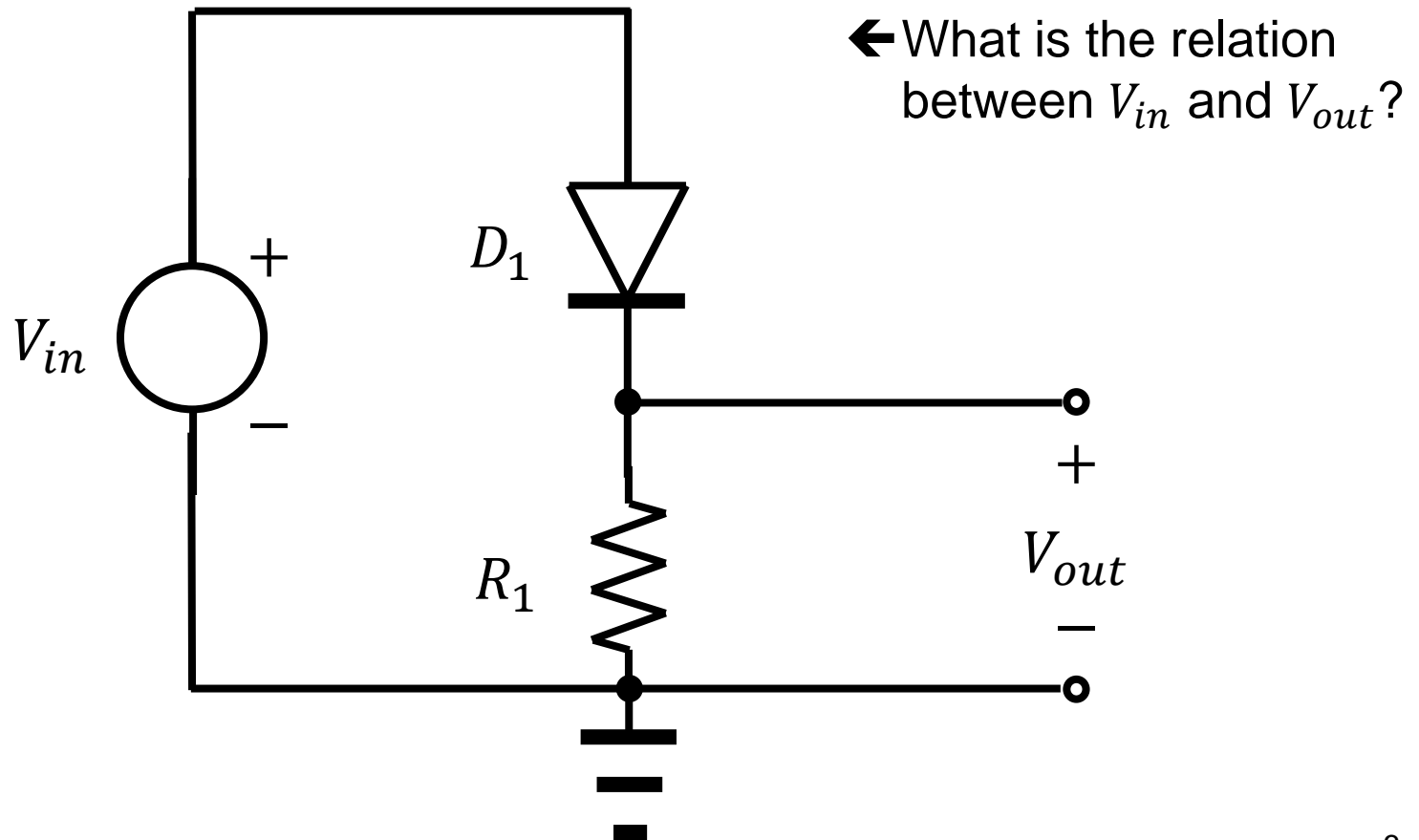- Revisiting our first example
 - Analyze it by using the constant-voltage model




Simulation result

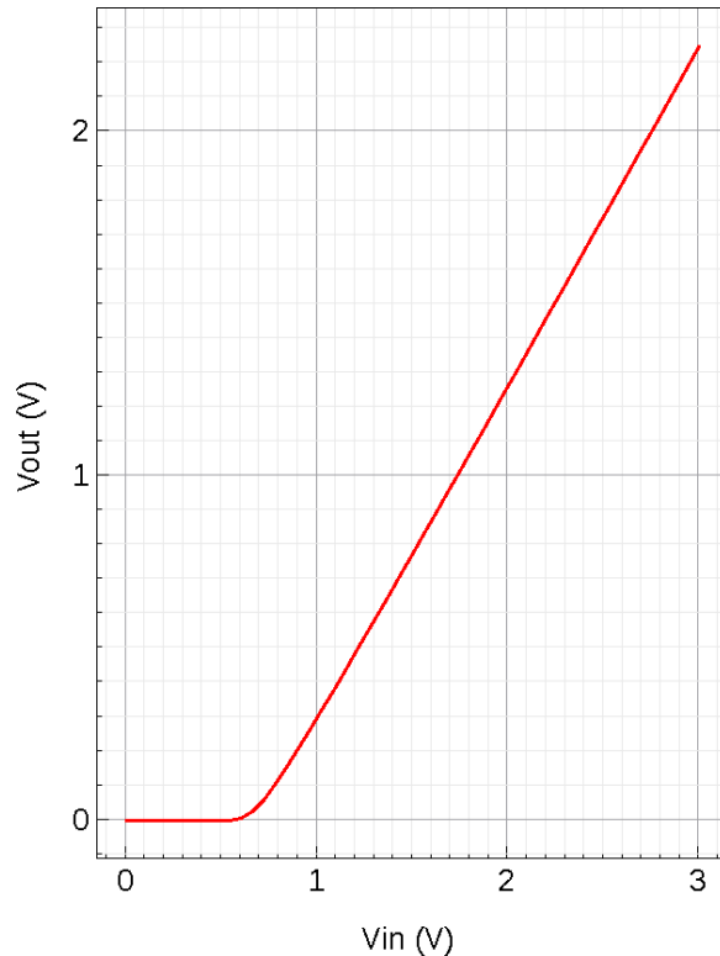 - Specific example of $I_S = 0.5 \text{ fA}$ and $R_1 = 1 \text{ k}\Omega$.




Time-varying voltage source

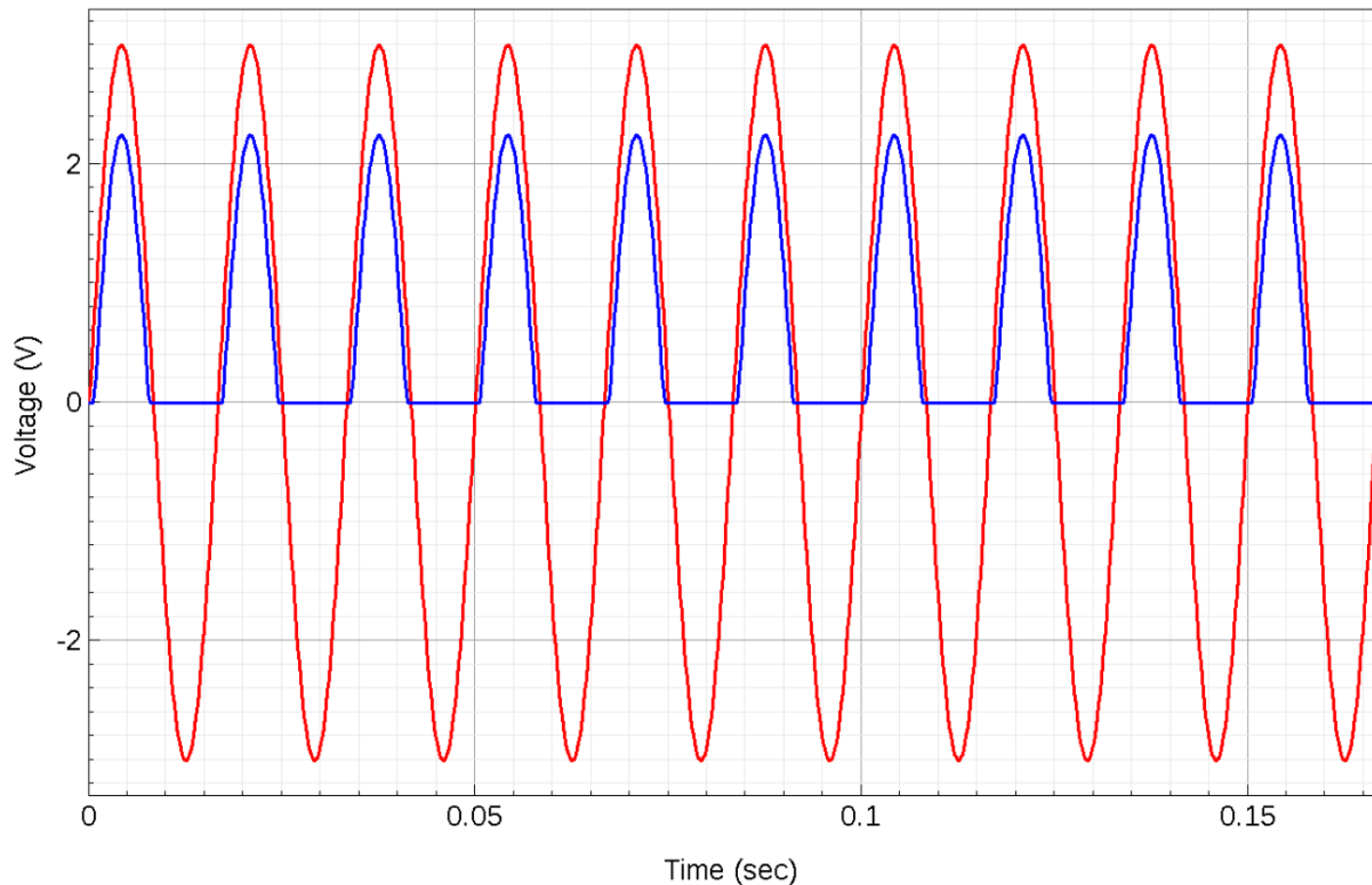- For example, $V_{in}(t) = 3 \sin(2\pi ft)$ V.
 - 60 Hz, 10 periods



Introducing a capacitor

 - Difference from the previous one?
 - First, consider the DC case. Remember that $I_C = C_1 \frac{d}{dt} V_{out}$.




Qualitative understanding

- Consider the first period.
 - When the input voltage exceeds $V_{D,on}$, the diode is turned on.
 - The charge is stored in the capacitor. Hence, the output voltage increases.
 - When the input voltage is lower than $V_{D,on}$, the output voltage does not change. (*Why?*)
- After the first period...
 - In the second period, the diode current is smaller than the one in the first period. (*Why?*)
 - After some periods, the diode current vanishes.
 - A DC output voltage is established.


Simulation result

- The capacitance, $C_1 = 1 \mu\text{F}$.

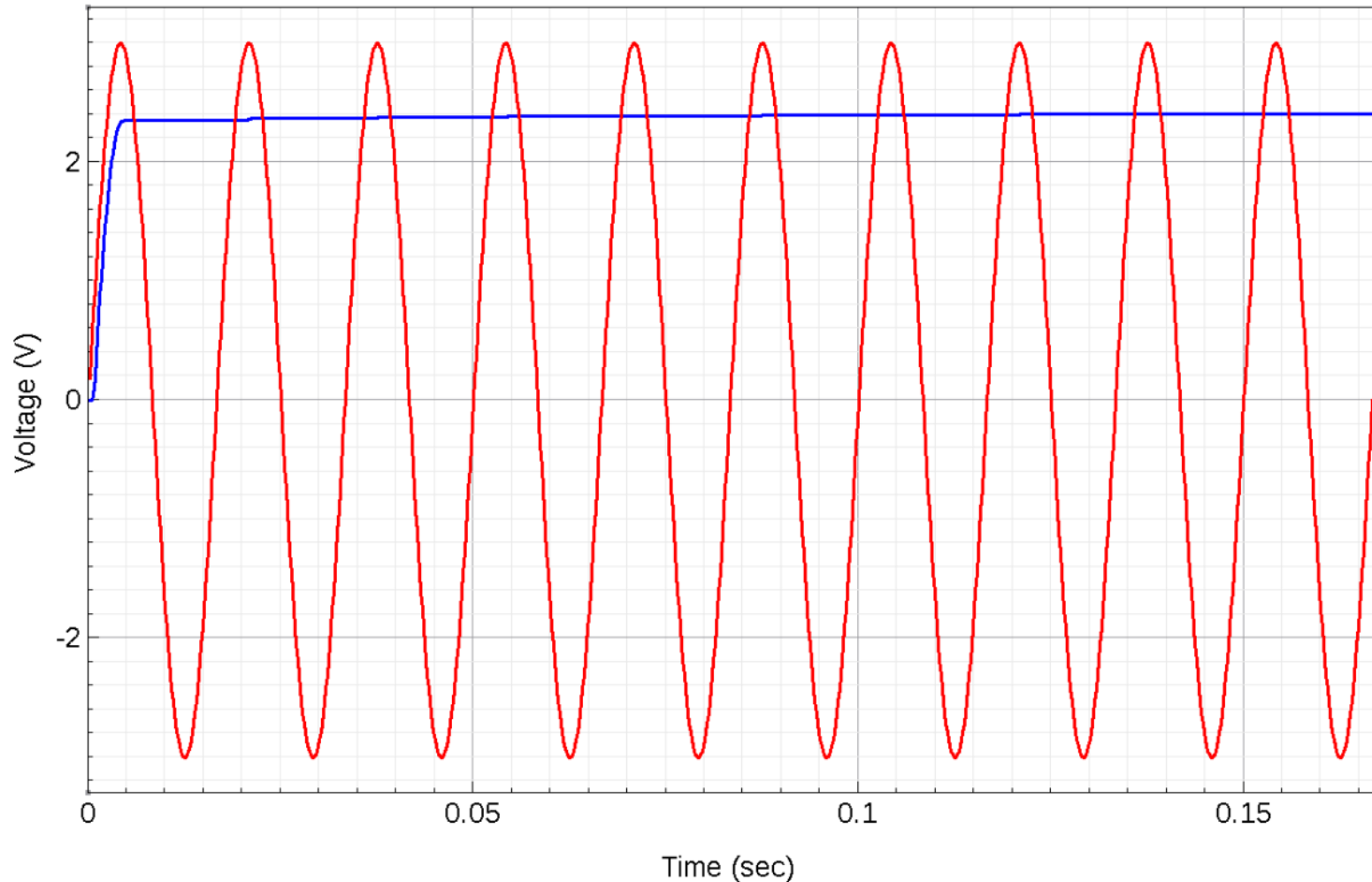

Example 3.6 (Razavi)

- An OR gate

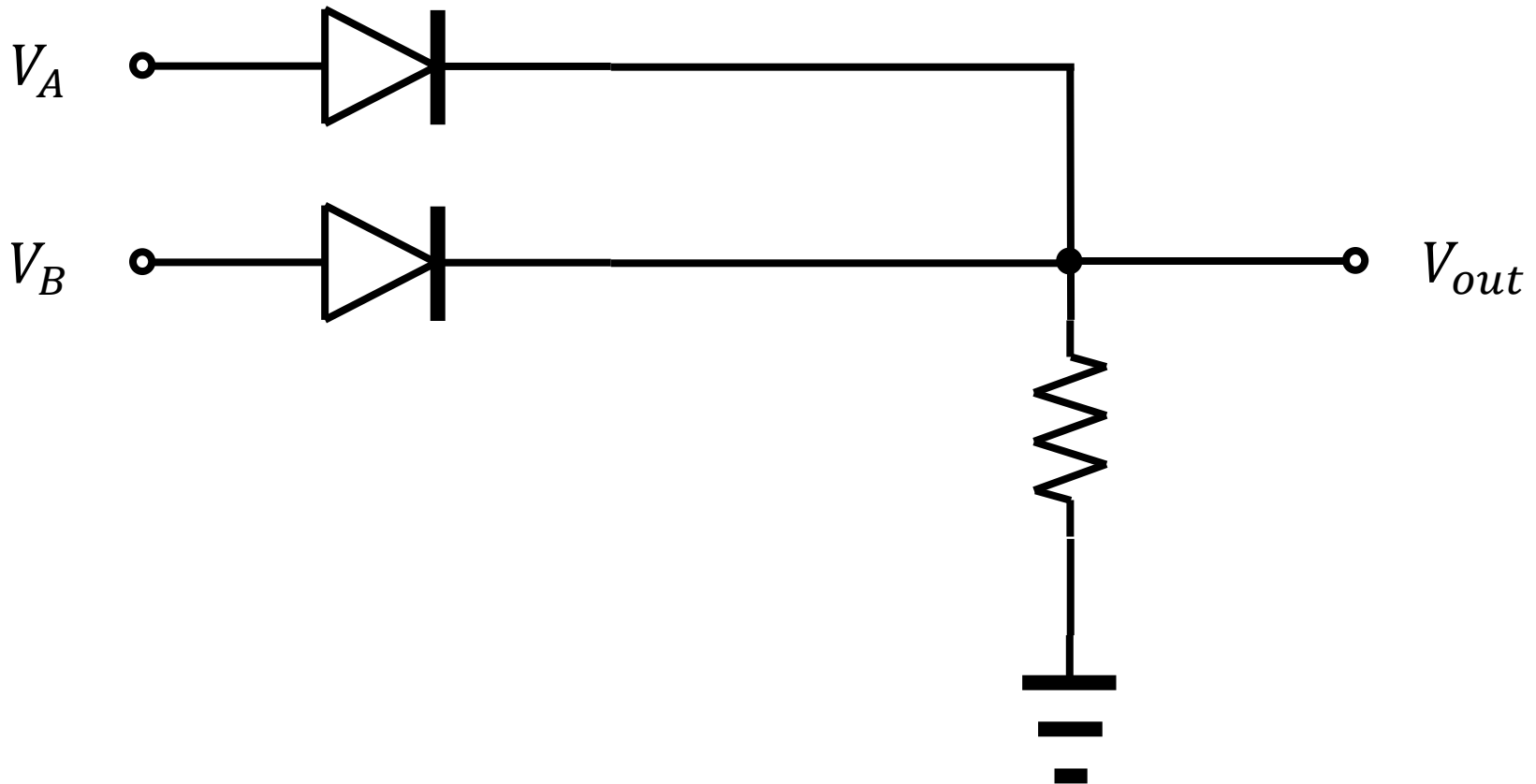

Limiter

- Level-shift for both half cycles

