

---

# Lecture16: Amplifier


Sung-Min Hong ([smhong@gist.ac.kr](mailto:smhong@gist.ac.kr))

Semiconductor Device Simulation Lab.  
School of Electrical Engineering and Computer Science  
Gwangju Institute of Science and Technology
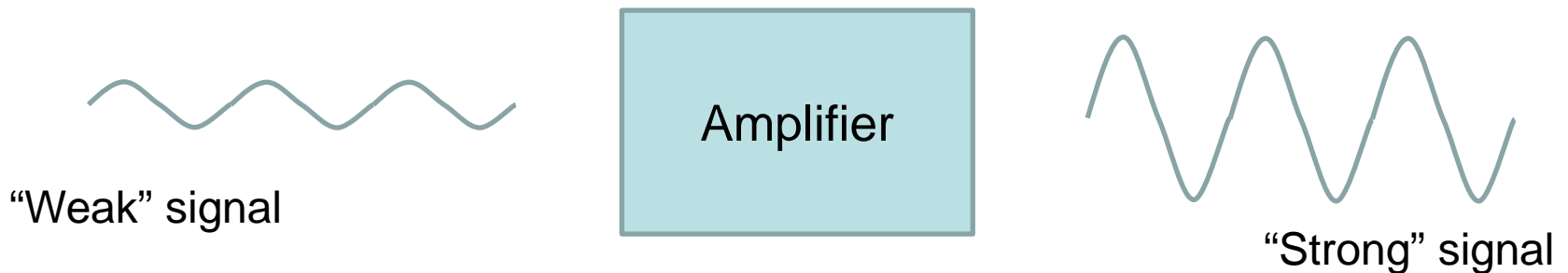
# Why amplifiers?

---

- Signal amplification
  - Usually, signals are “weak.” (in the  $\mu\text{V}$  or  $\text{mV}$  range)
  - It is too small for reliable processing.
  - If the signal magnitude is made larger, processing is much easier.



# Voltage gain


---

- Voltage gain
  - For example, a voltage amplifier amplifies the input voltage signal. Its output is also a voltage.
  - When  $V_{in}(t) = V_{DC,in} + v_{in}(t)$ , ideally, we want to have  $V_{out}(t) = V_{DC,out} + A_v v_{in}(t)$ .
  - $A_v$  is the voltage gain. (Of course, it is a unitless quantity.)
- How can we have a voltage-voltage relation?
  - Combining a transistor and a resistor!
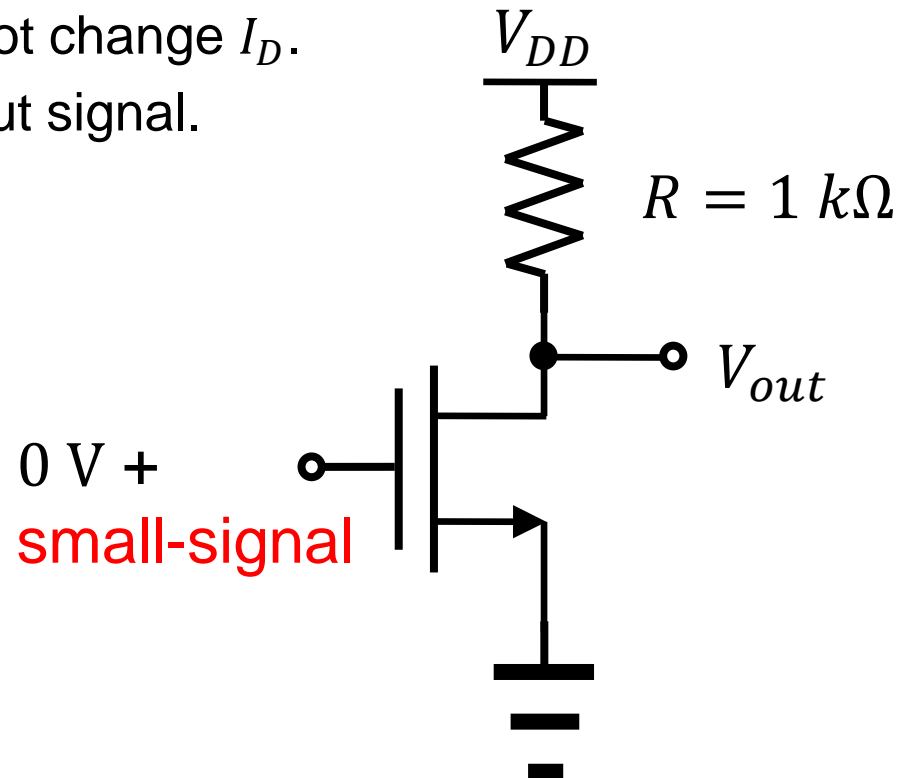
# Transistor turned off

---


- Note that  $V_{out} = V_{DD} - I_D R$ .
  - But, the transistor is not turned on. ( $I_D \approx 0$ )
  - The transconductance( $g_m$ ) is zero.
  - A small increase in  $V_G$  does not change  $I_D$ .
  - The circuit generates no output signal.


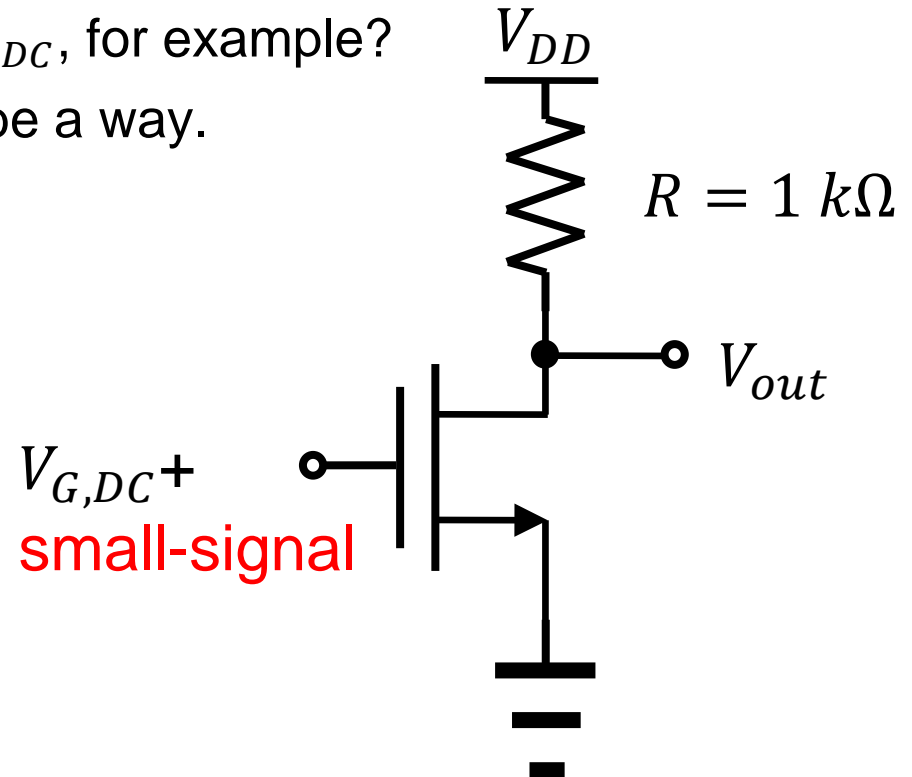
# This is a solution.

---

- The following circuit shows a revised circuit.
  - Assume that  $V_{G,DC} > V_{TH}$ .
  - It has a meaningful value of  $g_m$ .
  - Then, how can we generate  $V_{G,DC}$ , for example?
  - Use of a separate battery can be a way.



# Simple biasing (1/3)

---


- A better way to provide the gate voltage

- The gate bias voltage is

$$V_{GS} = \frac{R_2}{R_1 + R_2} V_{DD} \quad (\text{Razavi 17.10})$$

- The drain current is

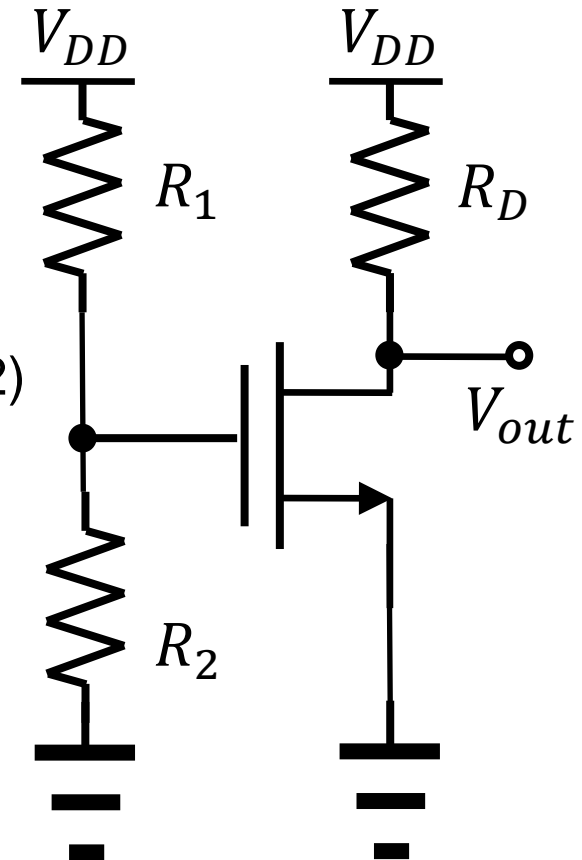
$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \left( \frac{R_2}{R_1 + R_2} V_{DD} - V_{TH} \right)^2 \quad (\text{Razavi 17.12})$$


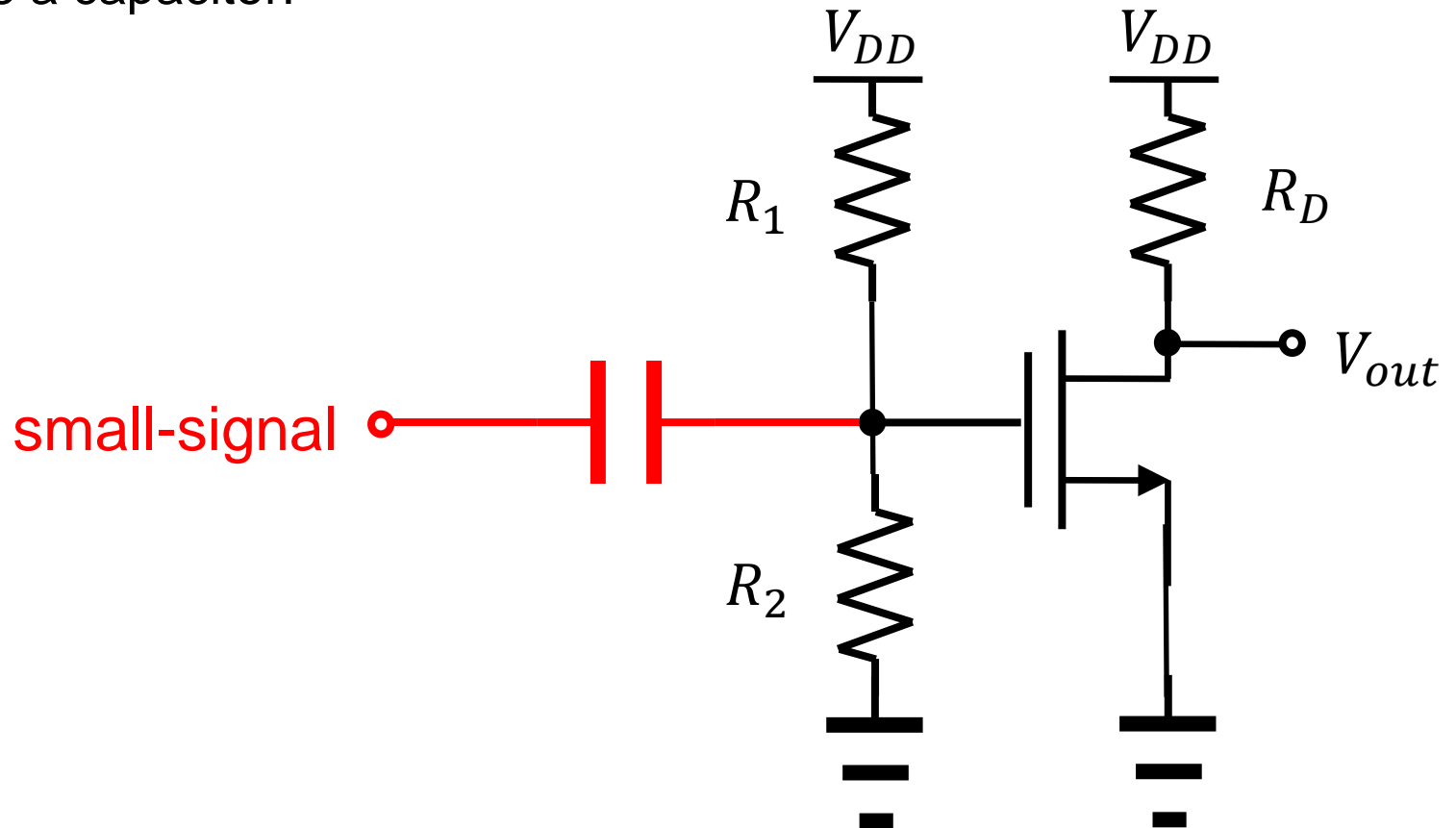
# Simple biasing (2/3)

---


- How to apply the small-signal input
  - Use a capacitor!



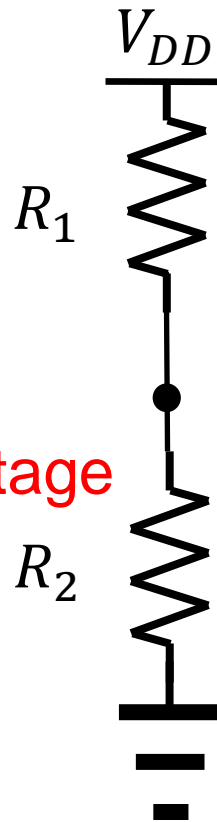
# Simple biasing (3/3)

---

DC:  
The capacitor  
& small-signal voltage  
do not contribute.



AC:  
small-signal  
voltage

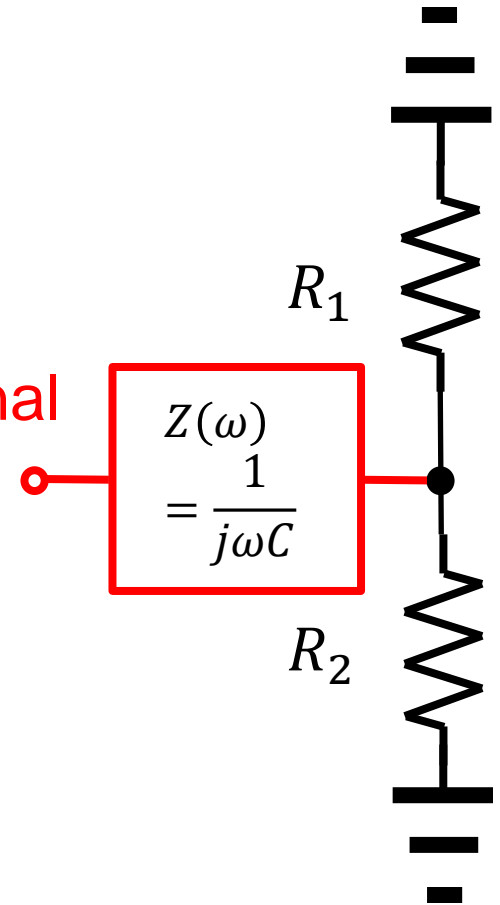



# Common-source amplifier


---

- The source terminal is the reference.

– The output voltage is  $V_{out} = V_{DD} - I_D R_D$ .

$$V_{out}(t) =$$

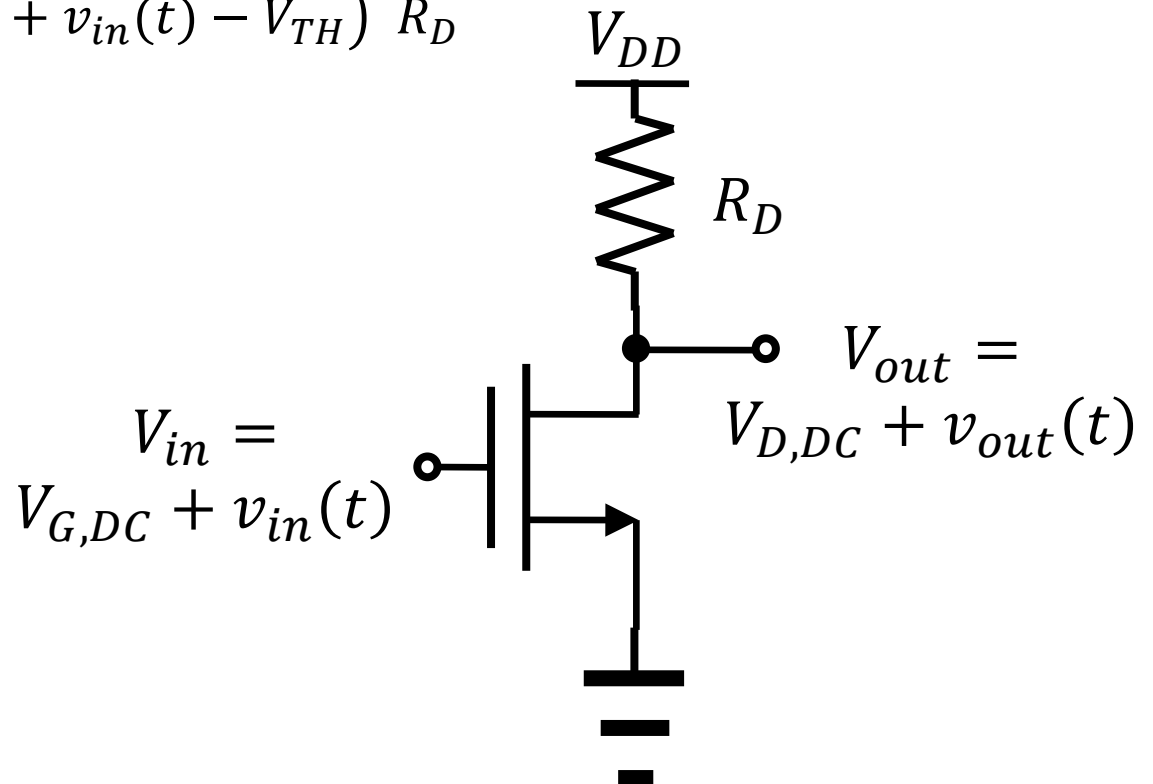
$$V_{DD} - \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{G,DC} + v_{in}(t) - V_{TH})^2 R_D$$


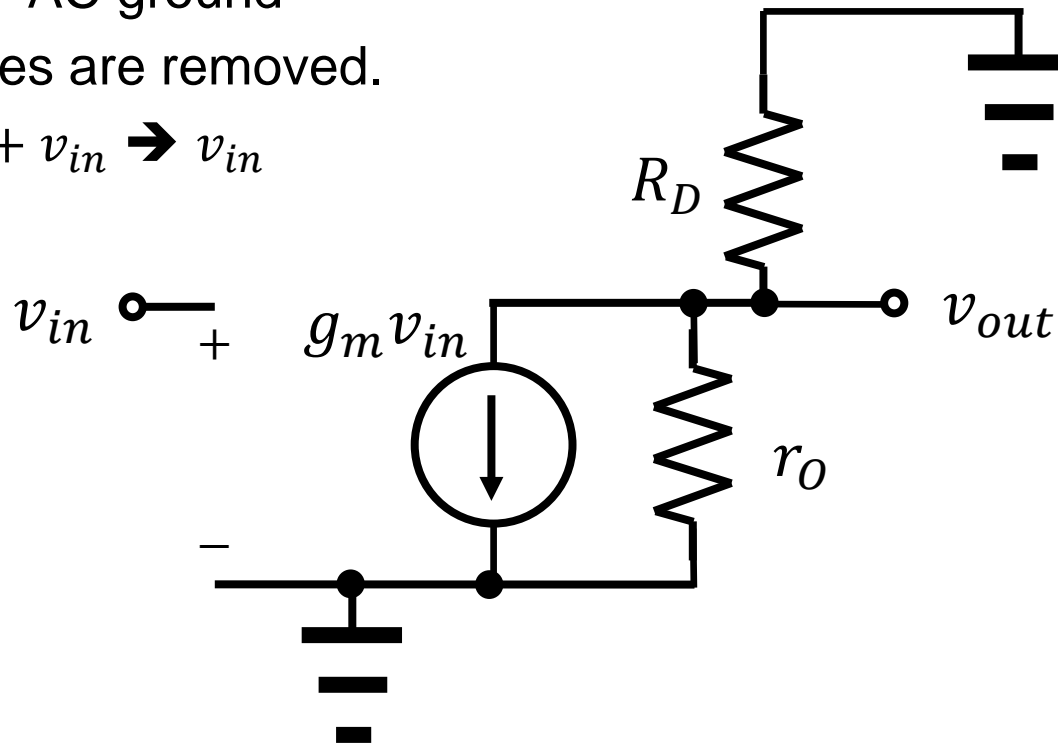
# Small-signal model

---

- Let's draw its small-signal model together!
  - A transistor small-signal model is introduced.
  - Resistors  $\rightarrow$  resistors
  - Ground  $\rightarrow$  AC ground
  - DC voltages are removed.
  - Ex)  $V_{G,DC} + v_{in} \rightarrow v_{in}$



# Homework#7

---

- Due: 09:00, **May 8 (Wed)**
- Solve following problems of the 2018 final exam.
  - P1
  - P2
  - P3
- Solve following problems of the 2017 final exam.
  - P22
  - P23
  - P24
  - P25

# Gain

---

- Now, calculate the  $v_{out}$ .
  - KCL for the  $v_{out}$  node gives
$$v_{out} = -g_m(R_D || r_o)v_{in}$$
  - Therefore, the voltage gain,  $A_v$ , is
$$A_v = -g_m(R_D || r_o)$$

