
Lecture7:

Diode models and circuits (1)


Sung-Min Hong (smhong@gist.ac.kr)

Semiconductor Device Simulation Lab.
School of Information and Communications
Gwangju Institute of Science and Technology


A simple math

- An input voltage, $V_{in}(t) = \sin \omega t$

- A system

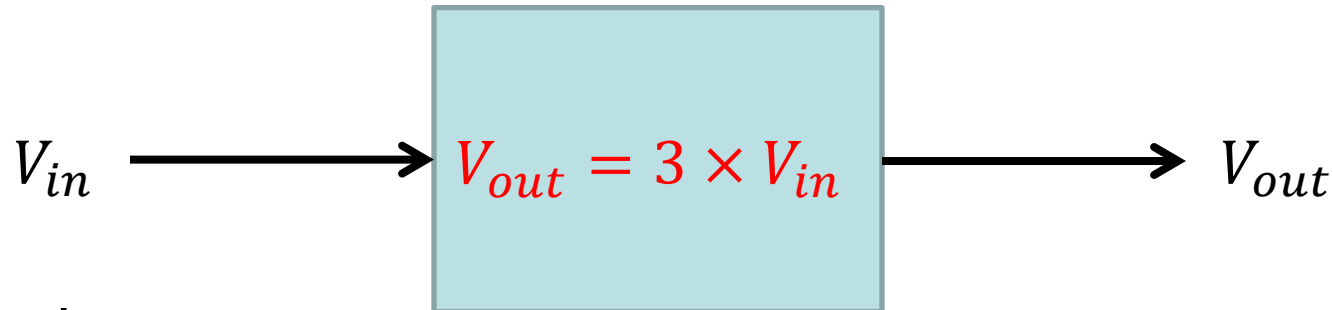


- Another system

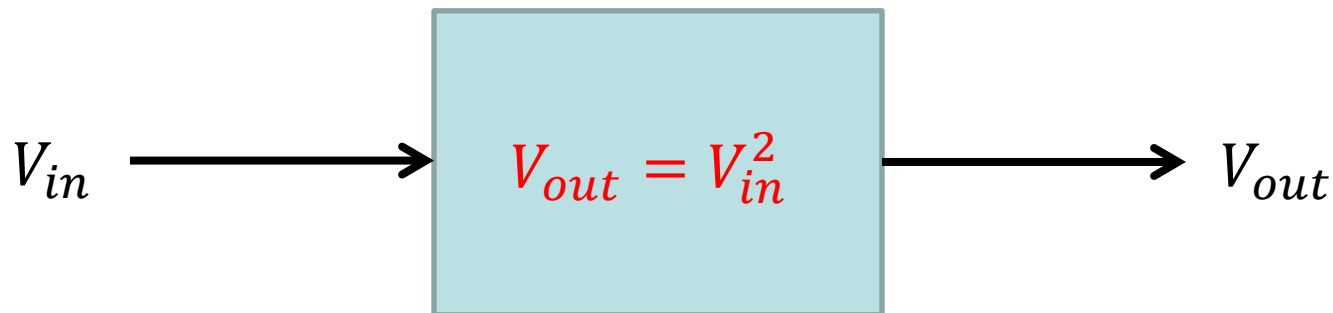


Which is nonlinear?

- A resistor

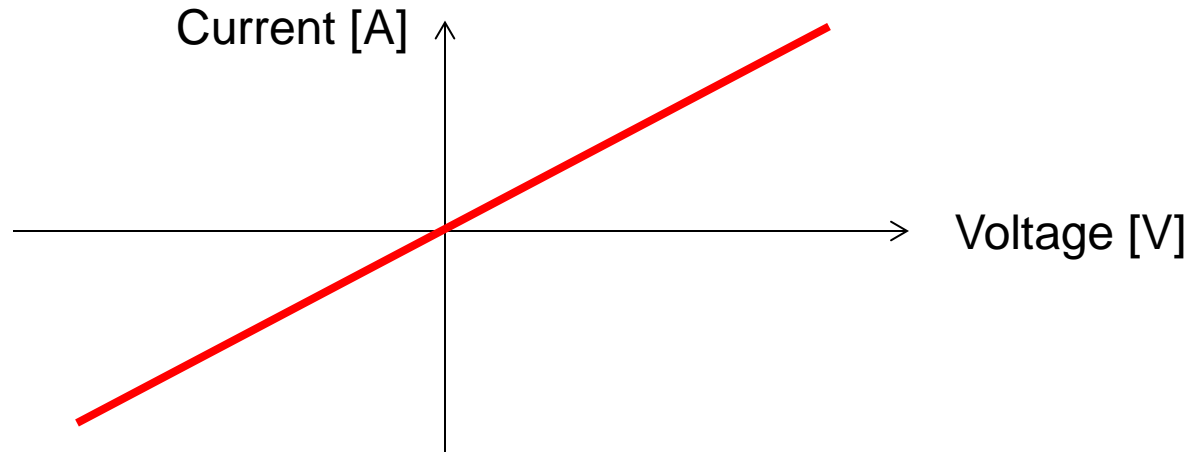


- A diode

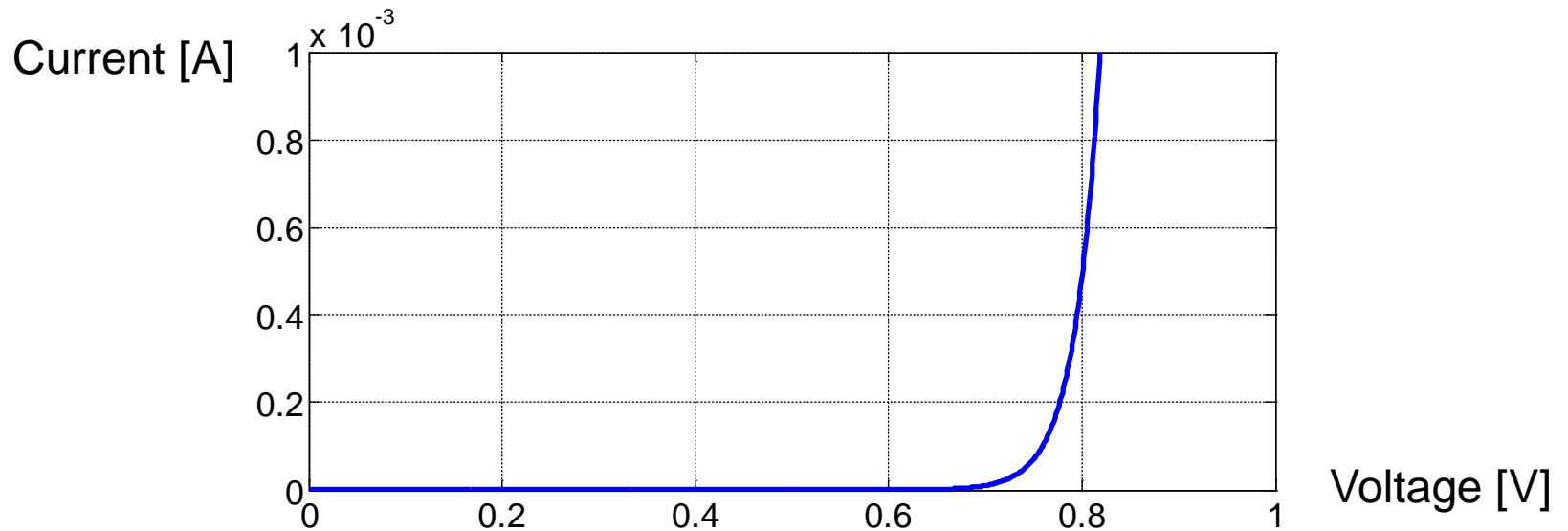


Diode

- Its symbol

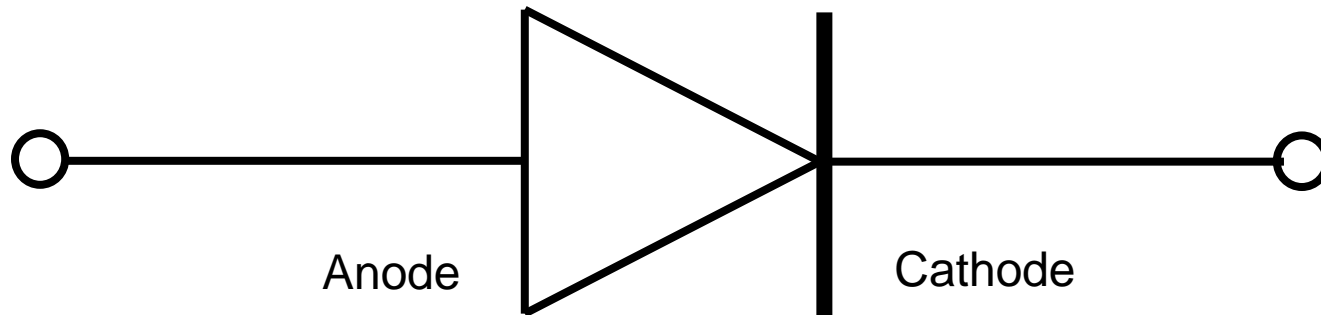


- Ideally, a perfect rectifier

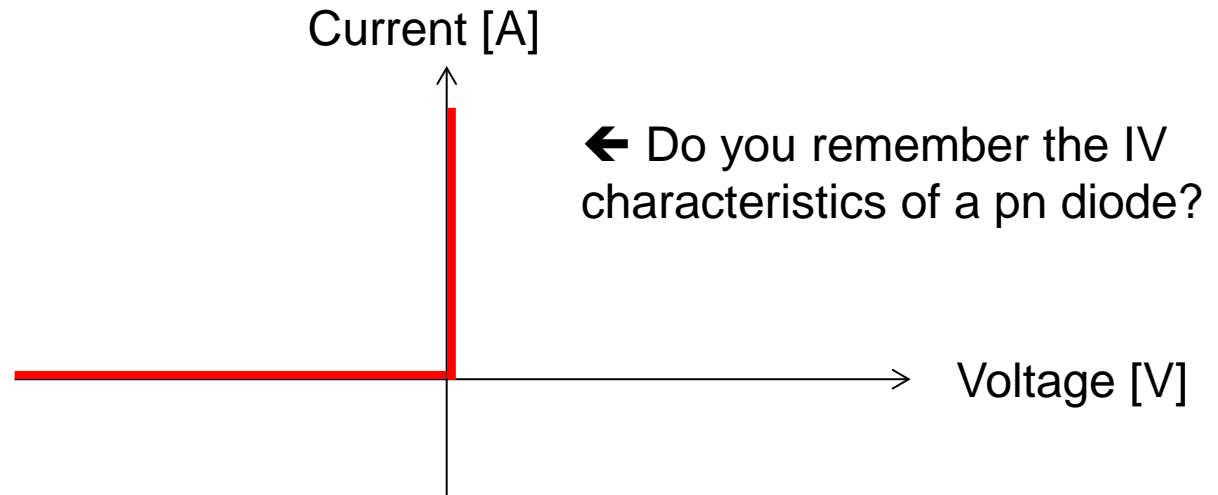

Example 3.4


- A diode-resistor combination

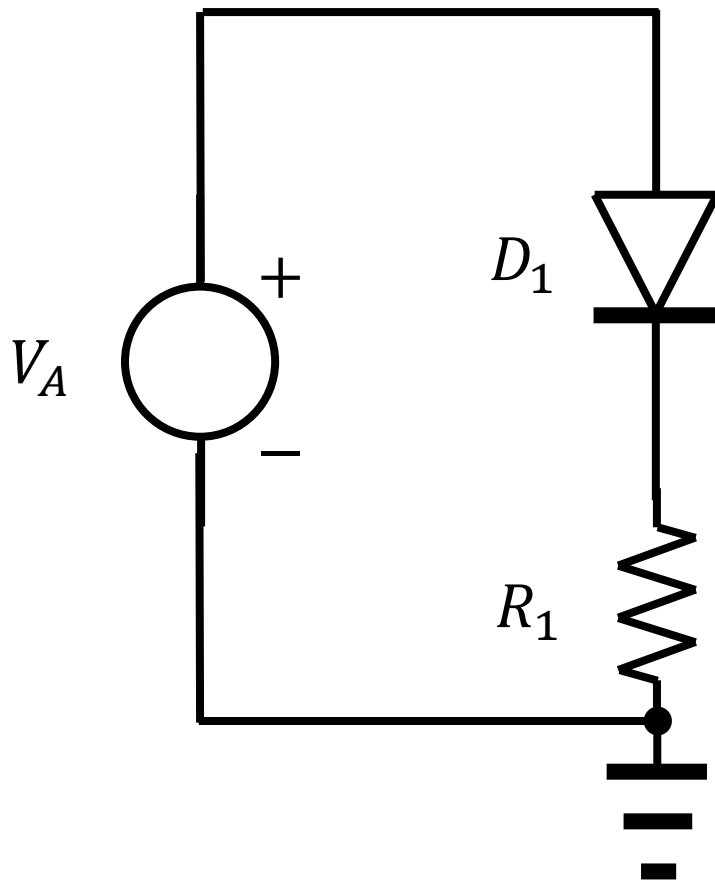

- ← Consider two cases, $V_A > 0$ and $V_A < 0$.
- ← Draw the IV curve.


Example 3.6

- An OR gate

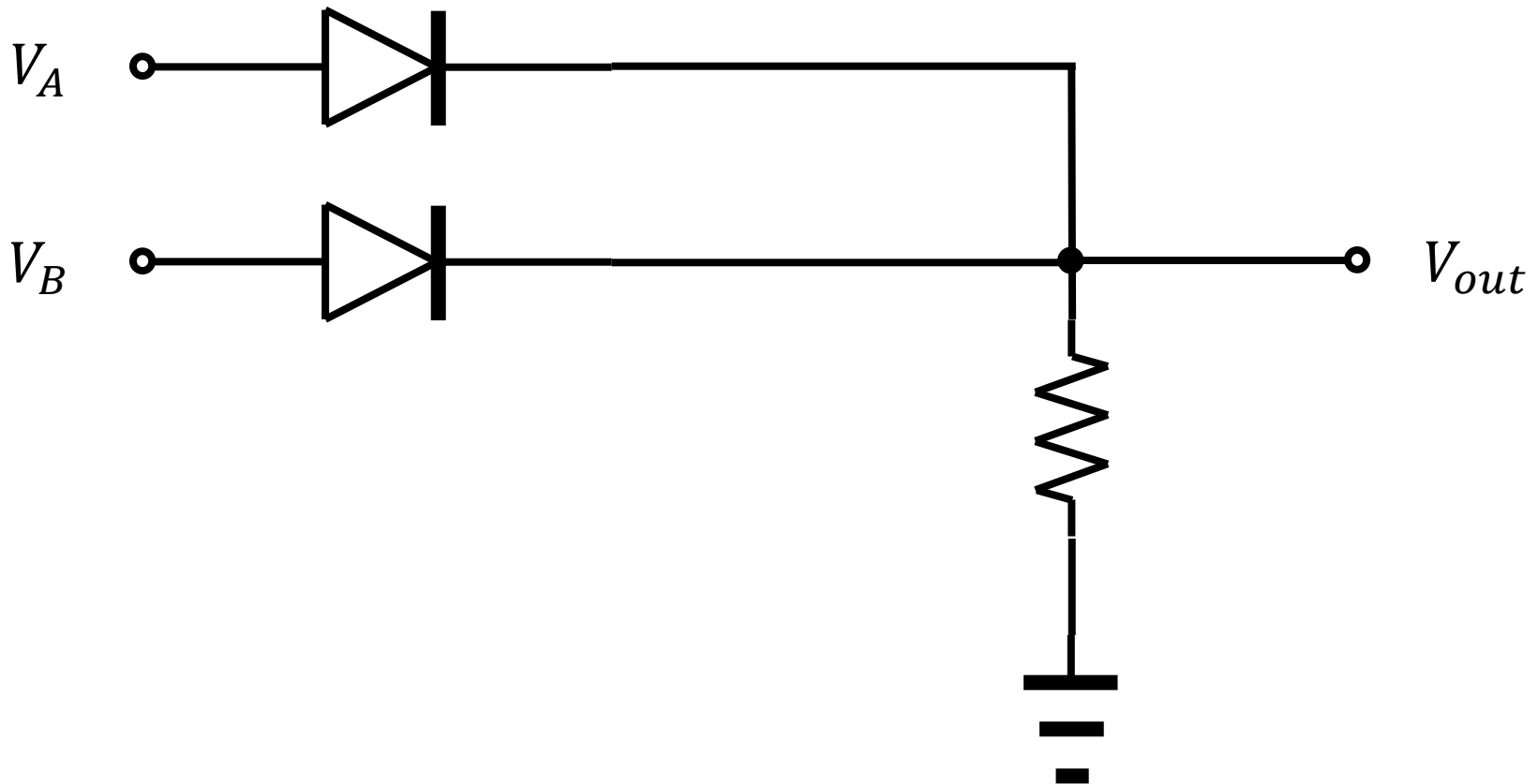

Rectifier


- Same circuit shown in Example 3.4.

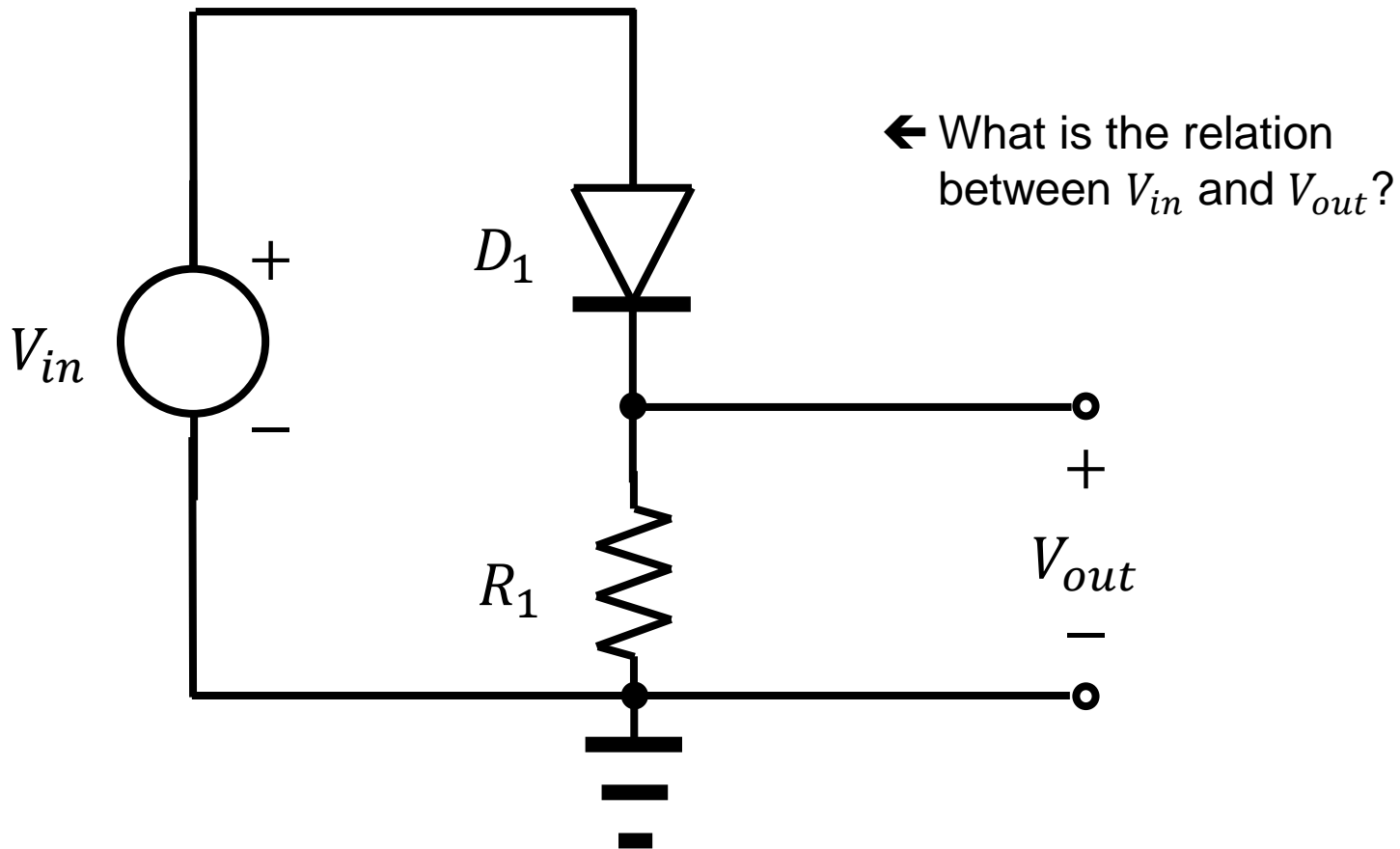

Input vs. output


- Input

- 50 Hz
- Pure sine
- No dc

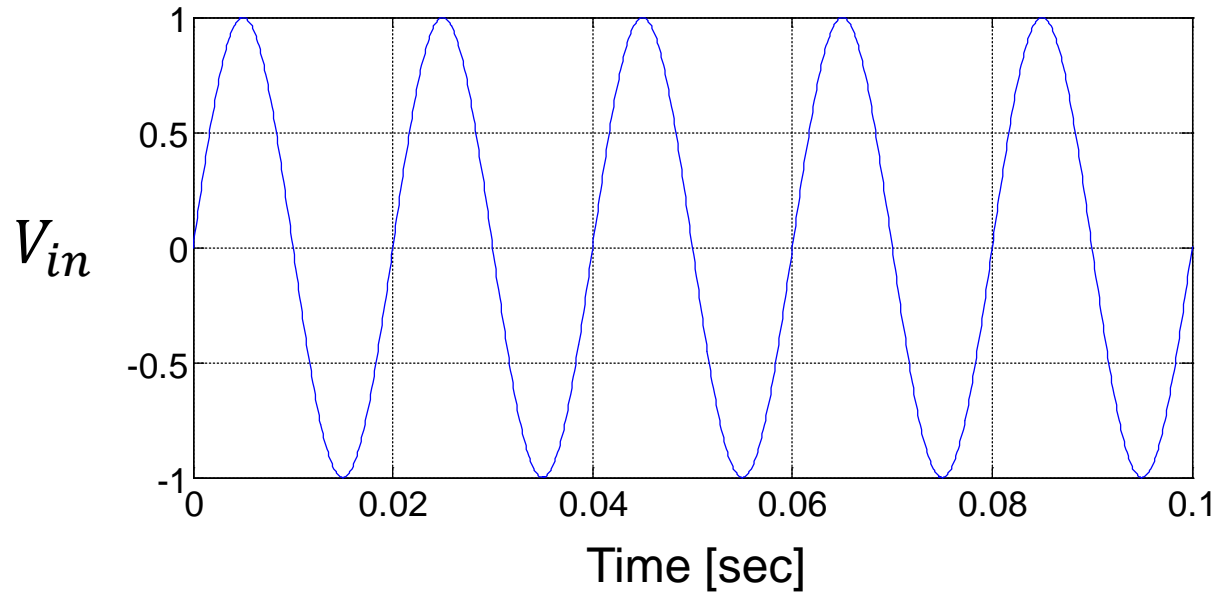

- Output

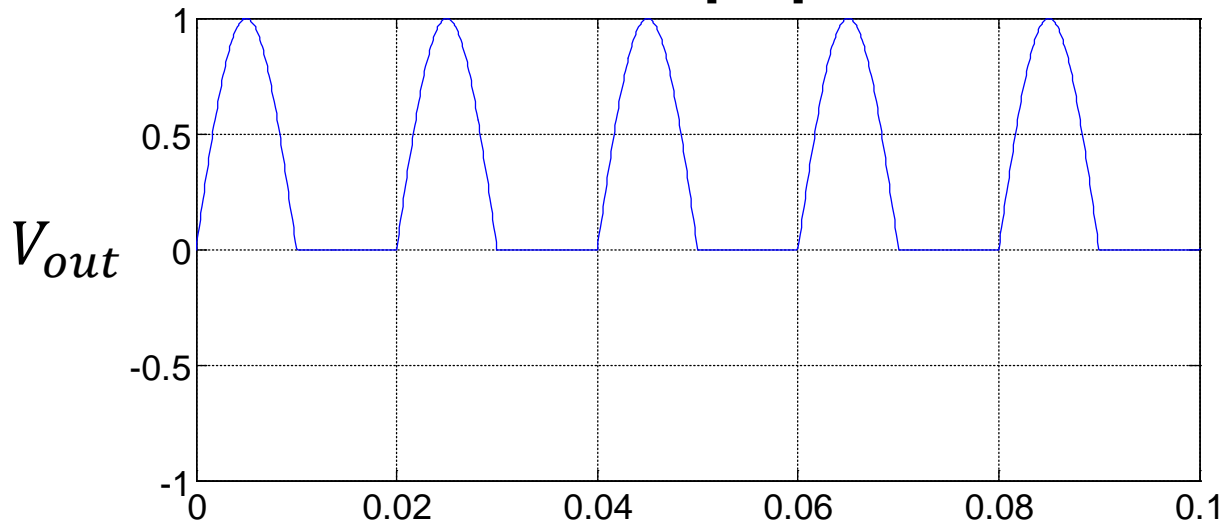
- 0, 50, 100, ... Hz
- dc voltage: $\frac{1}{\pi}$ V



Concept!

- How to detect the electromagnetic radiation
 - Nonlinearity is required.

Incident THz wave (High freq)

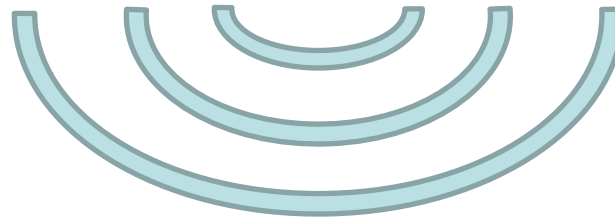


Output signal
(Low freq)



Rectifier, revisited

- Same circuit shown in Example 3.4.

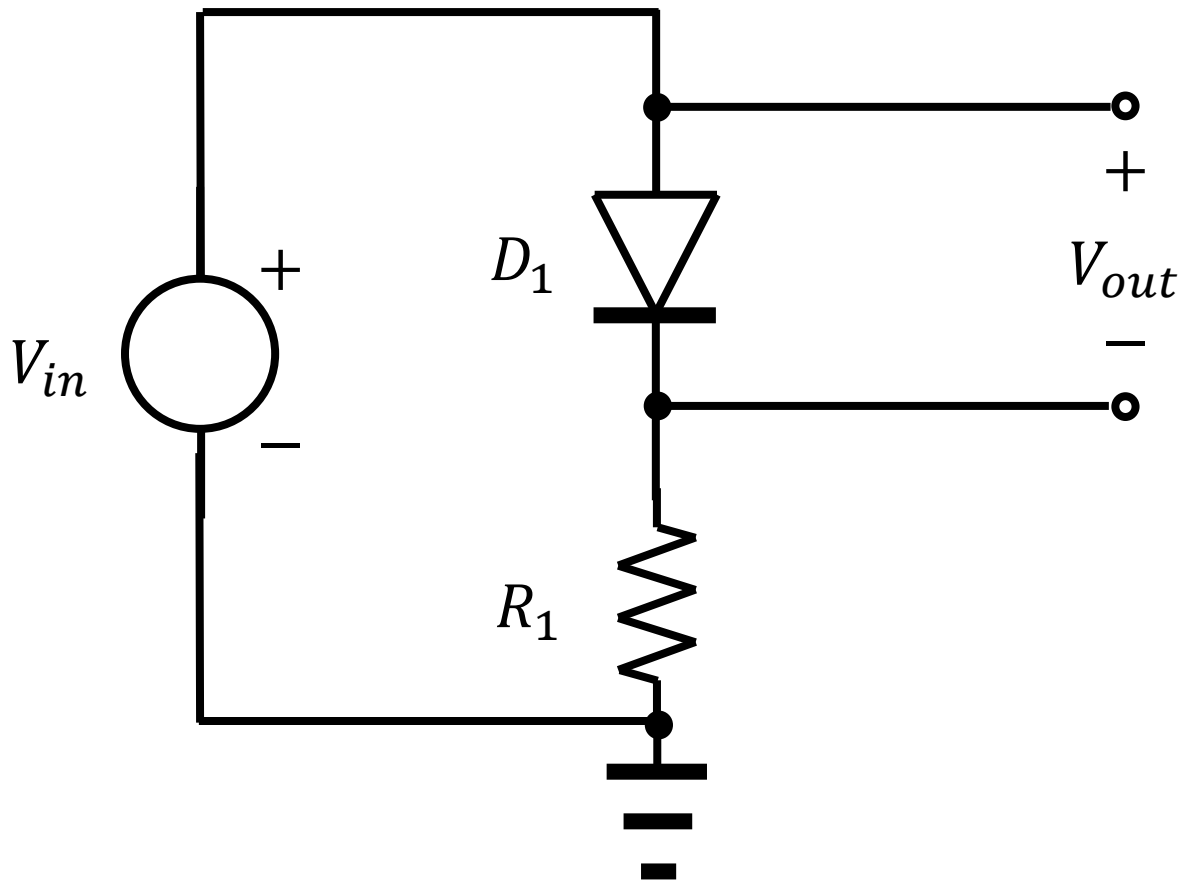


pn junction as a diode

- Exponential model

$$I_D = I_s \left(\exp \frac{V_D}{V_T} - 1 \right)$$

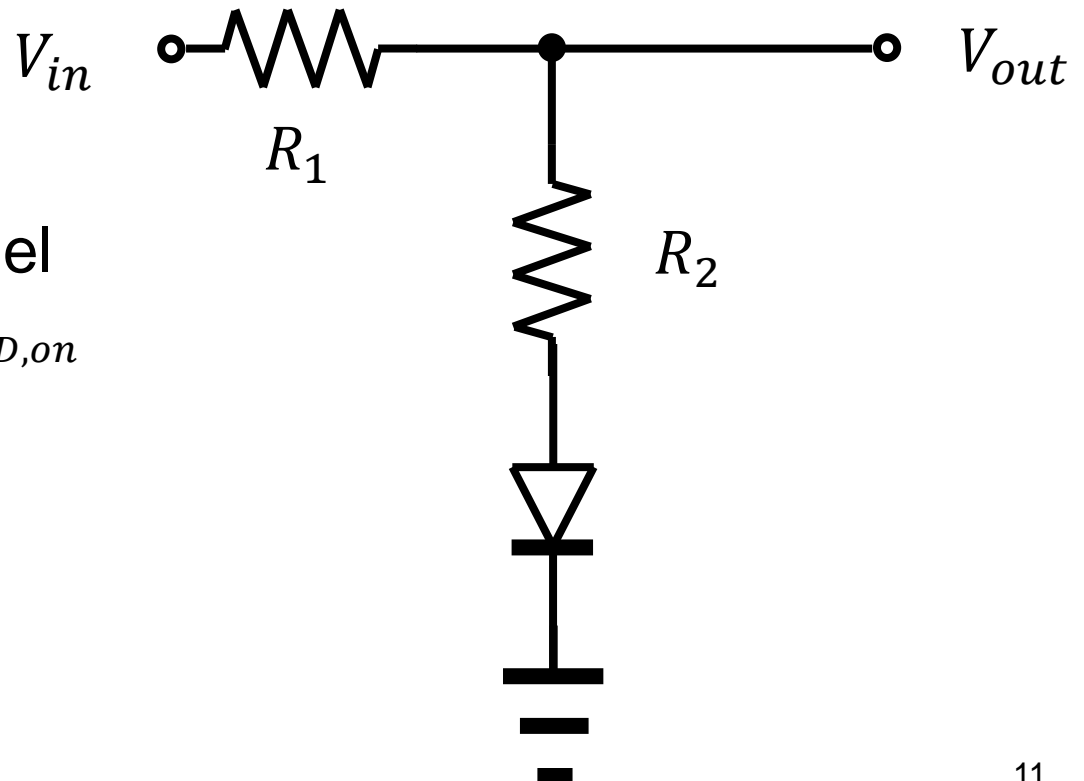- Constant-voltage model
 - An “offset” voltage of $V_{D,on}$



Read your textbook.

- Today, we have covered up to Sec.3.2.
 - Up to p. 59.
 - Sec. 3.3, “Additional examples,” will be skipped.
- On Wednesday, we will finish the short chapter, Ch. 4.
 - Read your textbook in advance.
 - Especially, Sec. 3.4.