


# Homework#7 – The last one

---

- Razavi, 2<sup>nd</sup> edition (international)
  - Device parameters in p. 796
  - 1) P17.4
  - 2) G-SPICE exercise of P17.4
  - 3) P17.20 (Assume that the gate of M1 is also biased at 1 V.)
  - 4) G-SPICE exercise of P17.20
  - 5) P17.25
  - 6) P17.38
  - 7) P17.43
  - 8) P17.50
- Due: Next Wednesday (Not Monday)
 
# Source degeneration (1/2)

- A resistor placed in series with the source terminal



# Source degeneration (2/2)

---

- Now we have to find the source voltage.
  - (Saturation current of the MOSFET) = (Current flowing through  $R_S$ )
  - After a simple manipulation, we can find

$$V_S = V_G + V_1 - V_{TH} - \sqrt{V_1^2 + 2(V_G - V_{TH})V_1}$$


- Here,

$$V_1 = \frac{1}{\mu_n C_{ox} \frac{W}{L} R_S}$$
 
# Effect of $R_S$ (1/2)

---


- Reduction of the gate-source voltage
  - Therefore, also reduction of the gain.
- For a while, neglect the channel-length modulation.



# Effect of $R_S$ (2/2)

- After a simple manipulation,

$$A_v = -\frac{g_m R_D}{1 + g_m R_S}$$

 


# Example 17.20

---


- CS with degeneration
 
$$A_v = -\frac{R_D}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}}$$



 
# Output impedance of CS (1/2)

- Still neglecting the channel-length modulation
  - No current!


 
# Output impedance of CS (2/2)

- Now considering the channel-length modulation
  - Output resistance is  $r_o + (g_m r_o + 1)R_S$ .






  
# Examples 17.23 and 17.24

---

- Compute the output resistance.
  - What is the difference?



---

# Lecture23:

# Bipolar junction transistors



Sung-Min Hong ([smhong@gist.ac.kr](mailto:smhong@gist.ac.kr))

Semiconductor Device Simulation Lab.  
School of Electrical Engineering and Computer Science  
Gwangju Institute of Science and Technology
  
# Bipolar transistor

---

- Bipolar junction transistor (BJT)
  - Three doped regions forming a sandwich



# The first transistor

---

- Invented in 1947 by Shockley, Barttain, and Bardeen
  - To be specific, on December 16, 1947
  - Demonstrated to executives, on December 23, 1947
  - (Not 1945!)




Replica of the first transistor, the point-contact transistor (Google images)
 
# Three key concepts of BJT





---

- Emphasized by the inventor of the junction transistor
  - 1) Minority carrier injection into the base layer which increases exponentially with forward emitter bias
  - 2) Application of reverse voltage at the collector junction
  - 3) Favorable geometry and doping levels so as to obtain good emitter to collector efficiency



William Shockley,  
the inventor of the  
BJT  
(IEEE TED, vol. 23,  
p. 597, 1976)

# How to fabricate it

    

# CMOS versus BJT


---

- Why do we still study the BJT? (Taken from Sedra and Smith)
  - The MOSFET is undoubtedly the most widely used electronic device.
  - CMOS technology is the technology of choice in the design of integrated circuits.
  - The BJT remains a significant device that excels in certain applications.
  - For instance, the reliability of BJT circuits under severe environmental conditions makes them the dominant device in certain automotive applications.
  - The BJT is the preferred device in very-high-frequency applications.
  - Finally, the BJT can be combined with MOSFETs. (BiCMOS)

# We will show that...

---

 - (a) The current flow from the emitter to the collector can be viewed as a current source tied between these two terminals.
- (b) This current is controlled by the voltage difference between the base and the emitter.
- In other words,
  - A voltage-controlled current source!





 
# Assumption

---



- Forward active region
  - Positive  $V_{BE}$
  - Negative  $V_{BC}$
  - For example, in the figure,  
 $V_{BE} = 0.8 \text{ V}$   
 $V_{BC} = -0.2 \text{ V}$


  
# Linux is not Unix.

---

- A bipolar transistor is not two connected diodes.
  - Positive



# Analogy

---

- A cliff
  - Potential barrier seen by electrons
- Two ways on top
  - Narrow path (to base)
  - Broad path (to collector)




(Both taken from Google images)


 
# Electron flux

---


- First, consider the electron flux.
  - There will be the flux generated by a positive  $V_{BE}$ .


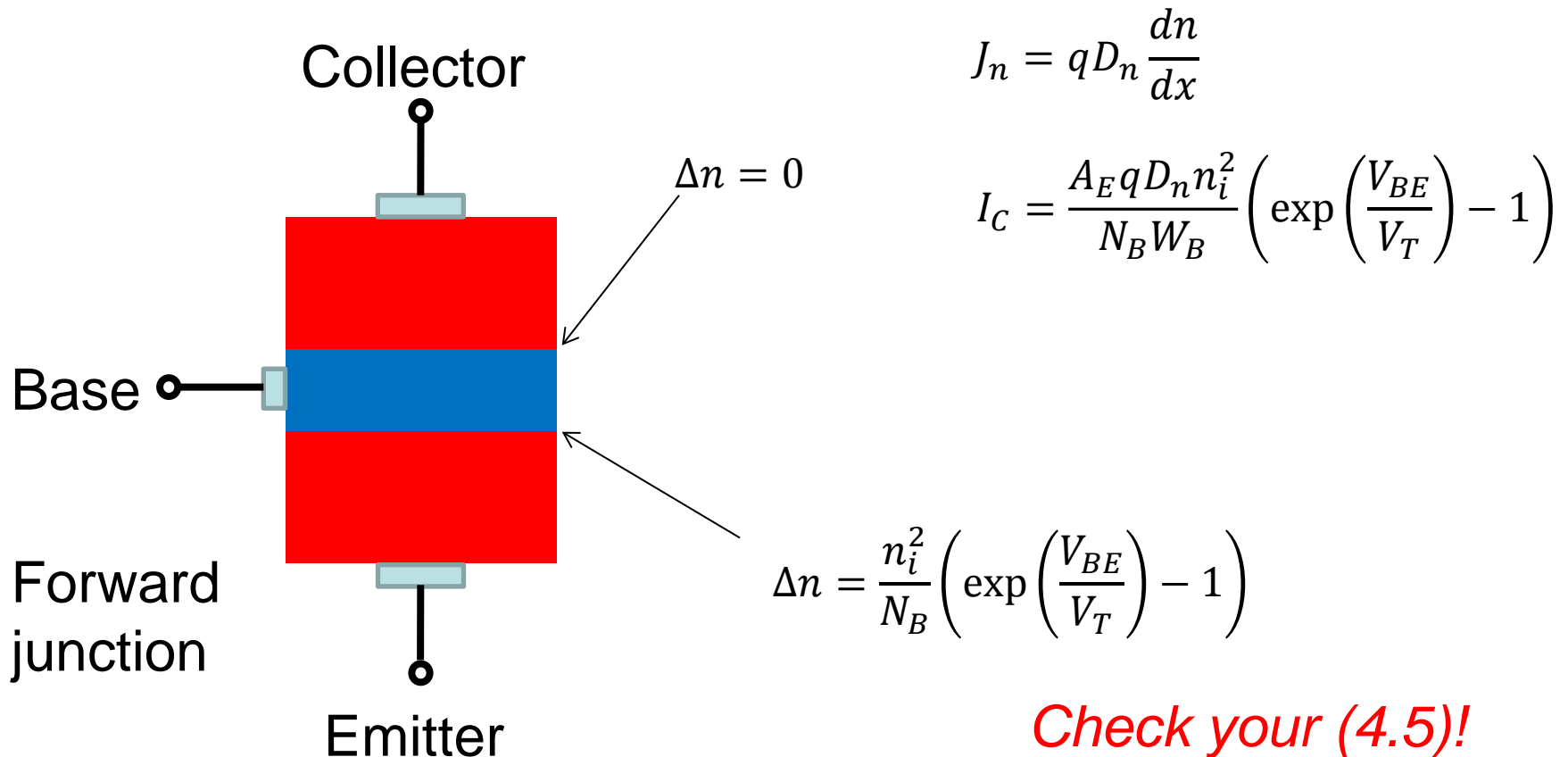
# Collector current

---


- Calculate it using the diffusion current.


 
# Base current

---

- Hole flux of the base-emitter junction
  - Doping levels, diffusion constants, diffusion lengths




$$I_C = \beta I_B$$
 
# Gummel plot

---

- IV curves for the BJT
  - Collector and base currents



Simulated Gummel plot  
of a HBT  
(Taken from Hong, JCE,  
vol. 8, p. 225, 2009)

Fig. 19 Gummel plot.  $V_{CB} = 0.1$  V

# Compare $g_m$

---

- Transconductance is given by  $g_m = \frac{dI_C}{dV_{BE}}$ .

$$I_C = I_S \exp \frac{V_{BE}}{V_T}$$

$$g_m = \frac{I_C}{V_T}$$

- How about the MOSFET?

$$I_D = ???$$

$$g_m = ???$$

- For a given current, which one has higher  $g_m$ ?




# Small-signal model

---

- Quite similar with the MOSFET model
  - Finite resistance between the base and emitter


$$r_{\pi} = \frac{\beta}{g_m}$$

 
 
# Early effect (1/2)

---

- For higher  $V_{CE}$ ,
  - The depletion region between the base and collector is widened.




# Early effect (2/2)

---

- Its modeling
  - The IV characteristics is now modified:
 
$$I_C = \left( I_S \exp \frac{V_{BE}}{V_T} \right) \left( 1 + \frac{V_{CE}}{V_A} \right)$$




# Output resistance

---

- It is easy to show that

 
$$\frac{dI_C}{dV_{CE}} = \left( I_S \exp \frac{V_{BE}}{V_T} \right) \frac{1}{V_A}$$
$$r_O \approx \frac{V_A}{I_C}$$



 
# Saturation?

---

- What was the saturation in the MOSFET?
  - Saturation of the drain current, as the drain voltage increases.
- What is the saturation in the BJT?
  - Saturation of the collector current, as the base current increases.



*Both junctions are forward biased.*

 


Typical output characteristics  
(Taken from Wikipedia)

# Small-signal model

---

- Useful expressions
 
$$g_m = \frac{I_C}{V_T}$$
$$r_\pi = \frac{\beta}{g_m}$$
$$r_o \approx \frac{V_A}{I_C}$$



# Biasing

---


- Example 5.7
  - DC analysis?
  - (Recall its MOS counterpart.)

- Specific values

$$V_{CC} = 2.5 \text{ V}$$

$$R_B = 100 \text{ k}\Omega$$

$$R_C = 1 \text{ k}\Omega$$

 

*Voltage?*

*It would be  $\frac{V_{CC} - V_{BE}}{R_B}$ .*

# Self-biased stage


---

- Which one is higher?
  - Collector voltage or base voltage?
  - In the forward active region!

$$I_C = \frac{V_{CC} - V_{BE}}{R_C + \frac{R_B}{\beta}} \quad \leftarrow \text{Why?}$$

- Uncertain  $V_{BE}$  and  $\beta$
- What can we do?

$$R_C \gg \frac{R_B}{\beta}$$

 



# Example 5.14

---

- Design the self-biased stage.

- In this example, we assume

$$R_C \approx 10 \frac{R_B}{\beta}$$


- It means  $I_C = \frac{V_{CC} - V_{BE}}{1.1 R_C}$ .

- We want to have  $g_m$  of  $\frac{1}{13 \Omega}$  in this example.

- For BJTs,  $g_m = \frac{I_C}{V_T}$ . Therefore,  $I_C = 2 \text{ mA}$ .



- Then,
 
$$R_C \approx \frac{V_{CC} - V_{BE}}{1.1 I_C} = 475 \Omega$$


  
# Common-emitter (1/2)

- You can easily imagine that
  - There is a common-emitter configuration.



# Common-emitter (2/2)

---

- Voltage gain?

- Same with the CS stage:

$$A_v = -g_m(R_C || r_o)$$

- Impedances?

- Input impedance

$$R_{in} = r_{\pi} = \frac{\beta}{g_m}$$

- Output impedance

$$R_{out} = R_C || r_o$$

# Common-emitter (2/2)

---

- Voltage gain?

- Same with the CS stage:

$$A_v = -g_m(R_C || r_O)$$

- When we have a very large  $R_C$ ,  $A_v \rightarrow -g_m r_O$ .

- For BJTs,  $g_m = \frac{I_C}{V_T}$  and  $r_O = \frac{V_A}{I_C}$ .

- Impedances?

- Input impedance

$$R_{in} = r_{\pi} = \frac{\beta}{g_m}$$

- Output impedance

$$R_{out} = R_C || r_O$$

# Example 5.21

---

- Collector current of 1 mA and  $R_C = 1\text{ k}\Omega$ .
  - Then,  $g_m$  is readily available.
$$g_m = \frac{1}{26\ \Omega}$$
  - When, the Early voltage is 10 V,  $r_o = \frac{10\text{ V}}{1\text{ mA}} = 10\text{ k}\Omega$ .
  - Overall,  $R_C || r_o = \frac{1}{1.1}\text{ k}\Omega \approx 0.91\text{ k}\Omega$ .