
Lecture25:

Bipolar junction transistors (3)


Sung-Min Hong (smhong@gist.ac.kr)

Semiconductor Device Simulation Lab.
School of Electrical Engineering and Computer Science
Gwangju Institute of Science and Technology

Small-signal model


- Quite similar with the MOSFET model
 - Finite resistance between the base and emitter

$$r_{\pi} = \frac{\beta}{g_m}$$

 

Early effect (1/2)

 
- For higher V_{CE} ,
 - The depletion region between the base and collector is widened.



Early effect (2/2)

- Its modeling
 - The IV characteristics is now modified:

 
$$I_C = \left(I_S \exp \frac{V_{BE}}{V_T} \right) \left(1 + \frac{V_{CE}}{V_A} \right)$$



Output resistance


- It is easy to show that
 
$$\frac{dI_C}{dV_{CE}} = \left(I_S \exp \frac{V_{BE}}{V_T} \right) \frac{1}{V_A}$$
$$r_O \approx \frac{V_A}{I_C}$$




Saturation?

 - What was the saturation in the MOSFET?
 - Saturation of the drain current, as the drain voltage increases.
- What is the saturation in the BJT?
 - Saturation of the collector current, as the base current increases.



Both junctions are forward biased.

 


Typical output characteristics
(Taken from Wikipedia)

Small-signal model

- Useful expressions
 
$$g_m = \frac{I_C}{V_T}$$
$$r_\pi = \frac{\beta}{g_m}$$
$$r_o \approx \frac{V_A}{I_C}$$



Biasing


- Example 5.7
 - DC analysis?
 - (Recall its MOS counterpart.)

- Specific values

$$V_{CC} = 2.5 \text{ V}$$

$$R_B = 100 \text{ k}\Omega$$

$$R_C = 1 \text{ k}\Omega$$

 

Current?

It would be $\frac{V_{CC} - V_{BE}}{R_B}$.


Self-biased stage

- Which one is higher?
 - Collector voltage or base voltage?
 - In the forward active region!

$$I_C = \frac{V_{CC} - V_{BE}}{R_C + \frac{R_B}{\beta}} \quad \leftarrow \text{Why?}$$

- Uncertain V_{BE} and β
- What can we do?

$$R_C \gg \frac{R_B}{\beta}$$

 

Example 5.14

- Design the self-biased stage.

- In this example, we assume

$$R_C \approx 10 \frac{R_B}{\beta}$$


- It means $I_C = \frac{V_{CC} - V_{BE}}{1.1 R_C}$.

- We want to have g_m of $\frac{1}{13 \Omega}$ in this example.

- For BJTs, $g_m = \frac{I_C}{V_T}$. Therefore, $I_C = 2 \text{ mA}$.



- Then,
 
$$R_C \approx \frac{V_{CC} - V_{BE}}{1.1 I_C} = 475 \Omega$$



Common-emitter (1/2)

  - You can easily imagine that
 - There is a common-emitter configuration.



Common-emitter (2/2)

- Voltage gain?

- Same with the CS stage:

$$A_v = -g_m(R_C || r_o)$$

- Impedances?

- Input impedance

$$R_{in} = r_\pi = \frac{\beta}{g_m}$$

- Output impedance

$$R_{out} = R_C || r_o$$

Common-emitter (2/2)

- Voltage gain?

- Same with the CS stage:

$$A_v = -g_m(R_C || r_O)$$

- When we have a very large R_C , $A_v \rightarrow -g_m r_O$.

- For BJTs, $g_m = \frac{I_C}{V_T}$ and $r_O = \frac{V_A}{I_C}$.

- Impedances?

- Input impedance

$$R_{in} = r_{\pi} = \frac{\beta}{g_m}$$

- Output impedance

$$R_{out} = R_C || r_O$$

Example 5.21

- Collector current of 1 mA and $R_C = 1\text{ k}\Omega$.

- Then, g_m is readily available.

$$g_m = \frac{1}{26\ \Omega}$$

- When the Early voltage is 10 V, $r_O = \frac{10\text{ V}}{1\text{ mA}} = 10\text{ k}\Omega$.




- Overall, $R_C || r_O = \frac{1}{1.1}\text{ k}\Omega \approx 0.91\text{ k}\Omega$.

Special topic

DIGITAL CMOS CIRCUITS


In circuit,

   - How can we represent 0 and 1?
 - V_{DD} is assigned to the logical value, 1.
 - GND is assigned to the logical value, 0.



Inverter

 - When the output becomes 0?
 - Only when the input is high.
 - *You have seen it before!*



V_{in}	V_{out}
0	1
1	0

Voltage transfer

- When $V_{in} < V_{TH}$,
 - Trivially, $V_{out} = V_{DD}$.
- When V_{in} is slightly larger than V_{TH} , the NMOSFET is in the saturation region.


$$V_{out} = V_{DD} - I_D R_D$$
$$V_{out} = V_{DD} - \frac{1}{2} \mu_n C_{ox} \frac{W}{L} R_D (V_{in} - V_{TH})^2$$

- When V_{in} is further increased, the NMOSFET is in the triode region.

$$V_{out} = V_{DD} - \frac{1}{2} \mu_n C_{ox} \frac{W}{L} R_D [2(V_{in} - V_{TH})V_{out} - V_{out}^2]$$



G-SPICE example (1)

 - Following parameters are used.
 - $\mu_n C_{ox} = 200 \mu\text{A}/\text{V}^2$, $V_{TH} = 0.4 \text{ V}$, $\frac{W}{L} = \frac{5}{0.18}$, $\lambda = 0.1 \text{ V}^{-1}$, $R_D = 2k\Omega$ and $V_{DD} = 1.8 \text{ V}$




G-SPICE example (2)

  - Different values of R_D (8000 Ohm and 500 Ohm)
 - $0 \rightarrow 1$ is always good, but, $1 \rightarrow 0$ depends on the situation.
 - Relative “strength” determines the VTC.




Standby(!) power

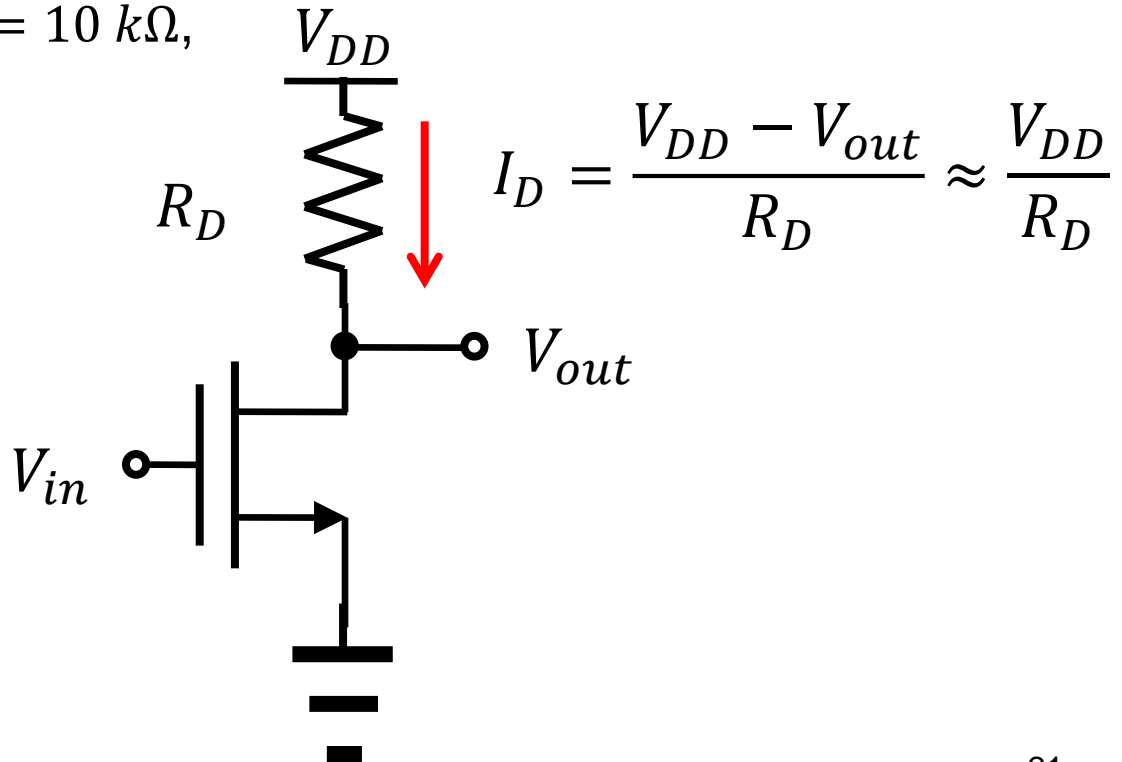- The biggest problem in the NMOS inverter
 - When $V_{in} = 0$, no standby power
 - When $V_{in} = V_{DD}$, the power consumption is (approximately) $\frac{V_{DD}^2}{R_D}$.
 - If $V_{DD} = 1.8 \text{ V}$ and $R_D = 10 \text{ k}\Omega$,
324 μW !




G-SPICE example (3)

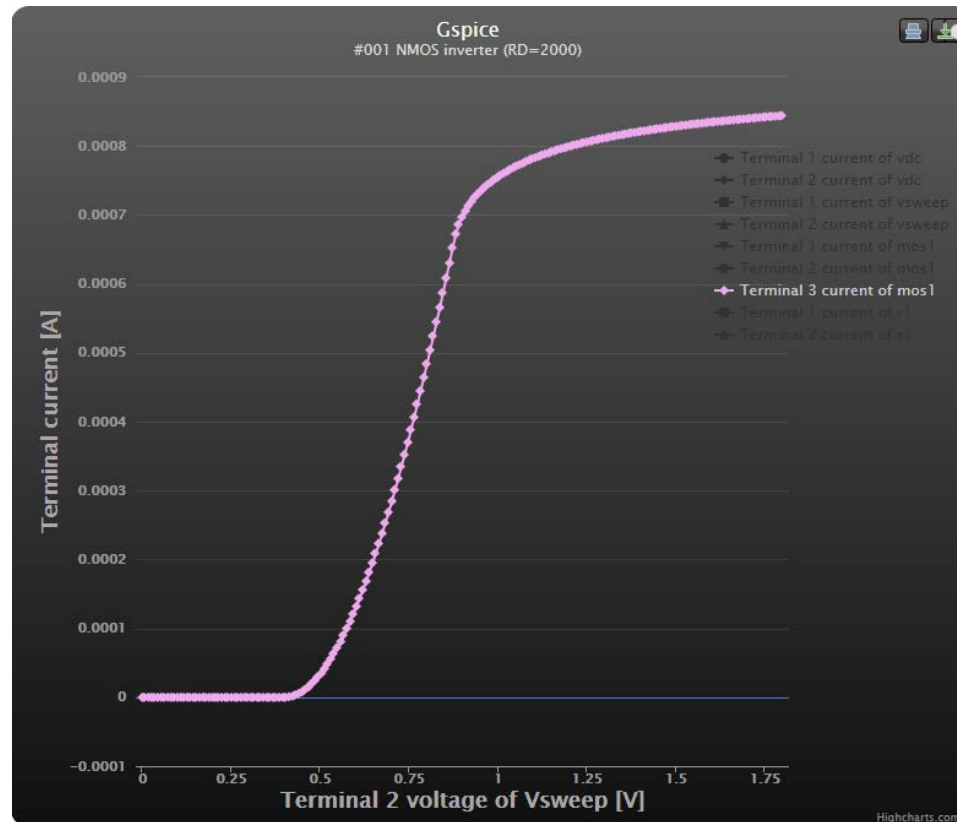- Current as a function of input voltage
 - Estimate the power consumption...





CMOS inverter

 - Ideal “pull-up” should have the following properties.
 - When $V_{in} = V_{DD}$, no current conduction.
 - When $V_{in} = 0$, improved current conduction.
- PMOS can do those jobs!





G-SPICE example (4)

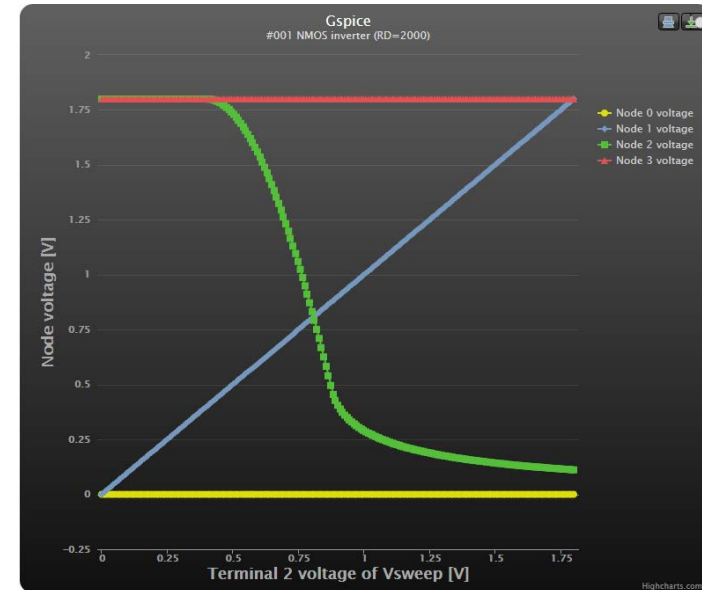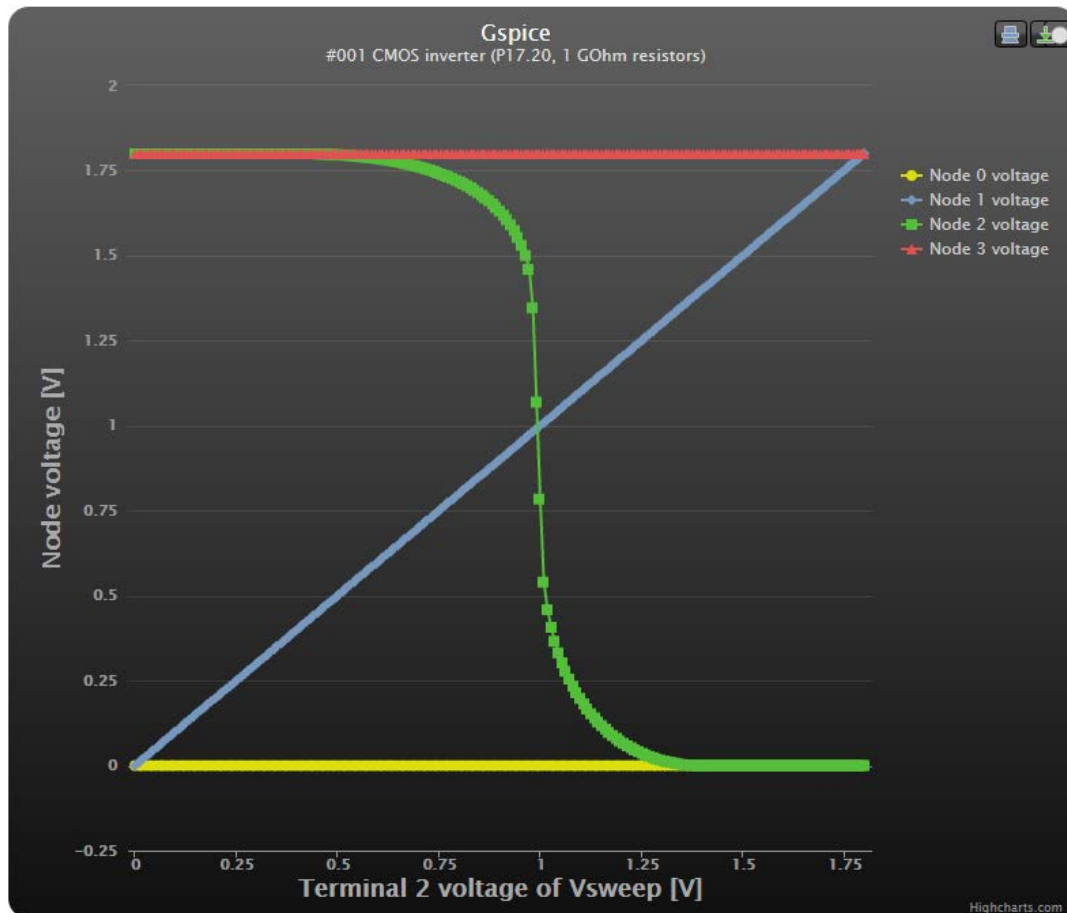- Parameters of P17.20
 - (Two large resistors are introduced.)



G-SPICE example (5)

 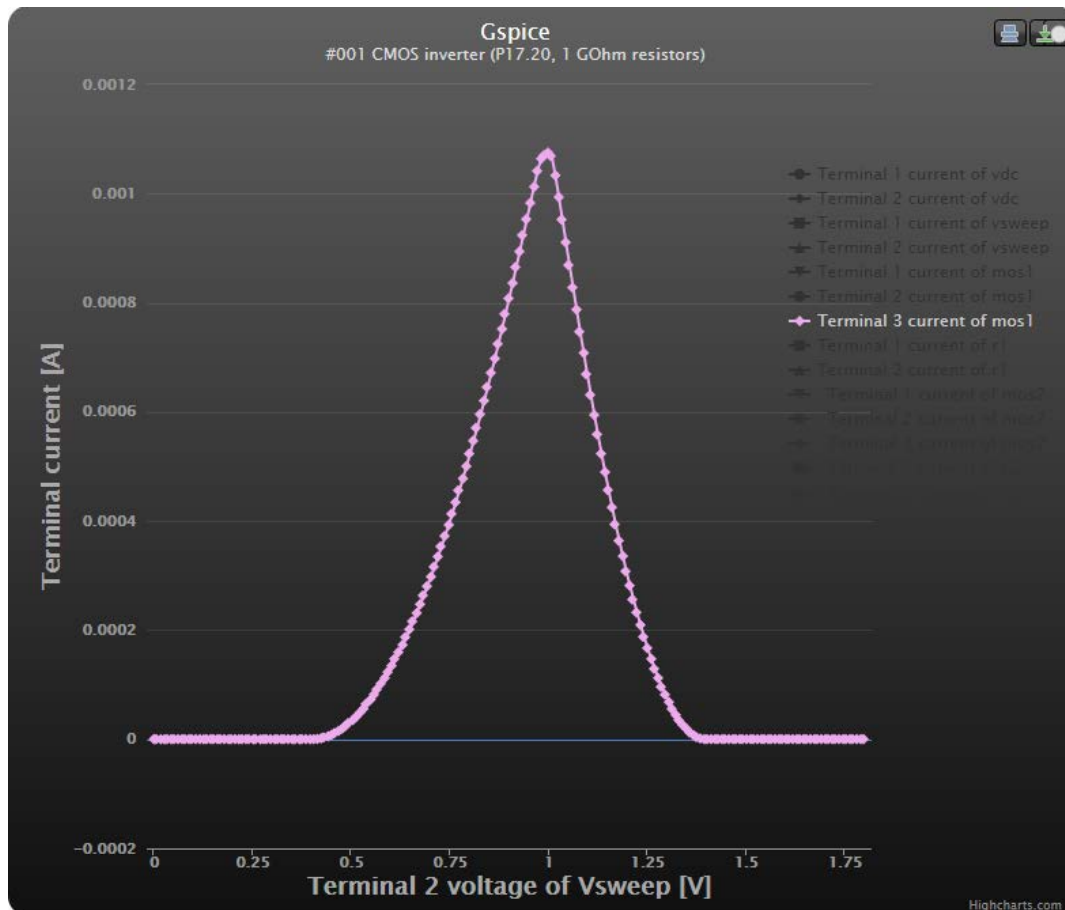- Even better news
 - No standby power is dissipated.



CLOSING REMARKS