
Lecture13:

CMOS amplifier, concept

Sung-Min Hong (smhong@gist.ac.kr)


Semiconductor Device Simulation Lab.
School of Electrical Engineering and Computer Science
Gwangju Institute of Science and Technology

NMOSFET


- In the NMOSFET, electrons are mobile carriers.
 - When V_{GS} is lower than V_{TH} , holes are depleted from the Si/SiO₂ interface.
 - When V_{GS} is larger than V_{TH} , electrons are collected at the Si/SiO₂ interface. (Electron inversion)
- Imagine its “dual” device.
 - Its V_{TH} is usually negative.
 - When V_{GS} is larger than V_{TH} ($|V_{GS}| > |V_{TH}|$), electrons are depleted from the Si/SiO₂ interface.
 - When V_{GS} is smaller than V_{TH} ($|V_{GS}| < |V_{TH}|$), holes are collected at the Si/SiO₂ interface. (Hole inversion)
 - Is there such a device? Yes.

PMOSFET

- The PMOSFET

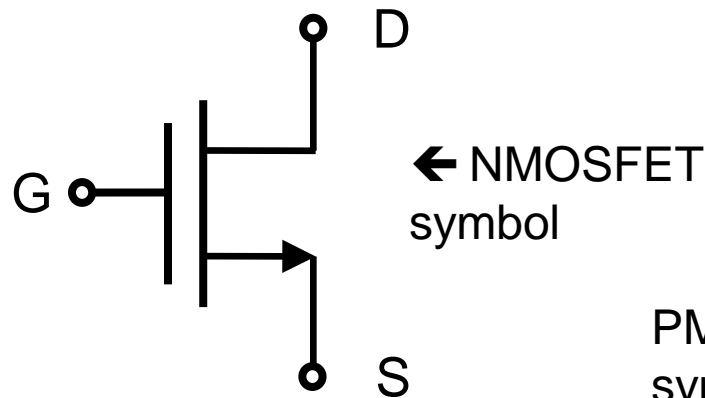


PMOSFET symbol →

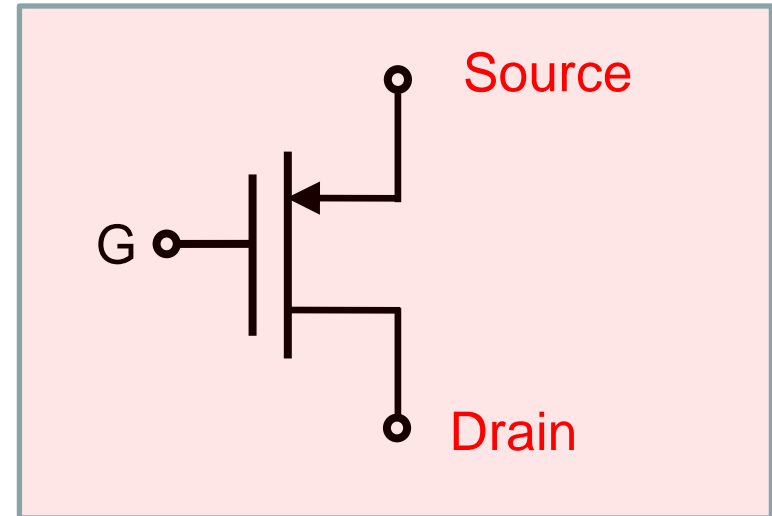

- The source voltage is the highest one.
- For example, $V_{TH,P} = -1.5$ V. Assume that V_S is 3 V. The gate voltage of 2 V does not turn on the transistor. The gate voltage of 1 V turns on the transistor.
- The drain voltage is lower than the source voltage. In the usual operation condition, the drain current is negative.

Biasing of PMOS devices

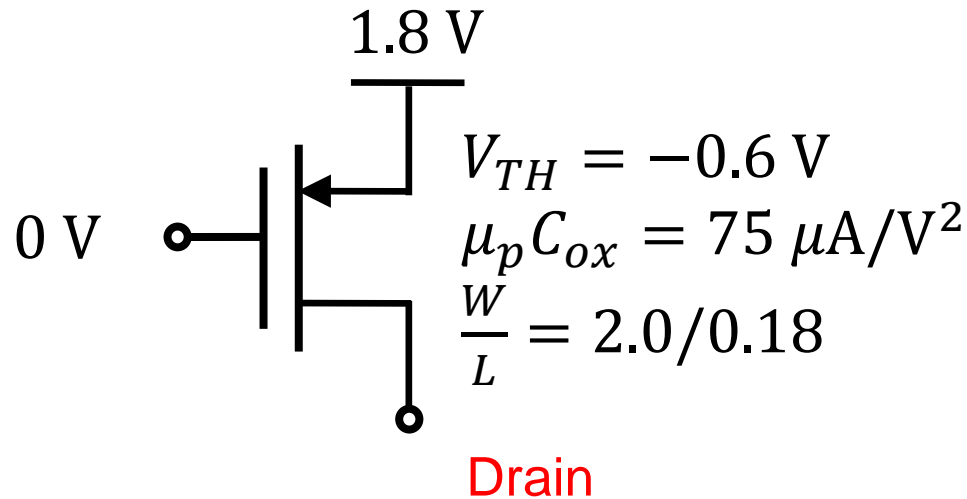
- Express the source current as a function of the drain voltage.
 - The absolute value of “gate overdrive” is 1.2 V.
 - It is not 0.6 V.



- Do the same job with the gate voltage of 1.8 V.

Why amplifiers?

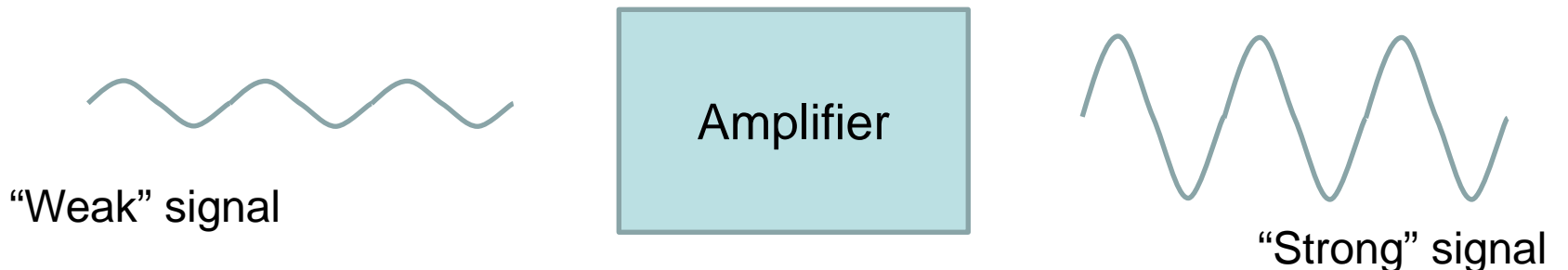
- Signal amplification
 - Usually, signals are “weak.” (in the μV or mV range)
 - It is too small for reliable processing.
 - If the signal magnitude is made larger, processing is much easier.



- For example, a voltage amplifier amplifies the input voltage signal. Its output is also a voltage.
- When $V_{in}(t) = V_{DC,in} + v_{in}(t)$, ideally, we want to have $V_{out}(t) = V_{DC,out} + A_v v_{in}(t)$.
- A_v is the voltage gain. (Of course, it is a unitless quantity.)


Transistor turned off

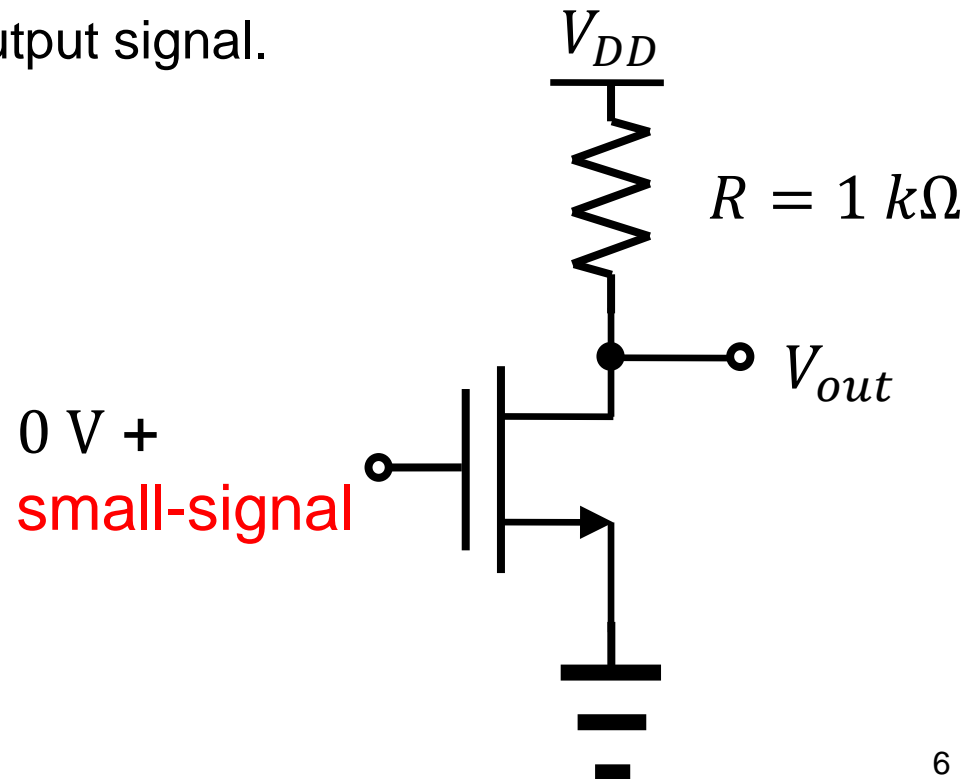- In the circuit shown in this slide, $V_{out} = V_{DD} - I_D R$.
 - But, the transistor is not turned on. ($I_D \approx 0$)
 - The transconductance(g_m) is zero.
 - The small-signal change of the gate voltage does not change I_D .
 - The circuit generates no output signal.



This is a solution.

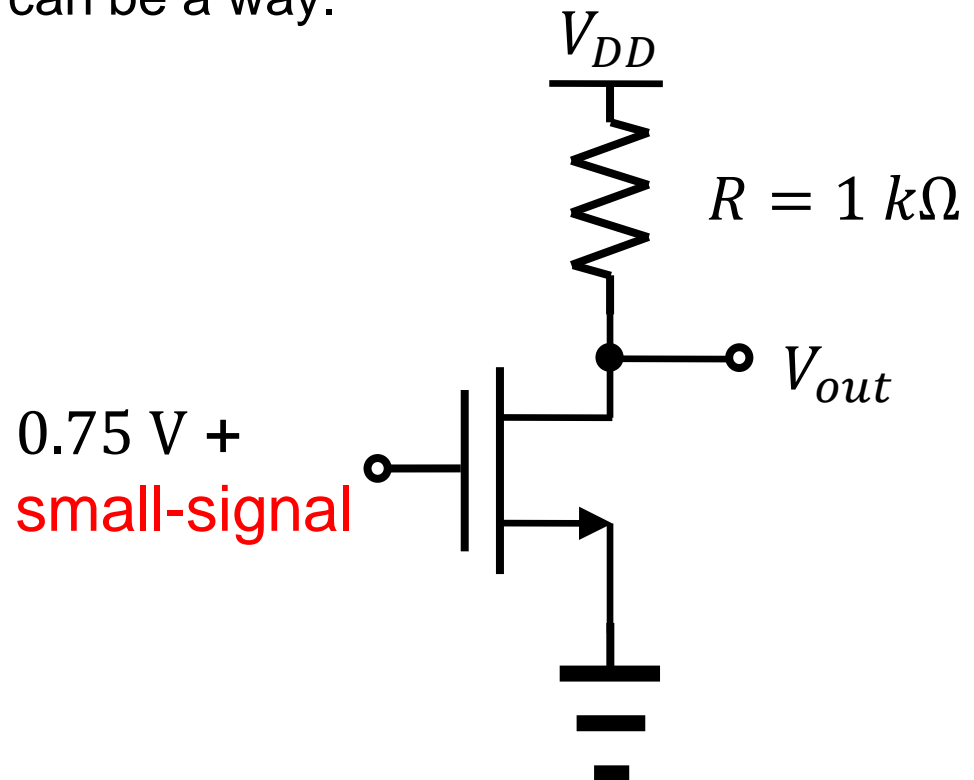- The following circuit shows a revised circuit.
 - It has a meaningful value of g_m . (As much as $V_{TH} < 0.75\text{ V}$)
 - Then, how can we generate 0.75 V , for example?
 - Use of a separate battery can be a way.



Homework#6 (1)

- Due: 09:00, April 30
- Write a program, which reads a netlist file.
 - In this program, the matrix describes a system:
 - For a voltage source:
 - The voltage difference between two terminals is fixed.
 - Sum of two terminal currents vanishes.
 - For a resistor:
 - The terminal current and the voltage difference satisfy Ohm's law.
 - Sum of two terminal currents vanishes.
 - For every element terminal, the terminal voltage is equal to the circuit node voltage.
 - For the GND node, the node voltage is zero.
 - For all other circuit nodes, the KCL is applied.

Homework#6 (2)

- (Continued)
 - For example, consider the example in Homework#4. A voltage source and a resistor are found.
 - The matrix is explicitly shown below.

$$\begin{bmatrix}
 0 & 0 & 1 & -1 & 0 & 0 & 0 & 0 & 0 & 0 \\
 1 & 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\
 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 & -1 \\
 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 & -1 & 0 \\
 0 & 0 & 0 & 0 & 1 & 0 & -1/R & 1/R & 0 & 0 \\
 0 & 0 & 0 & 0 & 1 & 1 & 0 & 0 & 0 & 0 \\
 0 & 0 & 0 & 0 & 0 & 0 & 1 & 0 & 0 & -1 \\
 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 & -1 & 0 \\
 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 & 0 \\
 1 & 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0
 \end{bmatrix} \times \begin{bmatrix} I_1^V \\ I_2^V \\ V_1^V \\ V_2^V \\ I_1^R \\ I_2^R \\ V_1^R \\ V_2^R \\ V_0 \\ V_{in} \end{bmatrix} = \begin{bmatrix} V_{source} \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

Homework#6 (3)

- (Continued)
 - In Homework#6, just solve the set of equations shown in the previous slide.
 - The fully functional code will be needed in Homework#7.

Homework#6 (4)

- Solve the following problems of the mid-term exam in 2018.
(Not 2017)
 - P4
 - P27
 - P28
 - P35
 - P36
 - P41
 - P42