

---

# Lecture16:

## Common-source amplifier (1)

Sung-Min Hong ([smhong@gist.ac.kr](mailto:smhong@gist.ac.kr))

Semiconductor Device Simulation Lab.  
School of Electrical Engineering and Computer Science  
Gwangju Institute of Science and Technology

# Common-source amplifier


---

- The source terminal is the reference.

– The output voltage is  $V_{out} = V_{DD} - I_D R_D$ .

$$V_{out}(t) =$$

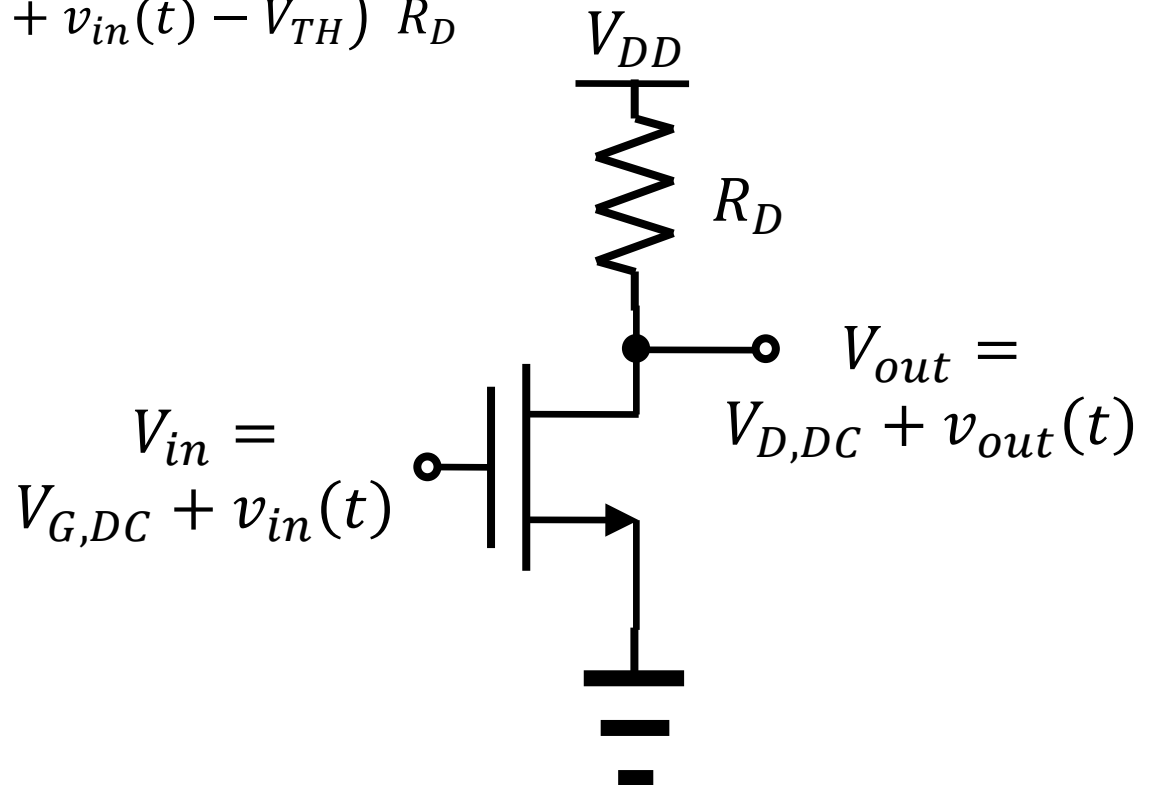
$$V_{DD} - \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{G,DC} + v_{in}(t) - V_{TH})^2 R_D$$


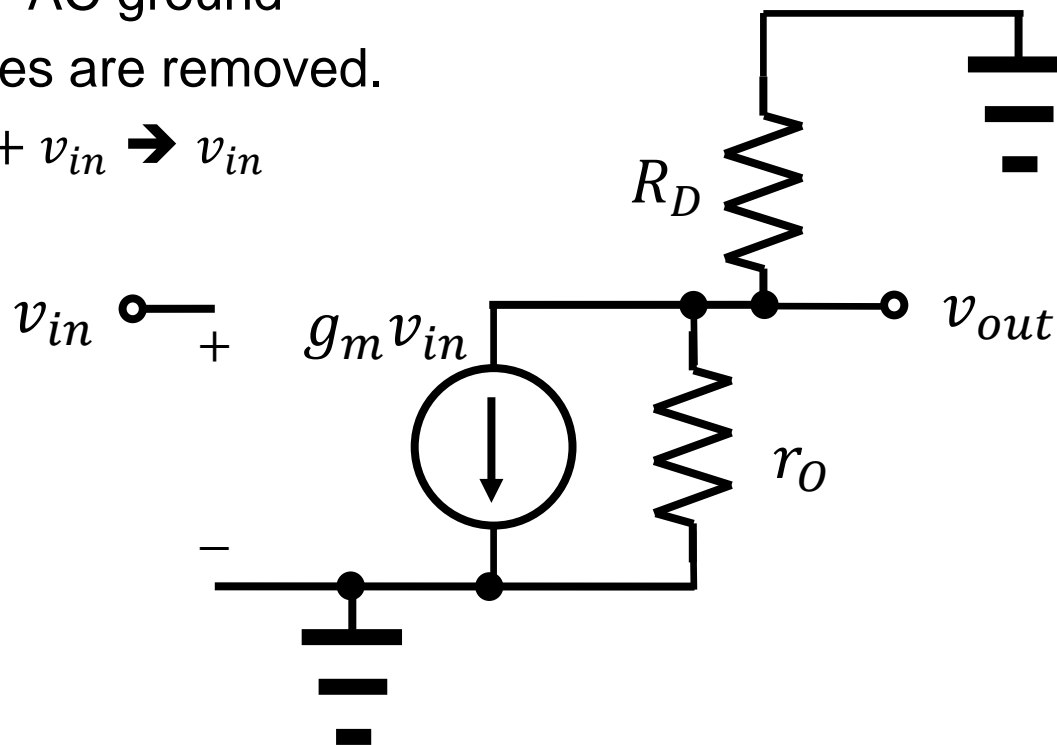
# Small-signal model

---


- Let's draw its small-signal model together!
  - A transistor small-signal model is introduced.
  - Resistors  $\rightarrow$  resistors
  - Ground  $\rightarrow$  AC ground
  - DC voltages are removed.
  - Ex)  $V_{G,DC} + v_{in} \rightarrow v_{in}$



# Gain

---

- Now, calculate the  $v_{out}$ .
  - KCL for the  $v_{out}$  node gives
$$v_{out} = -g_m(R_D || r_o)v_{in}$$
  - Therefore, the voltage gain,  $A_v$ , is
$$A_v = -g_m(R_D || r_o)$$

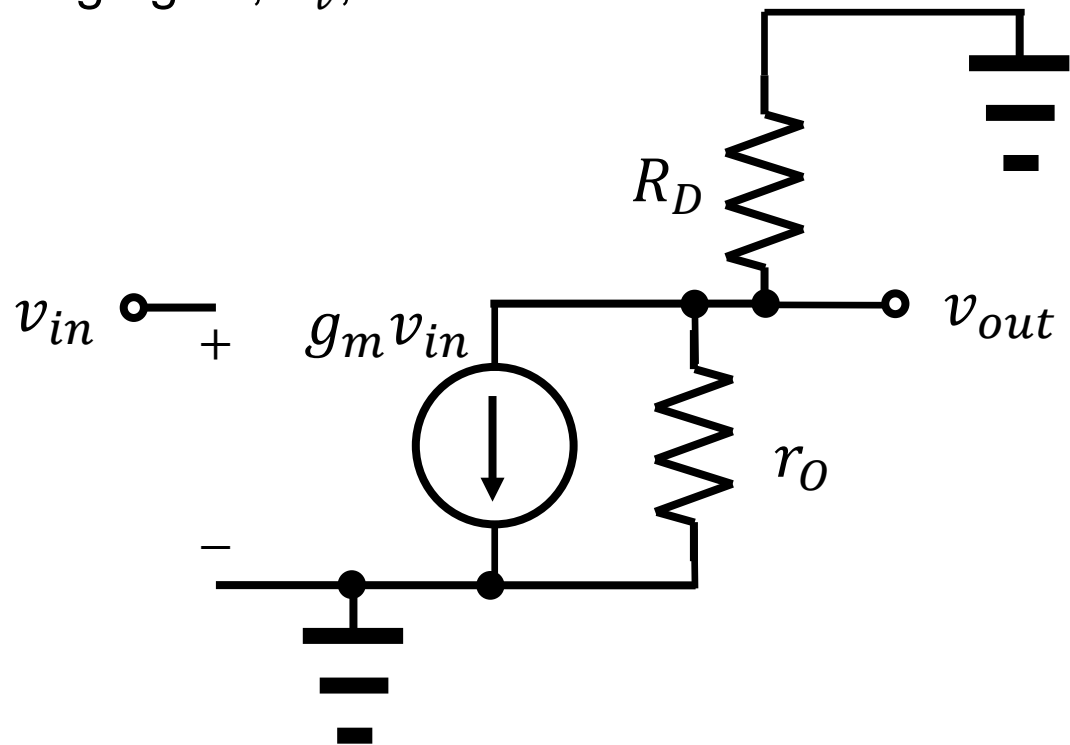

# Increasing the gain

---

- The voltage gain has two factors.
  - Transconductance( $g_m$ ): Selecting  $W$ ,  $L$ , and  $V_{GS}$  to maximize the transconductance
  - Resistance( $R_D || r_O$ ): A large  $R_D$  value is desirable. However, there is a restriction.


$$V_{D,DC} = V_{DD} - R_D I_{D,DC}$$

- A too large value of  $R_D$  reduces  $V_{D,DC}$  too much. The triode mode is not suitable for the amplification due to its smaller transconductance.
- A drain load other than a simple resistor can be tried.
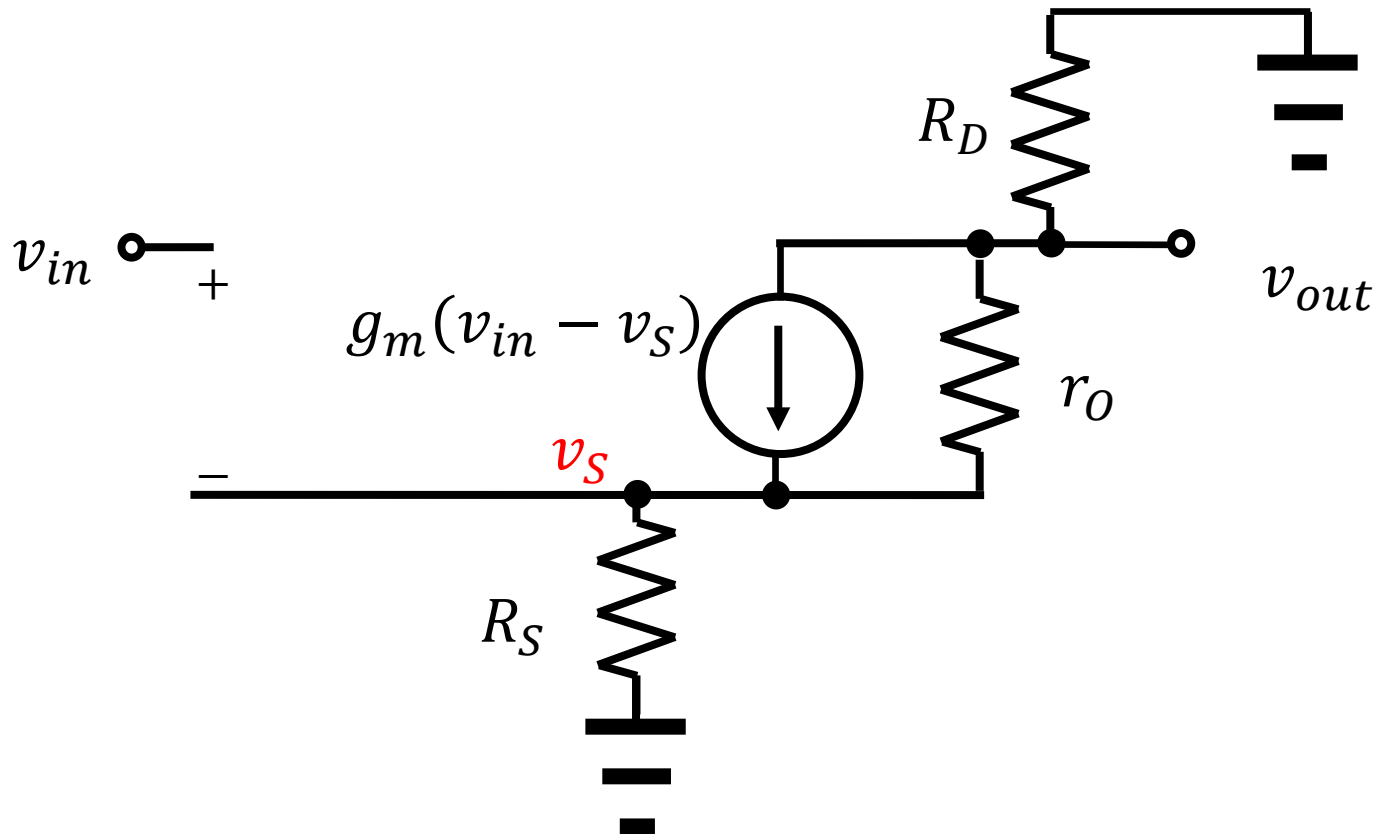
# Impact of $R_S$

---

- Consider a source resistance,  $R_S$ .
  - Repeat the previous slide.




# Input/output impedances

---

- When calculating the impedance, the voltage sources at other terminals are neglected.
- Input and output impedances

$$R_{in} = \infty$$


$$R_{out} = R_D || r_o$$

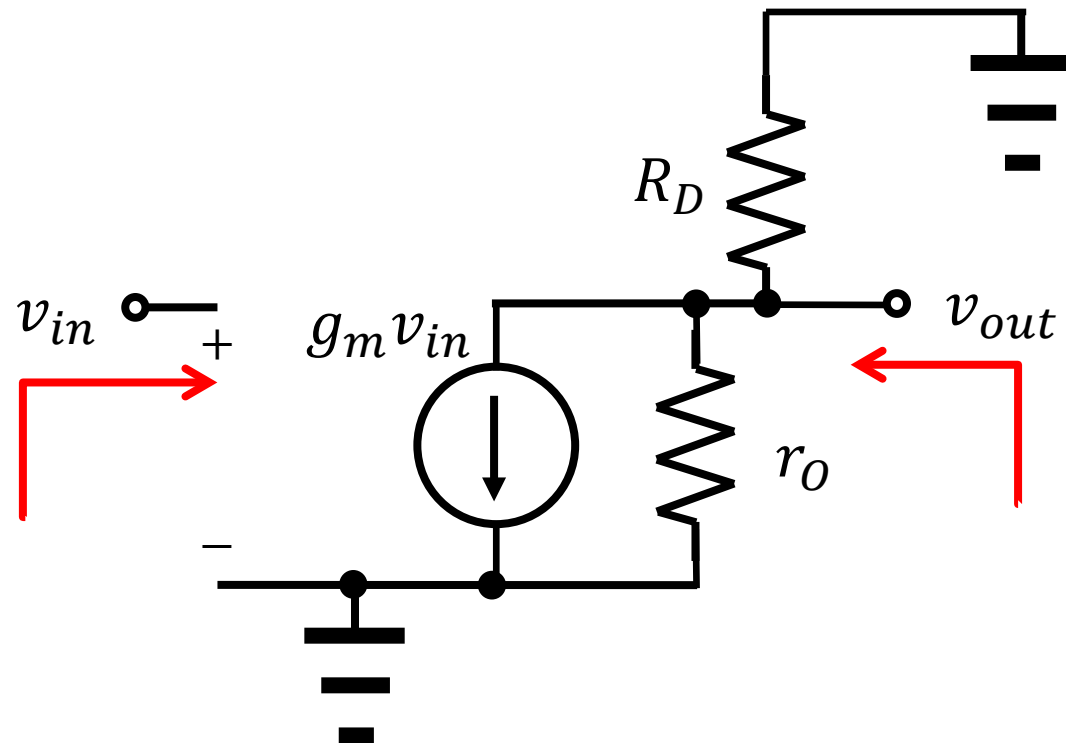
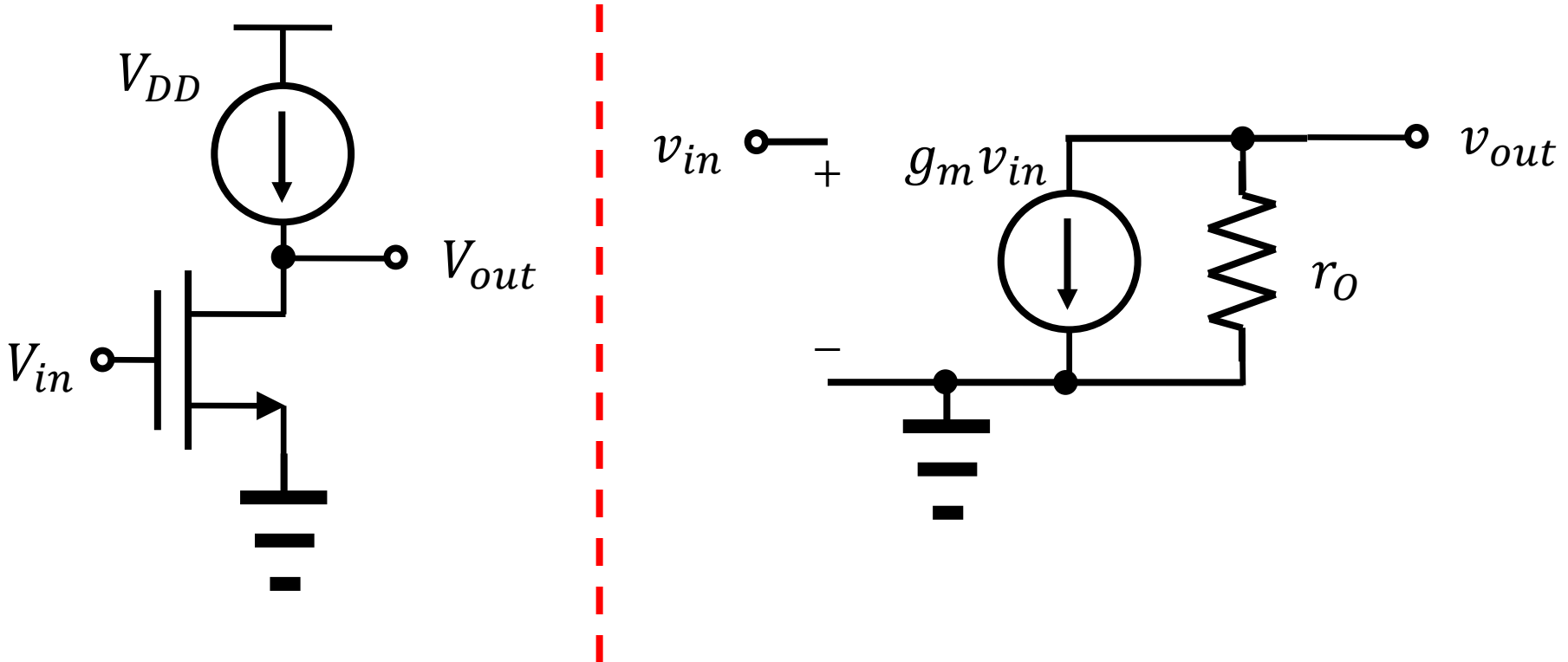
# Current-source load

---

- When  $R_D \rightarrow \infty$ ,
  - The gain can be maximized in its absolute value. ( $A_v \rightarrow -g_m r_o$ )





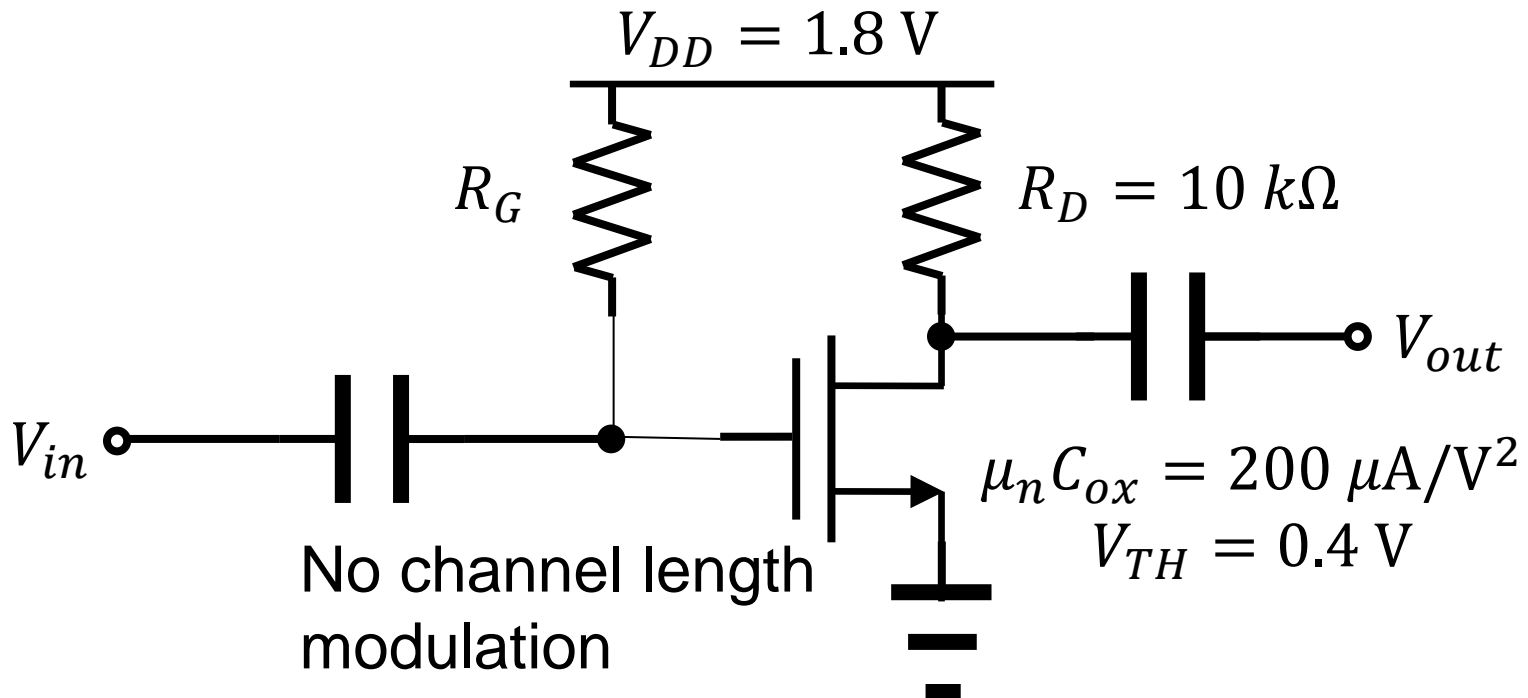
# Homework#8

---


- Due: 09:00, **May 13 (Mon)**
- Design the common-source state.
  - A voltage gain is 5 and an output impedance is  $1\text{ k}\Omega$ . Bias the transistor so that it operates 100 mV away from the triode region. Assume the capacitors are very large and  $R_D = 10\text{ k}\Omega$ .


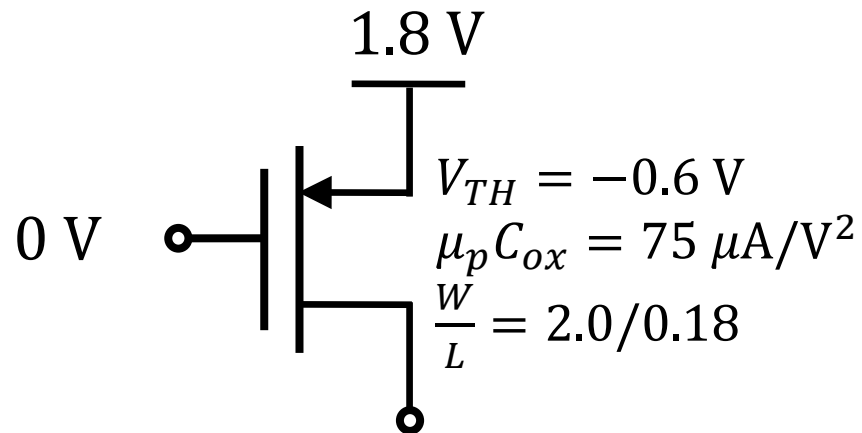
# Biasing of PMOS devices

---

- Use a PMOS as a current source
  - The absolute value of the “gate overdrive” is 1.2 V.
  - Of course, when the drain voltage is higher than 0.6 V, it is operated in the triode mode.




# Real current-source load

---

- Use a PMOS as a current source.
  - It is not an ideal current source.

$$v_{out} = -g_{m1}(r_{O1}||r_{O2})v_{in}$$


$$A_v = -g_{m1}(r_{O1}||r_{O2})$$

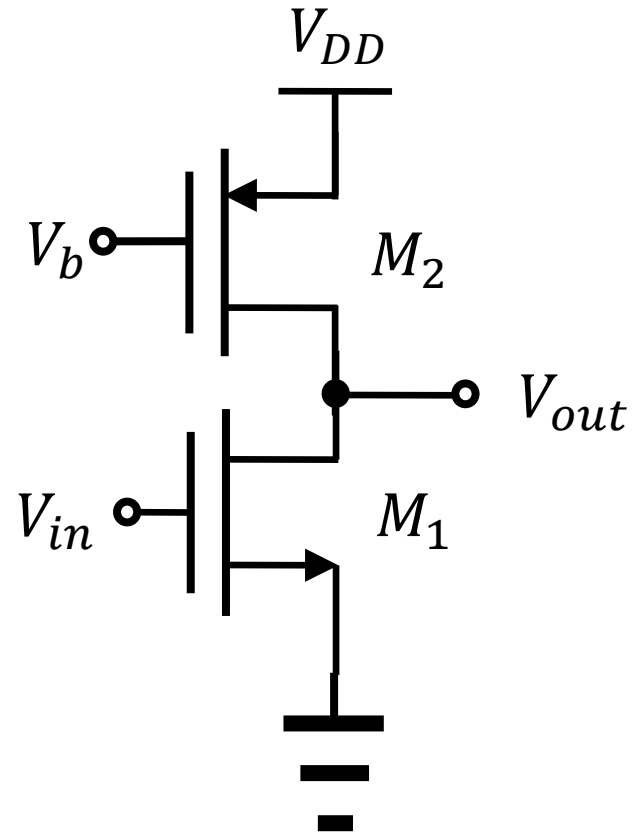
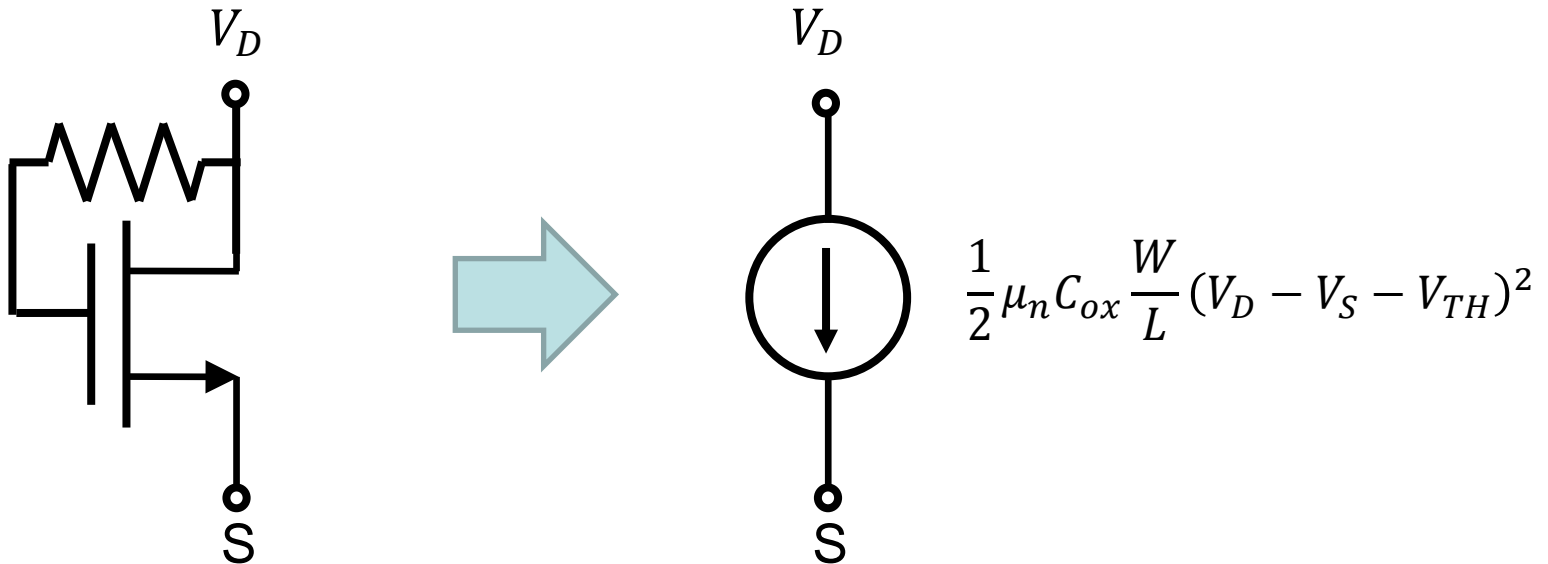
# Self-biasing

---

- Already covered in Razavi Example 6.13.
  - Always in the saturation region.



Gate and drain are tied.


# Diode-connected load

---

- Use a diode-connected load.
  - It is not an ideal current source.

$$v_{out} = -g_{m1} \left( r_{O1} \parallel \frac{1}{g_{m2}} \parallel r_{O2} \right) v_{in}$$

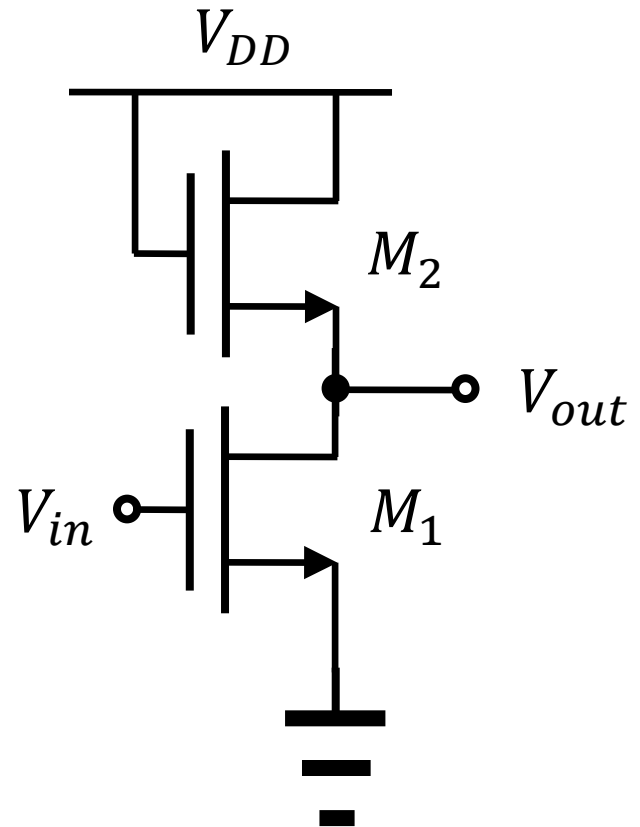
$$A_v = -g_{m1} \left( r_{O1} \parallel \frac{1}{g_{m2}} \parallel r_{O2} \right)$$


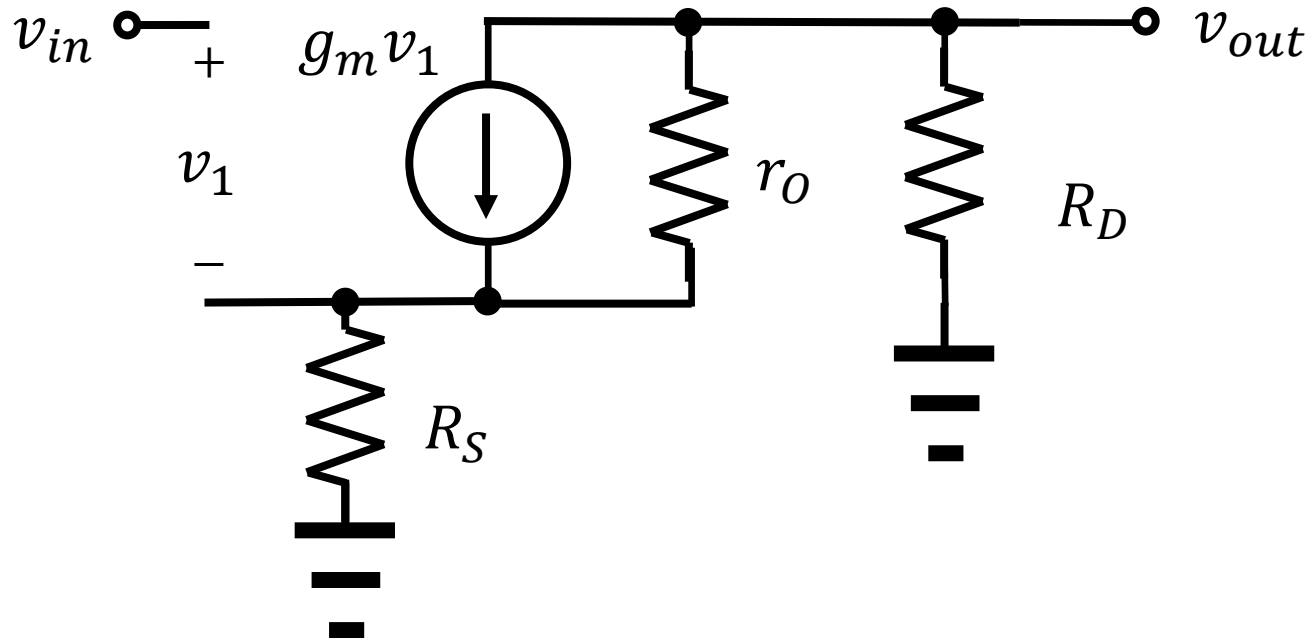
# Source degeneration

---

- Consider a case with a source resistor,  $R_S$ .
  - Calculate the gain and the output impedance.




# Razavi, example 17.8

---

- Biasing

- What is the gate voltage?
- Condition for saturation mode?

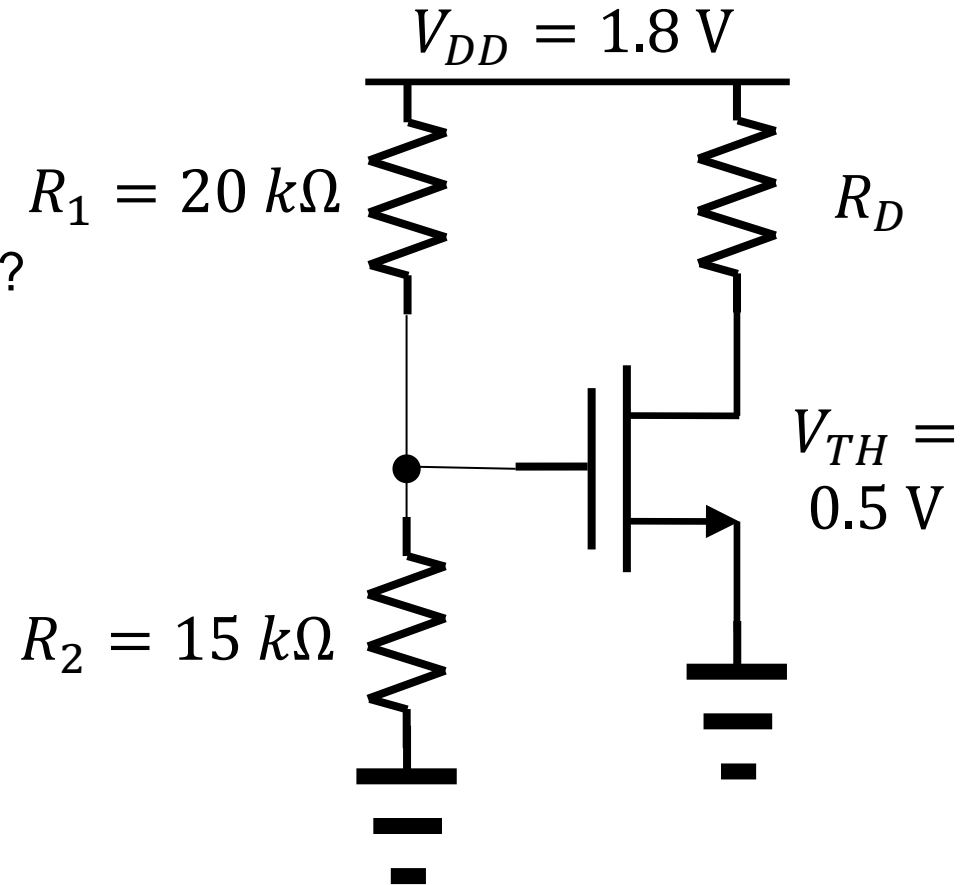
$$\mu_n C_{ox} = 100 \mu\text{A}/\text{V}^2$$
$$W/L = 5/0.18$$


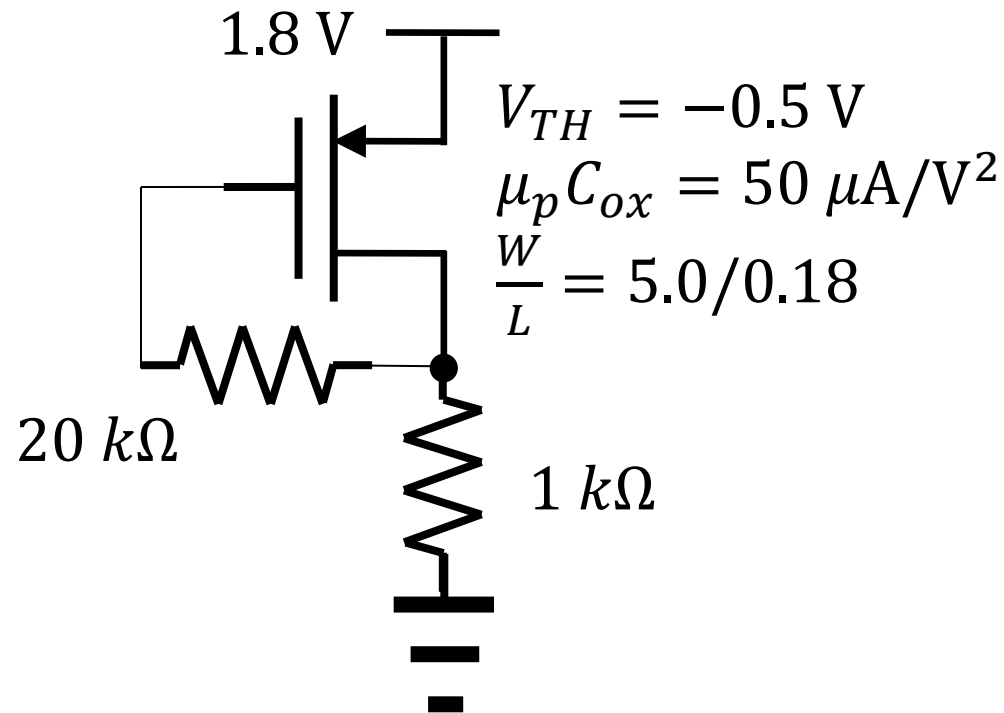
# Razavi, example 17.13

---

- Calculate the drain current. (BTW, where is the drain?)





# Razavi, example 17.14


---

- Calculate the gain.
  - The gain is given by  $A_v = -g_m R_D$ .
  - How can we get the transconductance?

$$\mu_n C_{ox} = 100 \mu\text{A}/\text{V}^2$$

$$V_{TH} = 0.5 \text{ V}$$

$$W/L = 10/0.18$$

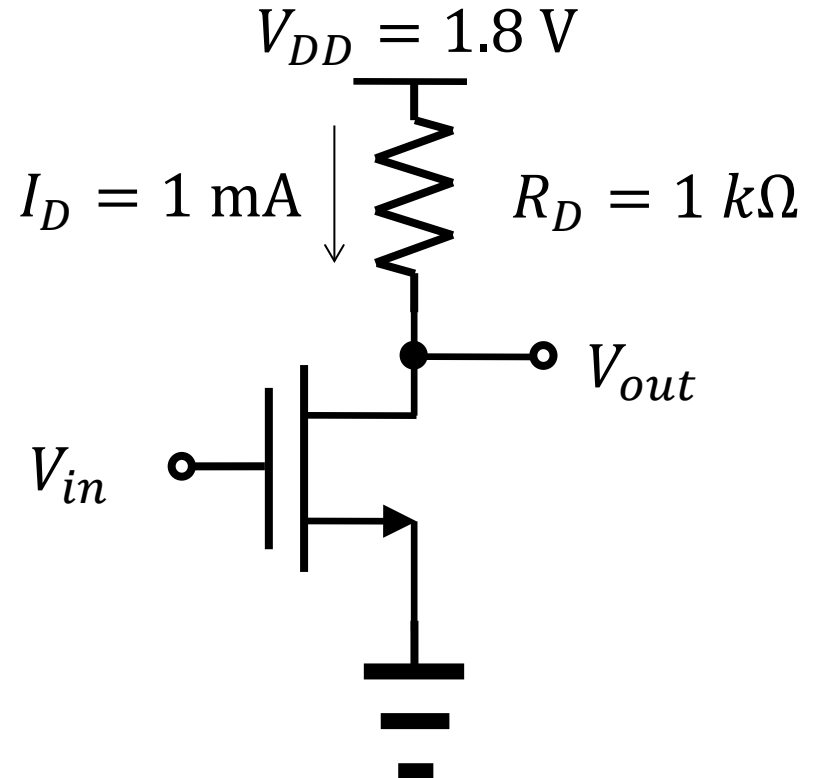

# Configurations

---

- Three terminals of the MOSFET
  - The common terminal, the input terminal, and the output terminal

Source	Gate	Drain	Remark
Common	Input	Output	Common-source amp.
Common	Output	Input	X
Input	Common	Output	It will be covered.
Output	Common	Input	X
Input	Output	Common	X
Output	Input	Common	It will be covered.