

---

# Lecture14: Impedance


Sung-Min Hong ([smhong@gist.ac.kr](mailto:smhong@gist.ac.kr))

Semiconductor Device Simulation Lab.  
School of Electrical Engineering and Computer Science  
Gwangju Institute of Science and Technology
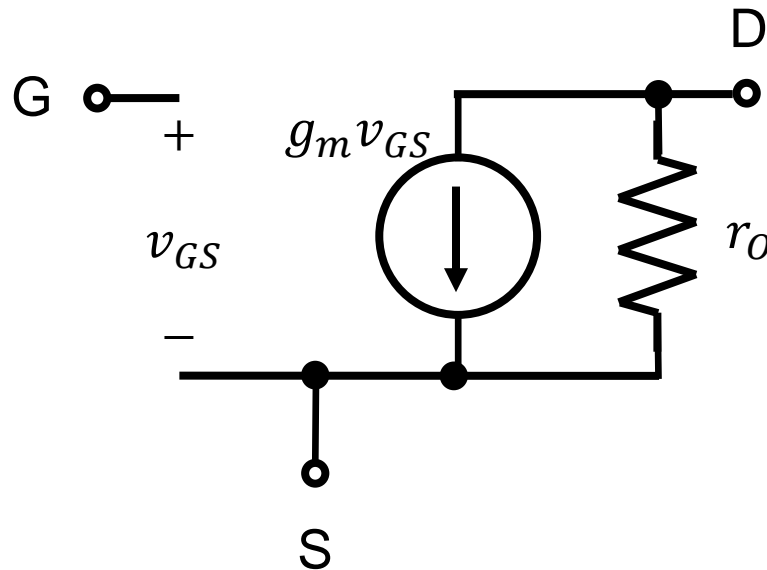
# Small-signal MOSFET model

---

- Small-signal MOSFET model
  - Two branches are related with two partial derivatives.



# Simple math

---

- Following relations are useful.
  - Sine and cosine functions can be expanded with  $e^{+j\omega t}$  and  $e^{-j\omega t}$ .

$$\sin \omega t = -\frac{j}{2} e^{+j\omega t} + \frac{j}{2} e^{-j\omega t}$$

$$\cos \omega t = \frac{1}{2} e^{+j\omega t} + \frac{1}{2} e^{-j\omega t}$$

- Therefore, for a function of  $f(t) = f_s \sin \omega t + f_c \cos \omega t$ , the expansion is


$$f(t) = \left( -j \frac{f_s}{2} + \frac{f_c}{2} \right) e^{+j\omega t} + \left( +j \frac{f_s}{2} + \frac{f_c}{2} \right) e^{-j\omega t}$$

- A single complex number,  $-j \frac{f_s}{2} + \frac{f_c}{2}$ , is enough to represent  $f(t)$ .
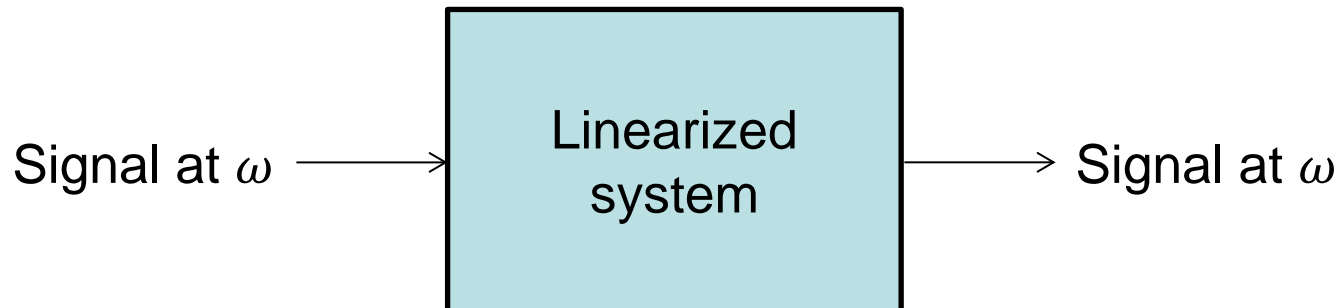
# Linearized system

---

- Our circuit is nonlinear in general.
- However, we have linearized it.
  - When the input signal has an angular frequency,  $\omega$ , the output signal has the same one.
  - It is sufficient to consider the input-output relation at  $\omega$ .



# Impedance

---

- Resistance,  $V(t) = R I(t)$ 
  - It is assumed that  $V(t)$  and  $I(t)$  are in the same phase.
- Impedance,  $V(\omega) = Z(\omega)I(\omega)$ 
  - Consider  $V(t) = V_0 \sin \omega t$  and  $I(t) = I_0 \cos \omega t$ . (Different phases)
  - We introduce a phasor voltage,  $V(\omega)$ , and a phasor current,  $I(\omega)$ .
  - The relation between  $V(t)$  and  $V(\omega)$  is  $V(t) = \text{Re}[V(\omega)e^{j\omega t}]$ .
  - When  $V(t) = V_0 \sin \omega t$ , the phasor voltage is  $V(\omega) = -jV_0$ .
  - When  $I(t) = I_0 \cos \omega t$ , the phasor voltage is  $I(\omega) = I_0$ .
  - In this example,  $Z(\omega) = -j \frac{V_0}{I_0}$ . A purely imaginary number.

# Multi-terminal devices


---

- When the number of terminals is 3,
  - We can define 9 ( = 3 X 3 ) different impedances.
- Termination condition is important.
  - Depending on the termination condition, the impedance can be heavily changed.
  - In many cases, it is obvious from the problem.
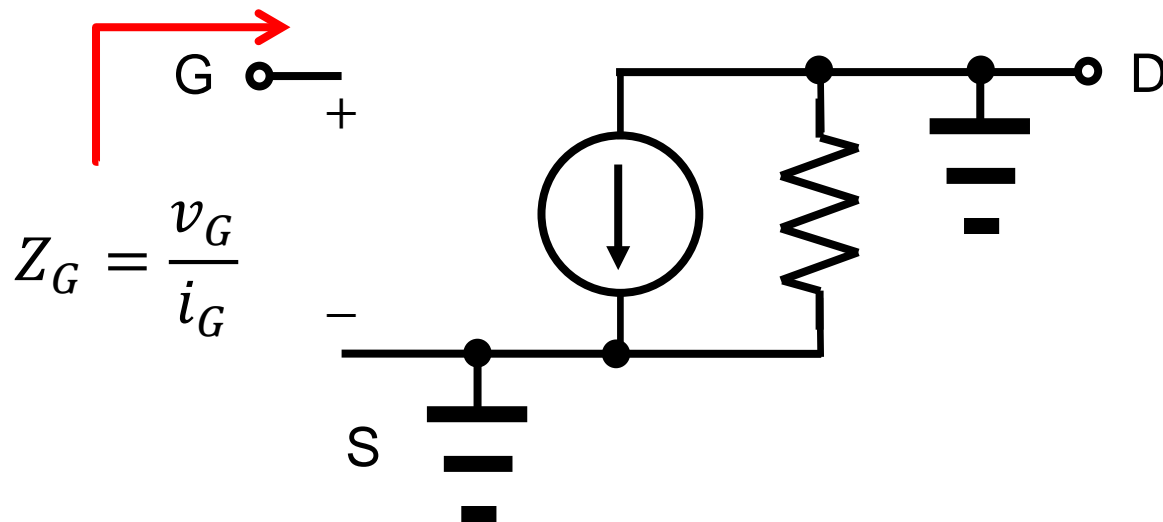
# Impedances of MOSFET

---

- “Looking into the TERMINAL,” we see the impedance of the TERMINAL.
  - Example) Looking into the gate. The source and drain are ac-grounded.




- Similar for other terminals

# Input impedance

---

- Consider a input signal with a finite internal resistance.
  - Usually, the internal resistance is small, but not zero.
  - The actual small-signal voltage applied to the gate terminal is given by
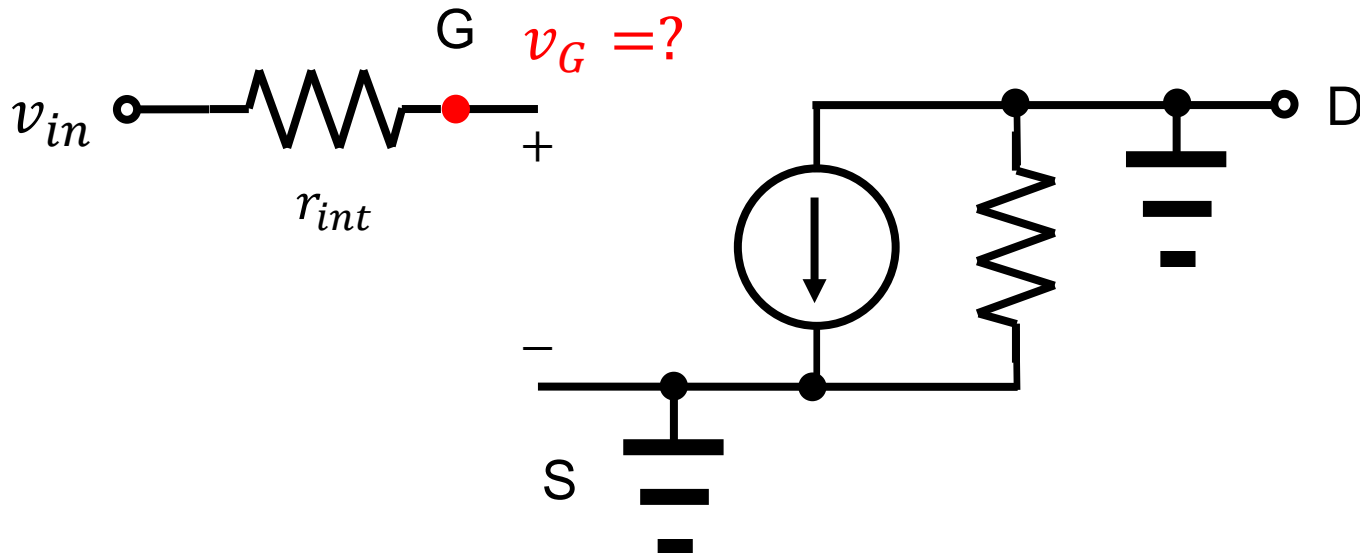
$$v_G(\omega) = v_{in} \frac{Z_G(\omega)}{r_{int} + Z_G(\omega)}$$





# Homework#6

---

- Due: 09:00, April 29 (Mon)
- Solve the following problems of the **2019** mid-term exam.
  - P9, P11, P14, P16, P18, P24, P26, P29, P32, P33, P34, P35, P37, P39, and P40
  - In total, 15 problems.