

---

# Lecture13:

# MOSFET, small-signal model


Sung-Min Hong ([smhong@gist.ac.kr](mailto:smhong@gist.ac.kr))

Semiconductor Device Simulation Lab.  
School of Electrical Engineering and Computer Science  
Gwangju Institute of Science and Technology
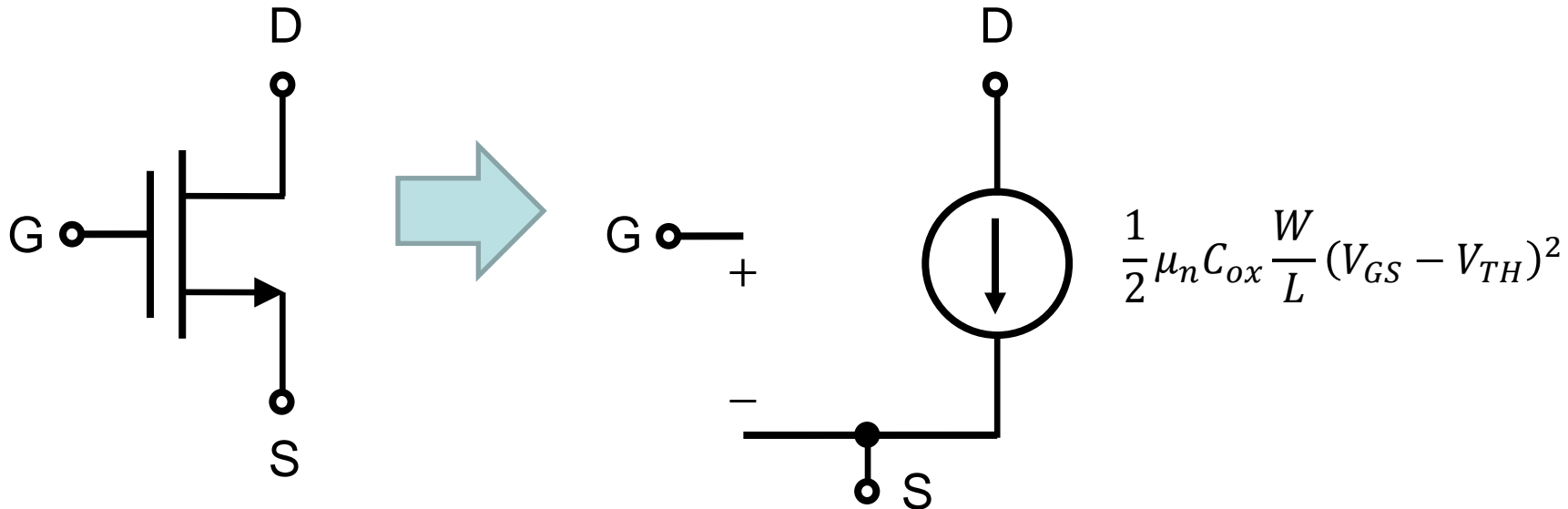
# Large-signal model (1/2)

---


- Saturation region
  - Drain current is determined by gate voltage. (*voltage-controlled current source*)


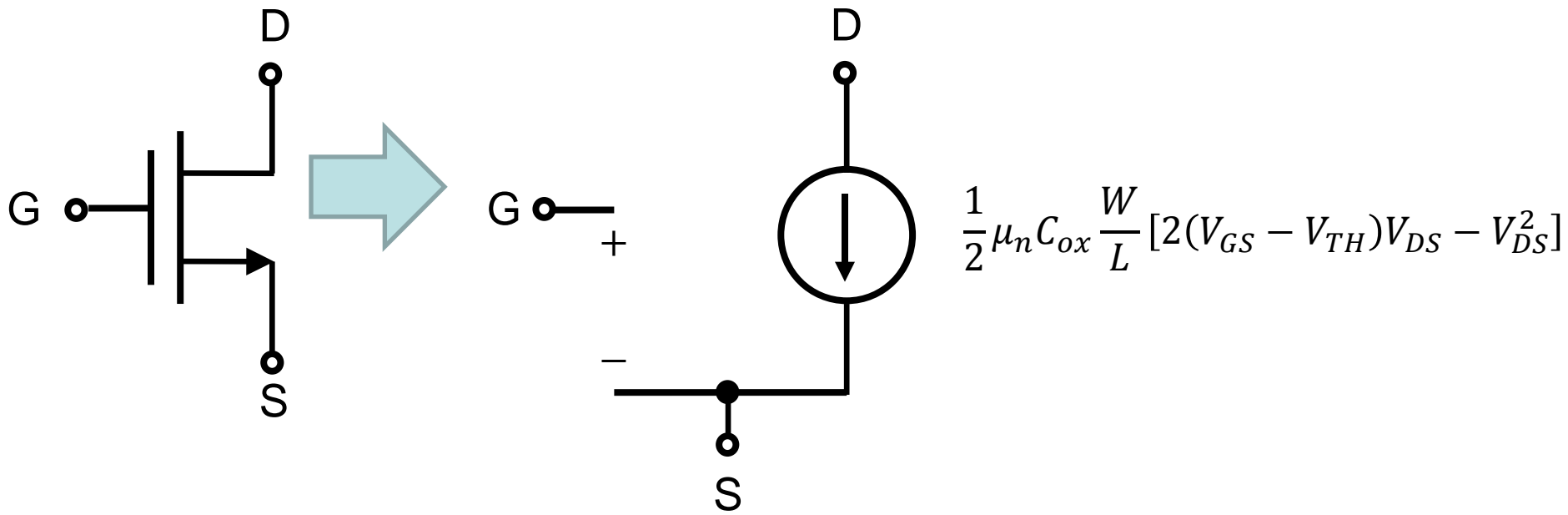
# Large-signal model (2/2)

---


- Triode region
  - Still, it can be described by a *voltage-controlled current source*.


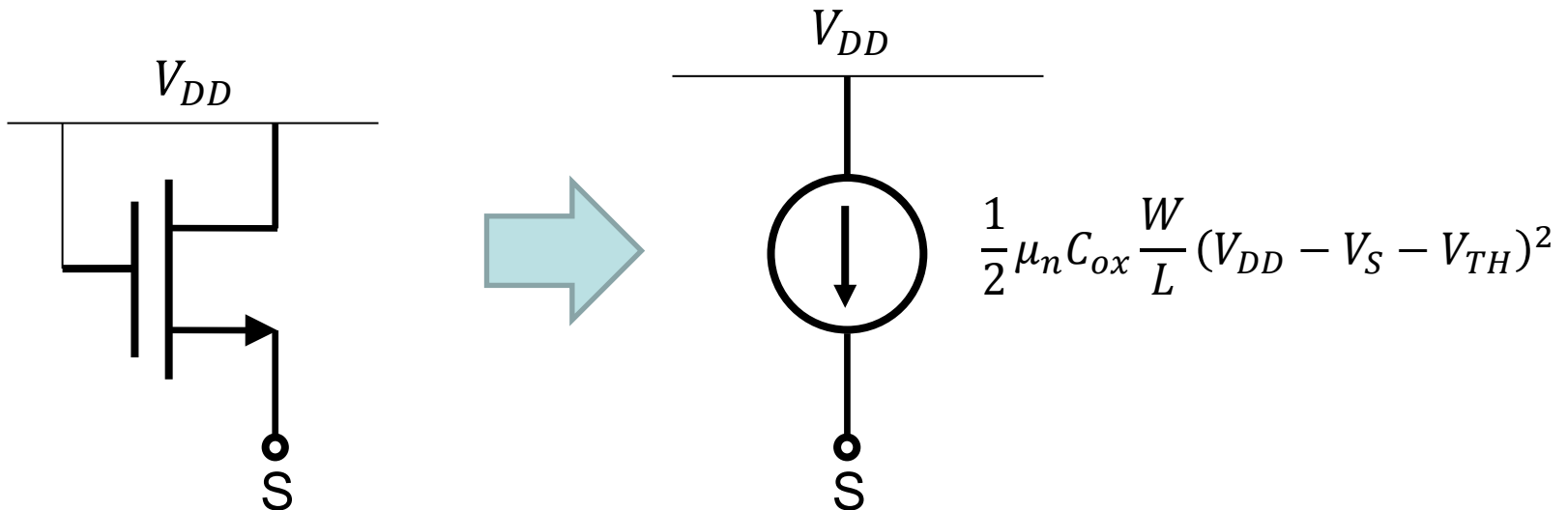
# Example 6.13 (Razavi)

---

- Always in the saturation region!
  - Any necessary condition?




Gate and drain are tied.  
They are connected to  $V_{DD}$ .
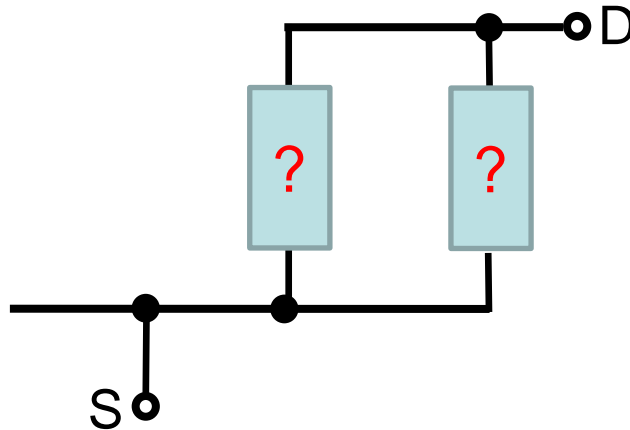
# Small-signal current

---



- Using the transconductance ( $g_m$ ) and the output resistance ( $r_o$ ),
  - The small-signal drain current is given as  $i_D = g_m v_G + \frac{v_D}{r_o}$ .
  - When we build a small-signal model, two contributions must be separately considered.


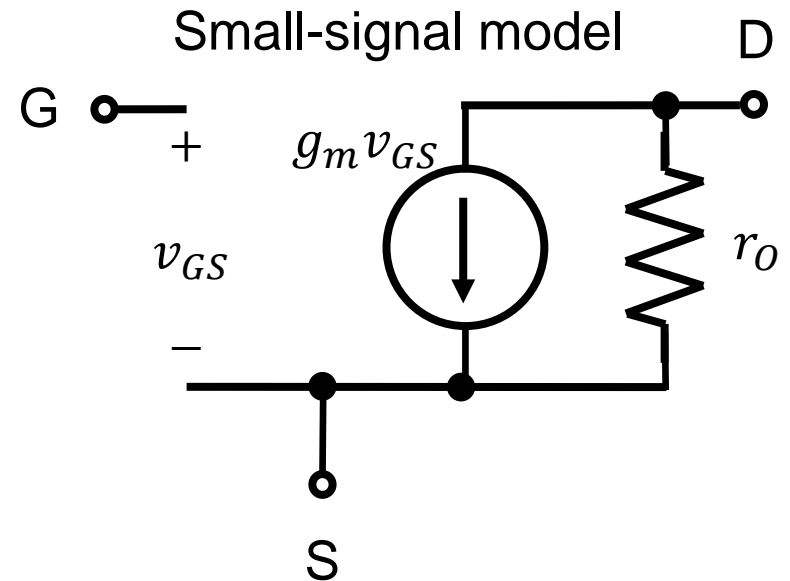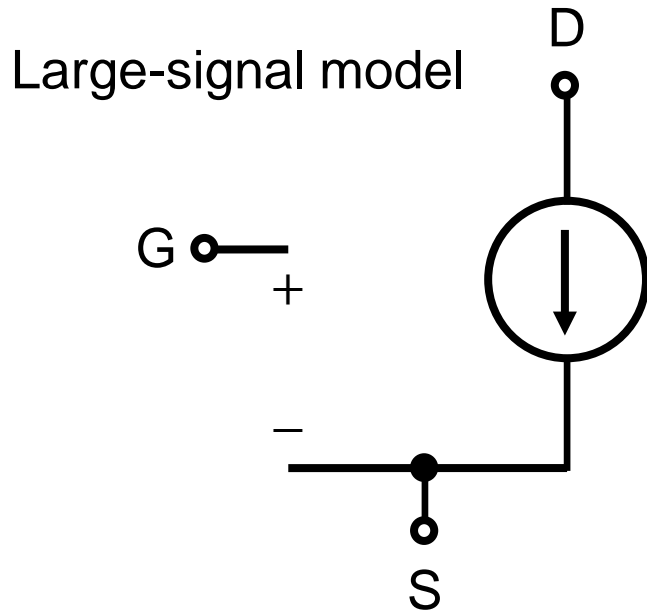
# Small-signal model

---


- For small-signal analysis, a small-signal model for the MOSFET is introduced.


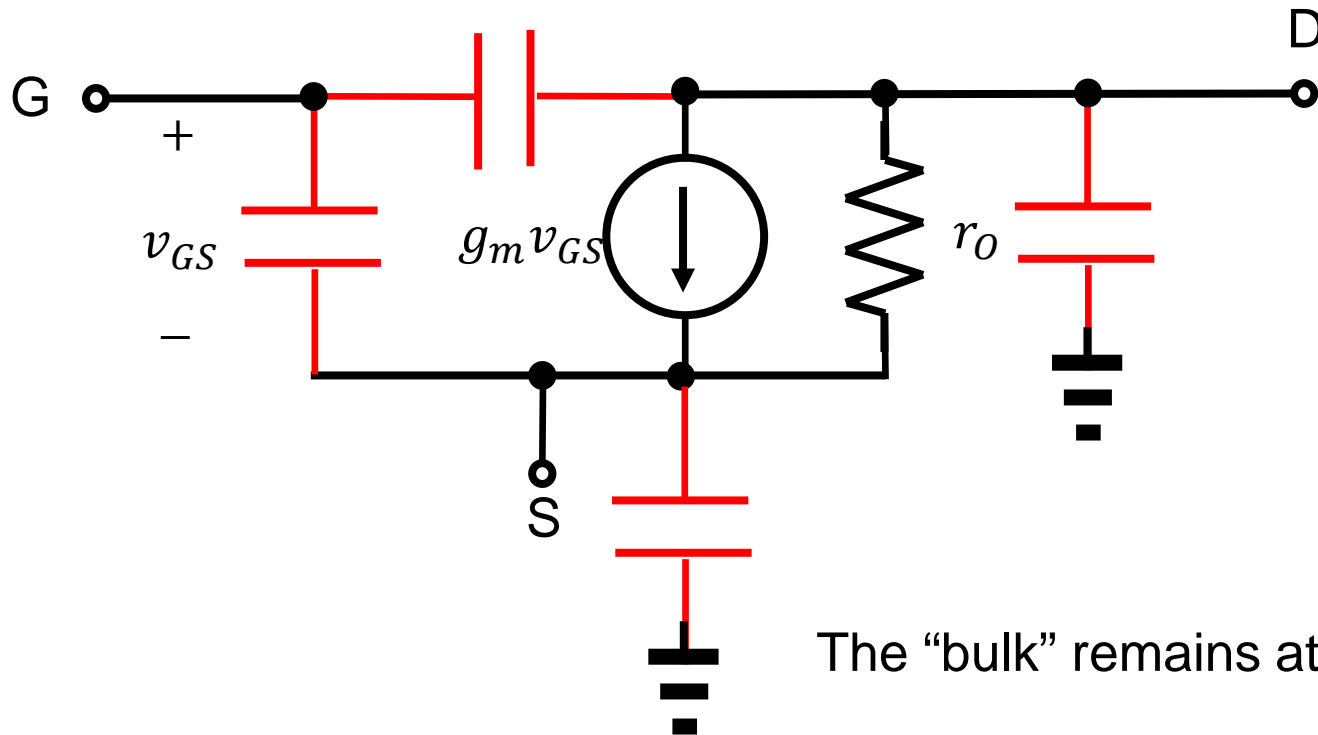
# Time-dependent one?

---

- In general, capacitive components can be seen.



The “bulk” remains at ac ground.

# At low frequencies

---


- Capacitor current is  $I = C \frac{dV}{dt}$ .
  - When a sinusoidal dependence, for example  $\sin \omega t$ , is assumed, the capacitor current is proportional to  $\omega$ .
  - At low frequencies,  $\omega$  can be regarded as a small number.
  - In other words, the electric conduction between two nodes becomes rather weak.
  - Therefore, we often neglect the capacitive components in the small-signal model.
  - Of course, at higher frequencies, they become very important.


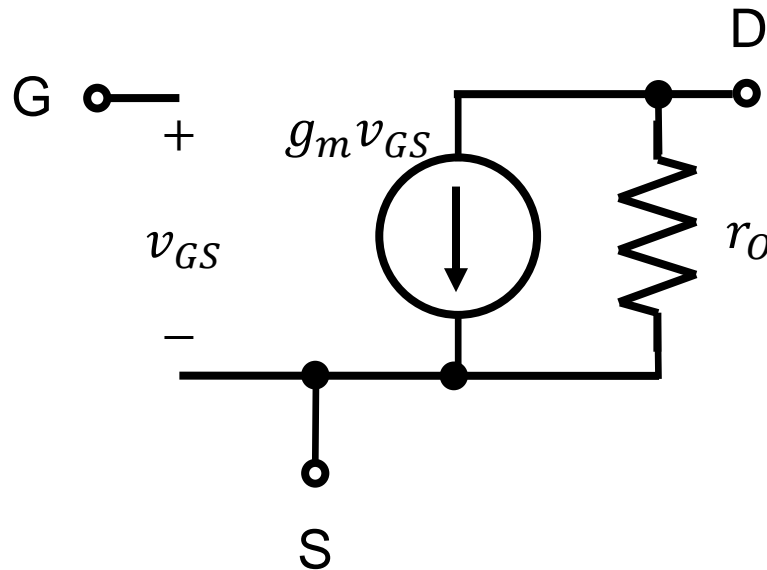
# Small-signal MOSFET model

---

- Small-signal MOSFET model
  - Two branches are related with two partial derivatives.



# Simple math

---

- Following relations are useful.
  - Sine and cosine functions can be expanded with  $e^{+j\omega t}$  and  $e^{-j\omega t}$ .

$$\sin \omega t = -\frac{j}{2} e^{+j\omega t} + \frac{j}{2} e^{-j\omega t}$$

$$\cos \omega t = \frac{1}{2} e^{+j\omega t} + \frac{1}{2} e^{-j\omega t}$$

- Therefore, for a function of  $f(t) = f_s \sin \omega t + f_c \cos \omega t$ , the expansion is


$$f(t) = \left( -j \frac{f_s}{2} + \frac{f_c}{2} \right) e^{+j\omega t} + \left( +j \frac{f_s}{2} + \frac{f_c}{2} \right) e^{-j\omega t}$$

- A single complex number,  $-j \frac{f_s}{2} + \frac{f_c}{2}$ , is enough to represent  $f(t)$ .
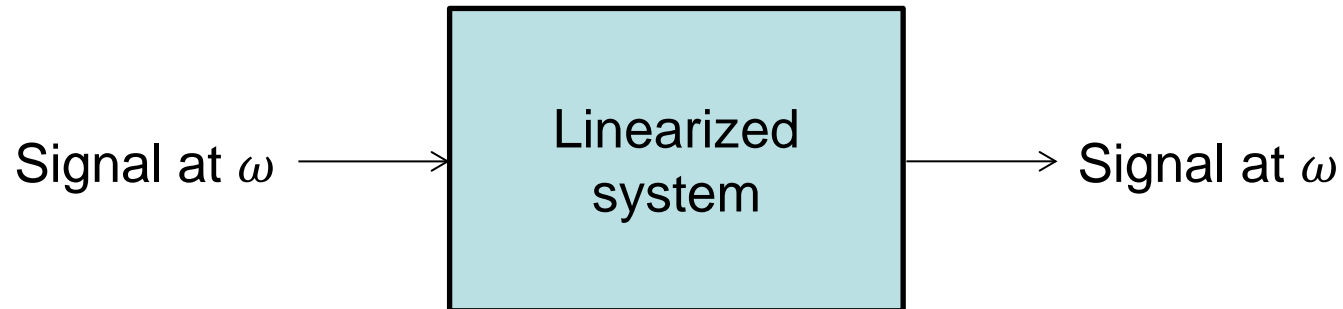
# Linearized system

---

- Our circuit is nonlinear in general.
- However, we have linearized it.
  - When the input signal has an angular frequency,  $\omega$ , the output signal has the same one.
  - It is sufficient to consider the input-output relation at  $\omega$ .



# Impedance

---

- Resistance,  $V(t) = R I(t)$ 
  - It is assumed that  $V(t)$  and  $I(t)$  are in the same phase.
- Impedance,  $V(\omega) = Z(\omega)I(\omega)$ 
  - Consider  $V(t) = V_0 \sin \omega t$  and  $I(t) = I_0 \cos \omega t$ . (Different phases)
  - We introduce a phasor voltage,  $V(\omega)$ , and a phasor current,  $I(\omega)$ .
  - The relation between  $V(t)$  and  $V(\omega)$  is  $V(t) = \text{Re}[V(\omega)e^{j\omega t}]$ .
  - When  $V(t) = V_0 \sin \omega t$ , the phasor voltage is  $V(\omega) = -jV_0$ .
  - When  $I(t) = I_0 \cos \omega t$ , the phasor voltage is  $I(\omega) = I_0$ .
  - In this example,  $Z(\omega) = -j \frac{V_0}{I_0}$ . A purely imaginary number.

# Multi-terminal devices


---

- When the number of terminals is 3,
  - We can define 9 ( = 3 X 3 ) different impedances.
- Termination condition is important.
  - Depending on the termination condition, the impedance can be heavily changed.
  - In many cases, it is obvious from the problem.
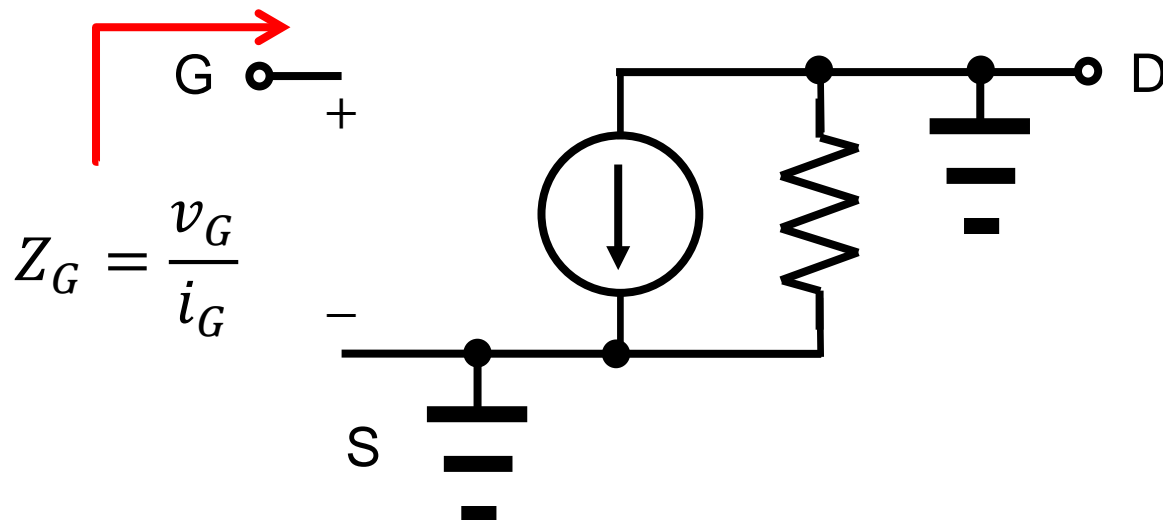
# Impedances of MOSFET

---

- “Looking into the TERMINAL,” we see the impedance of the TERMINAL.
  - Example) Looking into the gate. The source and drain are ac-grounded.



- Similar for other terminals