
Lecture7:

Diode circuit & small-signal analysis

Sung-Min Hong (smhong@gist.ac.kr)

Semiconductor Device Simulation Lab.
School of Electrical Engineering and Computer Science
Gwangju Institute of Science and Technology

PN junction


- Exponential model

$$I_D = I_s \left(\exp \frac{V_D}{V_T} - 1 \right)$$

- Constant-voltage model
 - An “offset” voltage of $V_{D,on}$



Rectifier

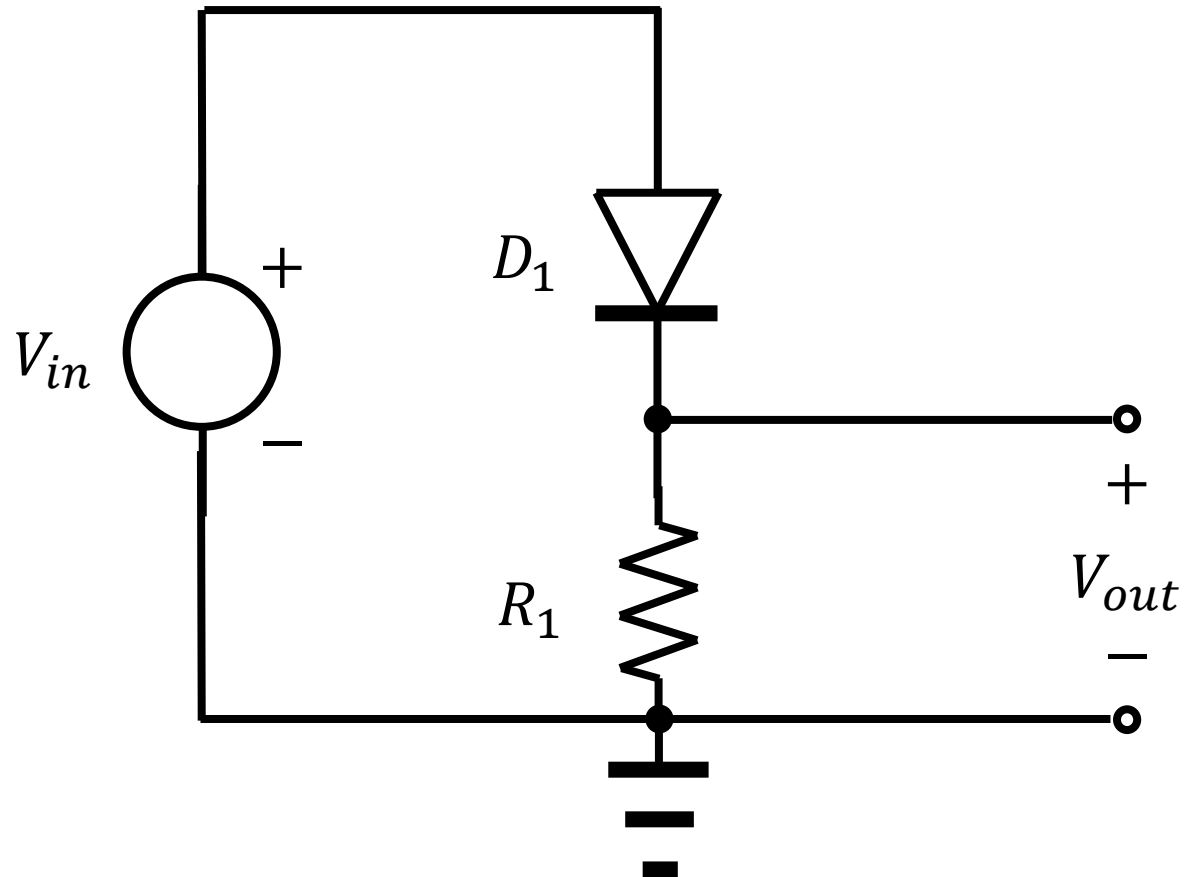- Analyze it!
 - When $V_{in} < V_{D,on}$?
 - When $V_{in} > V_{D,on}$?




Simulation result

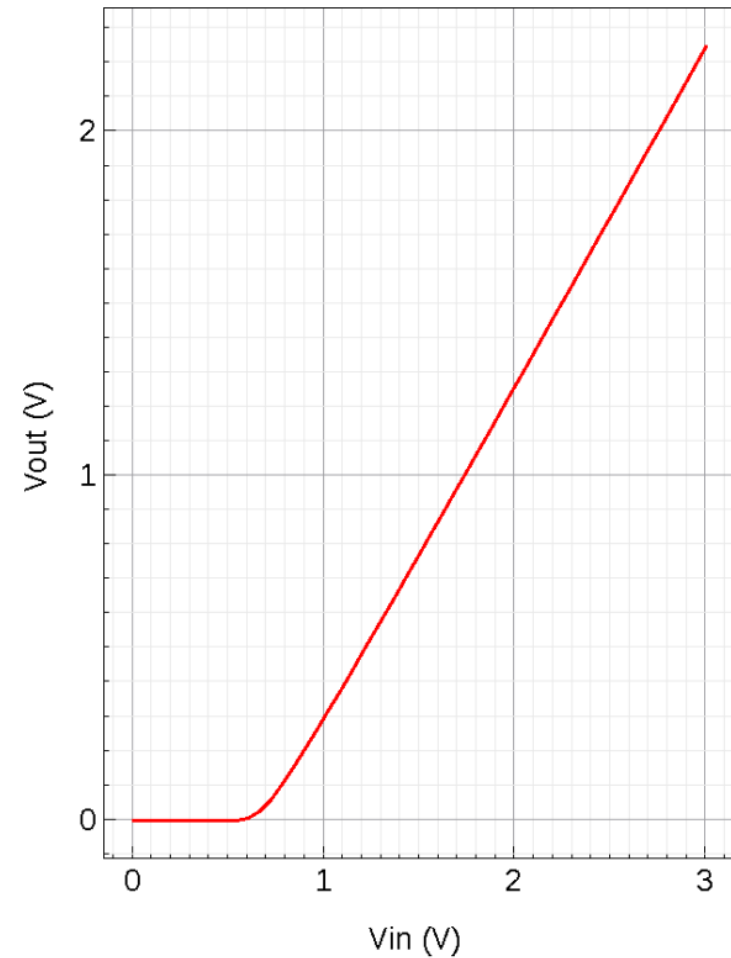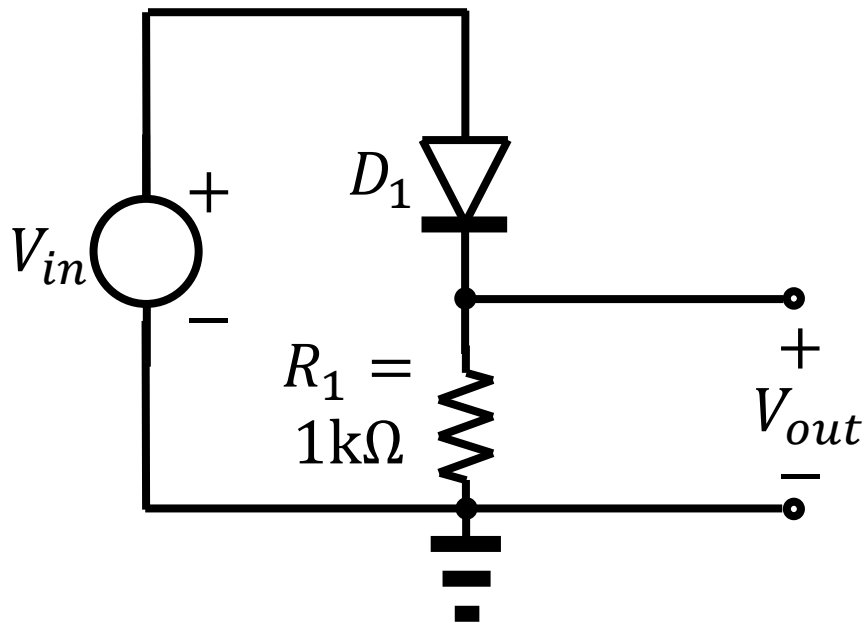- Example) $I_s = 0.5 \text{ fA}$ and $R_1 = 1 \text{ k}\Omega$




Time-varying voltage source

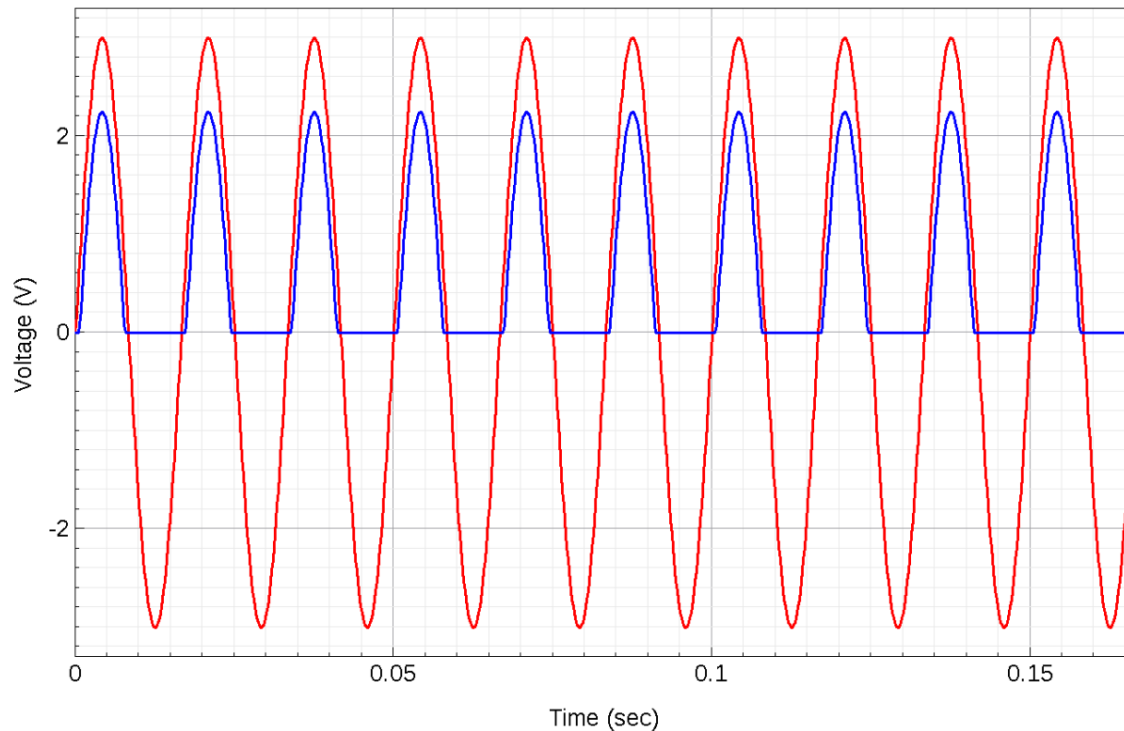- For example, $V_{in}(t) = 3 \sin(2\pi ft)$ V. 60 Hz. 10 periods



Introducing a capacitor

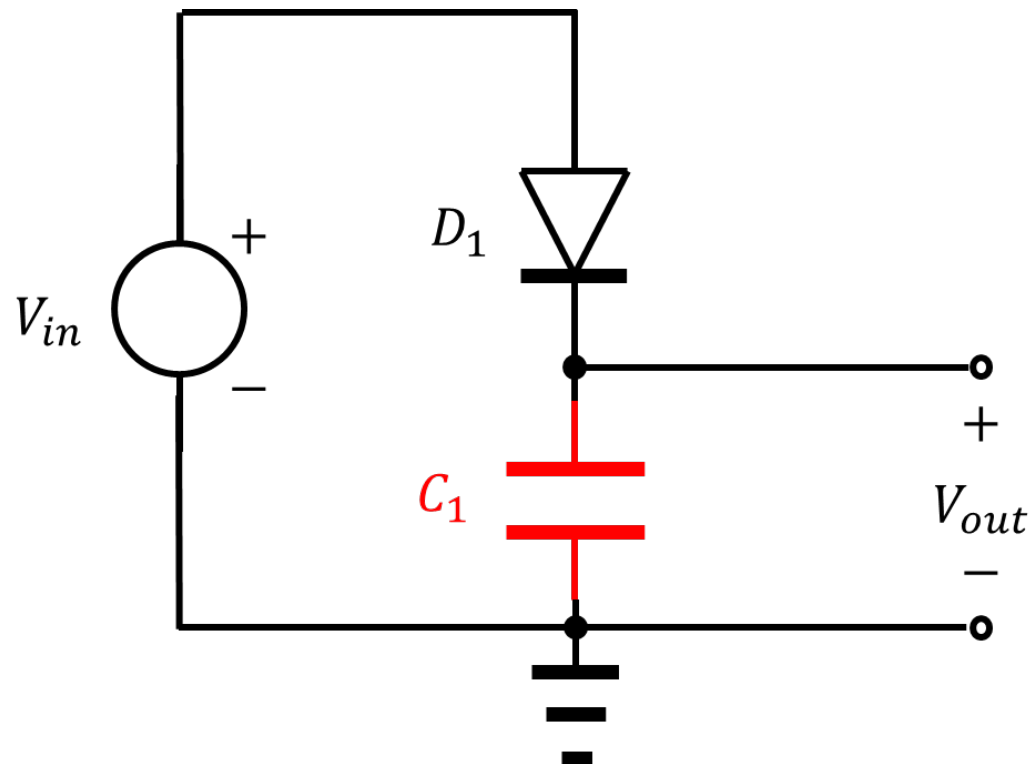- Difference from the previous one?
 - First, consider the DC case.
 - Remember that $I_C = C_1 \frac{d}{dt} V_{out}$.



Qualitative understanding (1)


- Consider the first period.
 - When the input voltage exceeds $V_{D,on}$, the diode is turned on.
 - The charge is stored in the capacitor. Hence, the output voltage increases.
 - When the input voltage is lower than $V_{D,on}$, the output voltage does not change. (*Why?*)

Qualitative understanding (2)

- After the first period...
 - In the second period, the diode current is smaller than the one in the first period. (*Why?*)
 - After some periods, the diode current vanishes.
 - A DC output voltage is established.

Simulation result

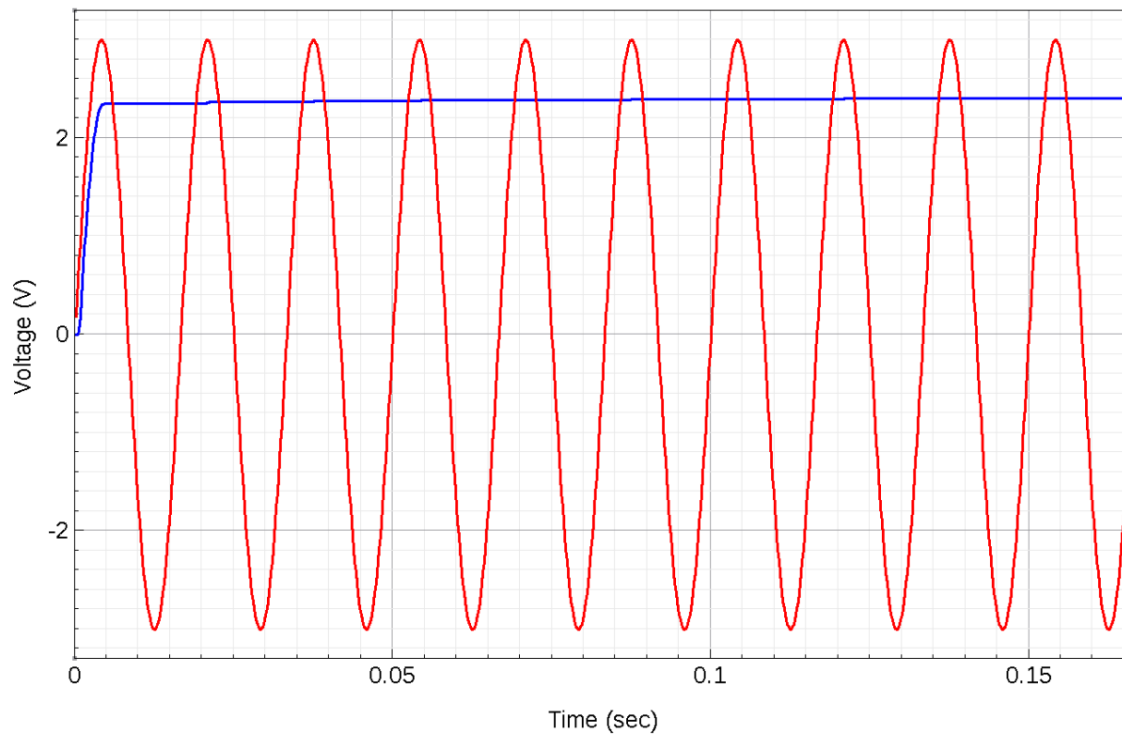- The capacitance, $C_1 = 1\ \mu\text{F}$.



Simple math

- Taylor series expansion

- Consider a function, $f(x)$.
- Then, at $x_0 + \Delta x$ (Δx is small.), the function value would be similar to that at x_0 :

$$f(x_0 + \Delta x) \approx f(x_0)$$




- A better approximation?

$$f(x_0 + \Delta x) \approx f(x_0) + \left. \frac{df(x)}{dx} \right|_{x=x_0} \Delta x$$

- Nonlinear function → linearly approximated!



Nonlinear system

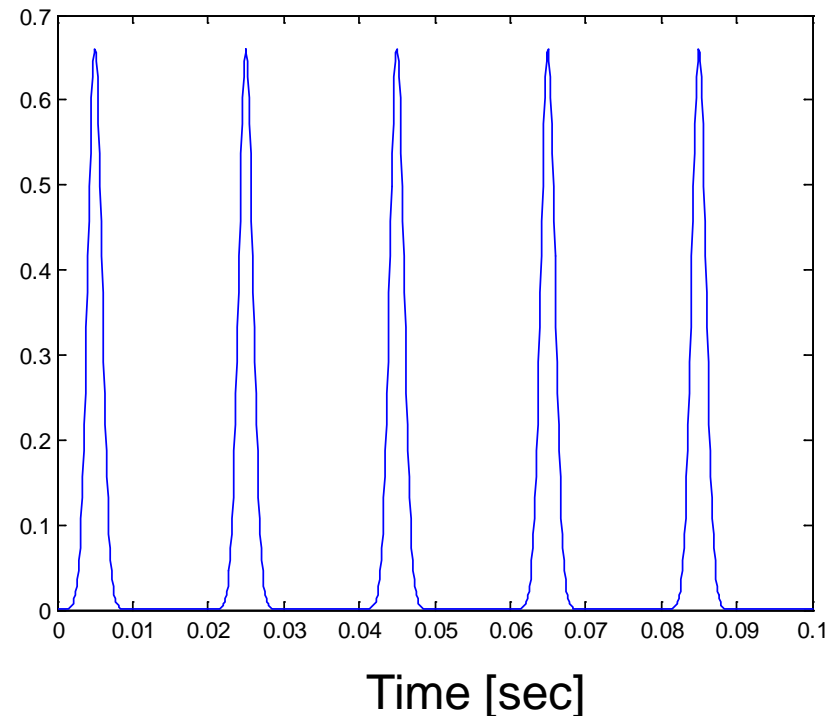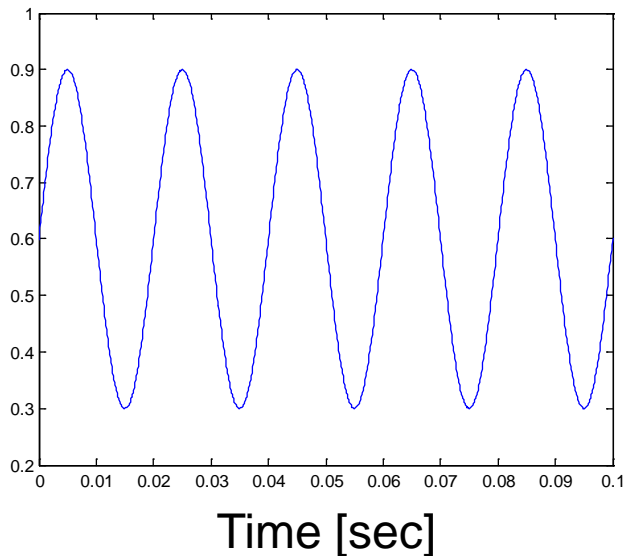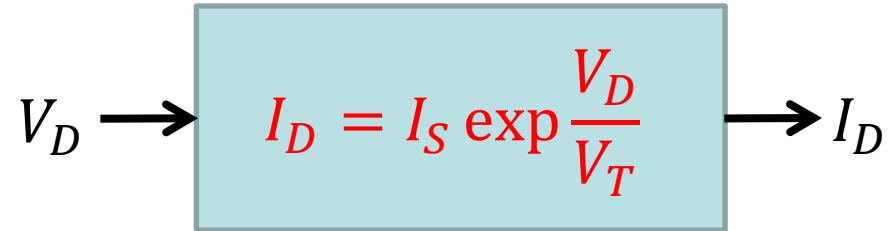- A diode: Input V_D , output I_D
- When $V_{in} = 0.6 + 0.3 \sin 2\pi f t$,



Small input amplitude

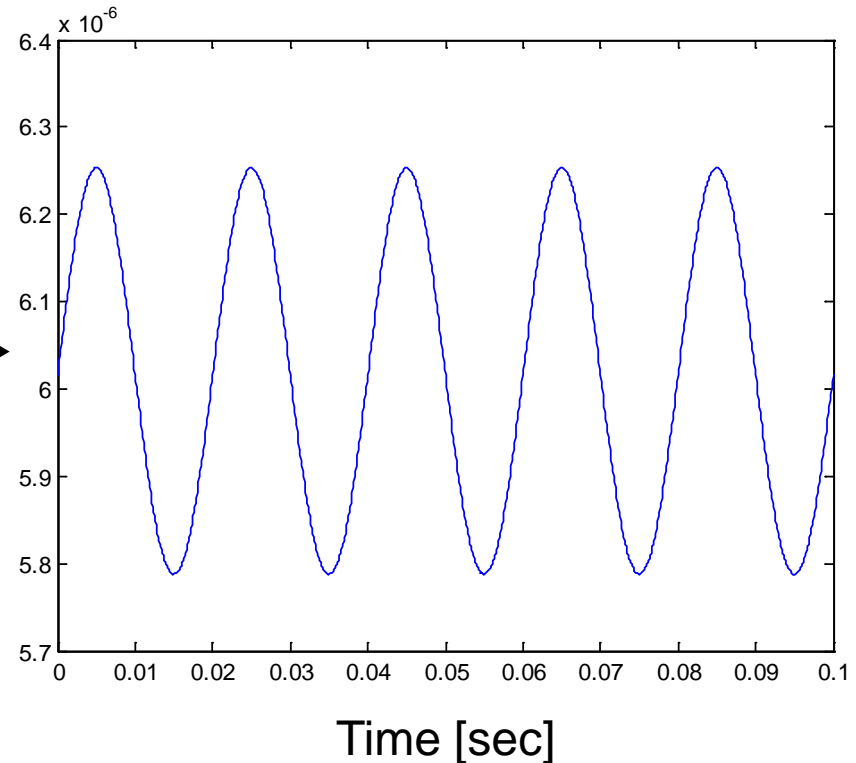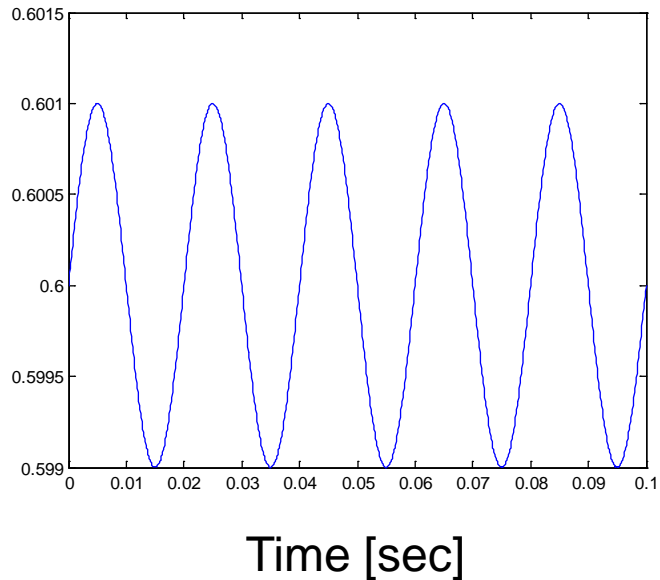- When $V_{in} = 0.6 + 0.001 \sin 2\pi f t$,
 - I_D is almost sinusoidal.



Small-signal analysis

- General case

$$V_{D,DC} + v_{D,AC}(t) \rightarrow \boxed{I_D = I_S \exp \frac{V_D}{V_T}} \rightarrow I_{D,DC} + i_{D,AC}(t)$$

- “Small-signal” case

– When $v_{D,AC}(t)$ is small, then, the AC current is given by

$$i_{D,AC}(t) \approx I_{D,DC} \frac{v_{D,AC}(t)}{V_T}$$

$$v_{D,AC}(t) \rightarrow \boxed{I_{D,AC}(t) = I_{D,DC} \frac{v_{D,AC}(t)}{V_T}} \rightarrow i_{D,AC}(t)$$

Application to a diode

- Small-signal resistance

- As far as small changes in the diode current and voltage are concerned, the device behaves as a linear resistor.

$$r_d = \frac{V_T}{I_D}$$

- When the small change in the diode voltage is time-varying,

$$I_D(t) = I_s \exp \frac{V_{D,DC} + \Delta V \cos \omega t}{V_T} = I_s \exp \frac{V_{D,DC}}{V_T} \exp \frac{\Delta V \cos \omega t}{V_T}$$

$$I_D(t) \approx I_{D,DC} \left(1 + \frac{\Delta V \cos \omega t}{V_T} \right)$$

- The output current has the same frequency!