
Lecture18:


Common-source amplifier (2)

Sung-Min Hong (smhong@gist.ac.kr)

Semiconductor Device Simulation Lab.
School of Electrical Engineering and Computer Science
Gwangju Institute of Science and Technology


Current-source load

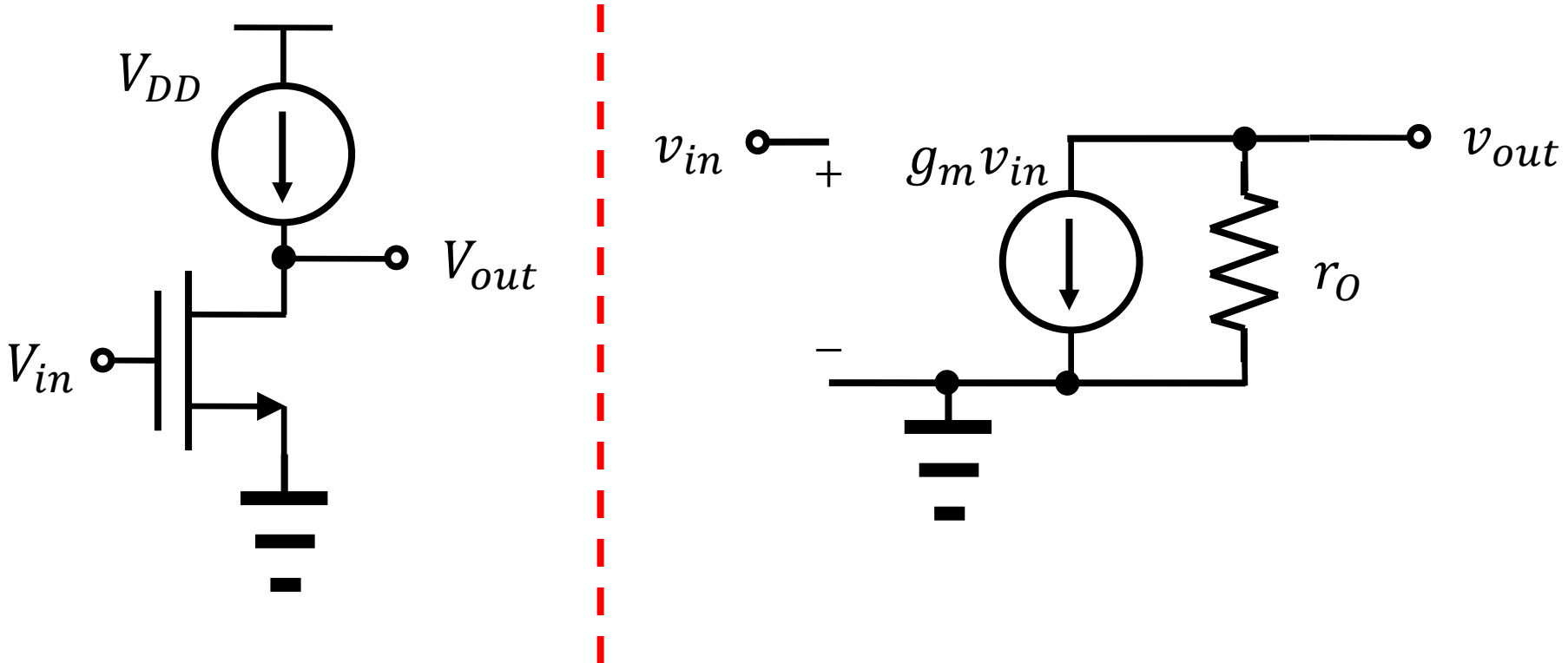- When $R_D \rightarrow \infty$,
 - The gain can be maximized in its absolute value. ($A_v \rightarrow -g_m r_o$)



Biasing of PMOS devices

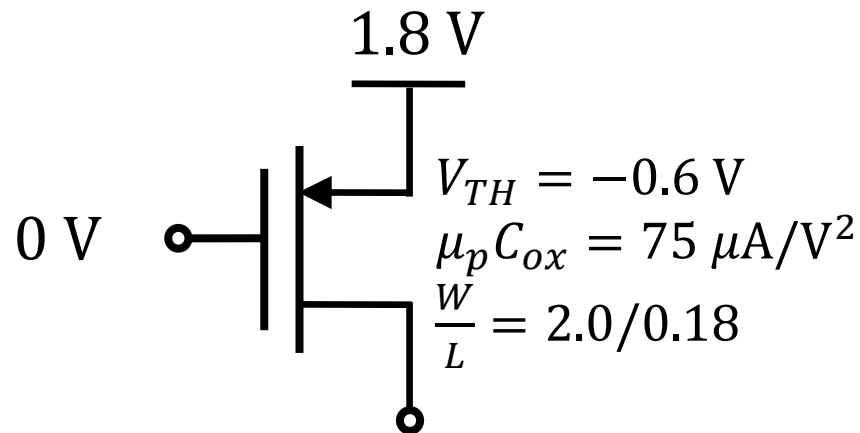- Use a PMOS as a current source
 - The absolute value of the “gate overdrive” is 1.2 V.
 - Of course, when the drain voltage is higher than 0.6 V, it is operated in the triode mode.




Real current-source load

- Use a PMOS as a current source.
 - It is not an ideal current source.


$$v_{out} = -g_{m1}(r_{O1}||r_{O2})v_{in}$$

$$A_v = -g_{m1}(r_{O1}||r_{O2})$$

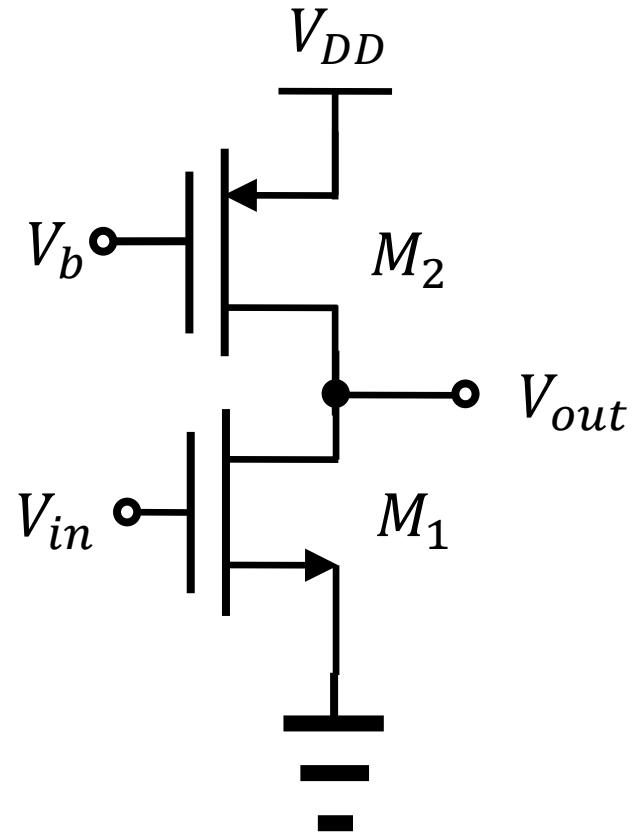

Self-biasing

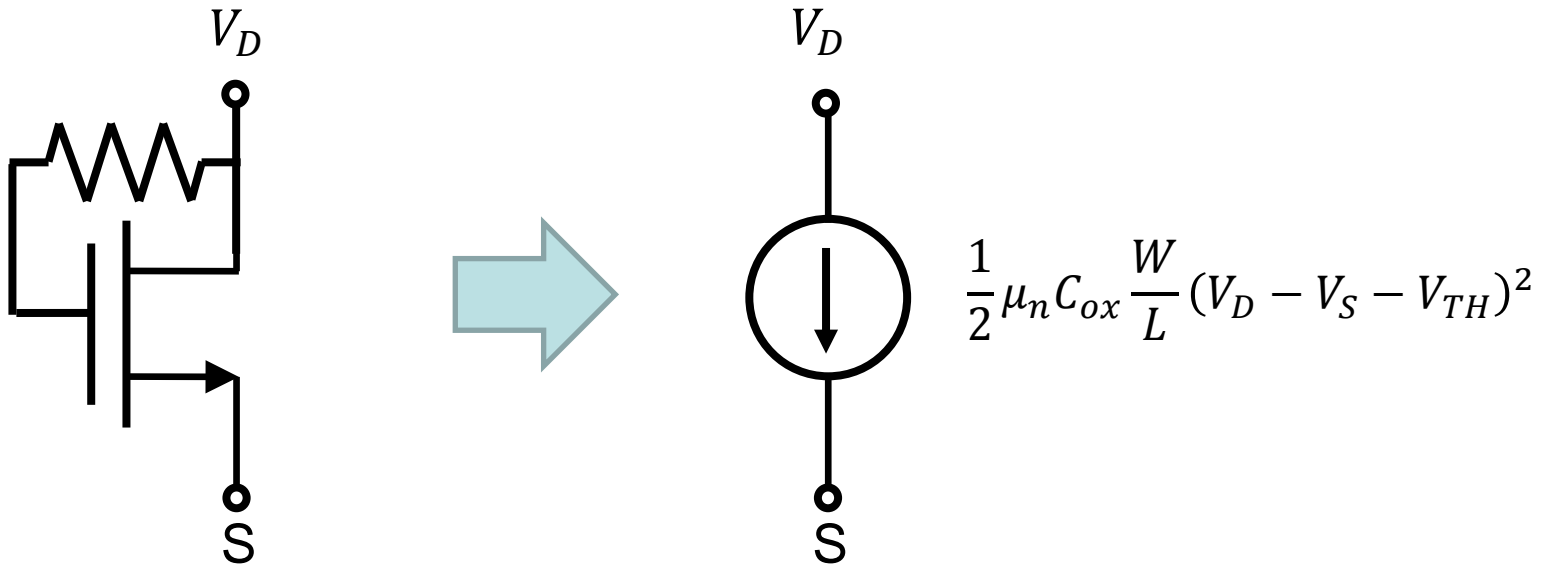- Already covered in Razavi Example 6.13.
 - Always in the saturation region.




Gate and drain are tied.

Diode-connected load

- Use a diode-connected load.
 - It is not an ideal current source.


$$v_{out} = -g_{m1} \left(r_{O1} \parallel \frac{1}{g_{m2}} \parallel r_{O2} \right) v_{in}$$
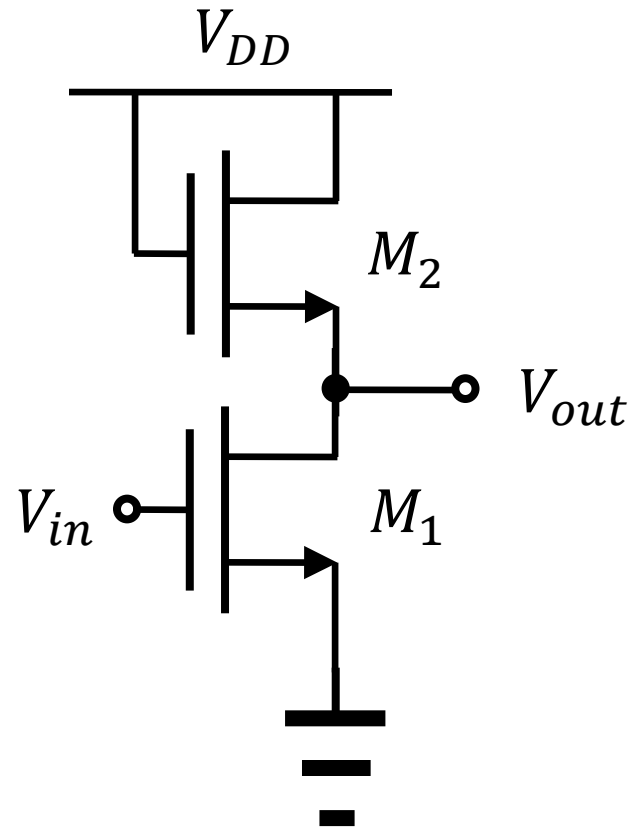
$$A_v = -g_{m1} \left(r_{O1} \parallel \frac{1}{g_{m2}} \parallel r_{O2} \right)$$



Source degeneration

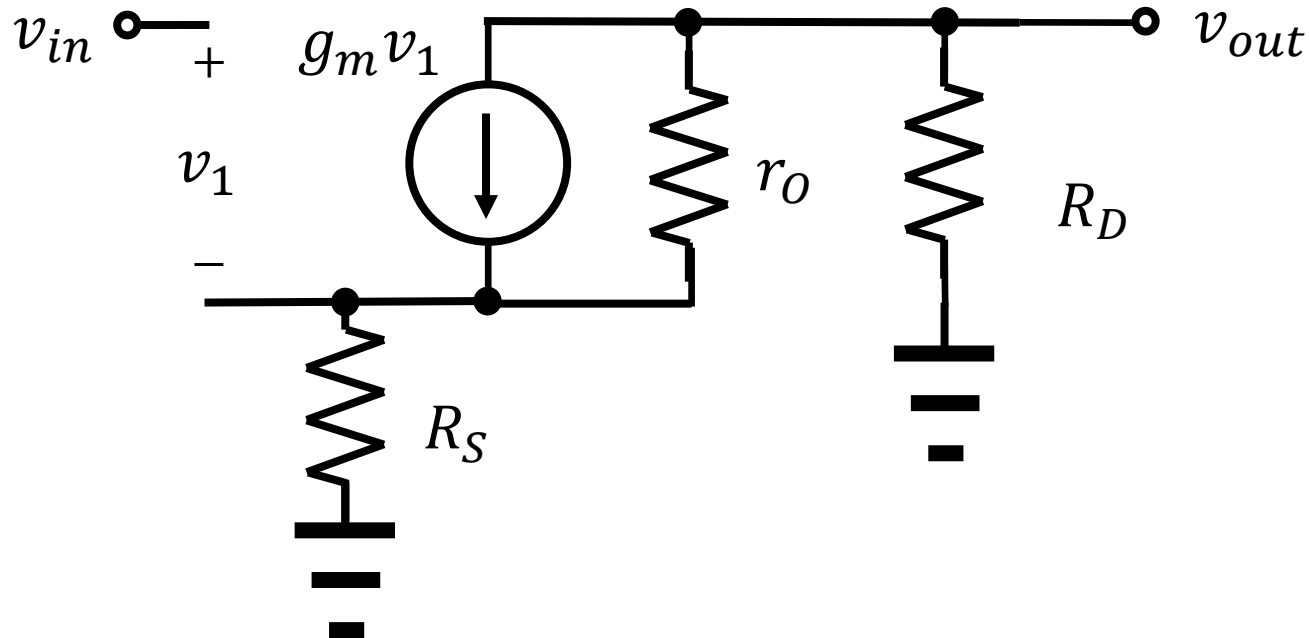- Consider a case with a source resistor, R_S .
 - Calculate the gain and the output impedance.




Razavi, example 17.8

- Biasing


- What is the gate voltage?
- Condition for saturation mode?
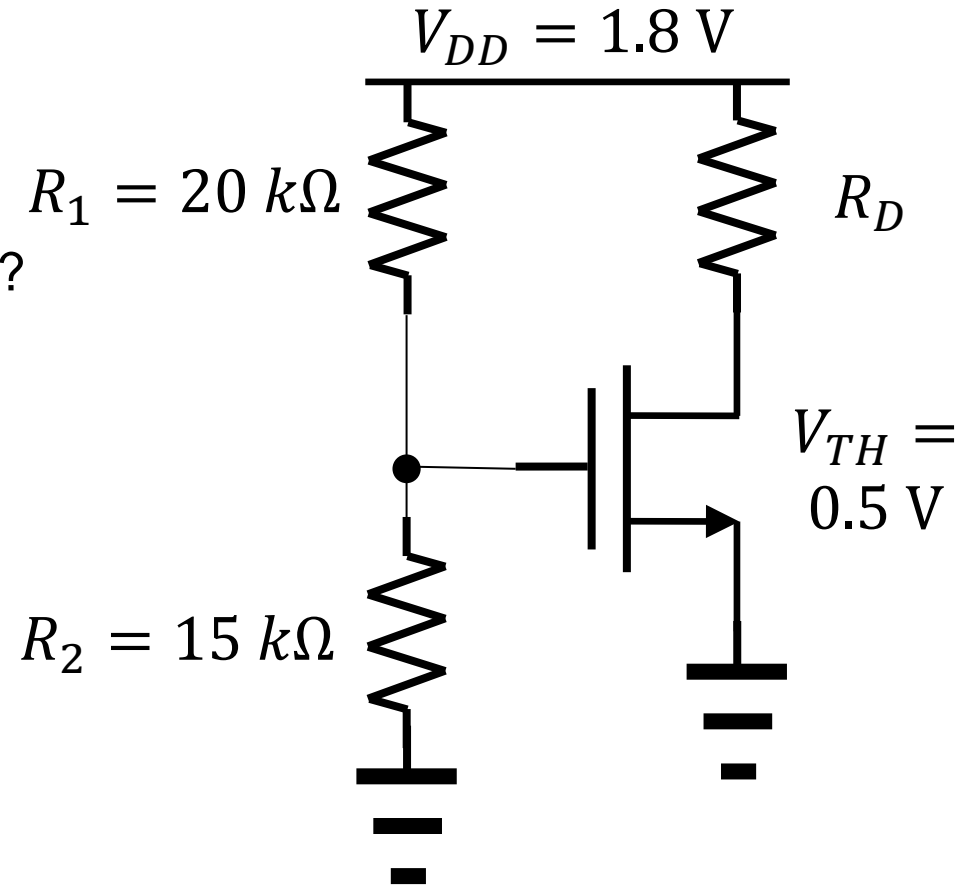
$$\mu_n C_{ox} = 100 \mu\text{A}/\text{V}^2$$
$$W/L = 5/0.18$$



Razavi, example 17.13

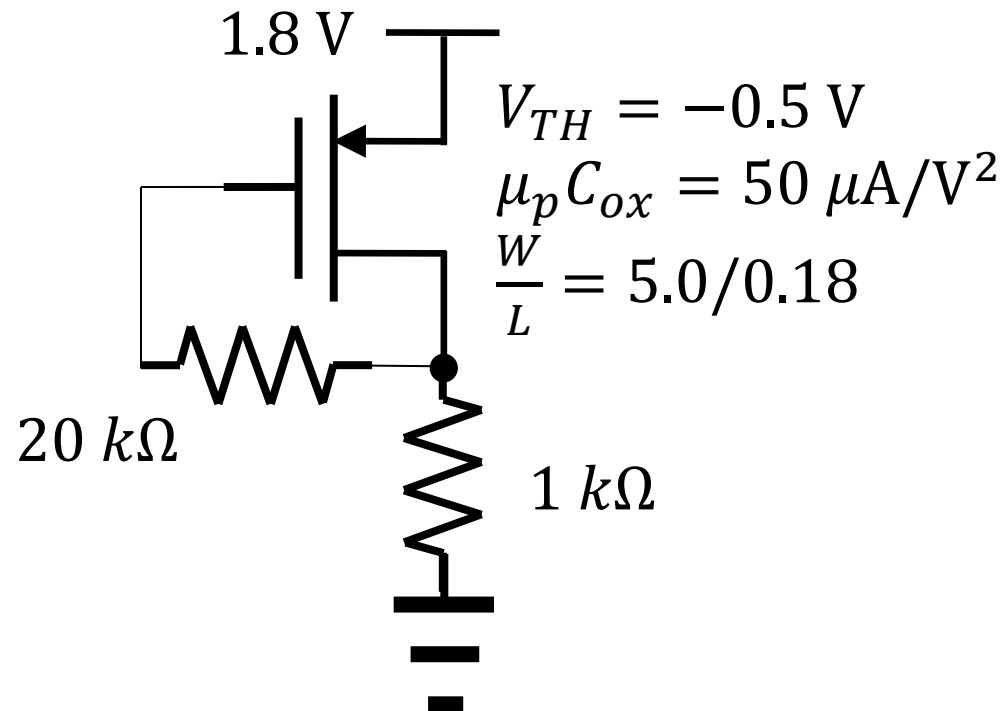- Calculate the drain current. (BTW, where is the drain?)




Razavi, example 17.14

- Calculate the gain.
 - The gain is given by $A_v = -g_m R_D$.
 - How can we get the transconductance?

$$\mu_n C_{ox} = 100 \mu\text{A}/\text{V}^2$$

$$V_{TH} = 0.5 \text{ V}$$

$$W/L = 10/0.18$$

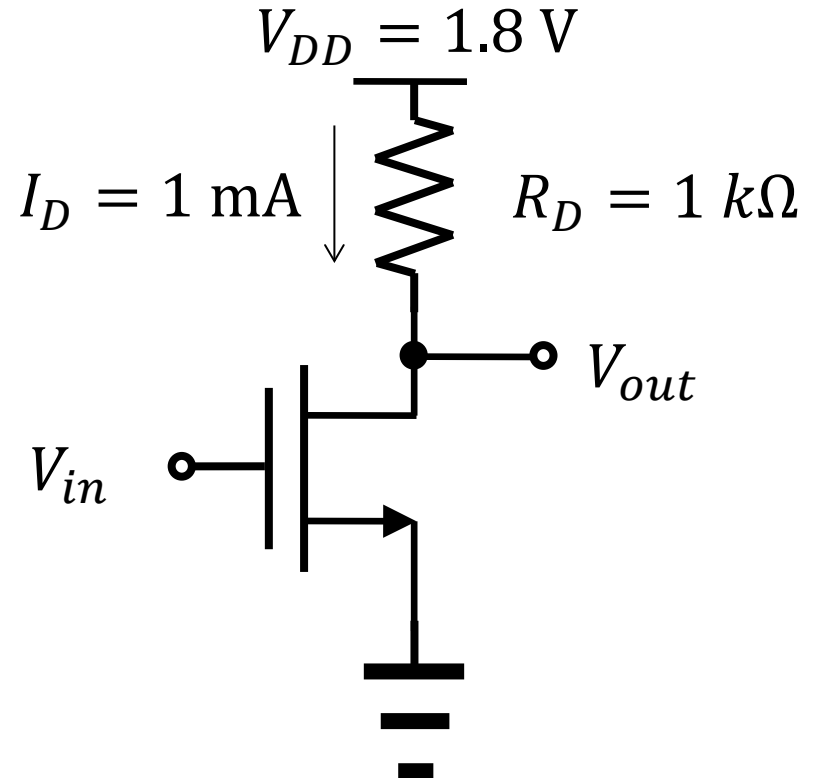

Configurations

- Three terminals of the MOSFET
 - The common terminal, the input terminal, and the output terminal

Source	Gate	Drain	Remark
Common	Input	Output	Common-source amp.
Common	Output	Input	X
Input	Common	Output	It will be covered.
Output	Common	Input	X
Input	Output	Common	X
Output	Input	Common	It will be covered.