
Lecture17: Common-source amplifier (1)

Sung-Min Hong (smhong@gist.ac.kr)

Semiconductor Device Simulation Lab.
School of Electrical Engineering and Computer Science
Gwangju Institute of Science and Technology


Common-source amplifier

- The source terminal is the reference.

– The output voltage is $V_{out} = V_{DD} - I_D R_D$.


$$V_{out}(t) =$$
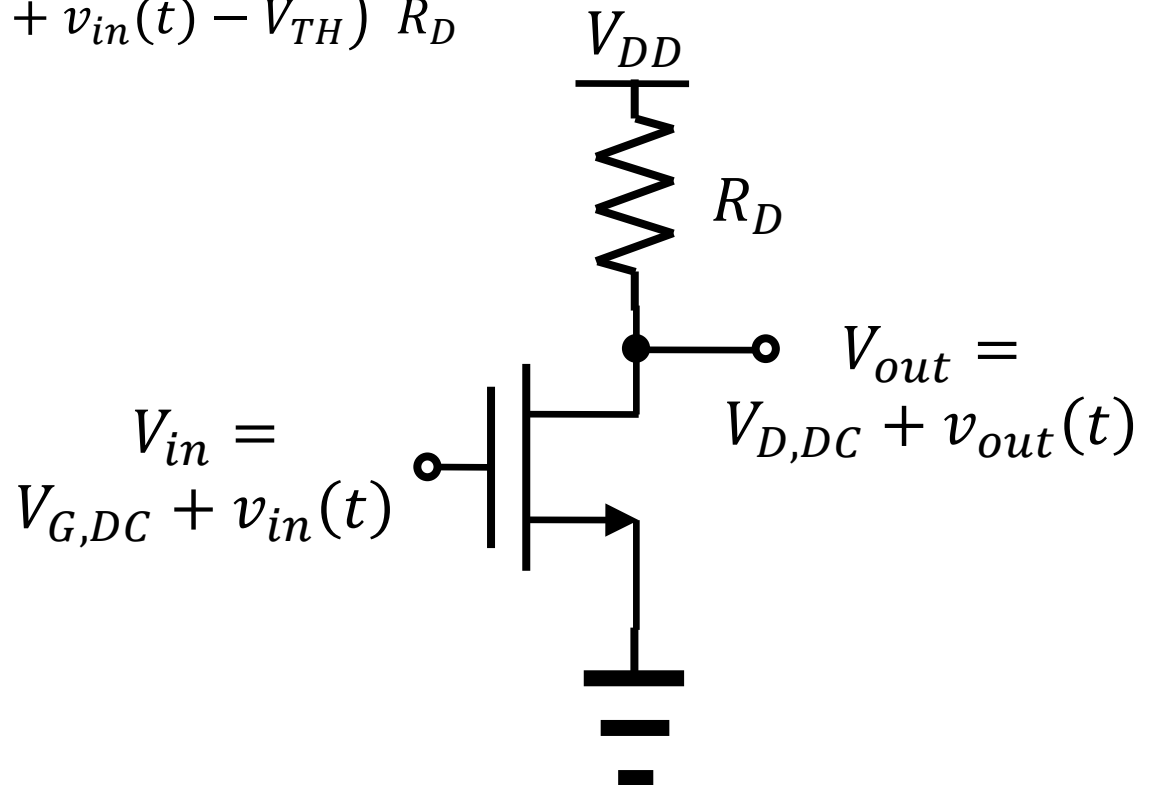
$$V_{DD} - \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{G,DC} + v_{in}(t) - V_{TH})^2 R_D$$




Small-signal model

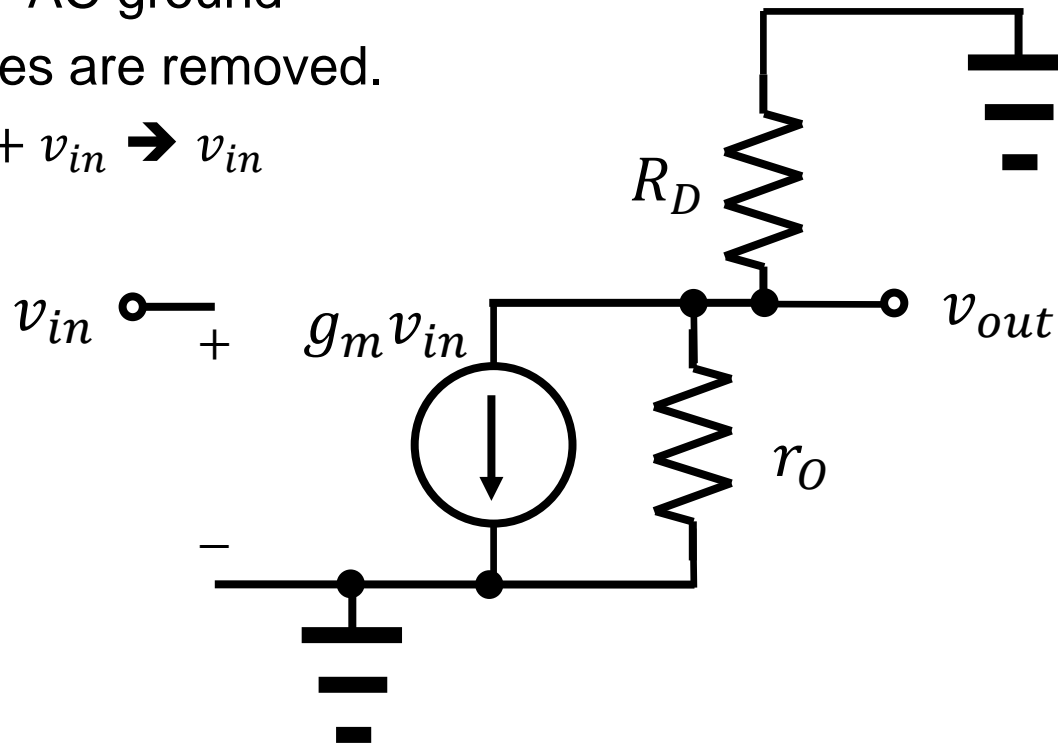- Let's draw its small-signal model together!
 - A transistor small-signal model is introduced.
 - Resistors \rightarrow resistors
 - Ground \rightarrow AC ground
 - DC voltages are removed.
 - Ex) $V_{G,DC} + v_{in} \rightarrow v_{in}$



Gain

- Now, calculate the v_{out} .
 - KCL for the v_{out} node gives
$$v_{out} = -g_m(R_D || r_o)v_{in}$$
 - Therefore, the voltage gain, A_v , is
$$A_v = -g_m(R_D || r_o)$$

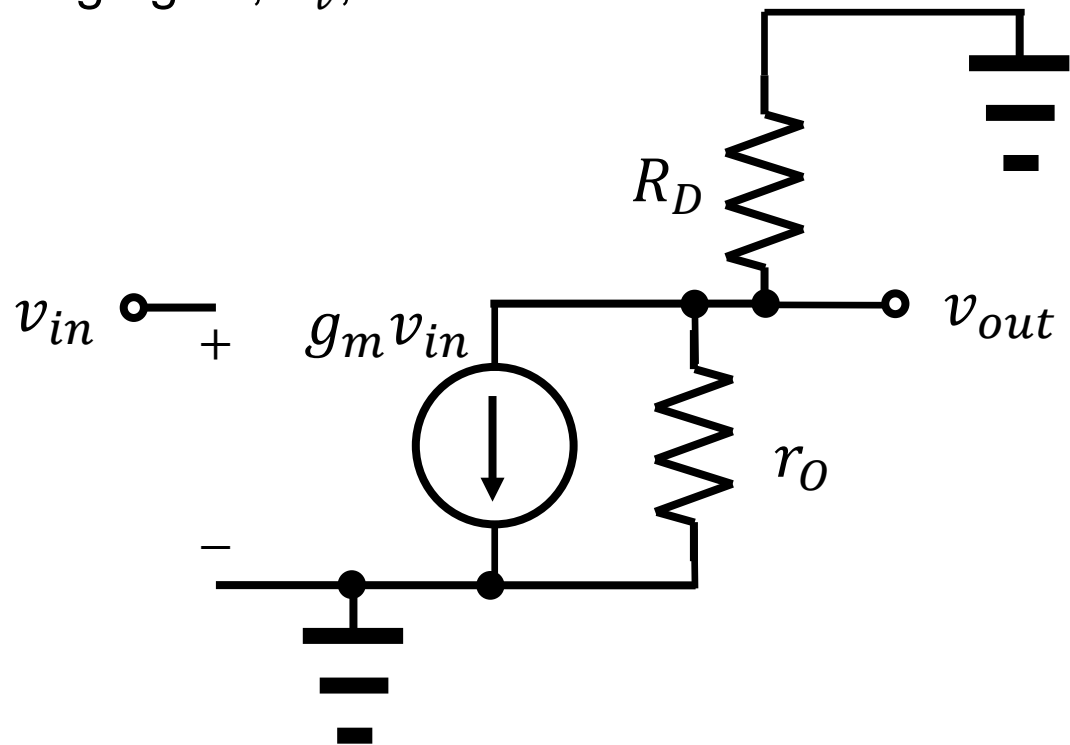

Increasing the gain


- The voltage gain has two factors.
 - Transconductance(g_m): Selecting W , L , and V_{GS} to maximize the transconductance
 - Resistance($R_D || r_O$): A large R_D value is desirable. However, there is a restriction.

$$V_{D,DC} = V_{DD} - R_D I_{D,DC}$$

- A too large value of R_D reduces $V_{D,DC}$ too much. The triode mode is not suitable for the amplification due to its smaller transconductance.
- A drain load other than a simple resistor can be tried.

Impact of R_S

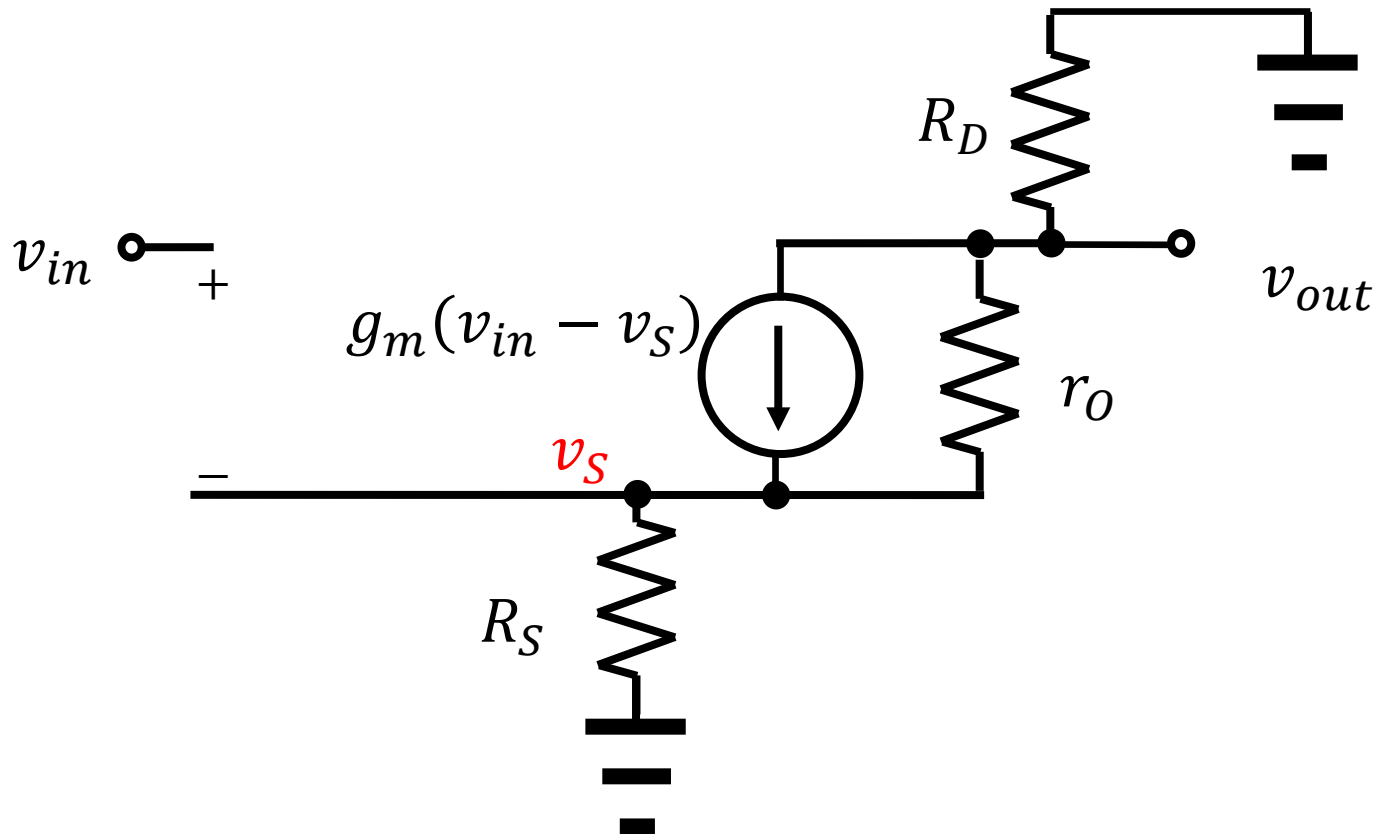- Consider a source resistance, R_S .
 - Repeat the previous slide.




Input/output impedances

- When calculating the impedance, the voltage sources at other terminals are neglected.
- Input and output impedances

$$R_{in} = \infty$$

$$R_{out} = R_D || r_o$$

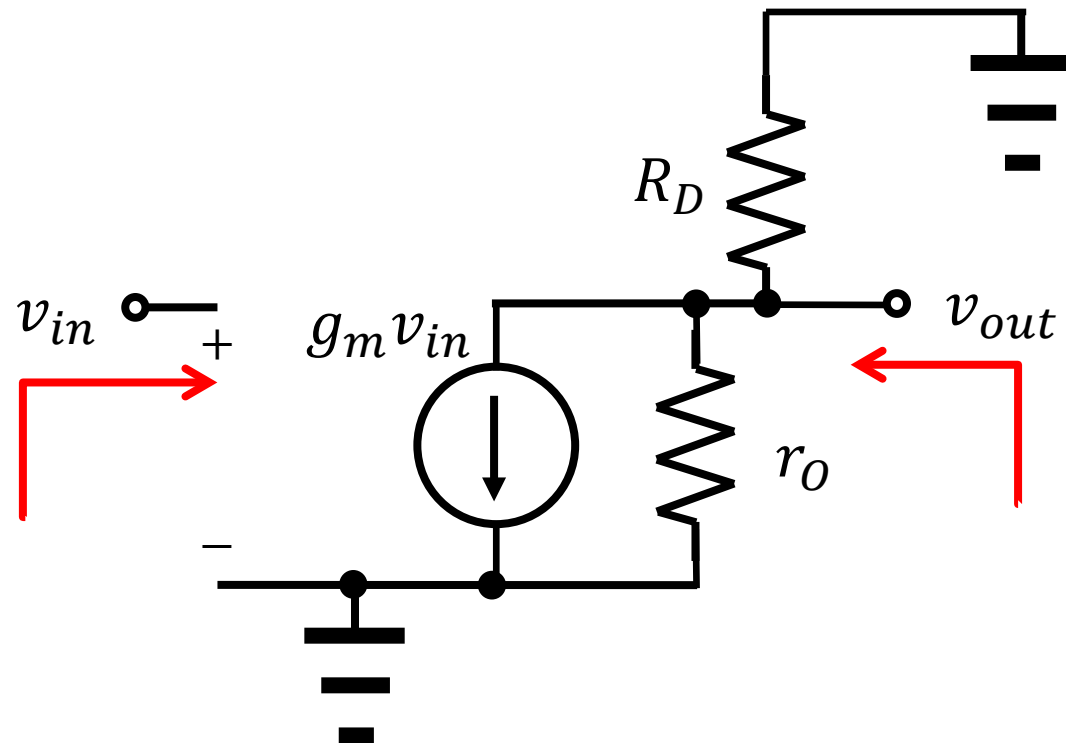

Homework#8

- Due: 09:00, **May 13 (Mon)**
- Design the common-source state.
 - A voltage gain is 5 and an output impedance is $1\text{ k}\Omega$. Bias the transistor so that it operates 100 mV away from the triode region. Assume the capacitors are very large and $R_D = 10\text{ k}\Omega$.

