

---

# Lecture12: MOSFET, transconductance

Sung-Min Hong ([smhong@gist.ac.kr](mailto:smhong@gist.ac.kr))

Semiconductor Device Simulation Lab.  
School of Electrical Engineering and Computer Science  
Gwangju Institute of Science and Technology

# Review on MOSFET IV

---

- When  $V_G < V_{TH}$ ,
  - No drain current!

$$I_D = 0$$

- When  $V_G > V_{TH}$ ,
  - Triode mode ( $V_{DS} < V_G - V_{TH}$ )
$$I_D = \mu_n C_{ox} \frac{W}{L} \left[ (V_G - V_{TH}) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$$
  - Saturation mode ( $V_{DS} > V_G - V_{TH}$ )
$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_G - V_{TH})^2$$
  - For a short channel device,  $I_D$  increases slightly as  $V_{DS}$  increases.


# Example 6.6 (Razavi)

- Assume the saturation region.
  - The saturation current becomes  $200 \mu\text{A}$ .

$$I_D = \frac{1}{2} 100\mu \frac{2.0}{0.18} (1 - 0.4)^2 = 200 \mu\text{A}$$

- Then, the drain voltage is
$$V_D = 1.8 - 200\mu \times 5k = 0.8 \text{ V}$$

- Is the MOSFET in the saturation mode?

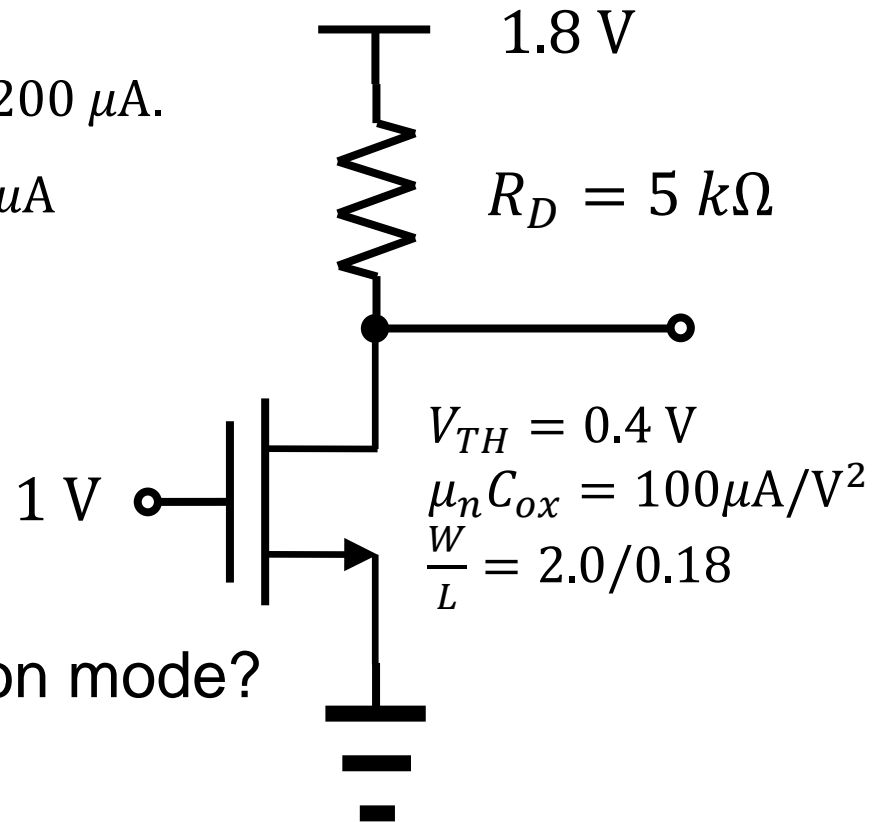

# $V_{out}$ versus $V_{in}$

---

- A table

$V_{in}$ (V)	$V_{out}$ (V)
0.0	1.8
<0.4	1.8
0.7	1.55
1.0	0.8
$X$	$X - 0.4$
1.8	$Y$

- What are the values of  $X$  and  $Y$ ?

# MOS transconductance

---

- “conductance” of a simple resistor:  $\partial I / \partial V = I / V$
- “trans” + “conductance” between different terminals

$$g_m = \frac{\partial I_D}{\partial V_{GS}} \quad (\text{Razavi 6.44})$$

- For the saturation region,


$$g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})$$

$$g_m = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D}$$

$$g_m = \frac{2I_D}{V_{GS} - V_{TH}}$$

# Channel length modulation

- Channel length modulation

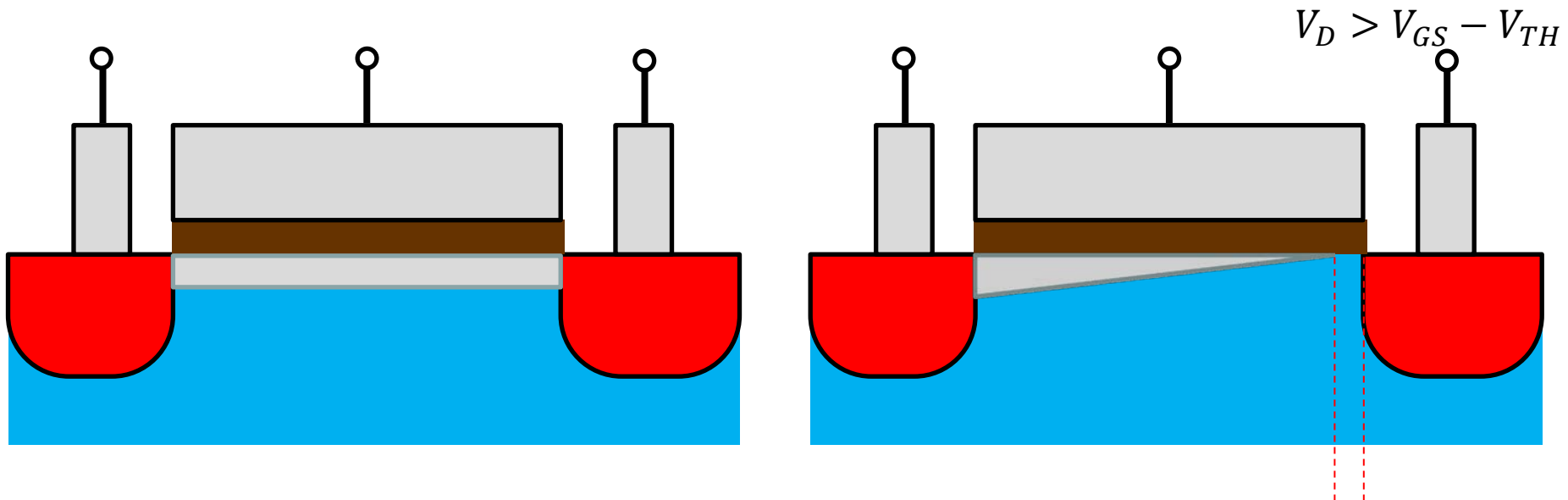




- Output resistance?

$$r_o = \frac{\Delta V_{DS}}{\Delta I_D}$$
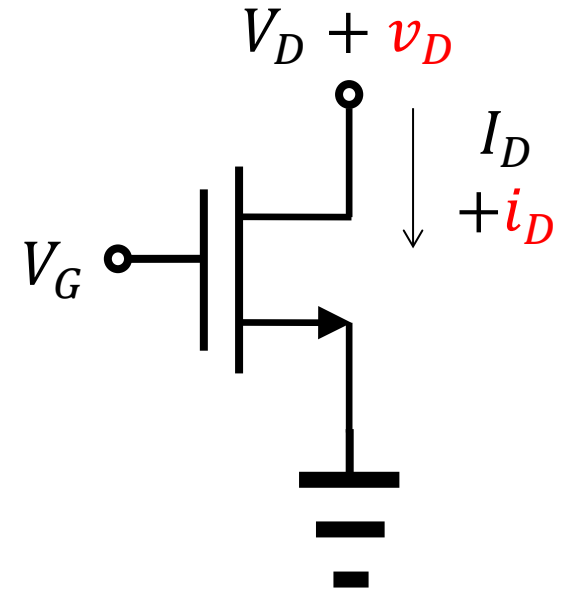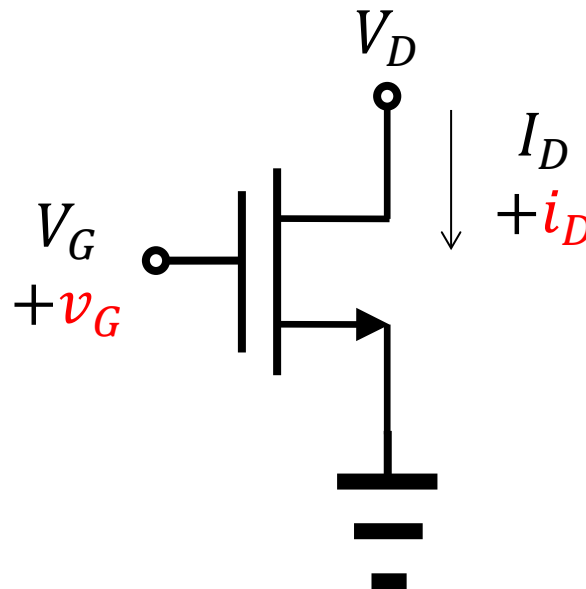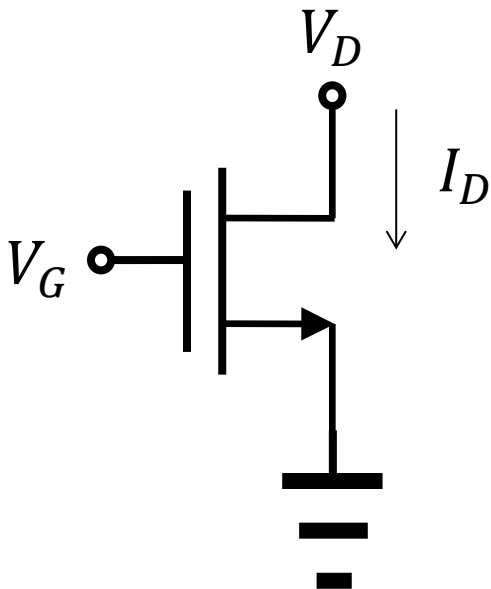
# Summary

---


- We can define two derivatives.
  - Transconductance,  $g_m$ . Output resistance,  $r_o$ .


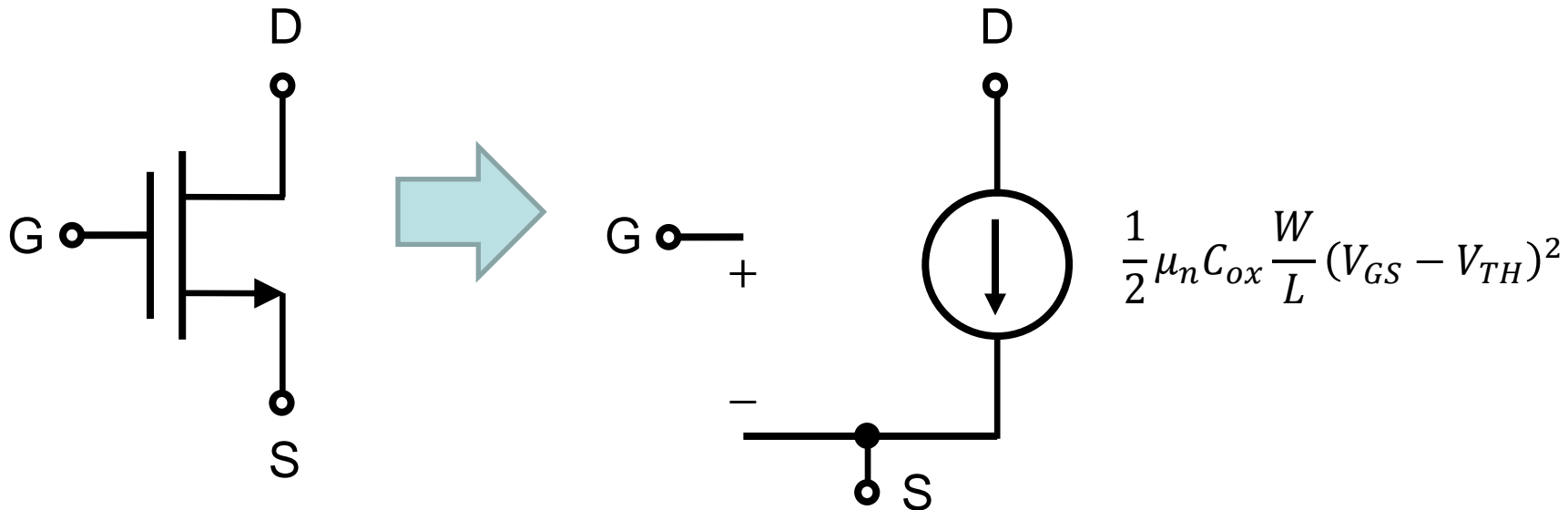
# Large-signal model (1/2)

---

- Saturation region
  - Drain current is determined by gate voltage. (*voltage-controlled current source*)





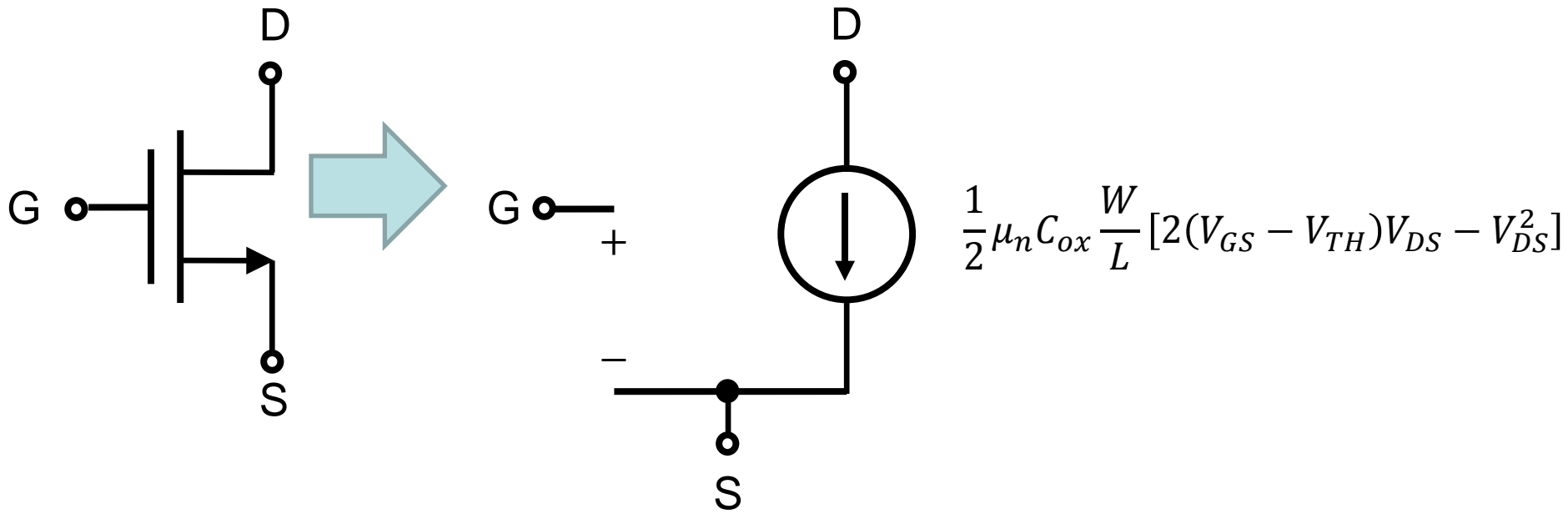
# Large-signal model (2/2)

---


- Triode region
  - Still, it can be described by a *voltage-controlled current source*.


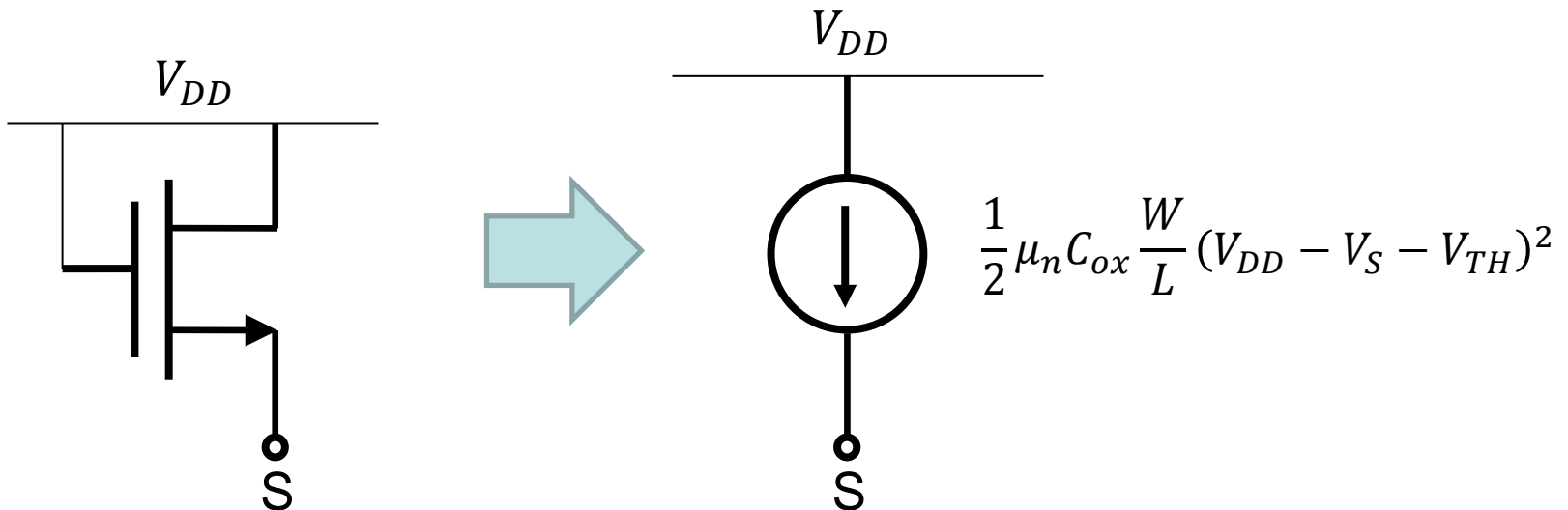
# Example 6.13 (Razavi)

---

- Always in the saturation region!
  - Any necessary condition?




Gate and drain are tied.  
They are connected to  $V_{DD}$ .
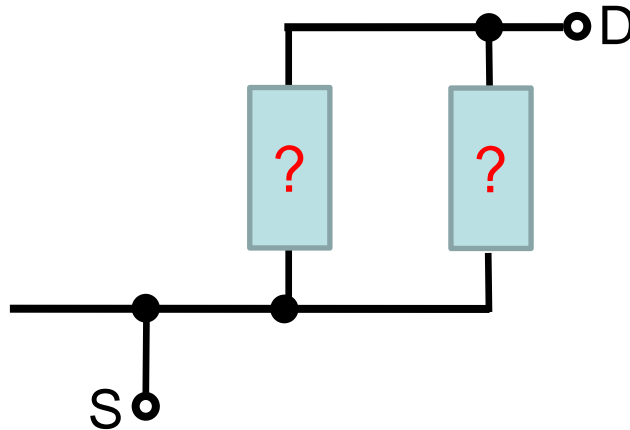
# Small-signal current

---



- Using the transconductance ( $g_m$ ) and the output resistance ( $r_o$ ),
  - The small-signal drain current is given as  $i_D = g_m v_G + \frac{v_D}{r_o}$ .
  - When we build a small-signal model, two contributions must be separately considered.


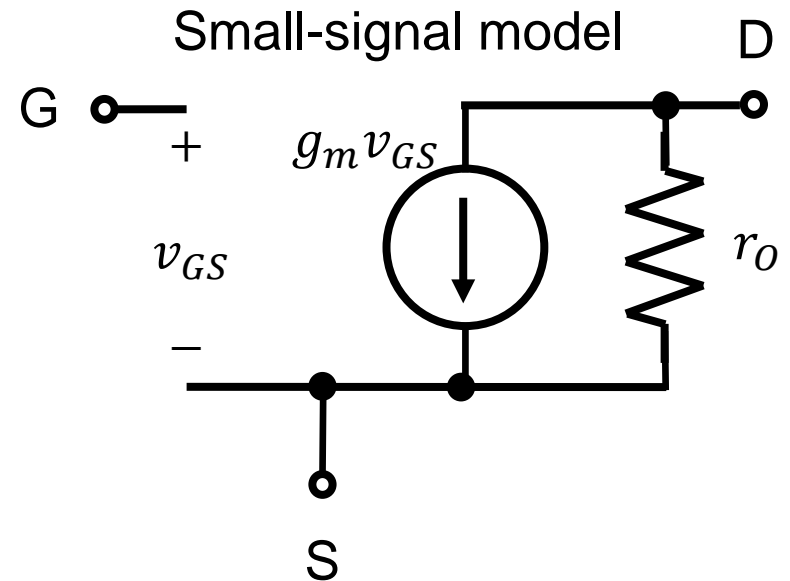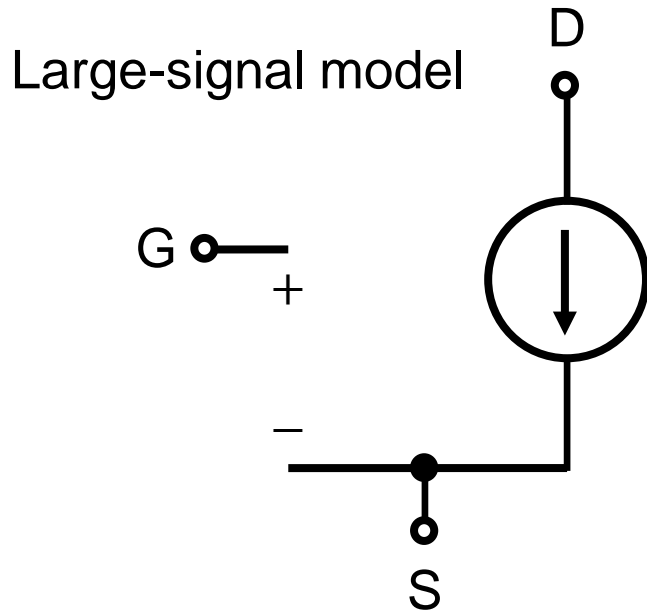
# Small-signal model

---


- For small-signal analysis, a small-signal model for the MOSFET is introduced.


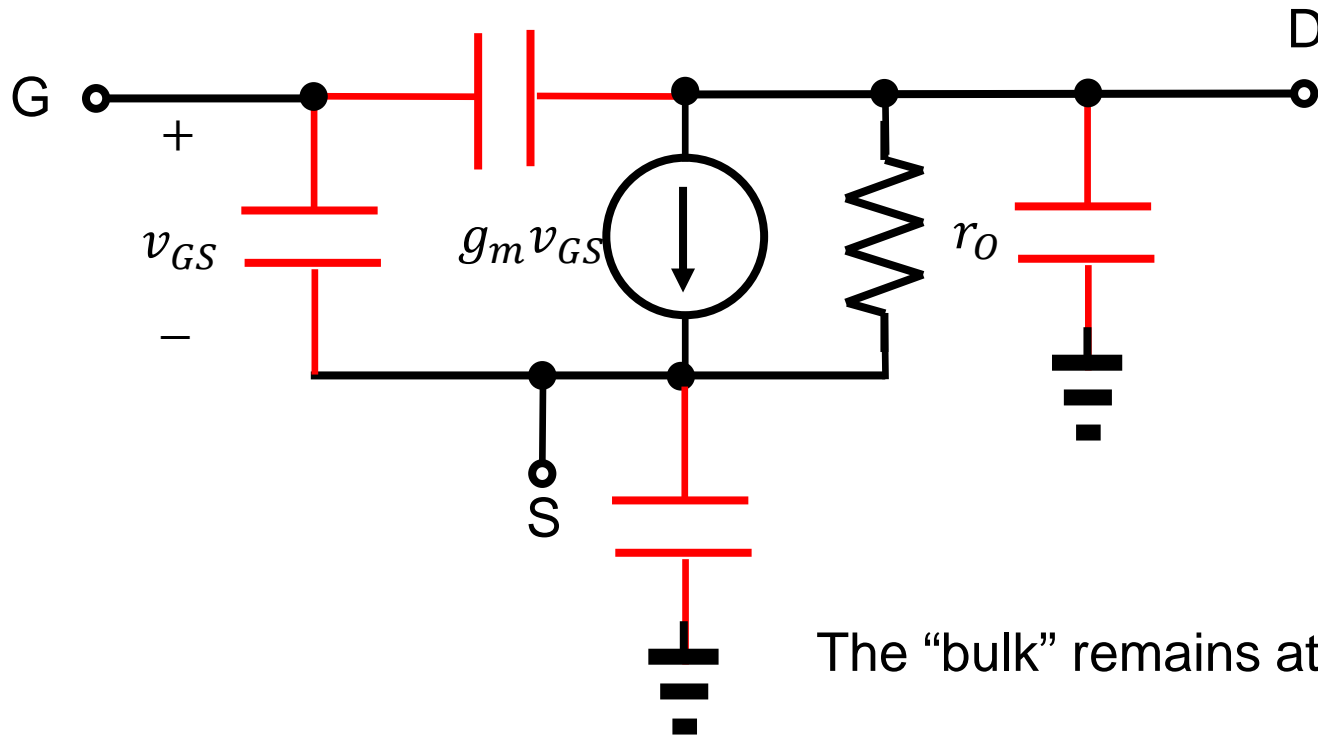
# Time-dependent one?

---

- In general, capacitive components can be seen.



# At low frequencies

---

- Capacitor current is  $I = C \frac{dV}{dt}$ .
  - When a sinusoidal dependence, for example  $\sin \omega t$ , is assumed, the capacitor current is proportional to  $\omega$ .
  - At low frequencies,  $\omega$  can be regarded as a small number.
  - In other words, the electric conduction between two nodes becomes rather weak.
  - Therefore, we often neglect the capacitive components in the small-signal model.
  - Of course, at higher frequencies, they become very important.