

---

# Lecture11:

## Diode models and circuits (3)


Sung-Min Hong ([smhong@gist.ac.kr](mailto:smhong@gist.ac.kr))

Semiconductor Device Simulation Lab.  
School of Information and Communications  
Gwangju Institute of Science and Technology


# Diode

---

- Its symbol

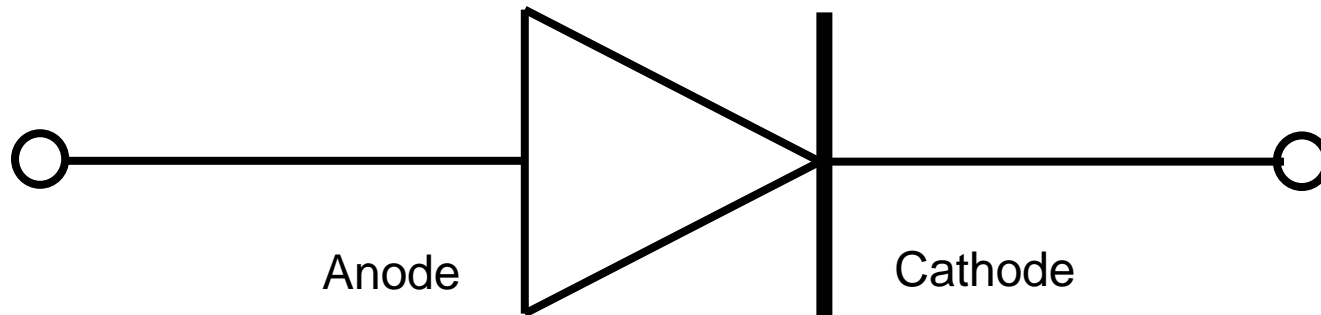


- Ideally, a perfect rectifier

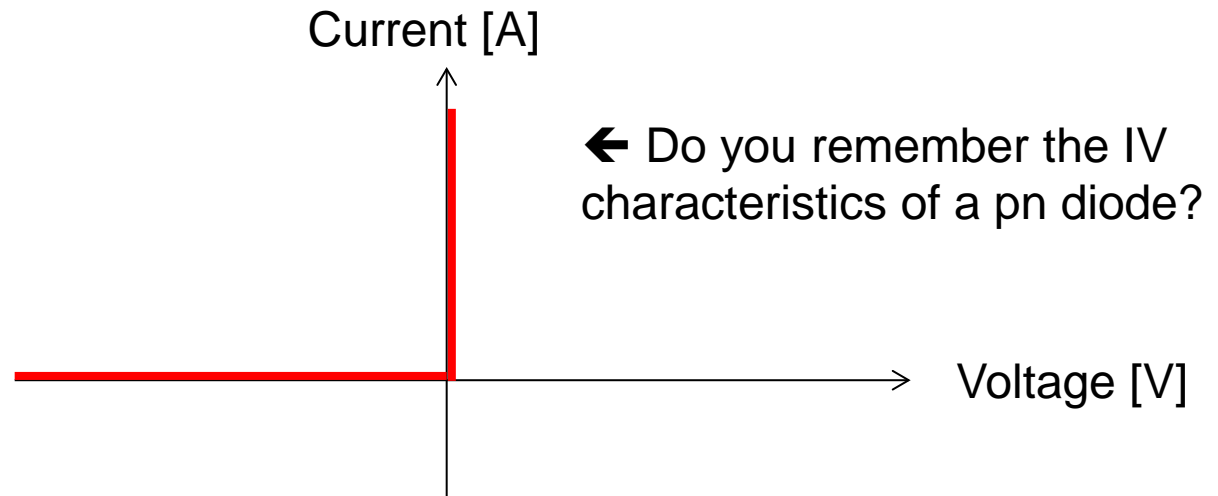

# Example 3.4

---

- A diode-resistor combination

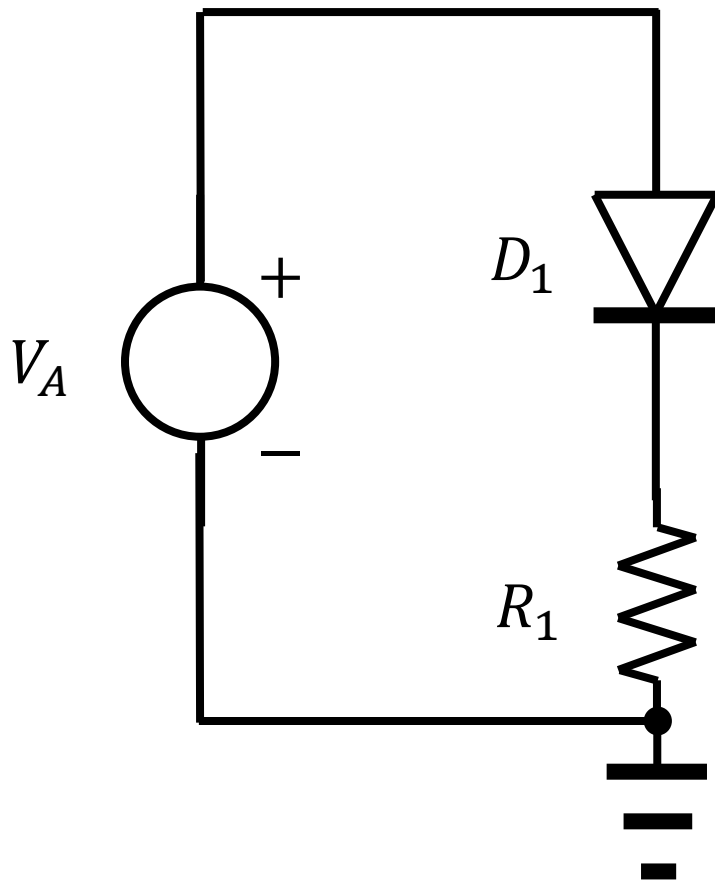


- ← Consider two cases,  $V_A > 0$  and  $V_A < 0$ .
- ← Draw the IV curve.

# Example 3.6

---


- An OR gate

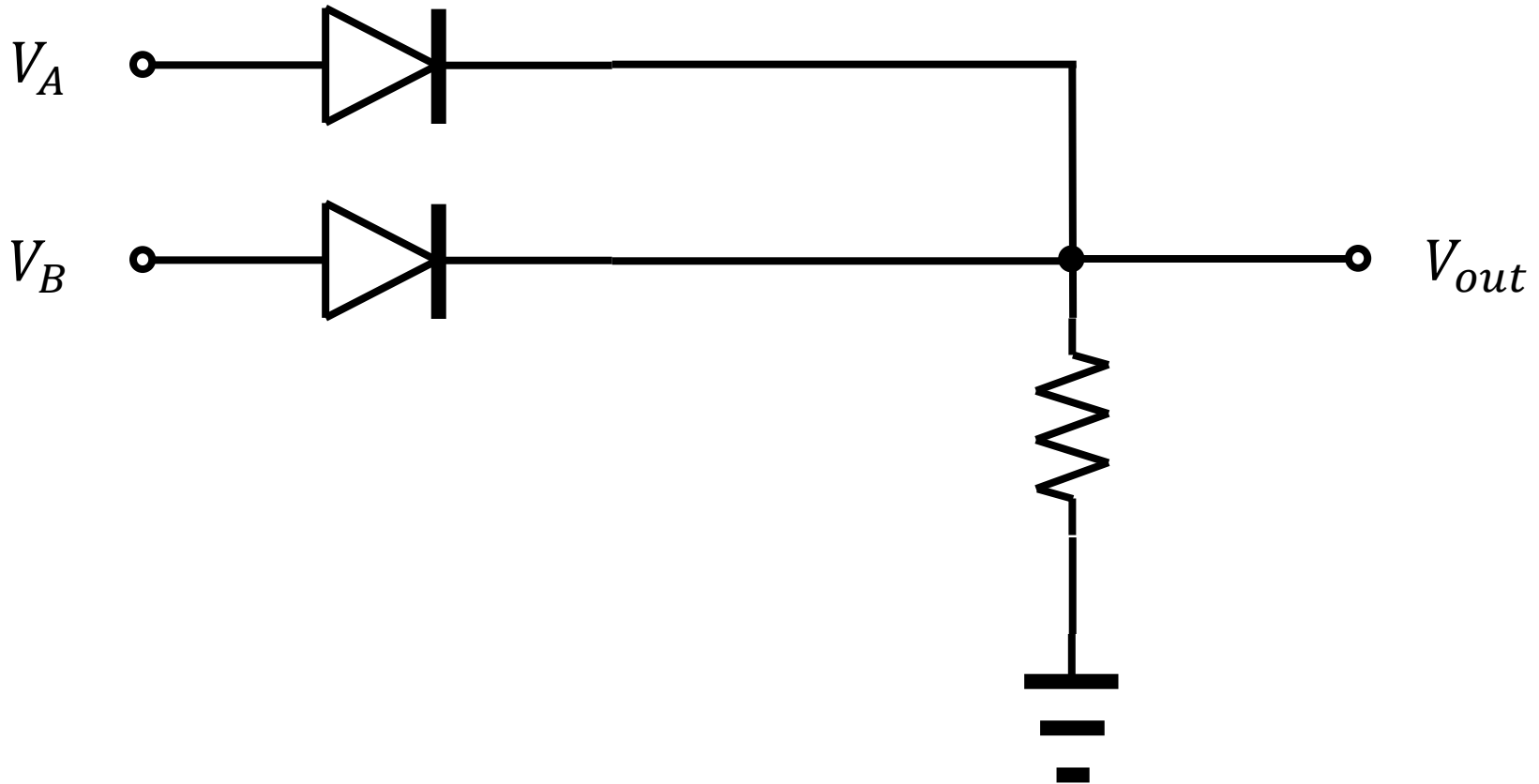

# Rectifier

---


- Same circuit shown in Example 3.4.

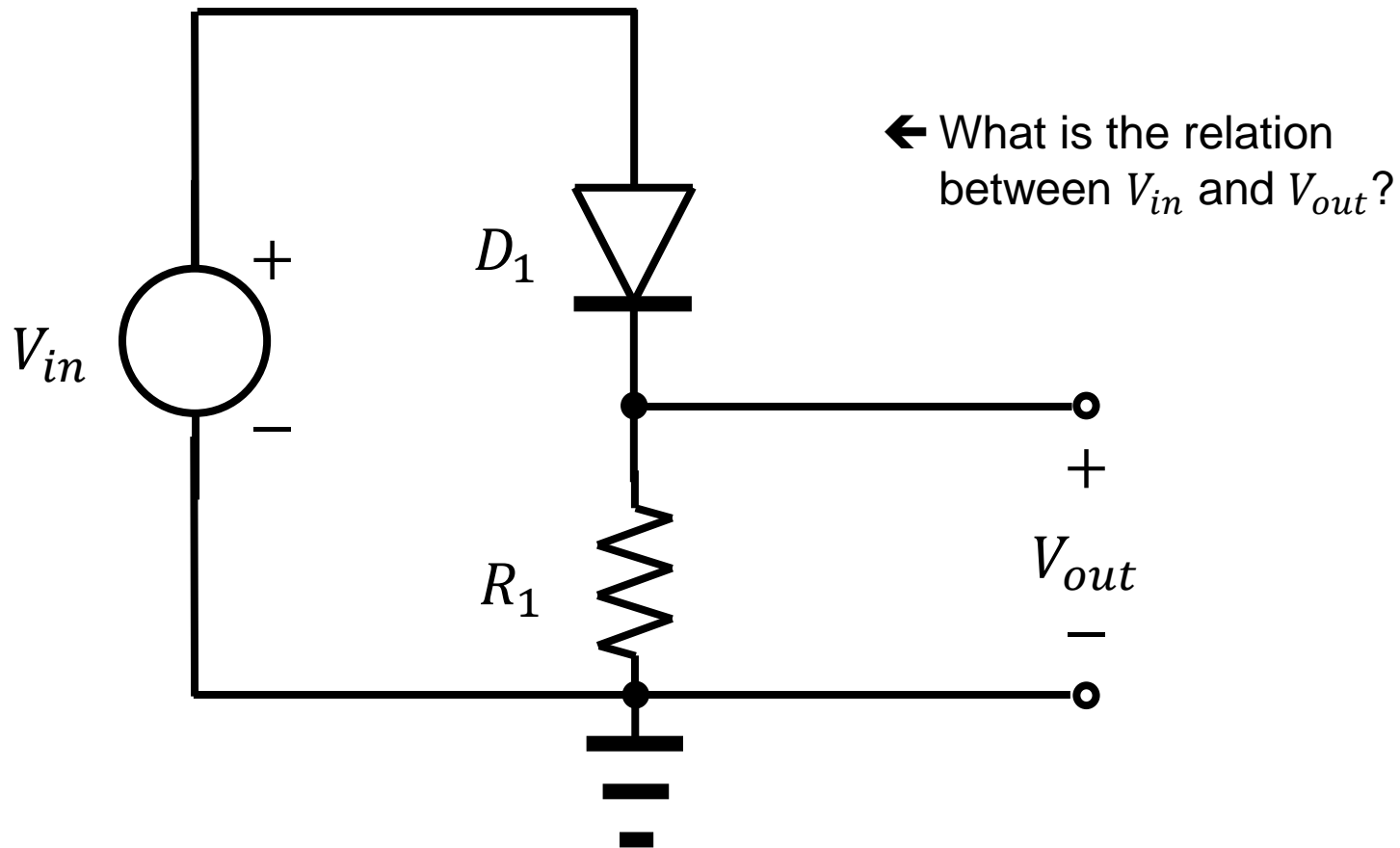

# Input vs. output


- Input

- 50 Hz
- Pure sine
- No dc

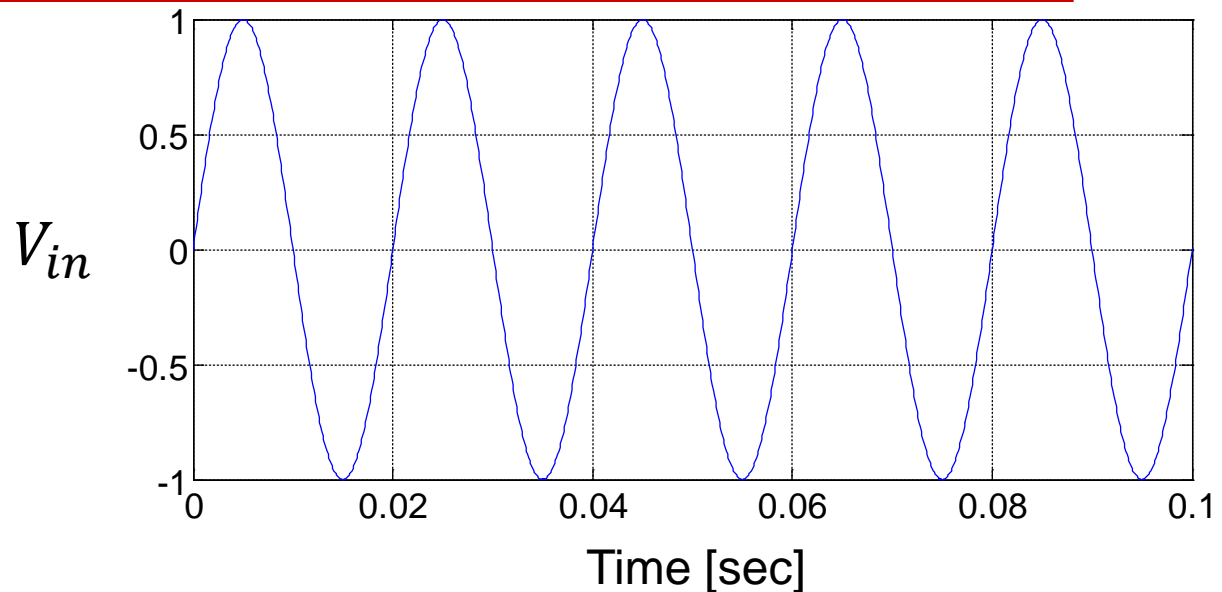

- Output

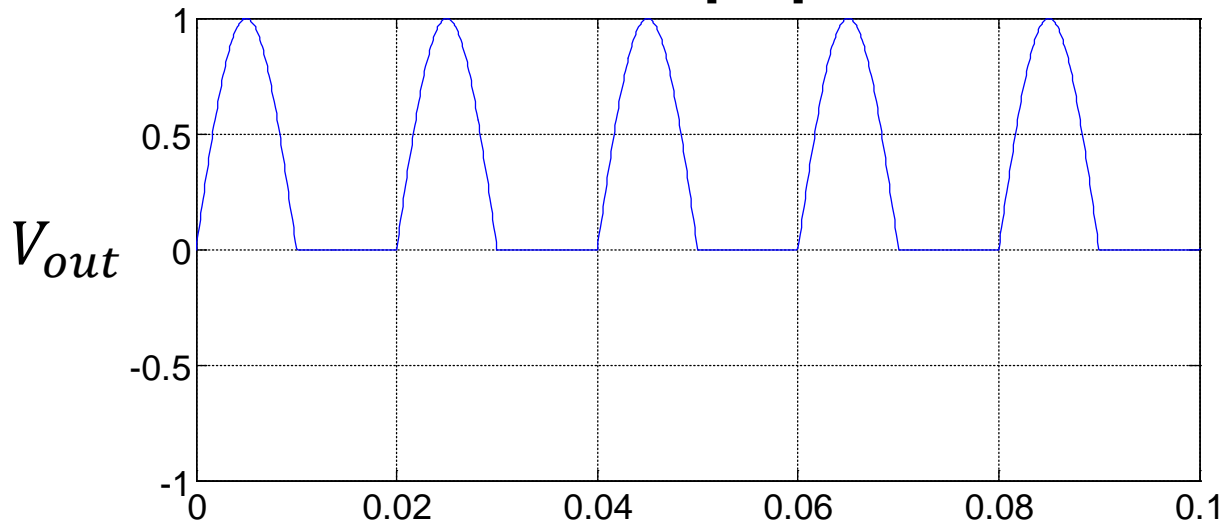- 0, 50, 100, ... Hz
- dc voltage:  $\frac{1}{\pi}$  V




# Concept!

---

- How to detect the electromagnetic radiation
  - Nonlinearity is required.

Incident THz wave (High freq)

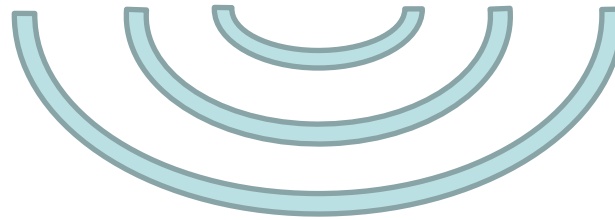

THz detector


Output signal  
(Low freq)



# Rectifier, revisited

---

- Same circuit shown in Example 3.4.

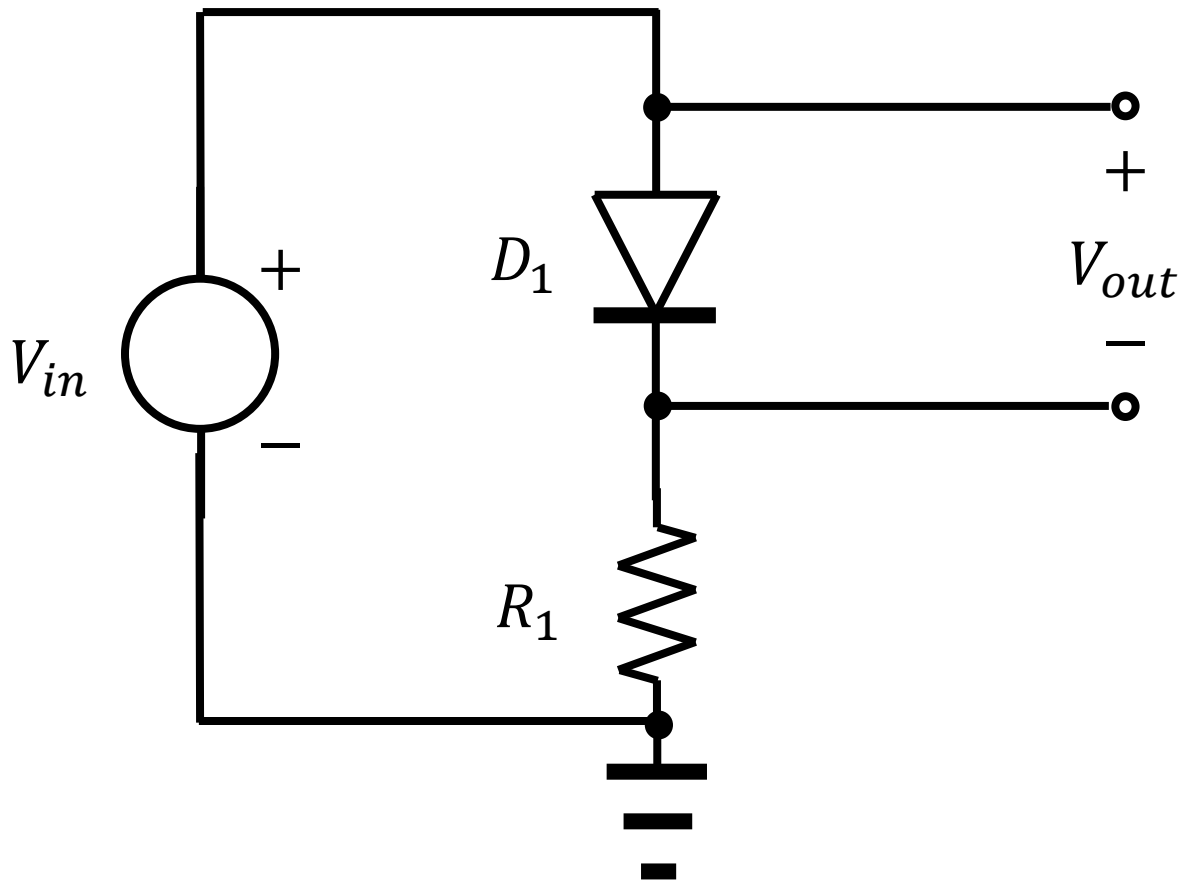




# pn junction as a diode

---

- Exponential model

$$I_D = I_s \left( \exp \frac{V_D}{V_T} - 1 \right)$$

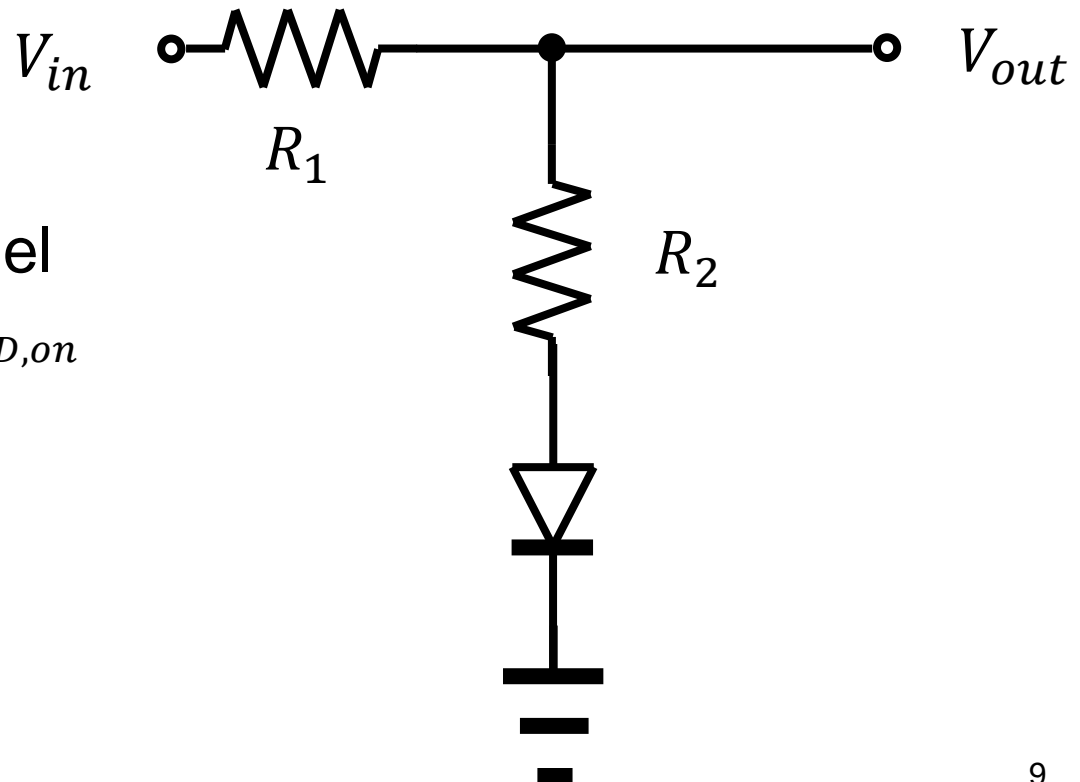- Constant-voltage model
  - An “offset” voltage of  $V_{D,on}$



# A simple math, again

---

- Taylor series expansion
  - Consider a function,  $f(x)$ .
  - Then, at  $x_0 + \Delta x$  ( $\Delta x$  is small.), the function value would be similar to that at  $x_0$ :

$$f(x_0 + \Delta x) \approx f(x_0)$$


- A better approximation?

$$f(x_0 + \Delta x) \approx f(x_0) + \left. \frac{df(x)}{dx} \right|_{x=x_0} \Delta x$$



- Nonlinear function → linearly approximated!
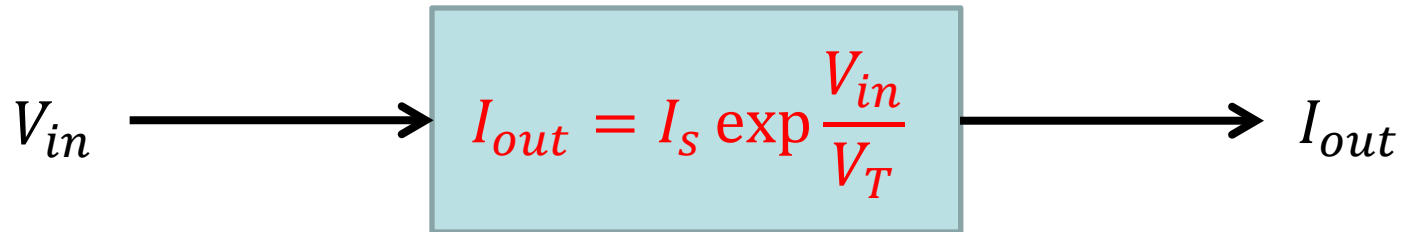
# A system

- A system (You know what it actually represents.)



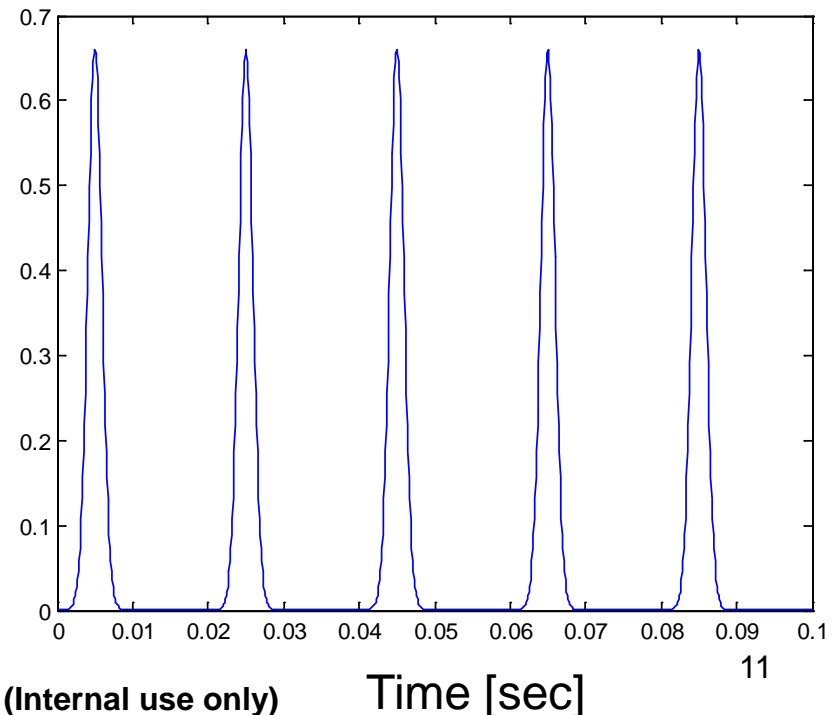
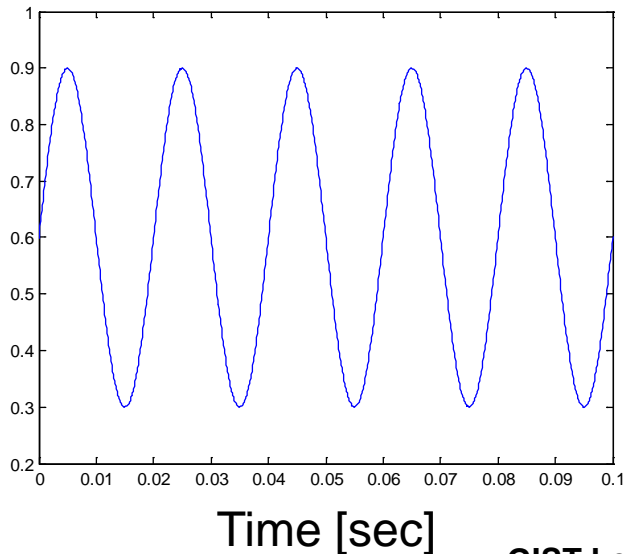
- When  $V_{in} = 0.6 + 0.3 \sin 2\pi f t$ ,
  - Certainly, nonlinear!


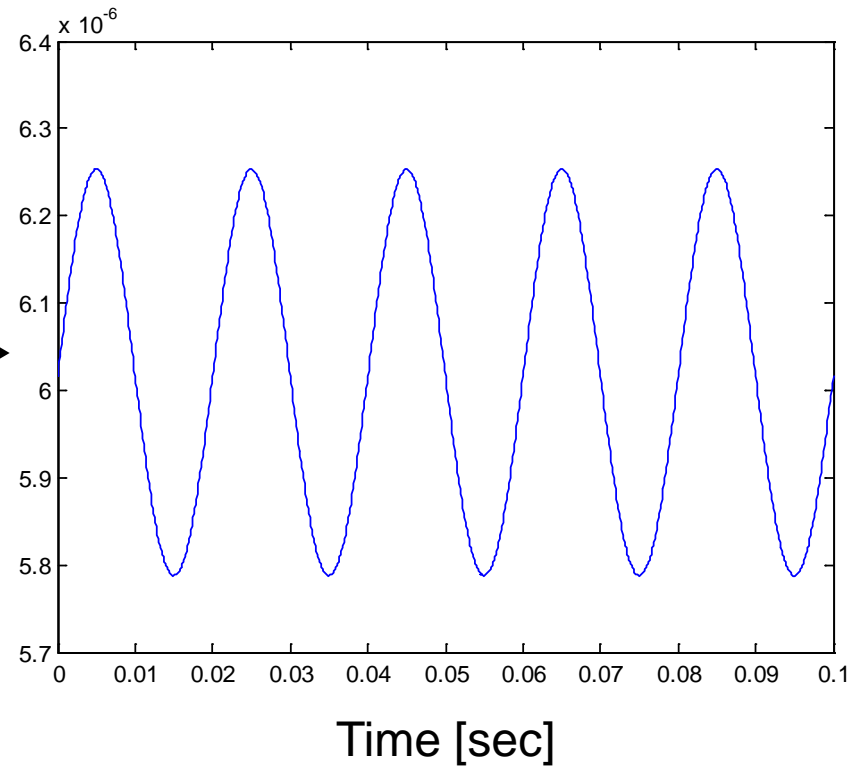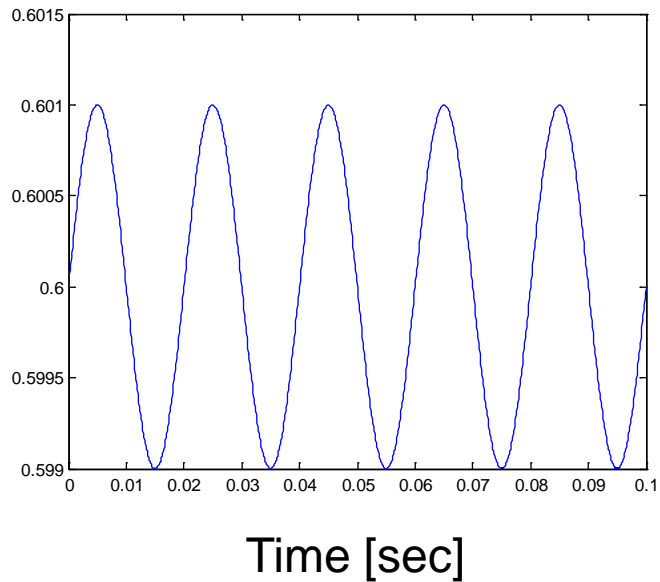
# Smaller amplitude?

---

- When  $V_{in} = 0.6 + 0.001 \sin 2\pi f t$ ,
  - Nonlinear?



# Verbatim (p. 66)

---

- These thought lead us to the extremely important concept of “small-signal operation,” whereby the circuit experiences only small changes in voltages and currents.
- Therefore it can be simplified through the use of “small-signal models” for nonlinear devices.
- The simplicity arises because such models are linear, allowing standard circuit analysis and obviating the need for iteration.

# Exponential

---

- Simple, but important example

- A diode is biased to a voltage  $V_{D1}$ .

- The current is given by  $I_{D1}$ .

$$I_{D2} = I_s \exp \frac{V_{D1} + \Delta V}{V_T} = I_s \exp \frac{V_{D1}}{V_T} \exp \frac{\Delta V}{V_T}$$

$$I_{D2} \approx I_{D1} \left( 1 + \frac{\Delta V}{V_T} \right)$$

# Example 3.18

---

- A diode is biased at a current of 1 mA.
  - Determine the current change if  $V_D$  changes by 1 mV.

$$\Delta I_D = \frac{I_D}{V_T} \Delta V_D \approx 40 \mu\text{A}$$

- Small-signal resistance
  - As far as small changes in the diode current and voltage are concerned, the device behaves as a linear resistor.

$$r_d = \frac{V_T}{I_D}$$

# Example 3.19

---

- When the small change in the diode voltage is time-varying,
  - What happens?

$$I_{D2} = I_s \exp \frac{V_{D1} + \Delta V}{V_T} = I_s \exp \frac{V_{D1}}{V_T} \exp \frac{\Delta V}{V_T}$$

$$I_{D2} \approx I_{D1} \left( 1 + \frac{\Delta V}{V_T} \right)$$



$$I_{D2} = I_s \exp \frac{V_{D1} + \Delta V \cos \omega t}{V_T} = I_s \exp \frac{V_{D1}}{V_T} \exp \frac{\Delta V \cos \omega t}{V_T}$$

$$I_{D2} \approx I_{D1} \left( 1 + \frac{\Delta V \cos \omega t}{V_T} \right)$$



# Rectifier, revisited


- Constant-voltage model?

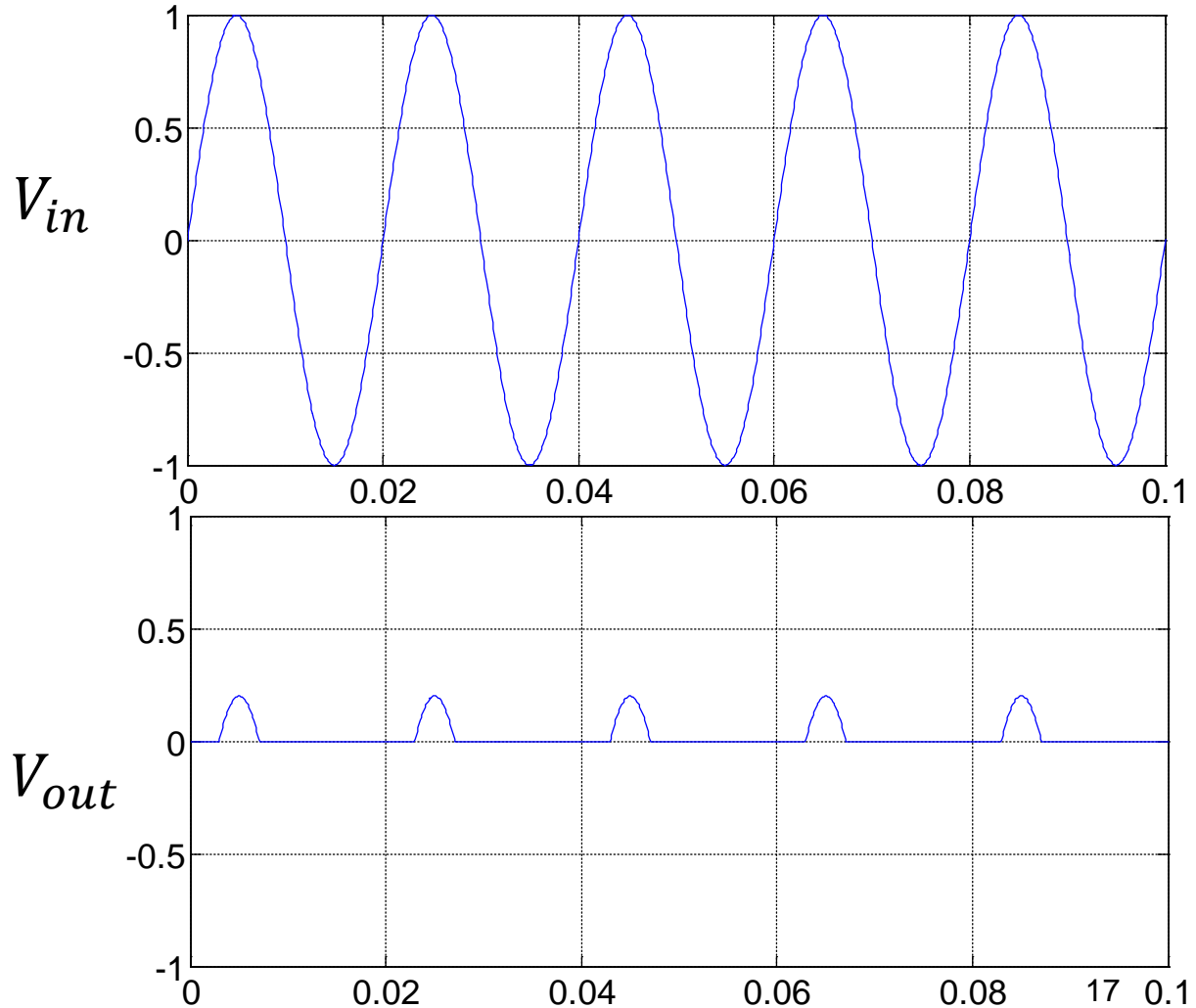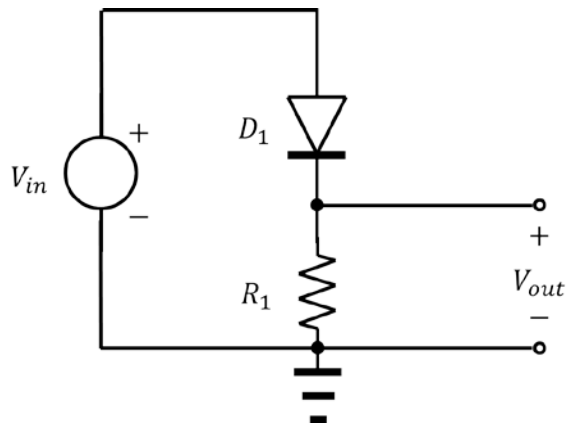

# Introducing a capacitor

---

- Difference from the previous one?

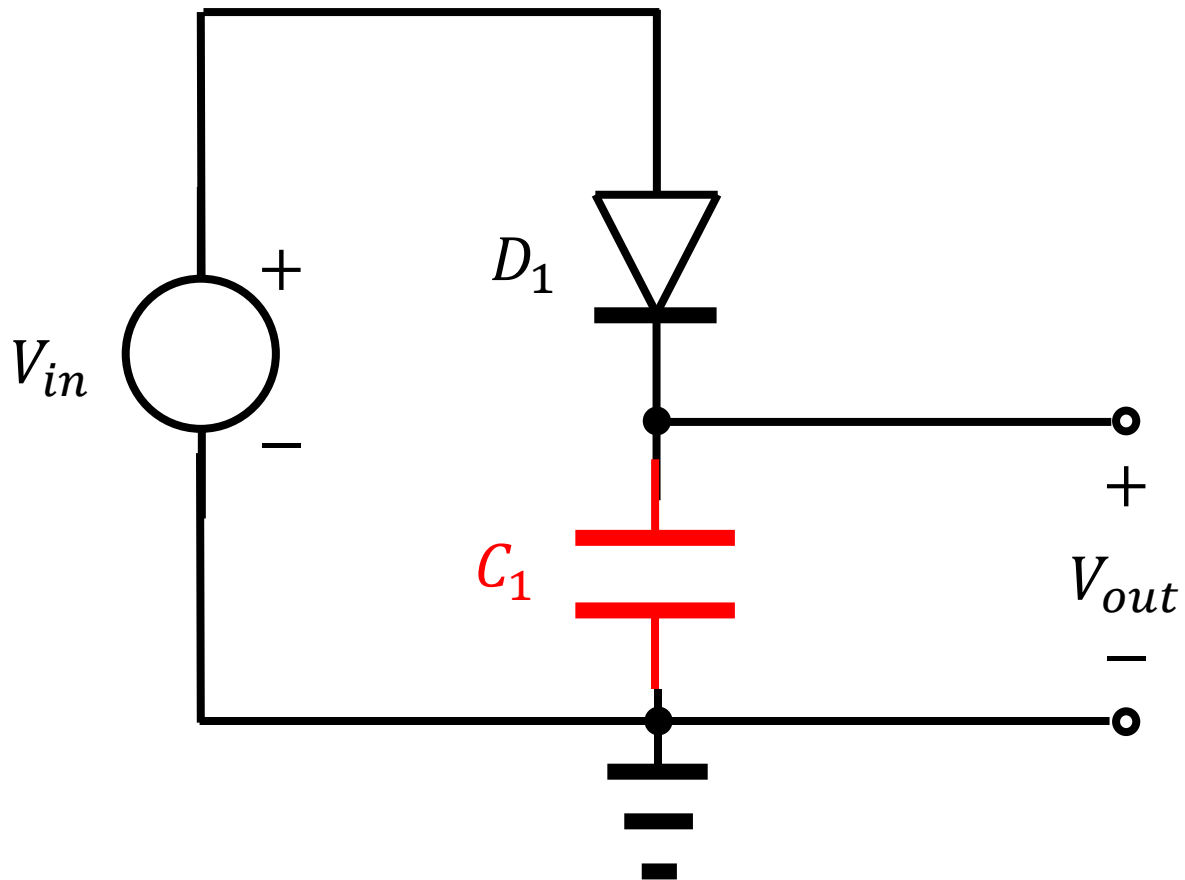


# Introducing a capacitor

---

- Difference from the previous one?


Voltage [V]

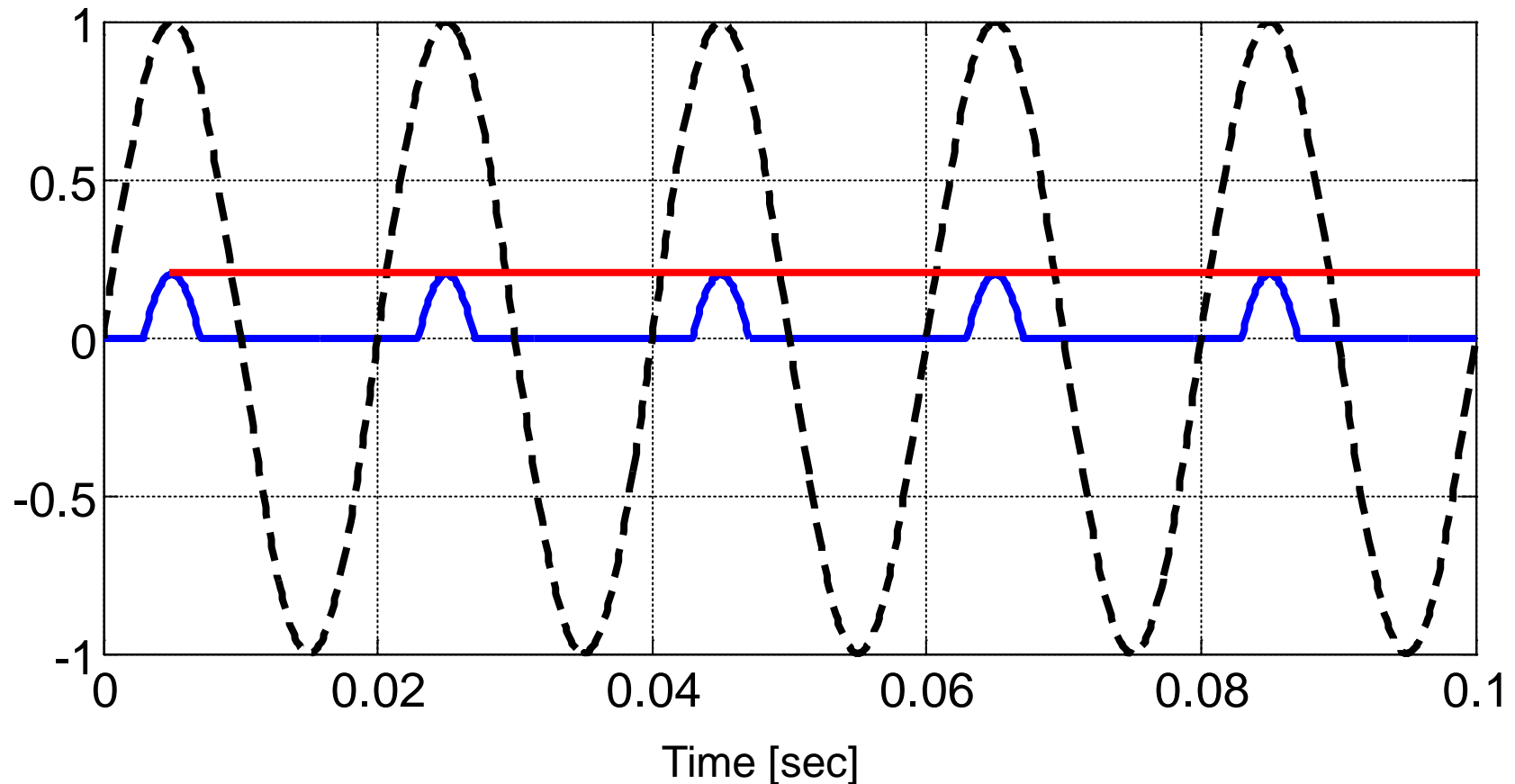

# Analogy

---

- A blood vessel

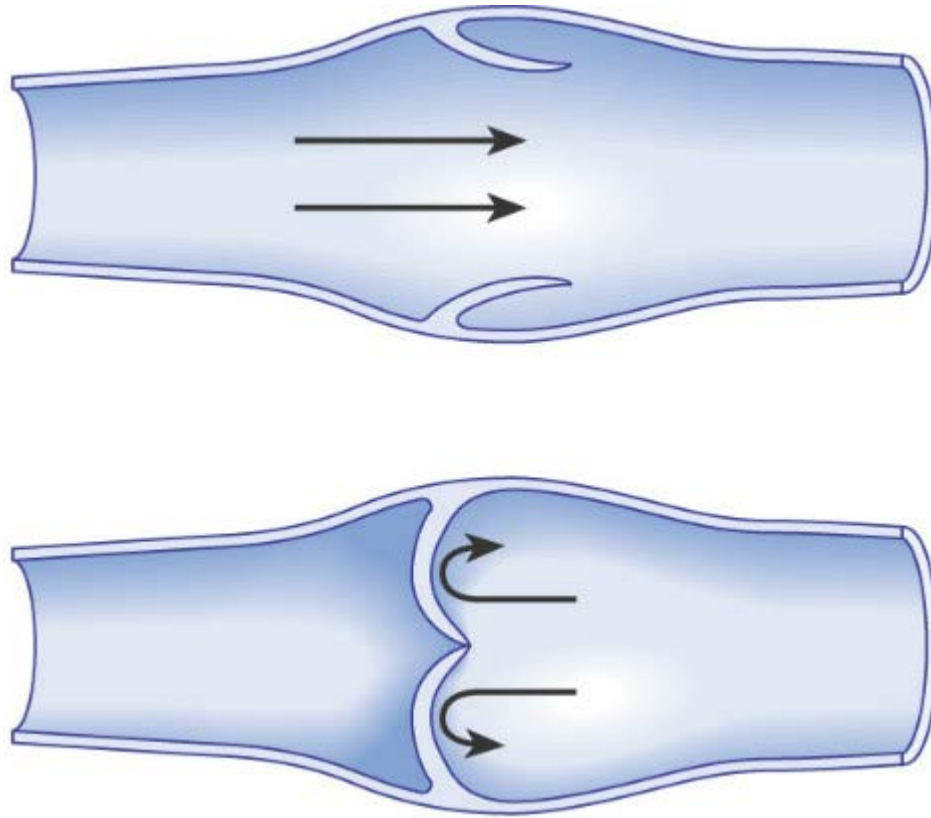


(Google image)

# Limiter

---

- Level-shift for both half cycles

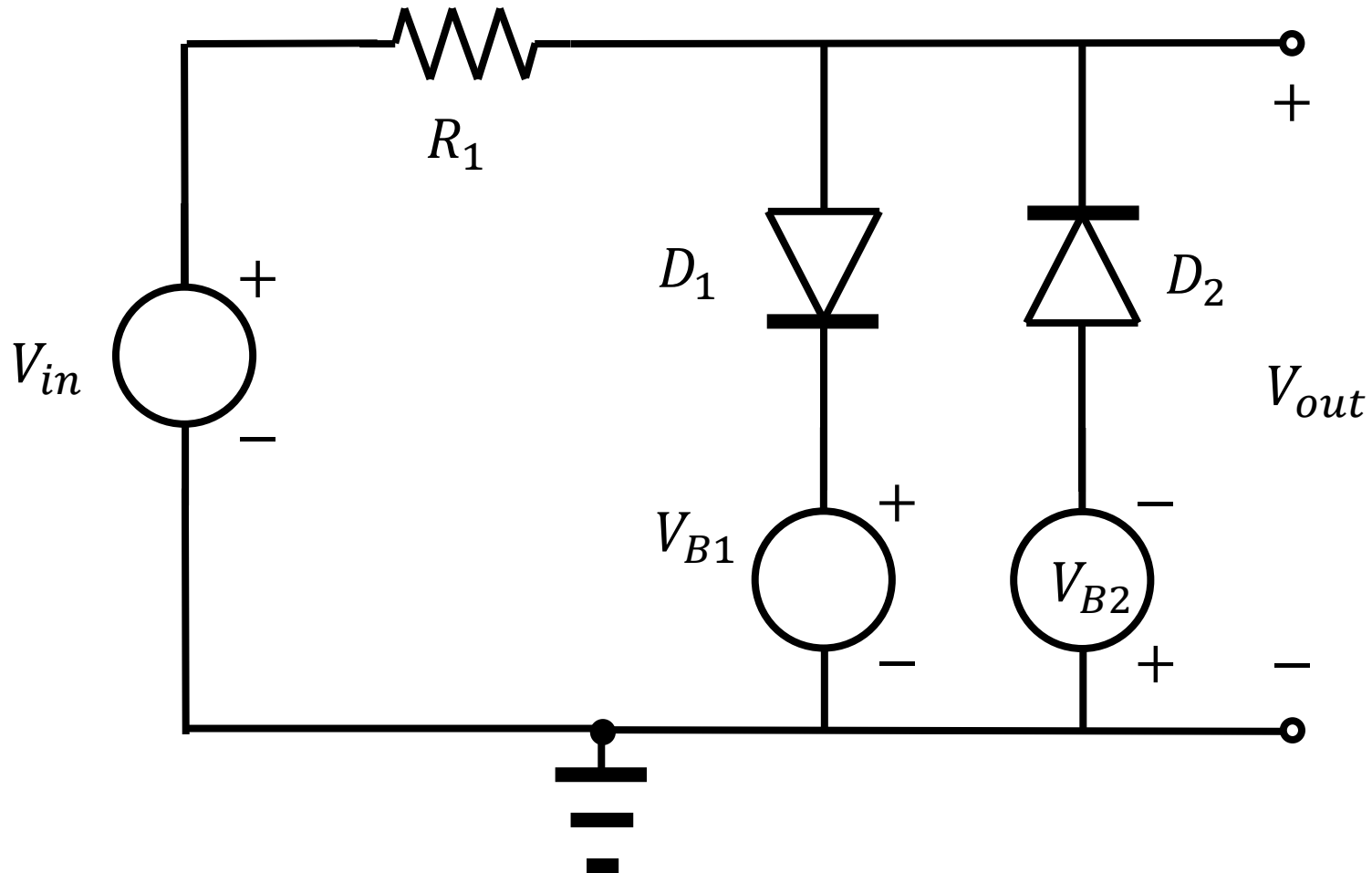


# MOSFET

---

- Metal-Oxide-Semiconductor Field-Effect Transistor
  - *How can I explain its importance properly?*
- In the biology,
  - All living organisms are composed of cell(s).

*Schem. XI.*

Fig. 1.

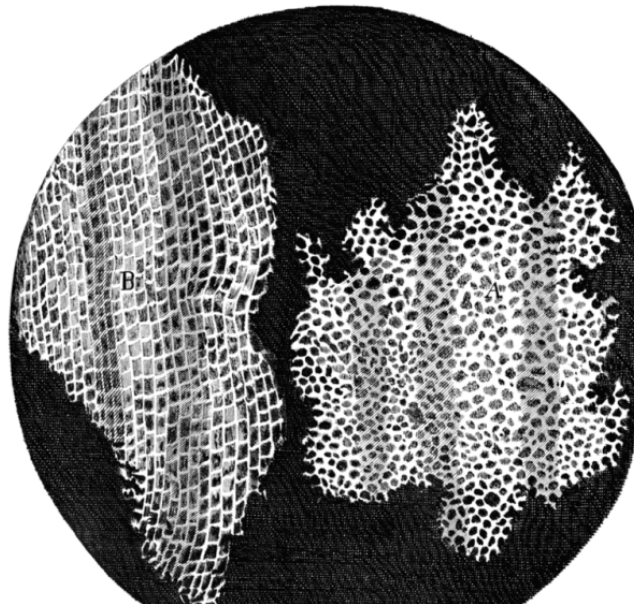


Structure of cork (Wikipedia)
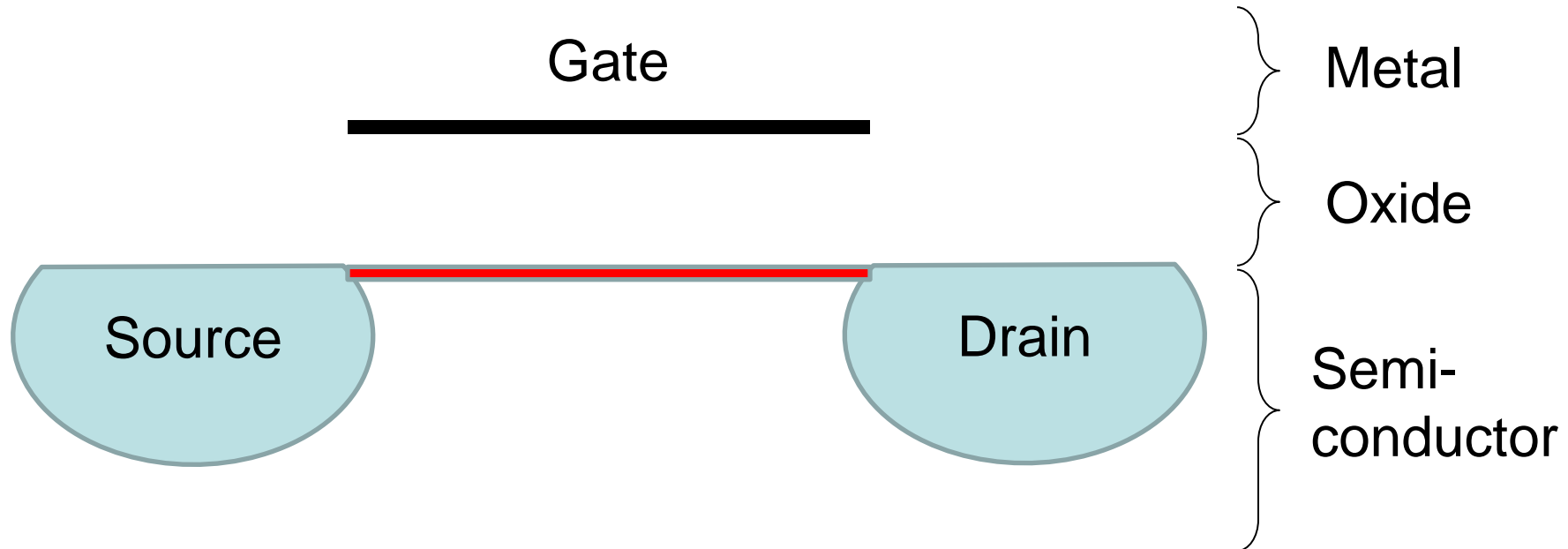
# Its generic structure

---


- Vertical structure
  - Metal-Oxide-Semiconductor
- Terminals
  - Gate, Source, Drain, (and substrate)


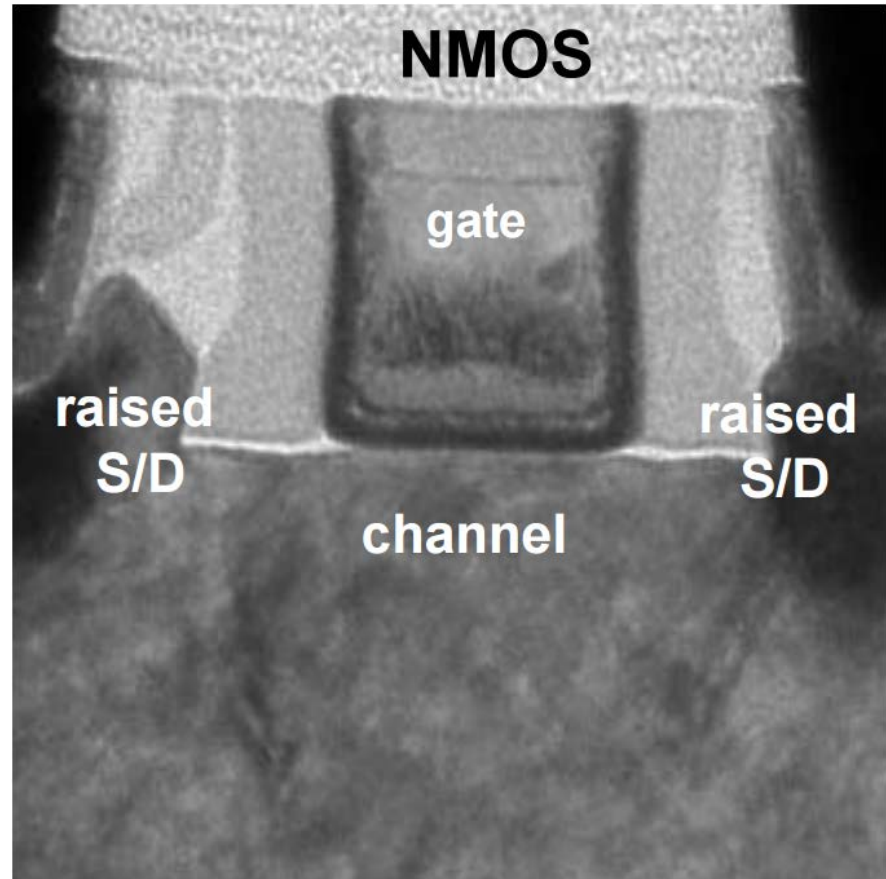
# Actual device

---

- TEM image of a MOSFET
  - 32nm node
  - (somewhat old...)




(Packan et al., IEDM 2009)




# How to fabricate it (1/6)

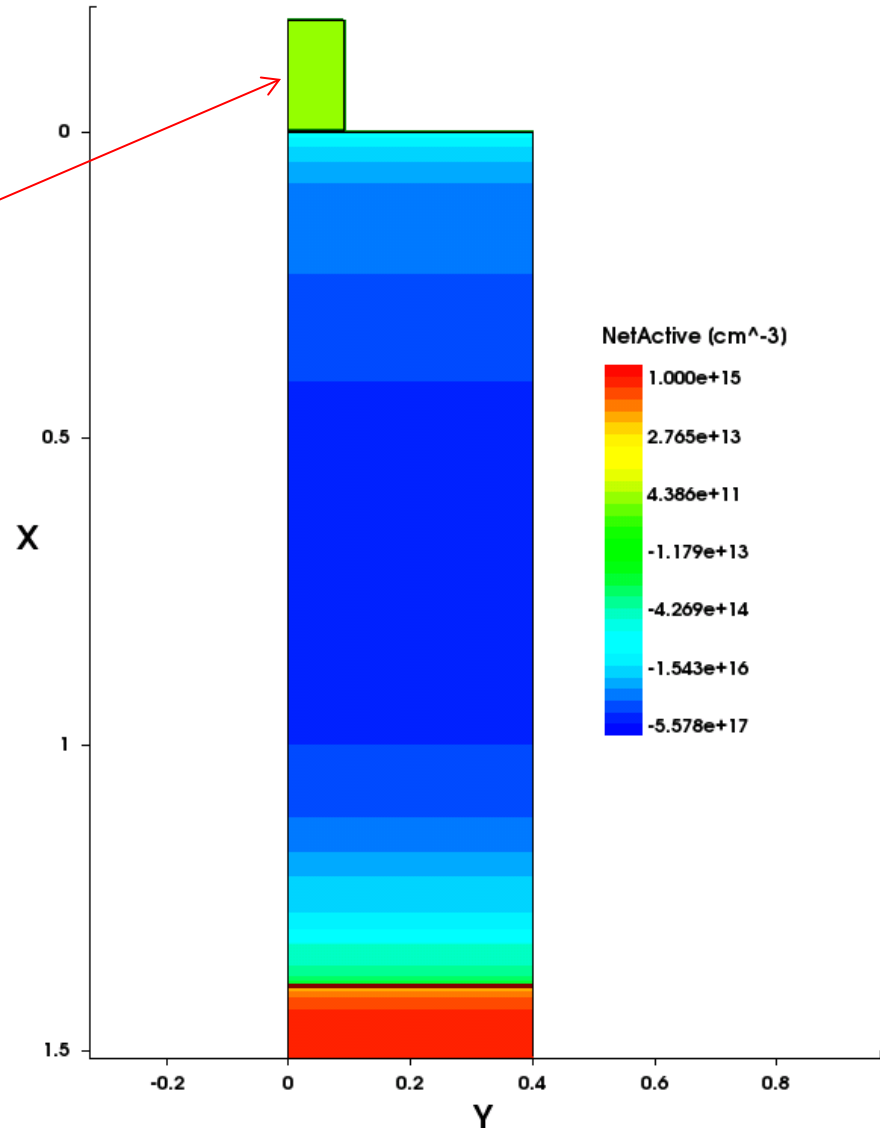- 0.18  $\mu\text{m}$  NMOSFET
  - P-well formation
  - Gate oxidation
  - Gate definition
  - (Half structure is shown.)




# How to fabricate it (2/6)

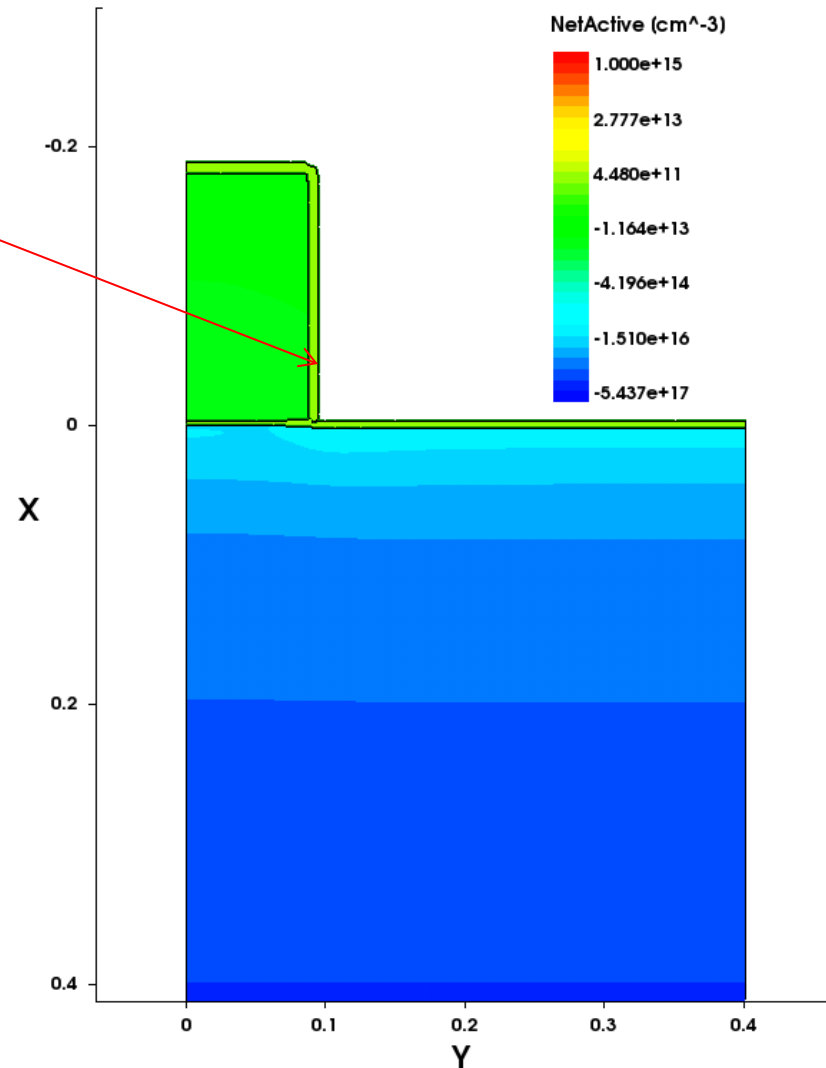- 0.18  $\mu\text{m}$  NMOSFET
  - Gate re-oxidation




# How to fabricate it (3/6)

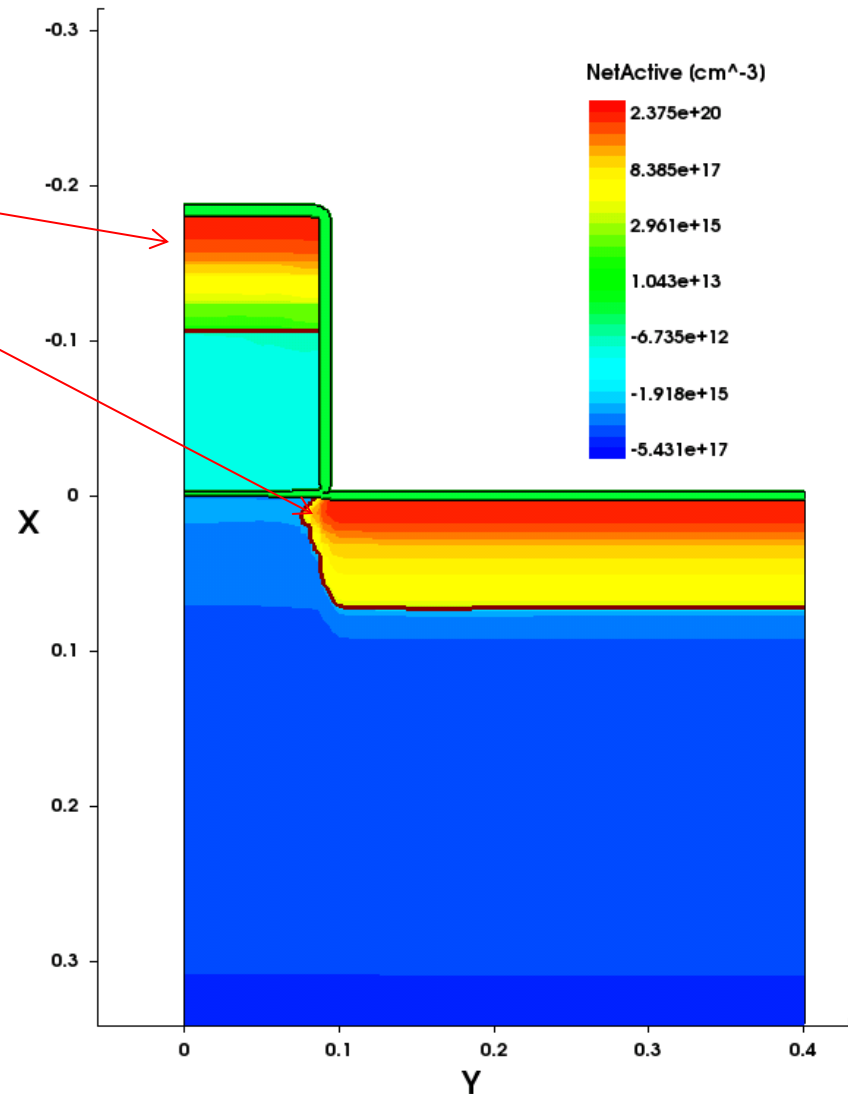- 0.18  $\mu\text{m}$  NMOSFET
  - LDD implant




# How to fabricate it (4/6)

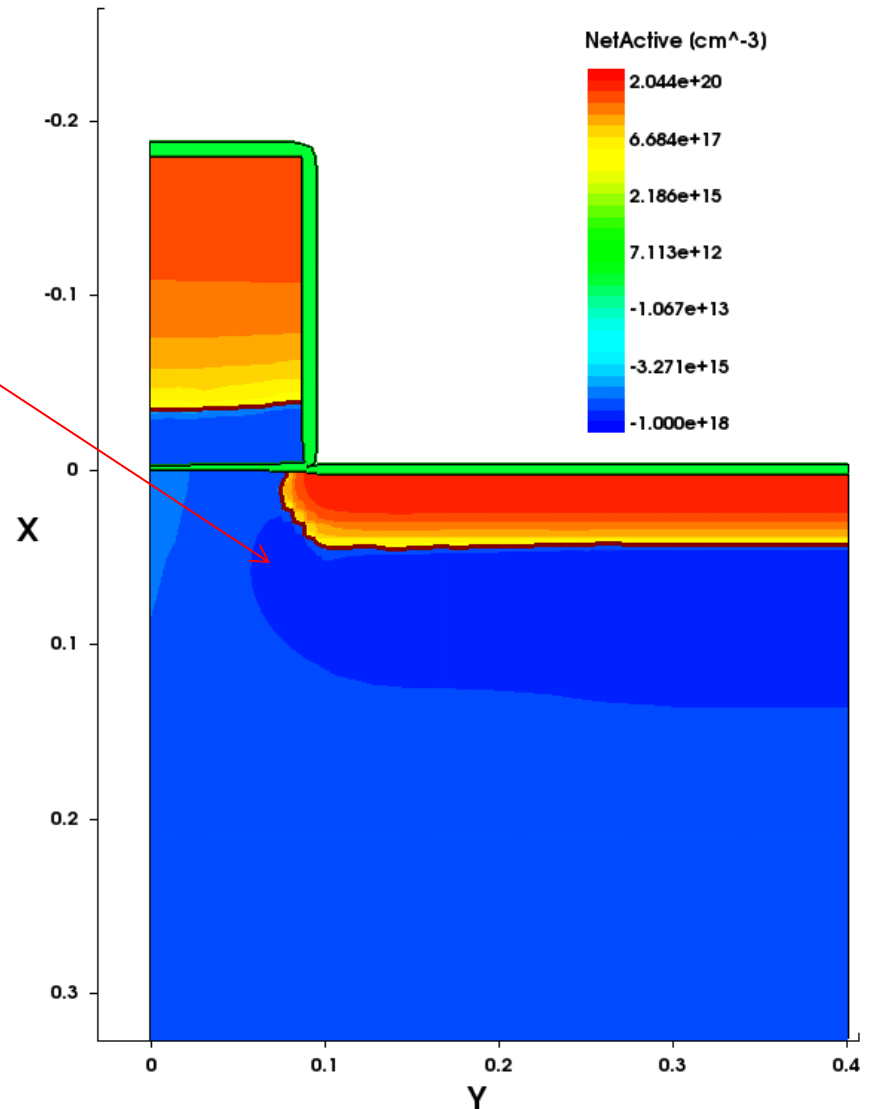- 0.18  $\mu\text{m}$  NMOSFET
  - Halo implant




# How to fabricate it (5/6)

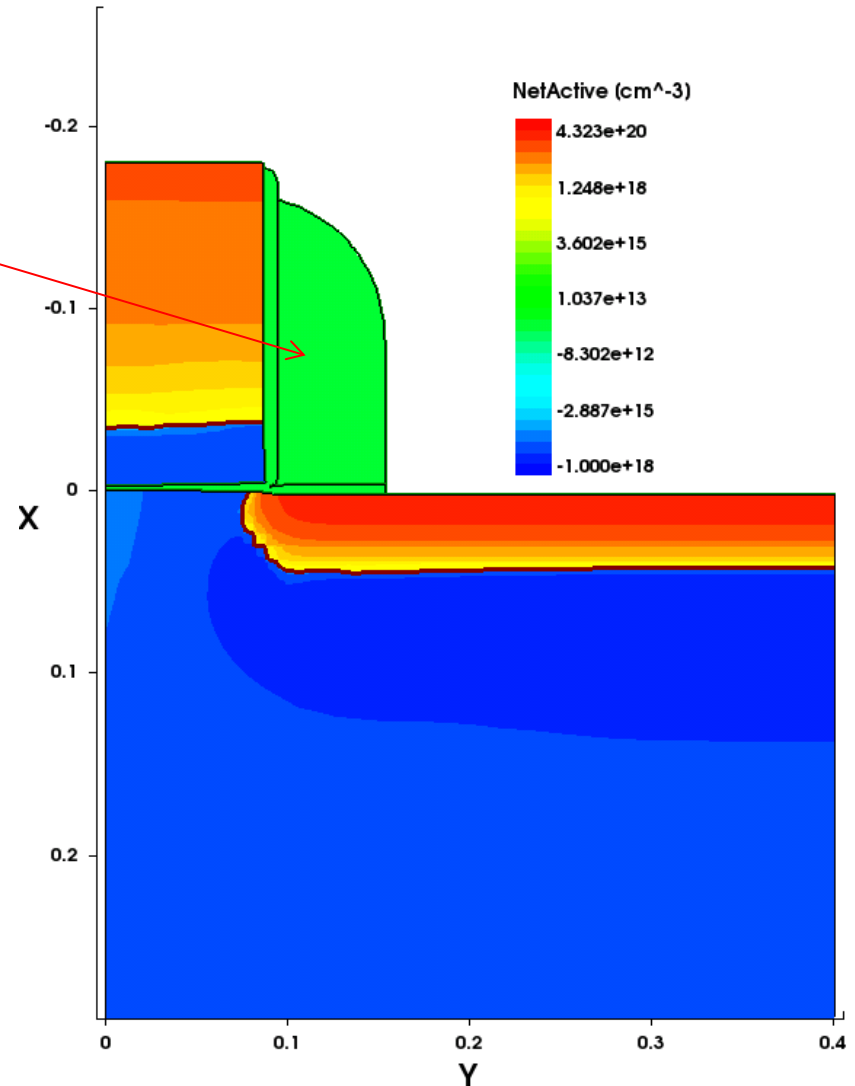- 0.18  $\mu\text{m}$  NMOSFET
  - Nitride spacer



# How to fabricate it (6/6)

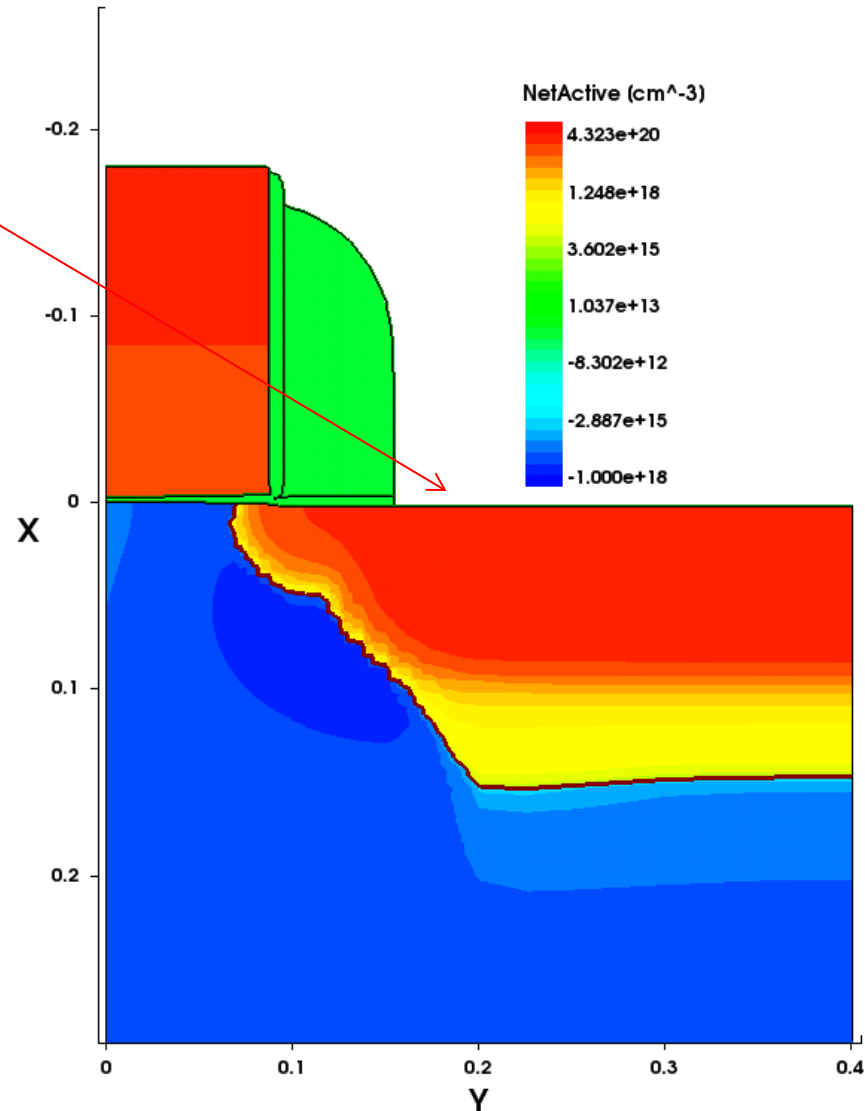
- 0.18  $\mu\text{m}$  NMOSFET
  - Source/drain implant


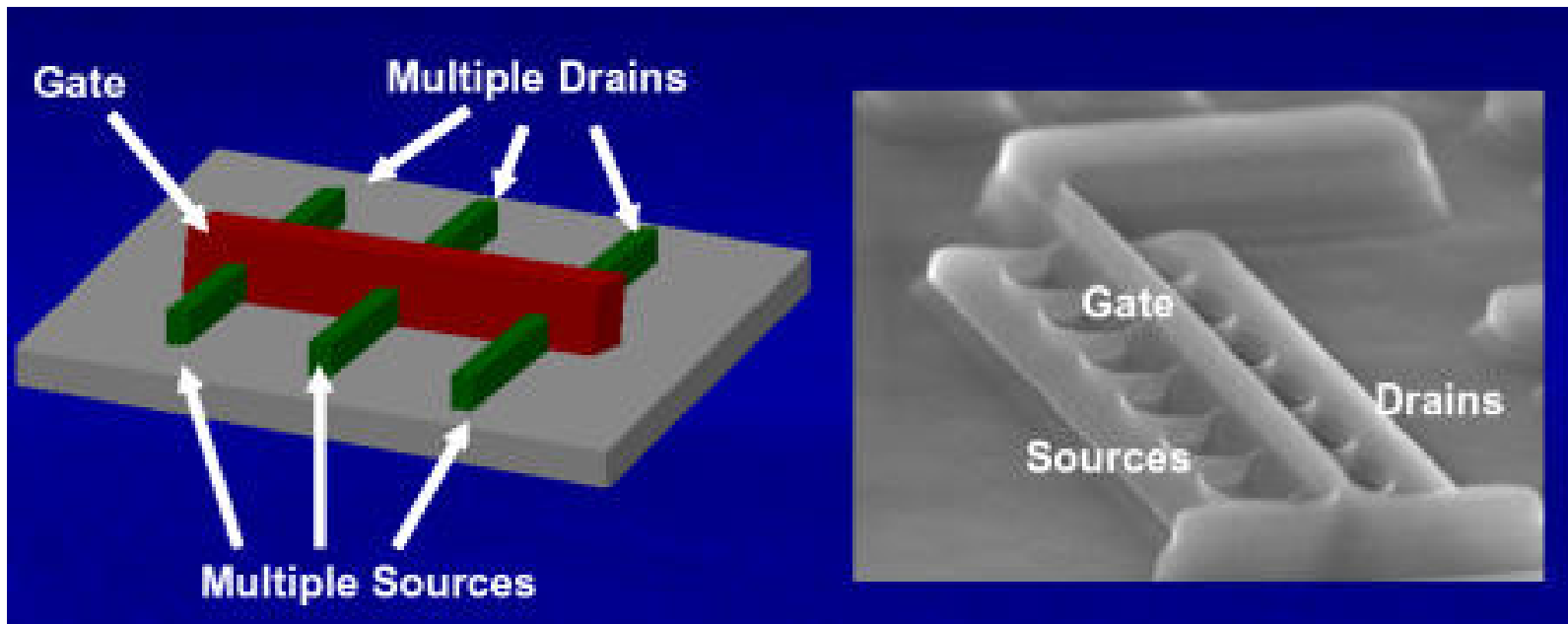
# Top view

---


- TEM image of a MOSFET
  - 22nm node
  - (a few years ago...)



(Wikipedia)


# Future

- Nanowire?

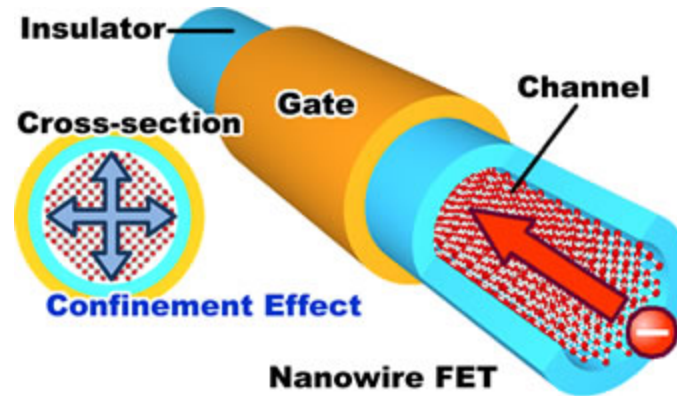

(Google images)

- III-V?

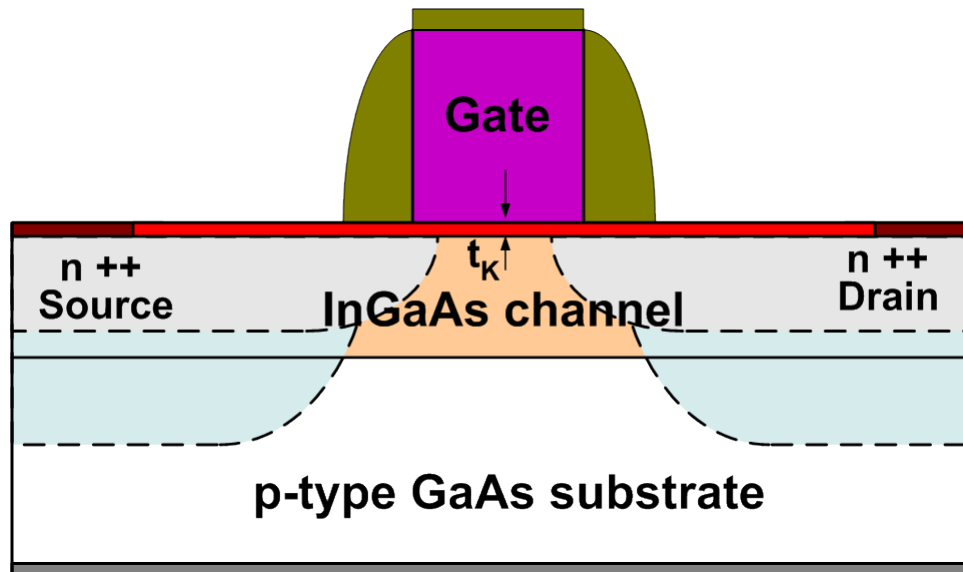

(Google images)



# Other application

---

- Up to now, we have seen the MOSFET used for the logic application.
  - CMOS RF
- However,
  - NAND Flash memory
  - Power device
  - Various sensors