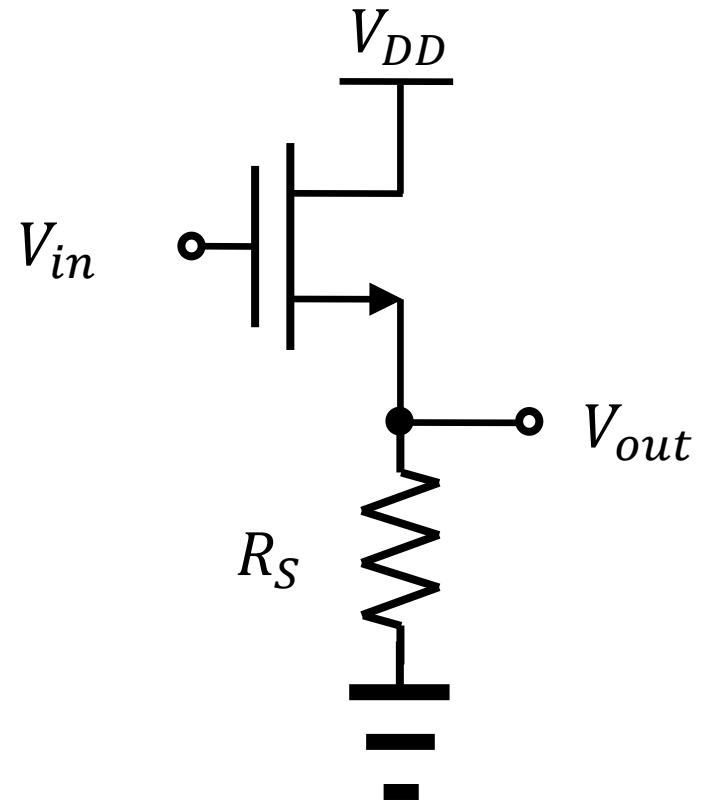
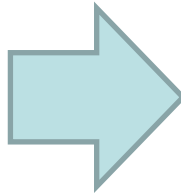
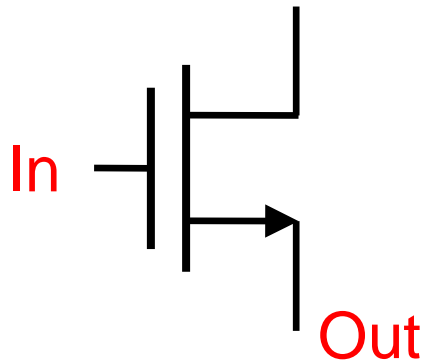

Lecture20: Source follower

Sung-Min Hong (smhong@gist.ac.kr)

Semiconductor Device Simulation Lab.
School of Electrical Engineering and Computer Science
Gwangju Institute of Science and Technology

Source follower


- Also called the “common-drain” stage
 - The drain is ac grounded.
- Wait a minute!
 - Is it a real amplifier?



Its core

- Gain is less than 1?? (Neglecting r_o)

$$A_v = + \frac{g_m R_S}{1 + g_m R_S}$$

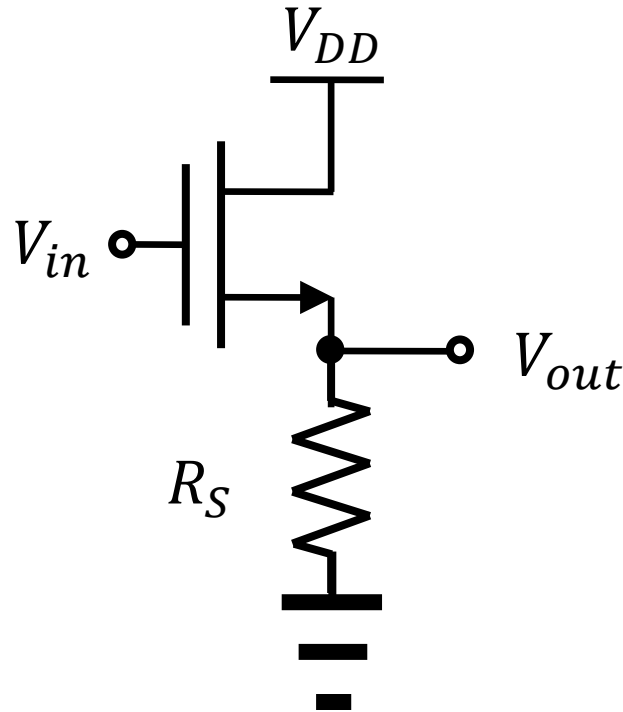


You should be able to draw the small-signal model.

Useless?

- Calculate the input and output impedances.
 - Since the gate is the input terminal, the input impedance is very high at low frequencies.
 - How about the output impedance?

$$R_{out} = \frac{1}{g_m} || r_o || R_S$$

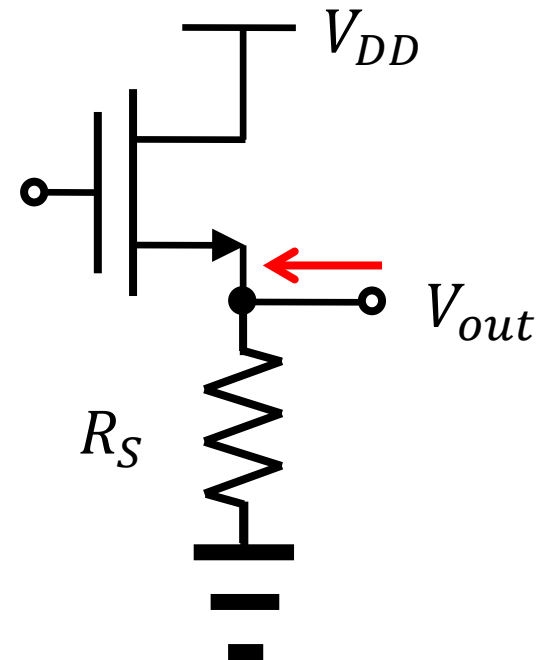- It is relatively low.
- High input imp., low output imp.
 - They can serve as good “buffers.”



Razavi, example 17.39

- Design the source follower.
 - Determine W/L and R_S .
 - The DC drain current is 1 mA.
 - The voltage gain is 0.8.

