
Lecture9: MOSFET, triode/saturation

Sung-Min Hong (smhong@gist.ac.kr)

Semiconductor Device Simulation Lab.
School of Electrical Engineering and Computer Science
Gwangju Institute of Science and Technology

Triode mode

- Equation

- A differential equation for $V(x)$

$$I_D = W C_{ox} [V_G - V(x) - V_{TH}] \mu_n \frac{dV}{dx}$$

- Solution

- Potential

$$V(x) = V_G - V_{TH} - \sqrt{(V_G - V_{TH})^2 - \frac{2I_D}{\mu_n C_{ox} W} x}$$

- Current

$$I_D = \mu_n C_{ox} \frac{W}{L} \left[(V_G - V_{TH}) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$$


Saturation mode

- Current usually increases as the voltage increases...
- Recall (6.3).

$$Q_{elec} = WC_{ox}[V_G - V(x) - V_{TH}] \quad (6.3)$$

- What happens when $V(x) = V_G - V_{TH}$?

Current

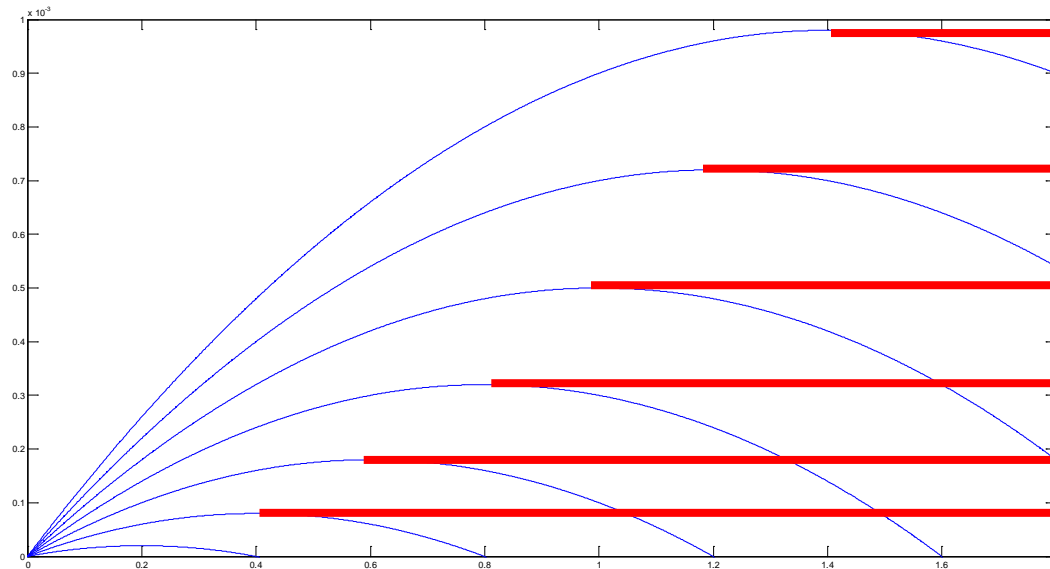


← Instead, the current is saturated. (Red lines)

Voltage

IEDM 2017

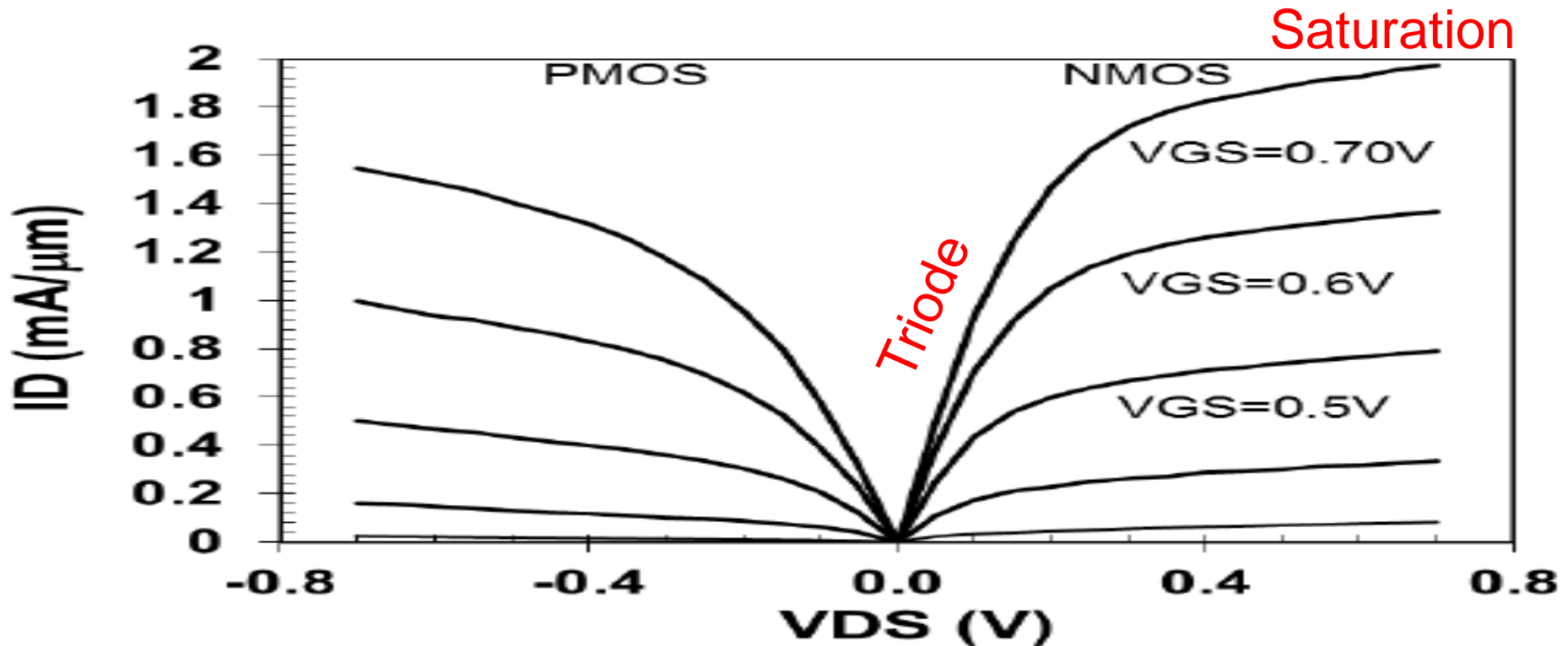- C. Auth et al. (Intel)
 - (Intentionally stretched for visibility)
 - Slight increase of I_D in the saturation region



Homework#5 (1)

- Due: 09:00, April 9
- Write a program, which reads a netlist file.
 - Construct a square matrix, whose size is $N \times N$. The matrix is related with the vector in Homework#4.
 - Each row of the matrix represents an equation.
 - In this program, the matrix describes a system:
 - For every element terminal, the terminal current vanishes.
 - For every element terminal, the terminal voltage is equal to the circuit node voltage.
 - For the GND node, the node voltage is zero.
 - For all other circuit nodes, the KCL is applied.

Homework#5 (2)

- (Continued)
 - For example, consider the example in Homework#4. A voltage source and a resistor are found.
 - The matrix is explicitly shown below.

$$\begin{array}{l}
 \text{Currents} \\
 \text{Voltages} \\
 \text{Currents} \\
 \text{Voltages} \\
 \text{GND} \\
 \text{KCL}
 \end{array}
 \begin{bmatrix}
 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\
 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\
 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 & -1 \\
 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 & -1 & 0 \\
 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 \\
 0 & 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 \\
 0 & 0 & 0 & 0 & 0 & 0 & 1 & 0 & 0 & -1 \\
 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 & -1 & 0 \\
 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 & 0 \\
 1 & 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0
 \end{bmatrix}
 \times
 \begin{bmatrix}
 I_1^V \\
 I_2^V \\
 V_1^V \\
 V_2^V \\
 I_1^R \\
 I_2^R \\
 V_1^R \\
 V_2^R \\
 V_0 \\
 V_{in}
 \end{bmatrix}
 =
 \begin{bmatrix}
 0 \\
 0 \\
 0 \\
 0 \\
 0 \\
 0 \\
 0 \\
 0 \\
 0 \\
 0
 \end{bmatrix}$$

Homework#5 (3)

- Solve the following problems of the mid-term exam in 2017.
 - P25
 - P26
 - P27
 - P28
 - P29
 - P30
 - P31
 - P32
 - P33